

Vidya Jyothi Institute of Technology

(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

B. Tech. II Year II Semester

L	Τ	P	С
0	0	2	1

ELECTRICAL MACHINES – I LABORATORY

Course Code:A14283

Course Outcomes: After the completion of this course, a student must demonstrate the knowledge and ability to

CO1. Identify losses, Output, and efficiency of DC motors

CO2. Identify losses, Output, and efficiency of DC generators

CO3 Apply speed control methods on DC motors.

CO4 Analyze the magnetization characteristics of DC shunt generator to determine its parameters.

CO5 Infer the efficiencies of DC Series Machines.

List of Experiments

Any ten of the following experiments are required to be conducted.

- 1. Magnetization characteristics of a DC Shunt Generator.
- 2. Load test on DC Shunt Generator
- 3. Brake test on DC compound motor.
- 4. Load test on DC Series Generator
- 5. Brake test on DC compound motor
- 6. Hopkinson's test on DC Shunt machines.
- Field's test on DC Series machines.
- 8. Separation of losses in DC shunts motor.
- 9. Retardation test on DC shunt motor.
- 10. Speed control of DC shunt motor.
- 11. Swinburne's test on DC shunt machine.
- 12. Brake Test on DC shunt Motor.



VIDYA AVORTI INSTITUTE OF 1035.

the Department

of Electrical Selectionics Enge



Vidya Jyothi Institute of Technology (An Autonomous Institution)

(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

Correlation of COs with Experiments

S. No	Name of the Experiment	COs Mapped
1	Magnetization characteristics of a DC Shunt Generator.	CO 4
2	Load test on DC Shunt Generator	CO2
3	Brake test on DC compound motor.	CO1
4	Load test on DC Series Generator	CO2, CO5
5	Brake test on DC compound motor	CO1
6	Hopkinson's test on DC Shunt machines.	CO1, CO2
7	Field's test on DC Series machines.	CO5
8	Separation of losses in DC shunts motor.	CO1, CO2
9	Retardation test on DC shunt motor.	CO2
10	Speed control of DC shunt motor.	CO3
11	Swinburne's test on DC shunt machine.	CO1, CO2
12	Brake Test on DC shunt Motor.	CO2



Vidya Jyothi Institute of Technology

(An Autonomous Institution)

(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

Programme Outcomes (POs)

Engineering Graduates will be able to:

1. Engineering knowledge: Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.

2. Problem analysis: Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.

3. Design/development of solutions: Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.

4. Conduct investigations of complex problems: Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.

5. Modern tool usage: Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.

6. The engineer and society: Apply reasoning informed by the contextual knowledge to assess societal, health,

safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.

7. Environment and sustainability: Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.

8. Ethics: Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.

9. Individual and teamwork: Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.

10. Communication: Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.

11. Project management and finance: Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.

12. Life-long learning: Recognize the need for and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.

Program Specific Outcomes (PSOs)

PSO 1: Apply the fundamentals of Electrical and Electronics Engineering to analyze and synthesize problems of Electric Circuits, Electronic Circuits, Control Systems, Electrical Machines and Power Systems.

PSO 2: Apply the appropriate techniques and modern engineering hardware and software tools in Electrical Engineering to engage in life-long learning and to successfully adapt in multi-disciplinary environments.



Vidya Jyothi Institute of Technology (An Autonomous Institution)

(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

CO – PO Mapping

A 1 4 9 9 2		ELECTRICAL MACHINES LAB- I										
A14283	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12
C227.1	3	3	2	3	-	-	-	-	3	-	-	2
C227.2	3	3	2	3	-	-	-	-	3	-	-	2
C227.3	3	3	2	3	-	-	-	-	3	-	-	3
C227.4	3	3	2	3	-	-	-	-	3	-	-	3
C227.5	3	3	2	3	-	-	-	-	3	-	-	3
	3	3	2	3	-	-	-	-	3	-	-	2.6

CO – PSO Mapping

	Electrical Machines - II LAB	
A14283	PSO1	PSO2
C227.1	3	-
C227.2	3	-
C227.3	3	-
C227.4	3	-
C227.5	3	-
	3	-



Vidya Jyothi Institute of Technology

(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

STUDENT PERFORMANCE EVALUATION

TOTAL MARKS (75M)

EXTERNAL EVALUATION (50 Marks)

Circuit Diagram	10M
Procedure	10M
Experiment connections & observations	10M
Calculations	10M
Viva Voce	10M

INTERNAL EVALUATION (25 Marks)

Day to day evaluation	10M
Record	5M
Internal Exam	10M



DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

Rubrics for Electrical Machines I Laboratory

I Otta					
S. No.	Assessment Criteria	Excellent (80 – 100%)	Good (60-80%)	Average (Below 60%)	
1	Theoretical Knowledge to perform the experiment (2M)	Student replied to all the questions posed by Laboratory teacher	Student replies to a minimum of 50% questions posed by the laboratory teacher	Student could not answer in the first session	
2	Preparation of list of equipment required (2M)	Correctness in the rating and type of the equipment required	Correctness in the rating and type of equipment required with minor corrections	Student could not prepare the list of equipment required	
3	Making the circuit connections as per the circuit diagram. (3 M)	Correctness of connections	Correctness of connections with minor corrections.	Unable to connect	
4	Performing the experiment and tabulating the values (3 M)	Independent performance of the experiment with correct values	Performance of the experiment with teacher assistance	Unable to perform the experiment	
5	Record book (based on calculations, results, graphs) (5 M)	Practical values matching with theoretical values/ Expected graph obtained.	Minor deviation in the practical values/ expected graph	Deviation of practical values with theoretical values / expected graph.	

Total Marks: 15M

1. MAGNETIZATION CHARACTERISTICS OF A D.C. SHUNT GENERATOR

AIM: - To plot the open circuit characteristics of D.C Shunt generator and determine its critical field resistance and critical speed.

THEORY:

The performance of the electrical machines can be found out by their characteristic curves. The magnetization characteristics is also known as no-load saturation characteristic curves or open-circuit characteristic curves. It is drawn between no-load generated emf in armature (E_0) and the field current (I_f) at a given fixed speed. Its shape is practically same for all the generators.

Critical field resistance: Critical field resistance is the cut-off resistance beyond which the generator fails to generate emf. To find the critical resistance, draw a tangent to the O.C.C. curve from its initial position. The slope of the resistance curve gives the critical resistance.

Critical speed: Critical speed is the minimum speed below which the generator fails to build up the voltage. The critical speed of a generator can also be easily found from the O.C.C curves easily.

CIRCUIT DIAGRAM: -



Fig 1.1

APPARATUS: -

S No	Apparatus	Range	Quantity
1	Voltmeter	(0-300) V, MC	1
2	Ammeter	(0-1.5) A, MC	1
3	Dhaostata	230Ω, 1.7A	2
	Kneostats	100Ω, 7A	1
4	Tachometer	(0-9999) rpm	1

NAME PLATE DETAILS: -

D.C Shunt Motor: K.W: Voltage: Current: Speed: Excitation Current: Excitation Voltage: D.C Shunt Generator: K.W: Voltage: Current: Speed: Excitation Current: Excitation Voltage:

FUSE RATING CALCULATIONS: -

For No-Load: 10% of rated current of motor:

For Full-Load: 125 % of rated current of motor:

PROCEDURE: -

- 1. Connect the circuit as per the circuit diagram.
- 2. Keep armature rheostat of the Motor in maximum position and field rheostat of the motor in minimum position and also keep field rheostat of the generator in maximum position.
- 3. Switch 'ON' the D.C. supply and start the M-G set to rated value with the help of armature rheostat of the motor, If rated speed is not reached then adjust the field rheostat of the Motor.
- 4. Adjust the speed of the M-G set to rated value with the help of armature rheostat of the Motor, if rated speed is not reached then adjust the field rheostat of the Motor.
- 5. When M-G set rotates at rated speed a small reading is observed in the Voltmeter even though there is no current in the field winding. In this case note down the readings of Voltmeter and Ammeter.
- 6. Now, vary the field rheostat of the Generator in steps to rated voltage and at each step note the note down the readings of Voltmeter and Ammeter.
- 7. Switch 'OFF' the D.C. Supply of M-G set by making all devices to initial position.

NOTE: -

Speed of the M-G set is to be kept constant throughout the experiment and field rheostat of the Generator should be vary in only one direction till the rated voltage of the Generator.

PRECAUTIONS: -

- Connection should be neat and tight.
- Before starting of the M-G set check the rheostats positions properly.
- Note down the readings without any parallax error.

OBSERVATION TABLE: -

S.NO	E _g (Volts)	I _f (Amps)	Speed (r. p. m)		

EXPECTED GRAPH: -



CALCULATIONS: -

Fig 1.2

Critical Resistance (R_c) = (E_g – OE) / I_f

Critical Speed (Nc) $= N_s * (BC/AC)$

RESULT: - Open Circuit Characteristics of DC Shunt generator are plotted and determined its critical field resistance and critical speed.

2. LOAD TEST ON D.C. SHUNT GENERATOR

AIM: - To perform load test on D.C Shunt generator and to determine its load characteristics

THEORY: -

The efficiencies of all D.C. machines can be computed in two ways:

- 1. Direct test
- 2. Indirect test

In direct method, the input and output power can be measured by suitable means and efficiency computed as a ratio of output to input.

A direct method is not used for large machines as:

a. It may not be possible to provide the necessary load.

b. Even if load is arranged, there would be enormous power loss during the test.

The performance of the electrical machines can be found out by their characteristic curves. The load test on D.C. compound generator is used to determine the load characteristics of the generator and also the change in efficiency when the load on the generator varies. The load characteristics are drawn between

- 1. Generated voltage (V_g) and Load current (I_{lg})
- 2. Efficiency and load current (I_{lg})

CIRCUIT DIAGRAM: -



Fig 2.1

APPARATUS REQUIRED: -

S No	Apparatus	Range	Quantity
1	Voltmeter	(0-300) V, MC	2
2	Ammeters	(0-20) A, MC	2
		(0-1.5) A, MC	2
3	Rheostats	230Ω/1.7 A	2
		15 Ω/17.5 A	1
	Tachometer	(0-9999) rpm	1

NAME PLATE DETAILS: -

D.C Shunt motor

D.C Shunt Generator

KW:	KW:
Voltage:	Voltage:
Load Current:	Load Current:
Speed:	Speed:
Shunt field current	Shunt field current:

FUSE RATING CALCULATIONS: -

For No-Load: 10% of rated current of motor:

For Full-Load: 125 % of rated current of motor:

PROCEDURE: -

- 1. Connect the circuit as per the circuit diagram.
- 2. Keep field rheostat of the motor in minimum position and armature rheostat of the Motor in maximum position.
- 3. Switch 'ON' the D.C supply and start the M-G set with the help of 3-point starter.
- 4. Adjust the M-G set speed to rated value with the help of armature rheostat of the motor. If rated speed is not reached, then adjust the field rheostat of the motor.
- 5. Now, adjust the field rheostat of the generator to rated voltage of the generator.
- 6. Note down the No-load readings of Voltmeters & Ammeters.
- 7. Now, vary the load in steps to rated current of the generator and at each step note down the readings of voltmeters and Ammeters and also at each step maintain constant speed with the help of field rheostat of the motor.
- 8. Switch 'OFF' the load to zero position and also switch 'OFF' D.C. supply by making all devices to initial position.

NOTE: - Field rheostat of the generator should be varied in only one direction till the rated voltage of the generator is reached.

PRECAUTIONS: -

- Connections should be neat and tight
- > Before starting of the M-G set ensure that there is no load on the Generator.
- > Before starting of the motor check the rheostat positions properly.
- > Note down the readings without any parallax error.

OBSERVATION TABLE: -

S.NO	V _M (V)	Im (Amps)	Vg (V)	ILg (Amps)	I _{shg} (Amps)	I _{ag} (Amps)	IagRa (Volts)	Eg (Volts)	Input (Watts)	Output (Watts)	Efficiency % (η)

CALCULATIONS:

Armature current $(I_{ag}) = I_{Lg} + I_{shg}$

 $\begin{array}{ll} E_g = V_g + I_{ag}R_a \\ INPUT &= V_M * I_M \mbox{ Watts} \\ OUTPUT = V_g * I_{Lg} \mbox{ Watts} \\ Efficiency = & \underline{OUTPUT} \mbox{ X 100} \\ \hline INPUT \end{array}$

EXPECTED GRAPHS: -



RESULT: - load test on D.C Shunt generator is performed and drawn its load characteristics.

3. LOAD TEST ON D.C. COMPOUND GENERATOR

AIM: - To perform load test on D.C Compound generator and to determine its load characteristics

THEORY:

The efficiencies of all D.C. machines can be computed in two ways:

- 1. Direct test
- 2. Indirect test

In direct method, the input and output power can be measured by suitable means and efficiency computed as a ratio of output to input.

A direct method is not used for large machines as:

a. It may not be possible to provide the necessary load.

b. Even if load is arranged, there would be enormous power loss during the test.

The performance of the electrical machines can be found out by their characteristic curves. The load test on D.C. compound generator is used to determine the load characteristics of the generator and the change in efficiency when the load on the generator varies. The load characteristics are drawn between Generated voltage (V_g) and Load current (I_{lg}), Efficiency and load current (I_{lg}).

CIRCUIT DIAGRAM: -



APPARATUS: -

S No	Apparatus	Range	Quantity
1	Voltmeter	(0-300) V, MC	2
2	Ammeters	(0-20) A, MC	2
		(0-1.5) A, MC	2
3	Rheostats	230Ω/1.7 A	2
		15 Ω/17.5 A	1
4	Tachometer	(0-9999) rpm	1

NAME PLATE DETAILS: -D.C Shunt motor

D.C Compound Generator

KW:	KW:
Voltage:	Voltage:
Load Current:	Load Current:
Speed:	Speed:
Shunt field current	Shunt field current:

FUSE RATING CALCULATIONS: -

For No-Load: 10% of rated current of motor:

For Full-Load: 125 % of rated current of motor:

PROCEDURE:

- 1. Connect the circuit as per the circuit diagram.
- 2. Keep field rheostat of the motor in minimum position and armature rheostat of the Motor in maximum position.
- 3. Switch 'ON' the D.C supply and start the M-G set with the help of 3-point starter.
- 4. Adjust the M-G set speed to rated value with the help of armature rheostat of the motor. If rated speed is not reached, then adjust the field rheostat of the motor.
- 5. Now, adjust the field rheostat of the generator to rated voltage of the generator.
- 6. Note down the No-load readings of Voltmeters & Ammeters.
- 7. Now, vary the load in steps to rated current of the generator and at each step note down the readings of voltmeters and Ammeters and at each step maintain constant speed with the help of field rheostat of the motor.
- 8. Switch 'OFF' the load to zero position and also switch 'OFF' D.C. supply by making all devices to initial position.

NOTE: - Field rheostat of the generator should be varied in only one direction till the rated voltage of the generator is reached.

PRECAUTIONS: -

- a. Connections should be neat and tight
- b. Before starting of the M-G set ensure that there is no load on the Generator.
- c. Before starting of the motor check the rheostat positions properly.
- d. Note down the readings without any parallax error.

OBSERVATION TABLE: -

S.NO	V _M (V)	Im (Amps)	V _g (V)	I _{Lg} (Amps)	I _{shg} (Amps)	I _{ag} (Amps)	Iag(Ra+ R _{se}) (Volts)	Eg (Volts)	Input (Watts)	Output (Watts)	Efficiency (η) %

CALCULATIONS: -

Armature current $(I_{ag}) = I_{Lg} + I_{shg}$

 $E_g = V_g + I_{ag}(R_a + R_{SE})$

INPUT $= V_M + I_M$ Watts

 $OUTPUT = V_g I_{Lg} Watts$

 $Efficiency = \frac{OUTPUT}{INPUT} X \ 100$

EXPECTED GRAPHS: -





RESULT: - load test on D.C Compound generator is performed and drawn its load characteristics

4. LOAD TEST ON D.C. SERIES GENERATOR

AIM: - To perform Load test on D.C. Series Generator and determine its Internal and external characteristics.

THEORY: -

In a series-wound DC generator, the armature winding, field winding and external load circuit, all are connected in series with each other, therefore, the same current flows through all parts of the circuits.

Internal characteristics: -

If there would not have been demagnetizing effect of armature reaction, this curve would have given the total flux, when the machine is supplying current to the external load circuit, but due to armature reaction the actual curve lies somewhat below the magnetization curve, Since the emf generated in the armature is directly proportional to the actual flux at a constant speed, this curve also gives emf generated in the armature to some other scale. This curve is internal or total characteristic because it also gives relation between generated emf E_g and armature current I_a since $I_a = I_f$.

External or Load Characteristic: -

The load current, armature current and field current in series wound generator are the same. The terminal voltage of the generator is equal to the emf generated E_g less the voltage drops in armature and series field respectively. If R_a and R_{se} are the resistances of the armature and series field respectively and load current is I, then the voltage drop in armature and series field = $I(R_a + R_{se})$. This voltage drop for different values of load current may be represented by a straight-line OA. So if the ordinates of this ohmic drop line OA are deducted from those of internal characteristics, the relation between terminal voltage and load current, known as external characteristic, is obtained. From external characteristic it is observed that the terminal voltage first increases with the increase in load current, reaches the maximum value and finally decreases. If the load circuit resistance is reduced sufficiently, the terminal voltage may fall to zero. So if the series generator is operated on initial straight portion of the characteristic, it gives voltage approximately proportional to the current and if it is operated on dropping portion of the characteristic, it gives approximately constant irrespective of the external load circuit resistance.

CIRCUIT DIAGRAM:



RESISTIVE LOAD

Fig 4.1

APPARATUS REQUIRED: -

S No	Apparatus	Range	Quantity
1	Voltmeter	(0-300) V, MC	2
2	Ammeters	(0-20) A, MC	2
3	Rheostats	230Ω/1.7 A	2
4	Tachometer	(0-9999) rpm	1

D.C Series Generator:

NAME PLATE DETAILS: -

D.C Shunt Motor:

K.W:	K.W:
Voltage:	Voltage:
Current:	Current:
Speed:	Speed:
Excitation Current:	Excitation Current:
Excitation Voltage:	Excitation Voltage:

FUSE RATING CALCULATIONS: -

For No-Load: 10% of rated current of motor:

For Full-Load: 125 % of rated current of motor:

PROCEDURE: -

- 1. Connect the circuit as per the circuit diagram.
- 2. Keep field rheostat of the motor in minimum position and armature rheostat of the Motor at maximum position.
- 3. Switch 'ON' the D.C supply and start the M-G set with the help of 3-point starter.
- 4. Adjust the M-G set speed to rated value with the help of armature rheostat of the motor. If rated speed is not reached, then adjust the field rheostat of the motor.
- 5. Note down the No-load readings of Voltmeters & Ammeters.
- 6. Now, vary the load in steps to rated current of the generator and at each step note down the readings of voltmeters and Ammeters and at each step maintain constant speed with the help of field rheostat of the motor.
- 7. Switch 'OFF' the load to zero position and also switch 'OFF' D.C. supply by making all devices to initial position.

PRECAUTIONS: -

- Connections should be neat and tight.
- > Before starting of the M-G set ensure that there is no load on the Generator.

OBSERVATION TABLE: -

S.NO	V _M (V)	I _{Lm} (Amps)	V _g (V)	$I_{Lg = I_{ag = I_{seg}}}$ (Amps)	I _{ag} (R _a +R _{se}) (Volts)	Eg (Volts)	Input (Watts)	Output (Watts)	Efficiency (η) %

CALCULATIONS: -

Armature current $(I_{ag}) = I_{Lg} = I_{seg}$

 $E_g = V_g + I_{ag}(R_a + R_{se})$

Input Power $= V_M I_{Lm}$ Watts

 $Output Power = V_g I_{Lg} \quad Watts$

% Efficiency = <u>Output Power</u> * 100 Input Power

EXPECTED GRAPHS: -



Fig 4.2



5. BRAKE TEST ON D.C COMPOUND MOTOR

AIM: - To perform brake test on D.C Compound Motor and plot its performance characteristics.

THEORY: - The efficiencies of all D.C. machines can be computed in two ways:

1. Direct test

2. Indirect test

In direct method, the input and output power can be measured by suitable means and efficiency computed as a ratio of output to input.

The brake test is a direct load test. The D.C. machine under test is a compound motor provided with a brake drum. There is a suitable arrangement for loading the motor mechanically.

The D.C. motor is started under no load, taking necessary precautions by applying rated voltage V_s . It is brought to its rated speed. It is then loaded. Loading is gradually increased, and for each load, ammeter, voltmeter, spring balance readings and speed are noted. Loading is continued till motor draws rated current from supply mains. The motor is shut down. By finding circumference, the radius of the brake drum is computed.

Input	power=	V _S	L	W	atts	
-------	--------	----------------	---	---	------	--

Output power= $(2\pi NT/60)$ Watts

where V_S is the supply voltage in volts I_L is the line current in amperes. where N is speed in r.p.m. T is Torque in N-m.

Efficiency= (output/input)

So, % efficiency of the motor= (output/input) *100 A direct method is not used for large machines as:

- a. It may not be possible to provide the necessary load.
- b. Even if load is arranged, there would be enormous power loss during the test.

CIRCUIT DIAGRAM: -



APPARATUS: -

S No	Apparatus	Range	Quantity
1	Voltmeter	(0-300) V, MC	1
2	Ammeters	(0-20) A, MC	1
3	Rheostats	230Ω/1.7 A	1
		6.1Ω, 17.5A	1
4	Tachometer	(0-9999) rpm	1

NAME PLATE DETAILS: -

D.C Compound Motor:

K.W: Voltage: Current: Speed: Excitation Voltage: Excitation Current:

FUSE RATING CALCULATIONS: -

For No-Load: 10% of rated current of motor:

For Full-Load: 125 % of rated current of motor:

PROCEDURE: -

- 1. Connect the circuit as per the circuit diagram.
- 2. Keep armature rheostat in maximum position and field rheostat at minimum position.
- 3. Switch 'ON' the D.C. supply and start the motor with the help of 4-point starter.
- 4. Now, adjust the motor speed to rated value, with the help of armature rheostat, if rated speed is not reached then adjust the field rheostat.
- 5. Note down the no-load readings of voltmeter, Ammeter, and also speed of the motor.
- 6. Now, vary the load in steps by using load arrangement to rated current of the motor and at each step note down the readings of voltmeter, Ammeter, loads and also speed of the motor.
- 7. Remove the load slowly to zero position and switch 'OFF' the D.C. supply by making all devices to initial position.

PRECAUTIONS: -

- > Connections should be neat and tight.
- > Before starting of the motor water should be poured into brake drum.
- > Note down the readings without any parallax error.

OBSERVATION TABLE: -

S.NO	Lo L ₁ (Kg)	ads L ₂ (Kg)	Current I _L (Amps)	Voltage V (Volts)	Speed (N) (rpm)	Torque (T) (N-M)	Input (Watts)	Output (Watts)	η (%)

CALCULATION: -

Input = V I_L watts

Torque = $9.81 * r * (L_2-L_1)$ N-M [r = radius of the Brake drum]

Output = $\underline{2\Pi NT}$ watts 60

Efficiency = \underline{Output} X 100 Input

EXPECTED GRAPHS: -



Fig 5.2

RESULT: - Brake test on D.C Compound Motor is performed and plotted its performance characteristics.

6. HOPKINSON'S TEST ON D.C. SHUNT MACHINES

AIM: - To perform Hopkinson's test on two identical D.C. Shunt machines and predetermine their efficiencies.

THEORY: It is also called as regenerative or back-to-back test. In this method, full-load test can be carried out on two shunt machines preferably identical ones without wasting their outputs. The two machines are mechanically and electrically coupled and are so adjusted electrically that one of them runs as a motor and the other runs as a generator. The mechanical output of the motor drives the generator, and the electrical output of generator is used in supplying the greater part of input to the motor.

ADVANTAGES:

- 1. Power required for the test is small as compared to the full load powers of the two machines.
- 2. As machines are being tested under full-load conditions, the temperature rise, and the commutation qualities of the machines can be observed.

The only disadvantage is regarding the availability of two identical machines.

CIRCUIT DIAGRAM: -





APPARATUS: -

S No	Apparatus	Range	Quantity
1	Voltmeter	(0-300) V, MC	1
		(0-600) V, MC	1
2	Ammeters	(0-20) A, MC	2
		(0-1.5) A, MC	2
3	Rheostats	230Ω/1.7 A	2
		30 Ω/15 A	1
4	Tachometer	(0-9999) rpm	1

NAME PLATE DETAILS: -

D.C Shunt motor

D.C Shunt Generator

KW:KW:Voltage:Voltage:Load Current:Load Current:Speed:Speed:Excitation currentExcitation current:Excitation Voltage:Excitation Voltage:

FUSE RATING CALCULATIONS: -

For No-Load: 10% of rated current of motor:

For Full-Load: 125 % of rated current of motor:

PROCEDURE: -

- 1. Connect the circuit as per the circuit diagram.
- 2. Keep field rheostat of the motor in minimum position and armature rheostat of the motor in maximum position and keep field rheostat of the generator in maximum position.
- 3. Switch 'ON' the D.C. supply and start the M-G set with the help of 3-point starter.
- 4. Adjust the M-G set speed to rated value with the help of armature rheostat of the motor. If rated speed is not reached, then adjust the field rheostat of the motor.
- 5. Adjust the field rheostat of the generator till Voltmeter (V_1) reads zero volts.
- 6. When voltmeter ' V_1 ' reads zero volts close the Switch 'S'
- 7. Now, Increase the field current of the generator in steps with the help of field rheostat of the generator to rated current and at the same time decrease the field current of the motor with the help of field rheostat of the motor to maintain constant speed.
- 8. At each step note down the readings of voltmeter and Ammeter.
- 9. Switch 'OFF' the D.C. supply by making all devices to initial position.

PRECAUTIONS: -

- Connections should be neat and tight
- > Before starting of the M-G set check the positions of rheostats and also switch.
- > Note down the readings without any parallax error.

OBSERVATION TABLE: -

S.NO	Voltage V (Volts)	Line Curren t (Iı) (Amps)	I2 (Amps)	I ₃ (Amps)	I4 (Amps)	Stray Losses (Watts)	Generato r Losses (Watts)	Motor losses (Watts)	Motor Input (Watts)	Generato r output (watts)	ηм (%)	ηց (%)

 $I_1 = Line \ current$

 $I_2 = Armature \ current \ of \ the \ Generator$

 $I_3 =$ Shunt field current of the Motor

 $I_4 =$ Shunt field current of the Generator

CALCULATIONS: -

Motor Armature Copper Loss = $(I_1+I_2)^2 r_a$ Generator Armature Copper Loss = $I_2^2 r_a$

Power Drawn from The Supply = VI_1

Total Stray Losses for The Two Machines (W) = VI₁ – $[(I_1+I_2)^2r_a + I_2^2r_a]$

Stray Loss for Each Machine = W/2

MOTOR EFFICIENCY: -

 $\begin{array}{ll} Motor\ Input & = V(I_1+I_2)+VI_3\\ Motor\ Losses = Armature\ copper\ losses + Shunt\ field\ copper\ losses + stray\ losses\\ & = (I_1+I_2)^2R_A+VI_3+W/2 \end{array}$

 $\eta_{M} = \frac{Motor \ Input - Motor \ losses}{Motor \ input}$

GENERATOR EFFICIENCY: -

 $\begin{array}{l} Generator \; Output = VI_2 \\ Generator \; Losses = Armature \; copper \; loss + shunt \; field \; copper \; loss + stray \; losses \end{array}$



Fig 6.2

RESULT: - Hopkinson's test on two identical D.C. Shunt machines is performed and determined their efficiencies.

7. FIELD'S TEST ON DC SERIES MACHINES

AIM: - To determine the efficiency of the two DC series machines by conducting field's test.

THEORY: - Generally, Swinburne's test is the most popular testing method of dc machine to determine losses and efficiency. It is an indirect method of testing a dc machine performed without loading the machine. Since it is a no-load test, a series motor at no-load attains dangerously high speed. Hence, it is difficult to perform Swinburne's test on large series motors. Therefore, Swinburne's test is only applicable for dc shunt and small series machines. This drawback can be overcome by performing field test.

A field's test uses two similar dc series motors, which are mainly used for electric traction works. In field's test, two similar dc series machines with their field windings connected in series are used to determine losses and efficiency. The two machines are coupled mechanically in which one runs as a motor and the other as a generator driven by the motor. The electrical output from the generator is passed through variable load resistance R and dissipated as heat.

As they are rotating, they have frictional losses and constant losses. The iron and frictional losses of the two are made equal by, Exciting the machines equally, which is achieved by joining the series field winding of the generator with the motor armature circuit. Synchronizing the machines by running them at equal speed.

CIRCUIT DIAGRAM: -



Fig 7.1

APPARATUS:

S No	Apparatus	Range	Quantity
1	Voltmeter	(0-300) V, MC	2
2	Ammeters	(0-20) A, MC	2
3	Rheostats	30 Ω/15 A	1
4	Tachometer	(0-9999) rpm	1
5	Resistive Load	5kW, 20 A	1

NAME PLATE DETAILS:

D.C Series motor KW: Voltage: Load Current: Speed: D.C Series Generator KW: Voltage: Load Current: Speed:

FORMULAE: -

Let, V₁= Supply voltage, I₁= Motor current. V₂= Terminal potential difference of Generator. I₂= Load Current. Input of whole set=V₁ I₁= Output = V₂I₂ Total losses in the set (W_T) = (V₁ I₁ - V₂I₂) = Armature & Field copper losses (W_C) = (R_a + 2 R_{se}) $l_1^2 + l_2^2$ R_a = Stray Losses in Two Machines = (W_T - W_C) = W_S Stray Losses for each Machine = W_S / 2 Motor Efficience:

Motor Efficiency:

Motor Input = V_1I_1 = Motor Losses = I_1^2 ($R_a + Rse$) + W_S /2= % Motor Efficiency = { [$V_1I_1 - (I_1^2 (R_a + R_{se}) + C/2)$] / V_1I_1 } * 100=

Generator Efficiency:

Generator output = V₂I₂= Generator Losses = $l_1^2 R_{se} + l_2^2 R_a + W_S / 2 =$ % Generator Efficiency = {V₂I₂ / [V₂I₂ + ($l_1^2 R_{se} + l_2^2 R_a + W_S / 2$)]} * 100

Result: - Efficiencies of the two DC series machines are determined by conducting field's test on them.

8. SEPARATION OF LOSSES IN D.C SHUNT MOTOR

AIM: - To separate stray losses in a D.C. Shunt Motor.

THEORY: -

The various losses that occur in a D.C shunt machine are

Copper Losses: -

a) $I_a{}^2R_a$ the armature copper loss (30 to 40% of total full load losses)

b) Field copper losses $I_{sh}^2 R_{sh}$ in a shunt winding (20 to 30% of total load losses)

c) Loss due to brush contact resistance.

Stray Losses: -

a) Iron Losses: Hysteresis loss and Eddy current loss (20 to 30% of total full load losses)

b) Mechanical Losses: Friction at bearing and commutator, Windage of rotating armature (10 to 20% of full load losses)

Iron losses and mechanical losses are together called stray losses.

Iron Losses: - Iron losses are a function of both flux and speed.

Hysteresis Losses: - The hysteresis loss P_h is a measure of the electric energy required to overcome the retentivity of the iron in the magnetic flux path, using watts as unit,

$$P_h = K_h B^x f V$$

Where, V = volume of iron in dynamo subject to change of flux,

 K_h = constant for the grade of iron employed,

B = flux density raised to the Steinmetz exponent. Which modern values of dynamo x is no longer 1.6 but closer to 2.0. This Is not to imply that for a given volume, V, of iron the loss has increased, because Kh has been reduced considerably, and

f = frequency (hz) of reversal of flux.

Eddy Current Losses: - These losses occur not only in the dynamo iron but in all conductive materials with the flux path of the rotating or varying magnetic field of the dynamo. The eddy current loss Pe in watts is,

$$P_e = K_e t^2 B^2 f^2 V$$

Where, $K_e = an$ eddy current constant for the grade of iron employed,

t = thickness of the laminations of the pole core and armature

B = flux density

f = frequency (hz) of reversal of flux

V = volume of iron subject to change of flux.

For a D.C dynamo the frequency, f, reversal of flux varies with speed. Thus the hysteresis loss varies directly with speed, where as the eddy current loss varies as the square of speed. Both hysteresis loss and eddy current loss vary approximately as the square of the flux density. For this reason core losses are

considered a function of both flux and speed.

Mechanical (or friction) Losses:- When a machine is running, there are various frictional forces to be overcome, each of which requires a continuous expenditure of energy and results in heating the rubbed parts. There is friction loss in the machine bearings, at the surface of the commutator due to the rubbing of the brushes, and in the armature core due to its fanning action. These losses depend upon the speed but are independent of the load on the machine. They are difficult to estimate by direct calculation but may be found by measurement.

CIRCUIT DIAGRAM: -



Fig 8.1

APPARATUS: -

S No	Apparatus	Range	Quantity
1	Voltmeter	(0-300) V, MC	1
2	Ammeters	(0-1.5) A, MC	1
		(0-3) A, MC	1
3	Rheostats	230Ω/1.7 A	2
4	Tachometer	(0-9999) rpm	1

NAME PLATE DETAILS: -

D.C Shunt Motor:

K.W: Voltage: Current: Speed: Excitation Voltage: Excitation Current:

FUSE RATING CALCULATIONS: -

For No-Load: 10% of rated current of motor:

For Full-Load: 125 % of rated current of motor:

PROCEDURE: -

- 1. Connect the circuit as per the circuit diagram.
- 2. Keep armature rheostat in maximum position and field rheostat at minimum position.
- 3. Switch 'ON' the D.C supply and start the Motor with the help of 3-point starter.
- 4. Adjust the speed of the Motor to rated value with the help of armature rheostat, if rated speed is not reached then adjust the field rheostat.
- 5. note down the readings of voltmeter, ammeters and speed of the motor.
- 6. Keep field current constant at normal value and vary the speed of motor in steps to lower value say 650 rpm with the help of armature rheostat.
- 7. At each step note down the readings of voltmeter, ammeters and speed of the motor.
- 8. Now, again bring the motor speed to rated value with the help of armature rheostat and keep field current constant at ³/₄ th of normal value and note down the readings of voltmeter, ammeters and speed of the motor.
- 9. Vary the speed of motor in steps to lower value say 650 rpm with the help of armature rheostat and at each step note down the readings of voltmeter, ammeters and speed of the motor.
- 10. Switch 'OFF' the D.C Supply by making all devices to initial position

PRECAUTIONS: -

- Connections should be neat and tight.
- ▶ Note down the readings without any parallax error.
- > Before starting of the Motor check the rheostat position properly.

OBSERVATION TABLE: -

At Normal field current ($I_{fl} = A$)

S.No	E _b (Volts)	I _a (Amps)	N (RPM)	W _S (Watts)	<u>Ws</u> N	W _h (Watts)	W _e (Watts)	W _f (Watts)	W _w (Watts)

At $\frac{3}{4}$ th of Normal field current (I_{f2} = A)

S.No	E _b (Volts)	I _a (Amps)	N (RPM)	Ws (Watts)	<u>Ws</u> N	W _h ' (Watts)	W _e ' (Watts)	W _f (Watts)	W _w (Watts)

CALCULATIONS: -

Stray losses $(W_S) = E_b Ia$

At Normal Field Current:

Hysteresis loss (W_h) \propto (Φ)^{1.6}N

 $W_h = AN (\Phi' = Constant)$

Eddy Current loss $(W_e) \propto (\Phi)^2 N^2$

 $W_e = BN^2$ (' Φ ' = Constant)

Iron losses $(W_i) = W_h + W_e$

 $W_i = AN + BN^2 \\$

Friction loss (W_f) \propto N

 $W_{\rm f} = CN$

Windage loss $(W_w) \propto N^2$

$$W_w = DN^2$$

Mechanical losses $(W_m) = W_f + W_w$

$$W_m = CN + DN^2$$

Stray losses $(W_S) = W_i + W_m$

$$\begin{split} W_S &= AN + BN^2 + CN + DN^2 \\ &= (A+C) \ N + (B+D) \ N^2 \end{split}$$

At ³⁄₄ th of Normal Field Current:

$$\begin{split} W_{h}^{'} &= A'N \\ W_{e}^{'} &= B'N^{2} \\ W_{f} &= CN \\ W_{w} &= DN^{2} \\ \end{split} \\ W_{S} &= A' N + B' N^{2} + CN + DN^{2} \\ W_{S} / N &= (A' + C) + (B' + D) N \quad ----- \quad At \quad ^{3}\!\!\!/ 4 \ ^{th} \ of \ Normal \ field \ current \\ A/A' &= (\Phi/\Phi')^{1.6} = (I_{fl}/I_{f2})^{1.6} \quad ----- \quad (1) \\ B/B' &= (\Phi/\Phi')^{2} = (I_{fl}/I_{f2})^{2} \quad ------ \quad (2) \end{split}$$

Determine (A + C), (A' + C), (B + D) and (B' + D) from the graph.

Determine A, B, C, D, A' and B' constants using eq-1, eq-2, and with above determined values.



Fig 8.2



9. RETARDATION TEST ON DC SHUNT MOTOR

AIM: - To separate the mechanical and iron losses of the given dc shunt machine.

THEORY: -

Another name for this test is running down test. In this method of testing, firstly motor is speeded up slightly above its rated speed and supply is cut off. Then starting the stopwatch till the speed come to below the rated speed. Speed time curve is drawn for various values of speed to obtain rate of change of speed. Secondly, by attaching flywheel of known moment of inertia to motor taking the reading for various values of speed to draw the speed time curve to obtain rate of change of speed, then by calculating moment of inertia of motor rotational losses can be found.

CIRCUIT DIAGRAM: -



Fig 9.1

APPARATUS REQUIRED: -

S No	Apparatus	Range	Quantity
1	Voltmeter	(0-300) V, MC	1
2	Ammeters	(0-2) A, MC	2
3	Rheostats	370Ω/1.7 A	2
4	Tachometer	(0-9999) rpm	1

NAME PLATE DETAILS: -

D.C Shunt Motor:

K.W: Voltage: Current: Speed: Excitation Current: Excitation Voltage:

FUSE RATING CALCULATIONS: -

For No-Load: 10% of rated current of motor:

For Full-Load: 125 % of rated current of motor:

PROCEDURE: -

- 1. Connections are made as per the circuit diagram.
- 2. Initially the switch S_2 is open and S_1 is closed then the motor is started with the help of three point starter.
- 3. The speed is adjusted to just above the rated speed by adjusting the field rheostat.
- 4. The voltage is noted then switch S_1 is opened and note down the time taken to reach the armature voltage to a voltage of 25% less than the initial value.
- 5. Again S_1 is closed immediately before the motor reaches to zero speed and rheostats are adjusted until the motor reaches its rated speed.
- 6. Then S_1 is opened and at a time S_2 is closed at this instant record the readings of ammeter and also note down the time taken to reach the armature voltage to a voltage of 25% less than the initial voltage.

PRECAUTIONS: -

- 1. Take care while using the starter.
- 2. The speed should be adjusted to rated speed.
- 3. There should be no loose connections.

OBSERVATION TABLE: -

$S_1 \ close \ and \ S_2 \ open$

S No	Vs (Volts)	I _f (A)	Time (t1)

$S_1 \mbox{ open at a time } S_2 \mbox{ close }$

S No	Va (Volts)	I _a (A)	Time (t2)

CALCULATIONS: -

Rotational losses or stray losses ${}_{2}P_{S} = P^{-1}$ (t /t -t) $P_{S}^{-1} = V_{avg^{*} Lavg}$ Input power = V I_L I_L = full load current of the motor Armature cu losses = Ia²Ra Ia = I_L-I_f Total losses = Armature cu losses + Stray lossesOutput power=Input -Total losses Motor efficiency $\dot{\eta}$ = output/input.

RESULT: - mechanical and iron losses are separated for a given dc shunt machine.

10. SPEED CONTROL OF D.C SHUNT MOTOR

AIM: - To study the variation of speed of a D.C Shunt motor by varying Voltage across the armature and shunt field current.

THEORY:

For a given motor, the factors which influence the speed of the motor are applied voltage, armature resistance and field current (or) flux per pole. So, there are three methods of speed control-

a. Voltage control method

- b. Armature control method
- c. Flux control method

ARMATURE CONTROL METHOD:

This method is also termed as Rheostatic control method. In this method, resistance of armature circuit is varied by introducing a variable resistance into the armature circuit.

With the variable resistance R fully cut in, it is observed that the speed is minimum. When R is maximum, there is maximum voltage drop across it and voltage across the motor armature is minimum. Hence, speed is minimum.

As R is cut put, more voltage gets applied across armature, and speed progressively increases. When R is fully cut out, the rated voltage V gets applied across the armature and motor would attain its rated no-load speed.

In this method, only speeds below the rated speed can be obtained. The demerit of this method is that there is considerable power loss as long as R is in the armature circuit.

FIELD CONTROL METHOD:

In this method of speed control, a variable resistance is incorporated in the field circuit. With the resistance R fully cut out, the speed is minimum (equal to rated speed) since field current is maximum and maximum flux is produced.

As resistance R is cut in more and more, less and less current flows through field windings. Hence, flux decreases more and more, with the result that speed increases progressively.

In this method, only speeds above the rated speed can be obtained. The power loss due to R is quite small since field current is generally small.
CIRCUIT DIAGRAM: -



3.

Fig 10.1

APPARATUS: -

S No	Apparatus	Range	Quantity
1	Voltmeter	(0-300) V, MC	1
2	Ammeters	(0-1.5) A, MC	1
3	Rheostats	230Ω/1.7 A	2
4	Tachometer	(0-9999) rpm	1

NAME PLATE DETAILS: -

D.C Shunt Motor:

K.W: Voltage: Current: Speed: Excitation Current: Excitation Voltage:

FUSE RATING CALCULATIONS: -

For No-Load: 10% of rated current of motor:

For Full-Load: 125 % of rated current of motor:

PROCEDURE: -

- 1. Connect the circuit as per the circuit diagram.
- 2. Keep armature rheostat in maximum position and field rheostat in minimum position.
- 3. Switch 'ON' the D.C supply and start the Motor with the help of 3-point starter.
- 4. Adjust the speed of the Motor to rated value with the help of armature rheostat, if rated speed is not reached then adjust the field rheostat.

Armature control method: -

- In armature control method keep shunt field current constant and vary the voltage across armature in steps to 1200 r.p.m with the help of armature rheostat.
- At each step note down the readings of speed and voltage across armature (E_b).

Field control method: -

- In field control method bring the Motor speed to rated value and keep the voltage across armature constant.
- Now, vary the shunt field current in steps to 1800 r.p.m with the help of field rheostat and at each step note down the readings of speed and shunt field current.
- Switch 'OFF' the D.C supply by making all devices to initial position.

PRECAUTIONS: -

- Connections should be neat and tight.
- > Note down the readings without any parallax error.
- > Before starting of the Motor check the rheostat position properly.

OBSERVATION TABLE: -

ARMATURE CONTROL METHOD ($I_f = constant$)

S.NO	E _b (VOLTS)	SPEED(N) (RPM)					

FIELD CONTROL METHOD

 $(E_b = constant)$

S.NO	Field current (I _f) (AMPS)	SPEED(N) (RPM)

EXPECTED GRAPHS: -



Fig 10.2

RESULT: - Variation of speed of a D.C Shunt motor is studied by armature control and shunt field current methods.

11. SWINBURNE'S TEST ON D.C SHUNT MACHINE

AIM: - To perform Swinburne's test on D.C Shunt Motor and predetermine the efficiency of a D.C. Shunt machine when it is working as a Motor and as a Generator.

THEORY:

Swinburne's test or no-load test is a simple method in which losses are measured separately and from their knowledge, efficiency at any desired load can be predetermined in advance. However, this test is applicable to those machines in which flux is practically constant i.e. shunt and compound-wound machines. The machine is run as a motor on no load at its rated voltage and rated speed. The speed is adjusted with the help of shunt regulator and note the reading of no load armature and shunt field current. The load line current

 $I_{L}=I_{a}$ - I_{sh} for generator $I_{L}=I_{a}+I_{sh}$ for motor.

This test is convenient and economical because power required to test a large machine small i.e. only no load input power. In this test, since constant losses are known. The efficiency of the D.C. machine can be predetermined at any load.

CIRCUIT DIAGRAM: -



Fig 11.1

APPARATUS: -

S No	Apparatus	Range	Quantity
1	Voltmeter	(0-300) V, MC	1
2	Ammeters	(0-3) A, MC	1
		(0-1.5) A, MC	1
3	Rheostats	230Ω/1.7 A	2
4	Tachometer	(0-9999) rpm	1

NAME PLATE DETAILS: -

D.C Shunt Motor:

K.W: Voltage: Load Current: Speed: Excitation Current: Excitation Voltage:

FUSE RATING CALCULATIONS: -

For No-Load: 10% of rated current of motor:

For Full-Load: 125 % of rated current of motor:

PROCEDURE: -

- 1. Connect the circuit as per the circuit diagram as shown in fig.
- 2. Keep armature rheostat in maximum position and field rheostat at minimum position.
- 3. Switch 'ON' the D.C supply and start the motor with the help of 3-point starter.
- 4. Adjust the speed of the Motor to rated value with the help of armature rheostat, if rated speed is not reached then adjust the field rheostat.
- 5. Note down the no-load readings of voltmeter and ammeters.
- 6. Switch 'OFF' the D.C. supply by making all devices to initial position.

PRECAUTIONS: -

- Connections should be neat and tight
- Before starting of the motor ensure that there is no-load on the motor and also check rheostat position properly.
- > Note down the readings without any parallax error.

OBSERVATION TABLE: -

No-load Readings: -

 $V = I_{a0} = I_{Sh} =$

CALCULATION: -

No-load Input = VI_{L0}

 $\left(I_{L0}=I_{a0}+I_{sh}\right)$

No-load Armature cu.loss = $I_{ao}^2 R_a$

Constant losses (Wc) = $VI_{L0} - I_{a0}^2R_a$

As a Motor: -

Load input = $X V I_L$ [Where, x = load factor]

Armature cu.loss = $I_a^2 R_a$

 $I_a = X I_L - I_{sh} \\$

Total losses = $W_c + I_a^2 R_a$

 $\eta_{M} = \frac{Input - Total \ losses}{Input} * 100$

S.No	IL (Amps)	V (V)	I _{Sh} (Amps)	Ia (Amps)	$I_a^2 R_a$ (Watts)	Total Losses (Watts)	Input (Watts)	Output (Watts)	η (%)

As a Generator: -

Load Output = $X VI_L$ [Where, x = load factor]

Armature cu.loss = $I_a^2 R_a$

 $Ia=XI_{\rm L}+I_{sh}$

Total losses = $W_c + I_a^2 R_a$

 $\eta_G = \underbrace{Output}_{Output + Total \ losses} * 100$

S.No	I _L (Amps)	V (V)	I _{Sh} (Amps)	I _a (Amps)	Ia ² Ra (Watts)	Ia2RaTotalInputOu(Watts)Losses(Watts)(W					

EXPECTED GRAPHS: -



Fig 11.2

RESULT: - Swinburne's test on D.C Shunt Motor is performed and predetermine the efficiency of a D.C. Shunt machine when it is working as a Motor and as a Generator.

12. BRAKE TEST ON D.C SHUNT MOTOR

AIM: - To perform brake test on D.C Shunt Motor and draw its performance characteristics.

THEORY: The efficiencies of all D.C. machines can be computed in two ways:

- a. Direct test
- b. Indirect test

In direct method, the input and output power can be measured by suitable means and efficiency computed as a ratio of output to input.

The brake test is a direct load test. The D.C. machine under test is a shunt motor provided with a brake drum. There is a suitable arrangement for loading the motor mechanically.

The D.C. motor is started under no load, taking necessary precautions by applying rated voltage V_s . It is brought to its rated speed. It is then loaded. Loading is gradually increased, and for each load, ammeter, voltmeter, spring balance readings and speed are noted. Loading is continued till motor draws rated current from supply mains. The motor is shut down. By finding circumference, the radius of the brake drum is computed.

Input power= $V_{S}I_{L}$ Watts	where V_s is the supply voltage in volts
	I_L is the line current in amperes.
Output power= $(2\pi NT/60)$ Watts	where N is speed in r.p.m.
	T is Torque in N-m.

Efficiency= (output/input)

So, % efficiency of the motor= (output/input) *100

A direct method is not used for large machines as:

1. It may not be possible to provide the necessary load.

2. Even if load is arranged, there would be enormous power loss during the test.

CIRCUIT DIAGRAM: -



APPARATUS: -

S No	Apparatus	Range	Quantity
1	Voltmeter	(0-300) V, MC	1
2	Ammeters	(0-20) A, MC	1
3	Rheostats	230Ω/1.7 A	1
		6.1Ω, 17.5A	1
4	Tachometer	(0-9999) rpm	1

NAME PLATE DETAILS: -

D.C Shunt Motor:

K.W: Voltage: Load Current: Speed: Excitation Voltage: Excitation Current:

FUSE RATING CALCULATIONS: -

For No-Load: 10% of rated current of motor:

For Full-Load: 125 % of rated current of motor:

PROCEDURE: -

- 1. Connect the circuit as per the circuit diagram.
- 2. Keep armature rheostat in maximum position and field rheostat at minimum position.
- 3. Switch 'ON' the D.C supply and start the motor with the help of 3-point Starter.
- 4. Now, adjust the motor speed to rated value with the help of armature rheostat, if rated speed is not reached then adjust the field rheostat.
- 5. Note down the no-load readings of input voltage and line current and speed of the motor.
- 6. Now, vary the load in steps by using load arrangement to rated current of the motor and at each step note down the readings of the voltmeter, Ammeter, loads and speed of the motor.
- 7. Remove the load slowly to zero position and switch 'OFF' D.C Supply by making all devices to initial position.

PRECAUTIONS: -

- Connections should be neat and tight.
- > Before starting of the motor water should be poured into Brake drum.

> Note down the readings without any parallax error.

OBSERVATION TABLE: -

	Lo	ad	Current	Voltage	Sneed	Torque				
S.NO	L ₁ (Kg)	L2 (Kg)	IL (Amps)	V (Volts)	(N) (rpm)	(T) (N-M)	Input (Watts)	Output (Watts)	η (%)	

CALCULATION: -

 $Input = V * I_L Watts$

Torque = $9.81 * r * (L_2-L_1)$ N-M [r= radius of the Brake drum]

Output = $(2\Pi NT) / 60$ watts

% Efficiency = (Output / Input) * 100

EXPECTED GRAPHS: -









VIDYA JYOTHI INSTITUTE OF TECHNOLOGY

(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanenty Affiliated to JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad - 500 075. Phone: Off. 76 76 637 637 Fax: 08413 - 235509 e-mail : info@vjit.ac.in www.vjit.ac.in





PRACTICAL RECORD BOOK

Academic year 202 -2022 Name: G. Kalyan Roll No: 19911 AO 229 Course: R. Steck Year/Sem Jugan Dem Subject: KM-TLa





XINDEX

S. No	et s@ man	Name of the EtnemineqxE and to emaN	Page No.	s: Ncexhander	
15	3/8/21	Magnetization Characteristic		(A)	
		OF DC Shunt Generator	26051	10/8 (202)	
2.	3/8/21	Swinburne's Test on	6	()	
		De Shunt Machines	0 (010	5/01/20	1
s.	5/8/21	Speed Control of DC	116014	A	
		Shunt Motor.		13/081	Tor
لو،	5/8/21	Load Test on DC Compound	126018	Delde	
		Generator.		13/8/20	2)
2.	7 8 21	Load Test on DC Shunt	196022	Blead	y
		Generator		V3/8/	Jost
6.	718121	Brake Test on DC Compound	232026	Spelde	1 - 24
y	1	Motor.		< € € € € 	()
7.	1018/21	Separation of Losses in	27603)	FILM	
₹.	1010101	De shunt motor.		R	
		Hopkinson's lest on DC Shunt	324035	tota	
٩.	10/8/21	Lood Terry DI San		1 2/8/21	
		Grenerator	-36 to31	(A)	
10.	10/8/21	Freid Test on DC Same	yotal	t bin	
		macherec	1, 104	1,001,	
		in the s			

										ω	2	2	2.	26	25	24	23	22	21		No				Z				
40	39	38	37	36	35	34	33	32	31	30 1	9 1	8	7 1	5 19	5 19	19	19	19	19						ame			(Gh	i. T
1991	1991	19911	1991	19911	19911	19911	19911	19911	19911	9911	9911	9911/	9911/	9911A	911A	911A	911A	911A	911A		umb	Roll			of th		Ì		
IA024	IA024	IA023	IA023	A023	A023	A023	A023	A023:	A023	A0231	A0230	A0229	10228	0227	0226	0225	0224	0223	0222		e r			Mac	e Lal		De	<	
19	9	50	1 8	7 9	1 9	215	4 9	3 9	2 10	01	4	9	0	Ò	_0		Л	٩	10	1				hines	borat		epa	'idy	
	10	0		9	0		P	9	9	01	5	10	0	11	5		4	٥	10	2				ľ	ory: l		rtm	â	
0	10	0	0	. 1		2	.1	q	9	a	ט	9	q	0	0		4	æ	10	3					Electr		ent		-
0			0	1		0	4	9	9	10	-1	S		T L	ø		5	50	10	4					ical		of E	thi Accre	
	1	S 	0	0 ~	1		a,	0	~	1	7 6	9	0	~	9		5	9		5				Bra			Elec	lins dited t	un of the second
0	0	0	0			9	8	80	0	0 10	6	藩	0	+1	0		0	0	0	6				inch/S			tric	DY NA	iton
8	0	9		00	9		8	9	0	0	03	9	0		0		0.	0					Da	Sectio			al a		
Ľ	0	0	0	P	9	0	a				5	9	8	00			5		6	7	1		ty to	n: A			inagar		
9	б	9	б	80	9	0	S	<i>a</i>		0	6	9	9	00			5	P	9	8	Wee		Day A			E	Gate		ni & D
	Ð	٥	5	S	٥	0	ø	٩	٩	10	6	9	ō	P	9		0	10.	6	9	k		SSessi			BA B	ctrc	ACTE	w Dell
ę	0	0	0	Ð	0	0	Ø	0	0	0	0	a	9	P.	9		0	٥	10	10			ment			SES	onic	New	
ς	÷		5	r				* ,	1.		r).					2	л 			11	n.,					SME	Ü Hyder ∏Ter	Delhi &	te o c
	3		d	5		s				ò		~				с. С	9			12			i.			Z T	ngi	4 Pern	lar Ga
			1.	÷		· · ·		~		÷.						3				13				Yeau			500 07	uddy .	ziznag
		. 1				· ·	2	- .			-							2a		14				r/Sem		Ċ	ring	ATT	Cal
,					1															15				: II-I				for pe	ctri
		2			-			Э.			-				ал. Т					16							CCre		911
	_			×.,	~							1									A M	Ī	Da				dite	it of	5
0	0	U	9	00	0	0	8	0	•	0	с С	-0	9	200	2		6	20	0		ient)ay	y To			1	db	her	i.
لم	T	5	ġ	4	T	d'	E .	e L	5	1	Ì	2	5	9ª	ס		ŕ	ŕ	÷		Marl	(S)	Dann	Page:			X N	Dart	
					-							No.									ks N						BP	Dep	1
90	10	09	10	90	99	09	8	90	0	0	% %	99	0	99	10	1 2	80	10	01		(10) Iarks	Exam	iterna						here
مح	29	20	R	80	2	R9 R9	29	20	25	24	18	20	24	21	24		18	20	2.0		Mai	T	-				ľ		le of
W	Ĺ	Ŵ																	1		rks 25	otal					1	;	Nan



Title: Magnetization (Characteristics Date: 3/8/2/ Page No.: 2						
Armi							
To plot the Open	Circuit Characteristics of						
DC Generator and also determine its Critical Field							
resistance and crite	cal speed.						
Apparatus Required:							
1. Voltmeter	(0-300) V MC 2NO'S						
2. Ammeter	(0-1.5)A MC INO						
3. Rheostat	230~, 107 A 2NO'S						
	100~,7A INO						
4. Techometer	Analog Digital INO						
Name Plate Details:							
De Shunt Motor :	DC Shunt Generator:						
Kow: 5.2	K.w? 3.7						
Voltage: 220V	Voltage: 220V						
Current: 27.5A	Current . 16.00						
Speed : 1500rpm							
Excitation Currents	speed: 1500 mm						
Example of the second sec	. OJA Excitation Current: 0.92A						
Lx Cababion Voltage: 2	-20V Excitation Voltage: 226V						

Tabular Column:

5.NO	EB(VOIES)	IFOMPS	Speed (rpm)
١.	8×5	0.02	1200
2	50×J	6. 1	1500 800
3	40×2	6.2	1500
ч.	60x2	0.3	1500 50 1000000
5-	80×J	0.44	1200
6.	110x2	0-6	1500
		2 Second St	

Expected Graph:



Date : $\mathfrak{G}/\mathfrak{F}/\mathfrak{P}$ Page No. : 3

Theory :

The performance of the electrical machines can be Found out by their Characteristic Curves. The magnetization is also known as notoad Saturation Characteristic Curves. It is drawn between no-load generated emf in armature (Eo) and the Field Current (If) at given Fixed Speed.

Critical Field Resistance. It is the Cutoff resistance beyond which the generator fails to generate emf. To Find the Critical Resistance drawa tangent to the Occ curve from its initial position. The Spe of the resistance curve gives the Critical resistance.

Critical Speed: Critical Speed is the minimum speed below which the generator Fails to buildup the voltage The critical speed of a generator can also be easily Found the From the OCC Curves easily.

Title :



Procedure:

1. Connect the Corcuit as per the Circuit dragram.

2. Keep armature Theostat of the motor in maximum position and Field Theostat of the motor in minimum position and also keep Field Theostat of the generators in maximum position.

3. Switch ON the De Supply and Start the MG set to rated value with the help of armature rheostet of the motor, "Frated Speed is not reached then adjust the Field rheostat of the motor.

4. Adjustine speed of the MG set to rated value with the help of armature rheostet of the motor, if rated speed is not reached then adjust the Field rheostat of the motor.

5. when MG Set rotates at rated Speed a small reading is Observed in the Voltmeter even though there is no current in the Field winding. In this case Notedown the readings of Voltmeter and Anneter.

Title :



	Date :	118/21
Title :	Dale .	.21116
	Page No. :	5

6. Now vary the Field rheostat of the Generator in Steps to rated voltage and at each Step note down the readings of Voltmeter and Anneter.

I Switch OFF the DC Supply of Mich Set by making all devices to initial position.

Pre cautionsi

1. Connections should be neat and tight.

2. Before Starting of the MG Set Check the Theostats positions properly.

3. Note down the readings without any parallax error.

Result?

Open Circuit Characteristics of DC Shunt generator has been Verified and Critical Field resistance and Critical Speed has been Venfied and determined.



CIVILIE DIAGTAM

Title: SWINBURNE'S TEST ON DC SHUNT Date : 58 MACHINE Page No.: 6

Ann:

To perform Swinburne's test on DC Shunt motor and predetermine the efficiency of a DC Shunt machine when it is working as a motor and as a generator.

2

Apparotus Required:

١.	Voltmeter	Q-300) v 19C	100
2.	Anneter	(0-3)A MIC (0-1-5)A MIC	IND
3.	Rheastat	2300, 1.7A	INO
		100~, 5A	INO

4. Tachometer Analog (100 Digital

Name Plate Details:

DC Emint Motor: K.W: 3.5 Voltage: 2200 Load Current: 18.6A Speed: 1500rpm Excetation Current: 0.9A Excitation Voltage: 2200

	Johod Readings	V= 710× 2=220V	100 = 0.79×2= 1.56 A	TLO = 2.16A	ringture redicton ce	Ra= 0.48	The formed and the second seco
					4		A server start and a server server and a server s
	رج، م	20. (97. Et	or or Tr	2000		Norman and Anna Anna Anna Anna Anna Anna Ann
	Dutgut	3301.66	10.994	5421-52	34.2		
	Topt	4082	2046	3069	1023		
	Total Losses	19033	66.942	てわらいの	88.W r		and in such a new of
	Tarka	しいてい	ti. nt	19-5 E	Earg		
	T (MMR)	61	t-8	13.37	1-0-5	-	Section 1.
2 1 > 0	ST I	2 6	<i>o</i> - <i>c</i>	9 0	9.0		
M° LL	(Volte)	077	077	220	520		
	J L (refine)	9.81	5.0	19.21	4.61		
	N 0	-	0	3	۶		

Tabular Column:

Date : 5 8 2 Page No. : 7

Theory :

Swinburne's Test is a Simple method in which losses are measured Separately and From their knowledge, efficiency at any desired load Can be predetermined in advance. However, this test is applicable to those machines in which Flux is practically constant i.e Shunt and Compound wound machines. The machine is run as a motor on noload its rated voltage and rated Specid. The Speed is adjusted with the help of Shunt regulator and note down the readings of no load armature and Shunt Field Current. The Load Line Current Ic = Iq - Ish Generator Ic = Iqt Ish Motor.

This test is convenient and economical becauce power required to test a large machine small ine only ho load input power. In this test since constant losses are known. The efficiency of the DC machine can be predetermined at any load.

Title :

Expected



	5	5	83.01	+2.54	0.18	tity			- 3 (1)-1		2.14		е 1	
	Output	(mor re)	4092	2046	3069	1023		Q	, - · ·	17 M		D j		
A.	Trput	(motts)	۲۹۹۲	673.9	J.PET	607.11	4 4.		. 2 4 - 12	- 5- E	2 - 2 - 2 - 0		i " O i "?"	
م رمار	Total	(Water)	to her	562.25	679.9J	499.32			• -	к ⁹ •	E.J.			
0-10-10	Larka Larka	(matt)	361.26	40.94	361.26	7 4.01								
اوہ و رہ	H	(North)	1.61	٩.٩	5	Silt	-	9, 1			,	0 · · ·		
9	L C C		90	0.60	ۍ ض	و ف								
	(201 C)		310	022	110	072								
	JL		6.6	en G	13.95	بله م نو	1							
ļ	02.5		2	à	0	ż								

Tabular Column

Date : 🔊 🖁

Procedure:

1. Connect the Carcuit as per the Carcuit diagram as Shaph in Figli

2. Keep armature rheostat in maximum position and Field rheostat at minimum position.

3. Switch ON the DC Supply and Start the motor with the help of 3-point Starter.

4. Adjust the Speed of the Motor to reted value with the help of armature rhedstat, if rated speed his not reached then adjust the Field rhedstat.

5. Note down the noload readings of voltmeter and anneter.

6 Switch OFF the DC Supply by making all devices to initial position.

Procedure For Finding Amature Resistance (Re):

1. Connect the Circuit as per the Circuit diagram as shown in Figz. 2. Do switch on the DC Supply and very the

Voltage across armature in Steps but should not

Title :

$$\begin{aligned} \text{Calculations:} \\ \text{No-Load II}[p: VILO \\ ILO = Iap + Ish \\ No Load armature \\ (uloss = Iap Raci (156) Rod (156) \\ = 2.38 \\ Canstant (0 Eses (200) = 1 \\ Ulos = 1ap Raci (156) Rod (156) \\ = 2.38 \\ Canstant (0 Eses (200) = 1 \\ Ulos = 1ap Raci (156) Raci (156) \\ Ulos = 1ap Raci (156) Raci (156) \\ Ulos = 1ap Raci (156) Raci (156) \\ Ulos = 1ap Raci (156) \\ = 1$$

Title :

exceed rated voltage.

3. Switch on the DC supply and]

3. At each Step note down the readings of Voltmeter and Ammeter.

4. Now calculate the armature Resistance (Ra)

by using given Formula Re = V Iq

5. Exact armature resistance (Ra) value is Obtained by taking mean of the readings.

Precautions:

1. Connections should be neat and tight

2. Before Starting of the motor ensure that there is no load on the motor. and also check

Theostat position properly, 3. Notedown the readings without any parallax error.

Generator?

$$I_{0} = I_{1} + I_{Sh}$$

$$I_{q} = 18.6 + 1 = 19.6 A$$
Fullload?
Soad output = X V I_{1} = 409100
What = I_{q}^{2} R_{q} = 345.74400

$$I_{0} = XI_{1} + T_{3h} = 1X18.641$$

$$= 19.6 A$$
To tallosses = what was
 $T_{0} tallosses = what was$

$$T_{0} tallosses = what was
 $T_{0} tallosses = what was$

$$I_{0} = \frac{0|p}{0|p + T_{1}} \times 100$$

$$VFull = 81.574.12$$
X Load -3
Load output = $\frac{1}{2}t = 204600$
What = I_{0}^{2}p = 95.48100
Totallosses = what was

$$I_{0} = I_{2} + I_{3h} = 10.300$$
Totallosses = what was

$$T_{0} = \frac{1006}{2006 + 673.861}$$
May = $\frac{1006}{2006 + 673.861}$$$

3/4 Load:
Load Output =
$$VI_{1}x^{3}/4$$

= 3069 w
Armature Culoss
 $V_{1}x = Ia^{2}Rq$
 $Iq = I_{1}x^{2}q + I_{3}h = 14.95A$
 $wcu = (4.95)^{2}v 0.9 = 201.152w$
Total losses = $wc+wcu$
 $= 779.532w$
 $V_{2}/4 = 3069$
 $V_{2}/4 = 1023 w cu = Iq^{2}Rq$
 $Iw = I_{1} + I_{3}h = 5.65A$
 $V_{1}w = (5.5)^{2}(0.9) = 19.33w$
Total losses = $wc + wcu$
 $= 609.11w$
 $V_{1}/4 = 1023 w (00)$
 $V_{1}/4 = 1023 w (00)$
 $V_{1}/4 = 61.75\%$



Title :

Date : 311 7 Page No. : 10

Result?

The experiment of the given DL machine was done and determined the efficiency of Full, 3/4, 1/2, 1/4 Loads when machine is working as generator as well as motor and neccessary graph were drawn.



Title: Speed Control OF DC Shunt Motor; Page No.: 11

A٩	3	•
		•

To Study the variation of Speed of a DC Shunt motor by varying voitage across the armature and Shunt Field Current

Apparetus Required?

1.	voltmeter	6-300)~	MC	1100
1-	Ammeter	(0-1-5)~	MC	100
રુ.	Rheostat	230~,1-7A		500,0

4. Tachometer Analog Digital 1

Name Plate Details!

DC Shunt Motor ! K. W : 3.F

Excitation Current: 0.6A Excitation voltage: 2200

20 ×18.6 = 3.72A

125 × 18-6=23.25 A


Date : 51PM Page No.: 12

Theory:

Armature Control Method:

This method is also termed as Rheostatic Control method. In this method resistance of armature circuit is varied by introducing a variable resistance anto the armature circuit.

with the Variable Resistance RFully Cutin, it is observed that the speed is minimum. when Ris mammum there is maximum drop across it and voltage across the motor armature is minimum Hence Speed is minimum.

Field Control Method: In this method of Speed Control a Variable resistance is incorporated in the Field Current. with the resistance R Fully what the Speed is minimum Since Field Current is maximum and maximum Flux

is produced.

Tabular (olumn:

Armature Control Method

2.12

TE=0.48 Constant

and should be a set of

8.NO	Eb (Voits)	Speed(N)
Υ.,	110×2)500 mar
2	104×2, 100	1400 and the second
3	100x2	1300 a crapt an and
4	95x2	1200 production alla

Field Control Method:

La parte su Field Current (h) poods 5.00 IF(Ampi) udr 0.48 1 500 ١ 0.44 2 1600 U 3 0.32 1700 4 1800 0.2

1. Connect the Circuit as per the Circuit diagram. 2. Keep armature theostat in maximum position and Field theostat in minance theostat. position. 3. Switch on the DC supply and start the Motor with the help of 3 point Starter. 4. Adjust the Speed of the motor to reted value with the help of armeture rheostat, if rated speed is not reached then adjust the Field Theostat. Armature Control Methods 1. In this method keep shunt Field Current Constant and vary the voltage across armature in steps to 1200 rpm with the help of armature shealtat At each step note down the readings of speed 2. and voilage across armature (Eb).

Title :

Procedure:

Speed Control of DC shunt motor



Date : $\int \langle \langle \rangle \rangle$ Page No. : $\langle \langle \rangle$

Field Control Method:

1. In Field Control Method bring the notor Speed to rated value and keep the Voltage across armature Constant

2. Now vary the Shunt Field Current in Steps to 1800 rpm with the help of Field Theostat and at each Step note down the readings of Speed and Shunt Field Current.

3. Switch OFF the DC Supply by making all devices to initial position.

Precautions:

1. Connections should be neet and tight.

2. Note down the readings without any parallax error. 3. Before starting of the motor check the

Theostot position properly.

Result:

The experiment on Veriation of Speed of a Di Shunt motor by Varying Voltage across the armeture and Shunt Field Current was done and graph were drawn.



Title: Load Test on	DC Compound	Gener	$a \leftarrow oy$ Date : $S = \mathcal{P} \mathcal{H}$ Page No. : $S = \mathcal{H} \mathcal{H}$
Arm:			
10 perform 10	ad test on	conto	und Generator
and to determine	e its load	Charac	Levistics.
Apparatus Requir	red:		
1. Voltmeter	(0-300)~	MC	2 No's
2. Anneter	(0-20)A	MC	2 NO'S
	(Q-1.5)A	MC	100
3. Resistive			
LOOD JKW, 20A			
4. Rheostat	230~, 1.7A	- 12	200%
	301,25A		100
5. Tachometer	Analog D:9	teal	$1 \infty_{o}$
Nome Plate De	40-16:		
DC Shunt Motor		DC Shi	unt benerator:
k.w: 5.2		K.w:	3.7
Voltage: 220		VOILO	3e: 2200
Current: 27.5		Load	current: 16.5A
Sheed: 1500 ypm	3	Spee	d: 1500 1pm
sound Field Cur	rent: D.OFA	Shur	nt Field Current: D-6 A

Tabular Column:

41.523 2952 25344 64.122 26.11.1 252 24-11 22 0 Tag (Ra Eg - Mure) (water) Cot 1414 P 145.2 0252 1080 1900 5-122 8.522 222 512 221.5 55.1 50.5 11.64 20.03 20.4 (sond) (sond) (sond) 5.4 14.9 200 بر بر ی 0 いい 24.0 95.0 ENT BIT <u>ه، و</u> <u>ه، و</u> ہ o 5 ; _ 0 3,0 9.11 022 7×8.9 1×601 7 012 5t/ 10542 12×2 202 220 3 67 ~ T Home 106×2 9×2 104×1 19×101 1×5 2×801 ş Ş S. NO ୁ ମ Ś **5** 6

2

Date : **よしましい** Page No.: へら

Theory

Computed in two days. I. Direct Test

2- Indirect Test.

In Direct Method the Input and Output Power can be measured by Suitable means and efficiency computed as a ratio of Output to Input.

A direct method is not used for large machines as)

a) It may not be possible to provide the neclessary

b) Even if load is arranged there would be enormous power loss during the telt.

It is used to determine the load characteristics of the generator and also change in efficiency '

when the load on the generator varies.

The load characteristics are drawn between

1. Generated Voltage(Vg) and Load Current (ILg).

2. EFFiciency and load Current (ILg)

Procedure?

1. connect the Circuit as per the Circuit diagram.

2. Keep Field Theostat of the motor in minimum position and armature Theostat of the Motor in maximum position.

3. Switch on the DC Supply and Start the MG Set with the help of Spoint Starter.

4. Adjust the MGSet Speed to rated value with the help of armature rheastot of the motor. If rated speed is not reached then adjust the Field rheastat of the motor.

5. Now, adjust the Field sheaster of the generator to rated voltage of the generator.

6. Note down the No-load readings of Voltmeter and Ammeters to Now vary the load in Steps to rated Current of the generator and at each step note down the readings of Voltmeter and Ammeter and also at

$$\begin{array}{l} \bigcup \ I ag = 0 + 0.6 = 0.6A \\ \hline Eg = \sqrt{g} + I ag \left(Ra + R_{5} e \right) \\ = 220 + 0.6 \left(2.52 + 0.43 \right) \\ \hline Eg = 22.5 + 0.6 \left(2.52 + 0.43 \right) \\ \hline Eg = 22.5 + 0.6 \left(2.52 + 0.43 \right) \\ = 1080 \\ 0 \\ P = \sqrt{g} \times I ug = 210 \times 0 = 0 \\ \hline V = \frac{0}{1080} \times 100 = 0 \\ \hline V = \frac{0}{1080} \times 100 = 0 \\ \hline V = \frac{0}{1080} \times 100 = 0 \\ \hline Eg = 22.5 + 2 \cdot 2 \left(2.52 + 0.43 \right) \\ \hline Eg = 22.5 + 2 \cdot 2 \left(2.52 + 0.43 \right) \\ \hline Eg = 22.5 + 2 \cdot 2 \left(2.52 + 0.43 \right) \\ \hline U = 105 \times 2 \times 0.8 \times 2 = 352 \\ \hline V = \frac{352}{1455} \times 100 = 24.181 \\ \hline V = \frac{352}{1455} \times 100 = 24.181 \\ \hline Eg = 210 + 4.4 \left(2.52 + 0.43 \right) \\ \hline Eg = 210 + 4.4 \left(2.52 + 0.43 \right) \\ \hline Eg = 210 + 4.4 \left(2.52 + 0.43 \right) \\ \hline Eg = 210 + 4.4 \left(2.52 + 0.43 \right) \\ \hline I/p = 408 \\ \hline U = 1008 \\ \hline V = \frac{798}{1980} \\ \hline V = \frac{1908}{1980} \\ \hline V = \frac{1908}{19$$

(5)
$$Iag = 4.9 \times 2 + 0.53 = 10.33$$

 $Eg = 96 \times 2 + 10.33(2.22 + 0.53)$
 $Eg = 219.30$
 $IIP = 210 \times 7.4 \times 2 = 3108$
 $0IP = 96 \times 2 \times 4.9 \times 2 = 1831$
 $N = \frac{1831.6}{3108} \times 100 = 60.54$

$$\begin{bmatrix} J & 2g = \frac{1}{2} \cdot 2 \times 2 + 0 \cdot 4g = 14 \cdot 8g \\ Eg = 8g \times 2 + 14 \cdot 8g E 2 \cdot 22 + 0^{14} \\ Eg = 215 \cdot 43V \\ T | p = 104 \times 2 \times 9 \cdot 8 \times 2 = 3952w \\ 0 | p = 8g \times 2 \times 7 \cdot 2 \times 2 = 2534^{-1} \\ h = 2534^{-1} \\ h$$

$$M = \frac{2534.4}{3952} \times 100 = 64.12\%$$

•



Date	:	8	81
Page No.	;	18	

each step maintain Constant Speed with the help of Field theostat of the motor.

8. Switch OFF the load to Zero position and also switch OFF DC Supply by making all devices to initial position. Precautions:

1. Connections should be neat and tight.

2. Before Starting of the MG Set ensure that there is no load on the Generator.

3. Before Starting OF the motor Check the rheoster positions properly.

4. Note down the readings without any parallax error.

Result! Load East on DC Compound Generator and its load characteristics are verified and determined.





Title: Load Test on DC Shunt	Date: 5/8/21 5 Grenerator: Page No.: 19
Arme To Conduct load Te	st on DC Shunt Generator
and draw its external	and Internal Characteristics.
Apparatus Required:	
1. Voltmeter (0-300) v	MC 1
2. Ammeter (0-20) A	MC I
(0-25)A 3. Rheostats 3700, 1.7 302, 25	MC 1 A 2 A 1
4. Tachometer Analog	Digital
5. Connecting wires	as per required.
Name Plate Details:	
Motor:	Generator'
K.w: 51ew	
Voltage: 2200	K.w: 3.7 Kw
Current: 20A	voltage: 2200
Excitation Current: 0. Pt	Excelorer 20A
Excitation Voltage: 2200 Fuse rating faltulation:	Excitation Voltage: 2204
Full Load 125 20=25A	No Load = 20 x20 = YA

ł

EFFICIENCY 1.27.54 69.69% 62.94.1 35.06.1 (1)2 60745 External Characteristi a ø (2016) Amps) (2016) (2016) (20165) (20065) (20045) Input Output 1.052 015 932 2002 13 81 0 208.2 8.07 t 9t. F12 hot.1 210-J4 Q41.6 201.87 2011.6 212.9 369.6 29966 K S 0.585 220.18 299.6 0) U He Be いいい 2.549 Lart 12-21 Tabular Column: Do H 29.4 12.46 و بو و ہ d.1 4 Tens 5.0 ر ن 3.252 0.53 0.0 و 6 9.0 Expected Graph: 5 Q-6×2 レメレ 6×2 Internal Characteristics P 100 214 1×2 Ο 51 022 216 201 J. Egre 8 p1 (2x2.5 2xEO) ht1 マメナ マメナの 3 3 (Amp) 1x7 L 1xtol The 2×2.1 2×901 12X75 1X EOI 1 4×5 12901 5 3 Eg Ver 5°00 2 3 5 し و

Theory ?

The efficiencies of all DC machines can be computed in two ways;

1. Derect Test 2. Indirect Test.

Internal and External Characteristics:

IF a Shunt generator is loaded its terminal voltage decreases due to armature resistance and armature reaction. As the machine supplies more and more load current, there is increased Iaka drop and greater demagnetizing effect. The combined effect is that the terminal voltage progressively decreases and diminishes with increase of load current, Hence the graph OF V VIS IL 1. e external Characteristics 95 a drooping curve. Fora loaded Shunt Generator

Iq = IL + ILh E= V+ IaRq.

Calculations:

) Vm= 106x 2=212V NO = 5500 Jum=1.2x2=2.4A 1.9 = 04 Ing = Ing + Ing 109 = 0+0-6 = 0.6A Rq = 0-98 Eg= vg + Ing Ra = 550+ 0.0(0:08) Eg=220.56V $IP = Vm \times ILg = 212 \times 24$ -1p= 508.800 O/P = Vg ILB = OW 2 = 0|p/ I|py100 N= 0 ×100 7=0 2) Vm = 106x2=212V ILM = 1.7x 2 = 3.4A Iog = Irg + Ish = (0.6x2) + 0.6 Igg = 1-PA Re=0.98 Vg=108×2=216V IL9 = 0.6x 2= 1.7A Eg = Vg + Igg Rg = 216+ 1.8× 0.98 Eg = 217.76V I/p = 1/m I 1/20-8 W 0/P= Vg Ing= 259.200 $l = \frac{259}{7108} \times 100$ 1-351.1

2) Vm=107×2=204V Icm= 2.2x 2= 4.44 Iag = Ing+ Ish = 2+06=2.6 Vg= 107×2= 214V I 9 = 1x 2= 2 A R=0.9801 + 1113 Eg = Vg + Iag Ra ···· = totx2+ 2.6(0.98) ES=216.54V I P = Vm I m = QUI. I W Olp = Varteg = 1381 w N= OIP X100 N= 43.0 ×100 n=46.5% 4) Ym= 107×2= 2140 Im = 3.2x2= 6.44 NB=101X J= 50BN ILS = 2x2EYA Iag = Iig + Ish = 4+0.6 =4.6A Eg = Vg+ IagRa Eg= 208+ 4.6(0.98)=212 Il P= Vm Icm = 1369.60 Olp = Ng ILg = 832w N= 832 ×100 2=60.7%

Procedure!

1. Connect the Circuit as per the Circuit diagram. 2. Keep Field Theostat of the notor in minimum position and armature Theostat of the motor at maximum position and also Generator Field Theostat at maximum position.

3. Supply ON the DC Supply and Start the MG Set with the help of 3-point starter.

4. Adjust the MG Set Speed to rated Value with the help of armature rheastat of the motor. If rated Speed is not reached then adjust the Field rheastat of the motor.

5. Now, adjust the Field Theostal of the generator to rated voitage of the generator. 6: Note days is

6. Note down the Norload readings of Voltmeter, and Ammeter.

t. Now vary the load on steps to rated current

Load Test on DC Shunt Generator



Date	;	58	2
Page No.	;	22)

of the generator and at each Step note down the readings of Voltmeter and Ammeter and also at each Step of maintain Constant Speed with the help of Field sheostat of the motor. 8. Switch OFF the load to Zero position and also Switch OFF DC Supply by making all devices

to initial position.

Precontions:

1. connections should be neet and light.

2. Before Starting of the MG Set ensure that there is no load on the generator. Result:

Load Test on DC Shunt Generator and 125

"internal and external characteristics are





Title: Brake Test	on DC Comp	ound h	ا محمع Pag	Date : 5 / 8 / 2 / e No. : 23
Aim: To perform	Brake Test	on Da	c compou	nd Motor
and determine	its perfor	r Do Ca	Charac	teristics.
Apperatus Req	uived?	× 5.		
1. Voltmeter	(0-300)~	MC	100	
2. Ammeter	(O-20)A	MC	INO	
3. Rheostat	2302, 1.7A		INO	
	6.12, 17.5	A	INO	
4. Tacho meter	Analos (Dig	ital	1100	
Name Plate D	etails:			
pc comp	ound Motor :			
K.w. 3.5				
Currents 10	22			
Speed: 150	norpm			
Excitation Cu	rrent: 0.6A	4		
Exceletion 1	voitage: 120	>		
	-			

			2.2.1		the and the faile	15 July	at the second	
ç		0	27.59	61.09	62.55	1031	2 b 0 8-	erice A eric. Of rollow
Output	(Watte)	0	325.69	1295.22	182150	2295.29		
traut	(Matter)	075	9576	2120	2012	2264	- 0-1	A PARAMINI
Torque	(1-N)	0	5.4936	9 612.0	14-1264	18-5213	6 i :	033 (\$ 1)019
Speed	(md)	1500	9 841	5181	121	hon hon	7 10	r L' OGICCO C
101 Eage	~ (Volta)	110×1	169 x 2	106×2	28401	1×201		
Curren	(lamp)	2241	3×1	225	1×t	てゃる	:	
4	5 3	Q	-ر	Ħ	Ξ	2		
Loa	(6)	0	Ь. О	-	101	2.2		
	0 2.	-	2	\sim	J	L3		

1-0-16

abular lovers

Theory :

The brake test is a direct load test. The DC machine under test is a compound motor provided with a brake drun. There is a suitable arrangement For loading the motor mechanically.

The DC motor is started under noload taking neccessary precautions by applying rated vollage vs. It is brought to its rated speed. It is then loaded. Loading is gradually increased and For each load anneter, voltmeter, spring balance readings and Speed are noted. Loading is continued till motor draws rated current From Supply mains. The motor is shut down. By Finding Circumference the radius of the brake drum is computed. Input power = VSIL watts. where VSisthe Supply Vollage in Volles. It is the line current in amperes.

Title : Date : 5/6/21 Page No. : 25
Output power = 2 TNT where N's speed rpm
les Torqueso N-m.
Procedure
1. Connect the Circuit as per the Circuit diagram.
2. Keep armature rheastat in maximum position and
Field theostat at minimum Position.
3. Switch on the DC Supply and Start the motor with
the help of 4-point Starter.
4. Now adjust the motor speed to rated value,
with the help of armature rheastat, if rated speed
is not reached then adjust the Field theostat.
5. Note down the no-load readings of voltmeter,
inmeter and also speed of the motor.
6. Now vary the load in Steps by using load
Show angement to rated current of the motor and at each
- + note down the readings of Voltmeter, Annal.
roads and also speed of the motor.



Remove the load Slowly be Zero position and switch OFF the DC Supply by making all devices to initial position. Precautions:

1. Connections should be neat and tight.

2. Before Starting of the notor weter should be poured anto brake drum.

3. Note down the readings without any parallex error.

Result:

Break test on DC Compound motor and its Characteristics are verified | determined.



		- G. C. L. 18		Killet M. H.
Title :	Separation	OF LOSSES in Da Motor	. Shunt	Date : $O(\mathcal{E}/\mathcal{V})$ Page No. : 27
[J	Apparatus Re	equired]		
An	~ °.			
	To Separat	e Stray losse	sing t	OC Shunt Motor.
Ą	pparatus Rea	eured:		
	1. Voltmeter	6-300)~	MC	1No
	2. Ammeter	(0-1.5)A	Mc	INO
		(2-3) A	MC	1N0
	3. Rheostat	230~, ~7A		2No's
	4. Tochomet	er Analog (Dig	sital	$1N_0$.
t	Vame Plate T	Details!		
	DC Shunt	Motor		
	K.w: 5		Fu	10 robus (o) where
	Voitage: 220	14	1 00	in any canadios
	Currente 20			12t
	Speed: 150	orpm		100×20=25A
	Excitation	Current: 1.2 N	\sim	o Load my
	Excitation	Noltage: 2200	,	20 100×20 54A
Ł	rocedure'			-

Observation Table !

· • • •

At Normal Field Current

						and the second sec		and the second se	
~NO	EB Voitad	Iq (Anps)	N (7P)	ws (works)	312	(2) ~ ~ ~ ~ ~ ~ ~ ~ ~ ~ ~ ~ ~ ~ ~ ~ ~ ~ ~	we	(Wates)	(La)
l	108× J	0-36×2	1500	164.16	5-109	40.5	19.5	91.10	125
2	10042	0.38×7	1400	152	0108	37.8	18.2	79.3	10.9
3	9242	0-39×2	1300	132.45	0-101	. 35.1	216.90	968.Y	9 .42
Y	80×5	0-34×2	1109	108.8	009	29.9	m. 4-	Q9.7	6.89
5	63×2	0-31×2	891	78.2	0.08	24.05	11-58	32.7	4.45
6	44x2	0-37×2	650	47.52	0.09	17.57	8.45	1411	2.37
				1					

At 3/1 of wormal Freld Current Charles

сыо	ED (VOIED)	Iq (Annes)	N (TP~)	vss (wetts)	<u>2</u>	(22 (13)	we (watts)	WF: (Loatts)	La.
١	10782	ง.วงหว	1612	154-04	5.095	27.4	61.9	209	14.57
2	9122	0-35x2	1358	27.04	0.093	23.08	43·8	17-0	10-34
3	7482	0-38×2	102	91.76	0.08	18-7	28.9	1432	68
4	64.42	0-2942	936	74.74	F0.0	15.9	20-9	12-15	4.31
5	45×2	0-27×2	694	48-8	0.07	11.7	11:40	9.02	2.7

Date : 10 P1 2

Theory: The Various Osses that occur in a Dishunt machine are: (opper Losses: a) Iara the armature Copper b) Loss due to brush contact resistance. Stray Loss es: a) Iron Losses: Hysteresis loss & Eddy Current Loss. b) Mechanical Losses: Friction at bearing and

commutator, windage of rotating armature.

Iron Losses:

Tron Losses are a Function of both Flux and Speed Hysteresis Losses.

The hysteres is loss Phis a measure of the electric energy required to overcome the recentivity of the iron in the magnetic Flux path, using watts as unit Phicks B*FV.

Eddy current Losses! These losses occur not only in the dynamo iron but in all Conductive materials with the Flux path of the rotating or varying MF of the dynamo.

al culations)

$$\frac{1}{2} - \frac{1}{2} - \frac{1}$$

Now,

$$B+D = 4.61\times10^{-1}$$

$$B+D = 2.941\times10^{-1}$$

$$B+D = 2.941\times10^{-1}$$

$$B-D' = 1.66A\times10^{-1}$$

$$B=(2.38\times10^{-1})^{2} = 1.7$$

$$B=(2.38\times10^{-1})^{2} = 1.6(9\times10^{-5})$$

$$D = 4.6(9\times10^{-5})^{2} = 1.6(9\times10^{-5})$$

$$D = 4.6(9\times10^{-5})^{2} = 1.6(0\times6^{-5})^{2}$$

$$D = 4.6(9\times10^{-5})^{2} = 1.6(1\times6^{-5})^{2}$$

$$D = 1.6(1.60\times10^{-5})^{2} = 1.6(1\times6^{-5})^{2}$$

$$D = 1.6(1.60\times10^{-5})^{2} = 1.260\times10^{-5}$$

$$D = 1.6(1.60\times10^{-5})^{2} = 1.260\times10^{-5}$$

$$D = 1.6(1.60\times10^{-5})^{2} = 1.260\times10^{-5}$$

$$D = 1.60\times10^{-5} = 1.260\times10^{-5}$$

Procedure:

1. Connect the circuit as parthe circuit diagram 2. Keep armature rheostat in max position and Field rheostat at min position.

3. Switch ON the DC Supply and Start the motor with the helpof 3-point Starter.

4. Adjust the Speed of the motor to rated Value with the help of armature rheostat if rated speed is not reached then adjust the Field Meostat.

S. Notedown the readings of voitmeter, anneters and Speed of the Motor.

6. Keep Field Current Constant at normal value and vary the Speed of motor in Steps to lower value vay 650rpm with the help of armature theostat.

4. At each Step note down the readings of voitmeter, ammeters and speed of motor.

8. Now again bring the motor speed to rated value with the help of armature rheostat and keep Field current constant at 3/4 of normal value and note down the readings of Voltmeter, ammeters and speed of motor.

9. Vary the Speed of motor in Steps to lower value say 650 pm with the help of armature rheostat and at each step note down the readings of Voltmeter, anneters and speed 02 the motor.

10- Switch OFF the DC Supply by making all devices to initial positions.

Precautions: → Connections Should be neat and tight. → Note down the readings without any parallax error. → BeFore Starting of the motor check the rheostat position Properly.




Title :

Date : State Page No. :

Result:

Separate Stray losses in a DC Shunt motor

is verified and determined and graphs were drawn.



Circuit Dragram

Castled on about the cast			
Title: Hopkinson's	Test on DCS	hunt	Date : 0/1/2/
۲	nachines		raye No J L
A::	Hopk - Jop' t	0 -12 9-	two identical DC
is perform	inoperiodins -		
Shunt machine	s and prede	ferming	e their efforciencies.
Apparatus Re	quived:		
1. Voltmeter	(0-300)~	MIC	IN O
	(0-600) v	MC	(NO
2. Anneter	(0-20) A	me	2003
	(0-1.5) A	Mc	200'5
3- Rheostat	2302, 1.7 A		21003
	302,25A		(m_0)
. 4. Tochomet	er AnalogID,	9:201	$1 m_{o}$
5. Switch	(129) 20A		100
Name Plate	Details!		
Deshurk w			
Kiloi Jelet	r0	DC	Shunt Motor.
Voltope: 25m		Kino	5.5
Lood (NOIF	age: 2200
Spaniasrent:	18-6 0	Loa	d current: 16.8 A
Sr	- der	Sp	ced: 1500 rpm
onunt Field (urrent: 0.9B	86	unt Field Current: 1.2M

· -	(Y. Y. K.	ד ק כ	54 54 54	20		
3	39.51		98	2 01		•
Generator Output	(1) (1) (1) (1) (1) (1) (1) (1) (1) (1)	65 65 65	09EL			
Hotor Harder	3-445	1304.6	2400.2	R S S		2 * 12 z tak ja
Losses	308.45	265.90	20 	and a second		
Losses Losses (watter)	18:4-54	300.15	39636			
Losser Losser	2.2.2	ht-8,87	319.19	9		
H, H	26.0	Г Ö	5	5	And the second	
LT3	0-0	Cs o	5.0	.0		anti 1 1997 - Antonio Martino, 1997 - 1997 - 1997 - 1997 - 1997 - 1997 - 1997 - 1997 - 1997 - 1997 - 1997 - 1997 - 19
HAN	0	J	P	1-3		
Line Lurrent	2	7:	2.7	rt é		
Voitag	210	520	220	5 20	and the second second	
2. S		0	~	5-		

Theory:

It is also called as regenerative or back toback test. In this method Full Load test can be carriedout on two shunt machines preferably identical ones without wasting their outputs. The bwo machines are mechanically and electrically coupled and are so adjusted electrica thet one of them runs as a motor and other runs as a generator. The mechanical output of the motor drives the generator and the electrical output of generator is used in Supplying the greater part of input to the motor.

The only disadvantage is with regard to the

availability of two identical machines.

Procedure: 1. Connect the Circuit as per the Circuit diagram. 2 Keep Field Theostet OF the motor in min Position

Calculations

1)
$$T_{1} = 1.2A$$
 $T_{2} = 0$ $T_{3} = 0.94A$ $T_{4} = 0.8A$
Total Strey losses = $VT_{1} - [T_{1} + T_{2}]^{2} R_{0} + T_{2}^{2} R_{0}]$
= $220 \times (1.2) - [(1.2 + 0)^{2} Q_{1} + 0]_{1+0^{2}}$
= 535.5ω

$$= \frac{1}{2} motor(2);$$

$$= \frac{1}{2} (p = 220(1 + 240) + 210; qu = 764.9400)$$

$$= \frac{1}{2} (p = 220(1 + 20) + 20) + 20 = 300.010)$$

$$= \frac{1}{2} \frac{1}{2$$

$$\frac{(u \text{ losses}}{w_{-}} = \frac{0}{\sqrt{p}} = \frac{0$$

$$IP = V(II + I_2) + VI_3 = 220(14+4) = 220(0.53) = 1304W$$

$$Total 1055es = (1.4+4)^{-1}(0.48) + 220(0.53) + \frac{288.74}{2}$$

$$T = 265.81W$$

$$T = 1304.6-265 = 79.6\%$$

Date : 101 Page No. : 34

and armature rheastat of the motor in maximum position and also keep Field rheostat of the generator in maximum position.

3. Switch on the DC Supply and Start the MG bet with the help of 3-point Starter.

4. Adjust the M-G Set Speed to rated value with the help of armature rheastat of the motor - If the rated speed is not reached then addies the Field Theostat of the motor.

5- Adrist the Field Theostat Eill Voltmeter (Vi) reads Zero Volts.

6. When voltmeter V, reads zero volts close the Switch 'S!

+ Now, increase the Field Current OF the generator in Steps with the helpof Field theostat of the generator

to rated current and at same time decrease the Field

Current of the motor with the help of Field Theostat

of the motor to maintain Constant Speed.

Hopkinson's Test



Title :	Date : 0/1/2/ Page No. : 35
8. At each step notedown the read,	ngs of Voltmeter
and Ammeter.	
9. Switch OFF the DC Supply by ma	King all devices
to enitial position.	
Precautions:	
1. Connections Should be neat and	Eight.
2. Before Starting of the M.G. Se	et check the
positions of the rheastats and also su	いい てい い い い い い い い い い い い い い い い い い
3. Note down the readings without	t any Parallax
error.	
Result:	
Hopkinson's Test on two Iden	itical DC Shunt
machines are verified and efficience	ses are
Predetermined.	



Creat Dragram

Title: Load Test on DC Series Generator Date 10/8/2) Page No.: 26
Ain: To perform Load Test on DC Series Generator and
determine its Internal and External Characteristics Apparatus Required?
1. Voltmeter 10-300) ~ MC 2NOS
2. Ammeter (0-20) A MC 2N0'S
3. Resistive load 5kw, 20A INO
4. Rheostat 2300, 1.7A INO
5- Techometer Analog [Digital INO
Name Plate Details:
DC Shunt Motor DC Series Generator?
K.W? SKW K.W: 3KW
Voltage! 2200 Voltage! 2200
Spannent: 20A Current: 11A
Even Speed: 1500 rpm
-xcitation current: 101A Excitation current: 1.1A
Excitation voltage: 2200 Excitation voltage: 2200

EFFICIEN ("n") 6-5-1 t 33.54 57.63 0.29 20.1 0 1939.2 output 3965 9.1401 3 5.0 t 6001 0 Trpet 3 2252 2464 264 2962 101 240 13.0t1 モン・モノス! 212.95 220.64 130.01 20 யீத Jeg Ra+ Rse (S-9102) 6.016 29.51 16.91 10-21 1.01 0 ILGE TOG 3-1×2-6-2 1.5 = 2 × 2 - 2 - 2 4.9.5 22 29.6 4.7×2-0.4 4-5×2=4 (Jon A) 0 1 hzu=2x29 10×2-201 -2225 1 10 2 2011 -2×26 USATS | 091 37 z 96 3 E H (Ampl) 2×9-0 5-9x2 1- 9×2 6. 5×2 JXYS 3.5.82 1 AXON ES, 10×2 NoxL LXOI TXOI 10×2 en.s ŝ Ľ بر 2 ن

Observation able

E=V+IQRQ

Theory :

The efficiencies of all DC machines can be computed in two ways: 1. Direct Test 2. Indirect Test.

Indirect method the Input and Output power can be measured by suitable means and efficiency computed as aratio of output to input.

a) It may not be possible to provide the neccessary load b) Even if load is arranged there would be enormous power loss during the test.

Internal and External Characteristics!

IF a Shunt generator is loaded its terminal Voltage decreases due to armature resistance and armature and armature reaction. As the machine supplies more and more load current there is increased Iaka drop and greater demagnetizing effect. The combined effect is that the terminal Voltage progressively decreases and diminishes with increase of load current. For a loaded Shunt Generator Iq=IL+Ish

21

Procedure:

1. Connect the Carcuit as per the Circuit diagram.

2. Keep Field theostat of the motor in mininum position

and armature rheostat of the motor at max position and also generator Field rheostat and maximum position.

3. Switch ON the DC Supply and Start the MG Set with the help OF 3-point Starter.

4. Adjust the MG Set Speed to rated Value with the help of armature rheostat of the notor. If rated Speed is not reached then adjust the Field sheostat of the notor.

5. Now adjust the Field "rheostat of the generator to rated voltage of the generator.

6. Note down the No-Load readings of Voltmeter and Ammeters.

I. Now vary the load in Steps to rated Current OF the generator and at each Step notedown the readings of Voltmeters and Ammeters and also

At cach Step maintain constant speed with the help





Date : Page No. : Title : of Field rheastat of the motor. 8. Switch OFF the load to Zeroposition and also switch OFF DC Supply by making all devices to initial position. Precautions: 1. Connections should be neat and tight. 2. Before Starting of the M-G set ensure that there is no load on the generator. Result! Internal and External Characteristics of load Test on DC Series generator are determined and



Title: Field Test ON I	DC Series Me	itimes	Date : 10/ JV Page No. : 🔍
Arm: To Find the eF	Fictency of g	ven DC S	series machines.
Apperatus Require	201		~
1. Voltmeter	(0-250)v	мс	$3 N_0$
2. Ammeter	(0-20)A	mc	$2N_{D}$
3. Rheostat	20 N, 10 A		120
4. Resistive Loc	ad 50Kw, 202		$l N_0$
5. Tachometer	Anatog (D.	gita h	
Name Plate Deb	01101		
be Series Motor	:	DC Serie	5 menerator:
Kow !	K		
Voitage!	\sim	oltage;	
Load Current:		oad Curre	st :
Speedl	S	peed;	
Excitation Curr	ent: 13	excitation	Current:
Excitation Volt	مععر	ミャレットのとうの	n vortage:

Japel	or set	Total	Calollos box Calollos	101967 Cr 101967	stray issies of ears be	Lot	Loc
1744-2	1465	279.2	1826	2+2	16.82	85.5	83.9

e . . .

5-10	L'VJ	Voltage Ocross Voltage	Input Laput	Load Vollage	Load Current
١.	2200	1881	112	IGIV	9.1A

Date : 10/8/2/ Page No. : ~

Theory?

Ina Series motor the Field and the armature are connected in Series. when the notor is switched on No-load then as the load is zero the load Current's very low and speed increases rapidly. Hence it is difficult to Find the efficiency of the Series motor. Also For a Series generator, with the increase in the load the Field Current also increases and stray losses vary with load. In Series Freid test the Series Field windings of both the motor and the generator are connected in series, so that even on increasing the load, the stray losses in both the machines are equal. This connections makes it easy to Find the efficiency of both the motor and generator.

Date : 10/12/ Page No. : 42
procedure.
i connect the circuit as per the Circuit diagram
as shown in Fig.
2. Keeping initially some load on the generator Switc
on the power Supply to the motor with shealtat
connected in Series Field at max position.
3. Gradually Cut the out the resistance so that the
reved voltage is obtained across the armature
terminals of the motor.
4. Now gradually apply the load on the generator
until the anneter connected in motor Circuit Shoulits
rated motor Current.
5. Notedown the readings of voltmeter and Ammeter.
6- Switch DEF the DC Supply by making all devices
to initial position.

motor
$$\eta$$
 Calculation!
Power I/p of the motor Pine VII - I Pie²
= 2100- 98.6 = 2000.00
Total 105505 in the motor (ω) = I Pie + I, R_{0} , thus
= 96.8 + 2424 10.85 = 355.65 = 1642.70
motor 0/p = Pinews 2003.2 - 355.65 = 1642.70
 $N = \frac{Pout}{2003.2}$ recore $92.2N$
Chenevator efficiency (e iculations:
Chenevator efficiency (e iculations:
Chenevator losses in generator $\omega_{3} + I_{1}^{2}R_{3}e_{2} + I_{1}^{2}V_{0}$
= 16.85+ 96.57 + 165 = 239.250
Power I/p to the generator (hin) = $hous + 239.27$
 $N = rub f = 1324.270$
 $N = rub f = 1224.270$



Date : 105 Page No. : 43

Precautions:

only.

Results

1. The motor rheastet should be kept at maximum

resistance position.

2. All the motor reading must be taken with out

parallazes error.

3. The power supply should be given to the motor

The efficiency OF De Series machines of Field

with some initial load applied across the generator

test is determined and verst 2d.