COURSE FILE INDEX

- 1. Vision and Mission of Institution
- 2. Vision and Mission of Department
- 3. PEOs, POs, PSOs
- 4. Academic Calendar
- 5. Syllabus
- 6. Course objectives and course outcomes
- 7. COs Mapping with POs and PSOs
- 8. Time table
- 9. Lesson Plan
- 10. Course delivery Plan and Record of Class work
- 11. Student list (HOD SIGNATURE)
- 12. Assignment I and II (CO, PO, BL) (please enclose two sample copies)
- 13. Mid I, MID-II Questions paper (CO, PO, BL)
- 14. Previous End semester Question papers
- 15. Content Beyond Syllabus MAPPING WITH Pos and PSOs
- 16. Teaching Learning Methods
- 17. Course Assessment/Attainment(Direct Attainment)
- 18. Course End Survey (Indirect Attainment)
- 19. Course closure report
- 20. Course Material

Had of the Department Department of Electrical & Electronics Engg Vidya Jyothi Institute of Technology HYDERABAD-600 075.

Vidya Jyothi Institute of Technology Himayatnagar (Vill), C.B. Post., Hyderabad-75.



Vidya Jyothi Institute of Technology (An Autonomous Institution)

(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Vision of the Institution

- To develop into a reputed Institution at National and International level in Engineering, Technology and Management by generation and dissemination of knowledge through intellectual, cultural and ethical efforts with human values.
- To fosters scientific temper in promoting the world class professional and technical expertise.

Mission of the Institution

- To create state-of-the-art infrastructure facilities for optimization of knowledge
- To nurture the students holistically and make them competent to excel in the global
- To promote R&D and consultancy through strong industry-institute interaction to address the societal problems.

Name of the Faculty: V. Vijaya Lakehroi Designation: Asoc. Prof	
a Develotion: R.Tech & R19 Academic rear.	
Program & Regulation: <u>Gree</u> Course Code: <u>A33204</u> Course Name: <u>Network Aralysis</u> Credits: <u>03</u> Department: <u>EEE</u> Year <u>I</u> Semester <u>I</u> Section – A	

Vision of the Department

To become a reputed department in the impartation of professional and technical expertise in the field of Electrical and Electronics Engineering

Mission of the Department

- Imparting Quality Technical Education by provision of state-of-the-art laboratories.
 - Preparing the students to think innovatively and find effective solutions to address engineering and societal problems with a multi-disciplinary approach maintaining
- Encouraging team work and preparing the students for lifelong learning with ethical responsibility for a successful professional career. .



(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Program Educational Objectives:

. **PEO1:** Equip graduates with a sound foundation in mathematics, science and engineering fundamentals, necessary to build a protective career

PEO2: Graduates will excel in giving solutions to real time problems through technical expertise and operational skill set in the field of Electrical Engineering

PEO3: Graduates will act with integrity in catering the need based requirements blended with ethics and professionalism.

Program Outcomes (POs)

Engineering Graduates will be able to:

1. Engineering knowledge: Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.

Problem analysis: Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
 Design/development of solutions: Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.

4. Conduct investigations of complex problems: Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.

5. Modern tool usage: Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.

6. The engineer and society: Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.

7. Environment and sustainability: Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.

8. Ethics: Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.

9. Individual and team work: Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.

10. Communication: Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.

11. Project management and finance: Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.

12. Life-long learning: Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.



(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Program Specific Outcomes (PSOs)

PSO 1: Apply the fundamentals of Electrical and Electronics Engineering to analyze and synthesize problems of Electric Circuits, Electronic Circuits, Control Systems, Electrical Machines and Power Systems.

PSO 2: Apply the appropriate techniques and modern engineering hardware and software tools in Electrical Engineering to engage in life-long learning and to successfully adapt in multi-disciplinary environments.



(Accredited by NAAC & NBA, Approved By A.I.C.T.E., New Delhi, Permanently Affiliated to JNTU, Hyderabad) (Aziz Nagar, C.B.Post, Hyderabad -500075)

B.Tech II & III Year Revised Academic Calendar for the Academic Year 2020-21

FIRST SEMESTER	Commencement of Class Work 17.07.2020			
	FROM	то	DURATION	
I Spell of Instructions (Online)	17.07.2020	09.10.2020	12 WEEKS	
Mid -II & End Semester Examinations of Previous Semester	14.10.2020	12.11.2020	5 WEEKS	
Practical Examinations of Previous Semester	16.11.2020	21.11.2020	1 WEEK	
Revision of Syllabi of Current Semester	23.11.202	05.12.2020	2 WEEKS	
Betterment Examinations of Previous Semester	02.12.2020	05.12.2020	4 DAYS	
I Mid Examinations of Current Semester	07.12.2020	15.12.2020	1 WEEK	
Practical Classes of Current Semester	16.12.2020	19.12.2020	4 DAYS	
II Spell of Instructions (Online)	21.12.2020	20.02.2021	9 WEEKS	
Practical Examinations	24.02.2021	03.03.2021	1 WEEK	
II Mid & End Semester Examinations	05.03.2021	22.03.2021	2 WEEKS	
Betterment Examinations	24.03.2021	27.03.2021	4 DAYS	
SECOND SEMESTE	R	Commencement of Class Wo 30.03.2021		
I Spell of Instructions	30.03.2021	22.05.2021	8 WEEKS	
I Mid Examinations	24.05.2021	29.05.2021	1 WEEK	
II Spell of Instructions	31.05.2021	24.07.2021	8 WEEKS	
II Mid Examinations	26.07.2021	31.07.2021	1 WEEK	
Practical Examinations	02.08.2021	07.08.2021	1 WEEK	
Betterment Examinations	09.08.2021	12.08.2021	4 DAYS	
End Semester Examinations	13.08.2021	28.08.2021	2 WEEKS	

COE

DEAN EXAMS. *

5 DIRECTOR



(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Course Objectives

- To introduce the basic concepts of circuit analysis which is the foundation for all of the Electrical Engineering discipline
- To emphasize on the basic analysis of circuits which includes three phase circuits, two port networks, transient analysis and network topology

CO 1	Apply network theorems for the analysis of electrical networks.
CO2	Obtain the transient and steady-state response of electrical circuits.
CO3	Apply graph theory to formulate network equations.
CO4	Analyze two port networks.
CO5	Evaluate circuits in the sinusoidal steady-state (Three-phase).

Course Outcomes (COs)



(An Autonomous Institution) Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

COs Mapping with POs & PSOs

Course Outcomes	Program Outcomes									Program Specific Outcomes				
	1	2	3	4	5	6	7	8	9	10	11	12	PSO1	PSO2
CO1	3	3	2	3	3	-	-	-	-	-	-	3	1	1
CO2	3	3	2	3	3	-	-	-	-	-	-	3	1	1
CO3	3	3	2	2	- 3	-	1942	-	-	-	-	3	1	1
CO4	3	3	2	3	3	-	-	-	-	-	-	3	1	1
CO5	3	3	2	2	3	-	-	3-1	-	-	-	3	1	1
Average	3	3	2	2.6	3	-	-		-	-	-	3	1	1

Assessment Plan

S.No.	Test/Examination	Units/ Topics Covered	COs covered	Proposed Date	Maximum Marks
1	Assignment I	Unit-1,Unit-2 and Unit- 3(Half)	CO1,CO2 and CO3	7.10.2020	5
2	Mid I	Unit-1,Unit-2 and Unit- 3(Half) CO1,CO2 and CO3		14.12.2020	20
3	Assignment II	Unit- 3(Half),Unit- 4 and Unit-5	CO3,CO4 and CO5	15.2.2021	5
4	Mid II	Unit- 3(Half),Unit- 4 and Unit-5	CO3,CO4 and CO5	20.3.2021	20

Direct Assessment (Internal Examination & External Examination)	Indirect Assessment (Course End Survey)
2.28	2.82

Course Faculty

Course Co-Ordinator

VIDYA JYOTHI INSTITUTE OF TECHNOLOGY (Autonomous)



(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziznagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL&ELECTRONICS ENGINEERING

Academic year: 2020-21 Section: EEE-A Year& Semester: II B.Tech- I Sem W. E. F: 18-07-2020

ONLINE CLASSES TIME TABLE

Day/ Hours	9.30 AM to 10.30 AM	10.45 AM to 11.45 AM	12.00 PM to 01.00 PM	02.00 PM to 03.00 PM
MON	EMF	NA	CAFT	MC-I
TUE	EDC	PS-I	EM-I	
WED	NA	CAFT	EMF	
THU	PS-I	EM-I	EDC	
FRI	CAFT	NA	EMF	MC-I
SAT	EM-I	EDC	PS-I	

Subject

Name of the Faculty

CAFT	Complex Analysis & Fourier Transforms	Mrs.Ch.Sridevi		
EDC Electronic Devices & Circuits		Mrs.A.Pavithra		
PS-I Power Systems-I		Mr.S.Suresh		
NA Network Analysis		Mrs.V.Vijaya Lakshmi		
EMF Electro Magnetic Fields		Mr.B.Sudhakar Reddy		
EM-I	Electrical Machines-I	Mr.P.Naga Muneendra		
MC-I	Gender Sensitization	Mrs.M.Hepsiba		

Class In charge

Mrs.V.Vijaya Lakshmi

Time Table I/C



(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Lesson Plan

Name of the Faculty: V.Vijaya Lakshmi

Year/ Sem:II-I

Course Name : Network Analysis

Course Code: A33204

S .No	Lecture Hour	Teaching Aids required	Topics to be covered	Books no./Page No.
		Unit-I: Network	k Theorems(Dc & Ac), Mesh And Nodal Analysis	
1	L1 .	Online Class(PPT)	Introduction	TB1(62-93)
O ₂	L2&L3	L2&L3 Online Analysis of Circuits using mesh methods Class(GJB)		TB1(62-93)
3	L4&L5	Online Class(GJB)	Analysis of Circuits using Nodal methods,	TB1(62-93)
4	L6 & L7	Online Class(PPT)	Norton's theorem	TB1(111- 120)
5	L8	Online Maximum Power Class(PPT) Transfer theorem		TB1(127- 130)
6	L9	Online Class(PPT)	Reciprocity theorem	TB1(133- 134)
7	L10	Online Class(PPT)	online Millmann's theorem	
8	L11	Online Class(PPT)	Compensation theorem	TB1(135- 136)
9	L12	Online Class(GJB)	Problems	TB1(62- 136)
		Unit-II:	D.C and A.C Transient Analysis	
10	L13	Online Class(PPT)	Introduction	TB1(333- 338)
11	L14 Transient response of series and parallel R-L circuits for D C excitation- Initial		TB1(339- 345)	
12	L15	Online Class(GJB)	Transient response of series and parallel R-C circuits for DC Excitation using differential equation-Initial conditions	TB1(349- 350)
13	L16 & L17	Online Class(GJB)	Transient response of series R-L-C circuits for DC Excitation using differential equation-Initial conditions	TB1(333- 338)



Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

14	L18	Online Class (CIP)	Transient response of series and parallel R-L circuits for D.C excitation- Initial conditions- Solution method using laplace	TD1/220
		Class(GJB)	transforms	TB1(339- 345)
15	L19	Online Class(GJB)	Transient response of series R-C circuits for DC Excitation using laplace transforms	TB1(349- 350)
16	L20 & L21	Online Class(GJB)	Transient response of series R-L-C circuits for DC Excitation using laplace transforms	TB1(349- 350)
17	L23	Online Class(GJB)	Transient response of series and parallel R-L circuits for sinusoidal excitation- Initial conditions- Solution method using differential	TB1(346- 348)
18	L24	Online Class(GJB)	Transient response of series and parallel R-C circuits for sinusoidal Excitation using differential equation-Initial conditions	TB1(350- 351)
19	L25	Online Class(GJB)	Transient response of series R-L-C circuits for sinusoidal Excitation using differential equation- Initial conditions	TB1(352- 353)
20	L26	Online Class(GJB)	Transient response of series and parallel R-L circuits for sinusoidal excitation- Initial conditions- Solution method using laplace transforms	TB1(346- 348)
21	L27	Online Class(GJB)	Transient response of series R-C circuits for sinusoidal Excitation using laplace transforms	TB1(350- 351)
22	L28	Online Class(GJB)	Transient response of series R-L-C circuits for sinusoidal1 Excitation using laplace transforms	TB1(352- 353)
23	L29 & L30	Online Class(GJB)	Problems	
			nit-III: Network Topology	
24	L31	Online Class(PPT)	Introduction	TB1(691- 697)
25	L32	Online Class(PPT)	Network Topology - Definitions, Graph, Tree	TB1(691- 697)
26	L33 & L34	Online Class(PPT)	Incidence Matrix, Basic Cut Set Matrices for planar networks	TB1(698- 702)
27	L35 & L36	Online Class(PPT)	Basic Tie set Matrices for planar networks	TB1(698- 702)
28	L37 & L38	Online Class(PPT)	Loop method for analysis of Networks with Voltage and Current Sources	TB1(706- 710)
29	L39 & L40	Online Class(PPT)	Nodal method for analysis of Networks with Voltage and Current Sources	TB1(706- 710)
30	L41	Online Class(PPT)	Duality & Dual Networks	TB1(711- 725)
31	L42 & L43	Online Class(GJB)	Problems	TB1(706- 710)



(An Autonomous Institution)

(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to

JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

	Station and a	U	nit- IV: Two Port Networks	
32	L44	Online Class(PPT)	Introduction	TB1(566- 597)
33	L45	Online	Two port network parameters – Z parameters	TB1(566-
34	L46	Online Class(PPT)	Two port network parameters – Y parameters	TB1(566- 597)
35	L47	Online Class(PPT)	Two port network parameters -ABCD parameters	TB1(566- 597)
36	L48	Online Class(PPT)	Two port network parameters –Hybrid parameters	TB1(566- 597)
37	L49	Online Class(PPT)	Inter Relations	TB1(599- 601)
38	L50	Online Class(PPT)	Series connection of two port networks	TB1(599- 601)
39	L51	Online Class(PPT)	Parallel connection of two port networks	TB1(599- 601)
40	L52	Online Class(PPT)	Cascaded connection of two port networks	TB1(677- 680)
41	L53	Online Class(PPT)	Concept of transformed network	TB1(677- 680)
42	L54	Online Class(PPT)	Two port network parameters using transformed variables	TB1(566- 597)
43	L55	Online Class(PPT)	Problems	
	AT THE SECOND		nit- V: Three Phase Ciruits	
44	L56	Online Class(PPT)	Introduction	TB1(301- 302)
45	L57	Online Class(PPT)	Three phase Circuits – Generation of Three Phase Voltage	TB1(302- 303)
46	L58	Online Class(PPT)	Review of Voltage and Current relations in Star system	TB1(307- 330)
47	L59	Online Class(PPT)	Review of Voltage and Current relations in Delta system	TB1(305- 306)
48	L60	Online Class(PPT)	Analysis of balanced three phase circuits- Measurement of active and reactive power	TB1(301- 330)
49	L61 & L62	Online Class(PPT)	Analysis of unbalanced three phase circuits- Measurement of active and reactive power	TB1(301- 302)



- L Lecture
- A Assignment
- T Text Books
- R References



GJB - Google Jam Board

- **PPT** Power Point Presentation
- MD Model Demo
- FV Field Visit



(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Course Delivery Plan & Record of class work

Unit-I

S	Proposed		Tania Ta Da Gaunal	Teaching	Execution		
No	DATE	HOURS	- Topics To Be Covered	Aids used	DATE	HOURS	
	20.7.2020	1	Introduction	Online Class(PPT)	20.7.2020	1	
2	22.7.2020&24.7.2020	2	Analysis of Circuits using mesh methods	Online Class(GJB)	22.7.2020	2	
3	27.7.2020&29.7.2020	2	Analysis of Circuits using Nodal methods	Online Class(GJB)	27.7.2020	2	
4	31.7.2020	1	Norton's theorem	Online Class(PPT)	3).7.2020	1	
5	3.8.2020	1	Maximum Power Transfer theorem	Online Class(PPT)	3.8.2020	J	
6	5.8.2020	1	Reciprocity theorem	Online Class(PPT)	5.8.2020	1	
7	10.8.2020	1	Millmann's theorem	Online Class(PPT)	10.8.2020	Ţ	
Ő	12.8.2020	1	Compensation theorem	Online Class(PPT)	12.8.2020	1	
9	14.8.2020	1	Problems	Online Class(GJB)	14.8.2020	1	

Justification for deviation (if Any)

No deviation

Jalus .

Hava



JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

S No	Proposed		Topics To Be Covered	Teaching	Execution	
0110	DATE	HOURS	Topics to be covered	Aids used	DATE	HOURS
1	17.8.2020	1	Introduction	Online Class(GJB)	17.8.2020	» I
2	19.8.2020	1	Transient response of series and parallel R- L circuits for D.C excitation- Initial conditions- Solution method using differential equation	Online Class(GJB)	19.8.2020	, J
3	21.8.2020	1	Transient response of series and parallel R- C circuits for DC Excitation using differential equation-Initial conditions	Online Class(GJB)	2).8.2020	1
4	24.8.2020	1	Transient response of series R-L-C circuits for DC Excitation using differential equation-Initial conditions	Online Class(GJB)	24.8.2020	1
5	26.8.2020	1	Transient response of series and parallel R- L circuits for D.C excitation- Initial conditions- Solution method using laplace transforms	Online Class(GJB)	26.8.2020	. /
6	28.8.2020	1	Transient response of series R-C circuits for DC Excitation using laplace transforms	Online Class(GJB)	28.8.2020	. 1
7	31.8.2020	2	Transient response of series R-L-C circuits for DC Excitation using laplace transforms	Online Class(GJB)	31.8.2020	2
8	2.9.2020	1	Transient response of series and parallel R- L circuits for sinusoidal excitation- Initial conditions- Solution method using differential equation	Online Class(GJB)	2.9.2020	I
9	4.9.2020	1	Transient response of series and parallel R- C circuits for sinusoidal Excitation using differential equation-Initial conditions	Online Class(GJB)	4.9.2020	J
10	7.9.2020	1	Transient response of series R-L-C circuits for sinusoidal Excitation using differential equation-Initial conditions	Online Class(GJB)	7-9.2020	J
11	9.9.2020	1	Transient response of series and parallel R- L circuits for sinusoidal excitation- Initial conditions- Solution method using laplace transforms	Online Class(GJB)	9.9.2020	1
12	11.9.2020	1	Transient response of series R-C circuits for sinusoidal Excitation using laplace	Online Class(GJB)	11.9.2020	1

Unit-II



(An Autonomous Institution) ccredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated (JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

13	14.9.2020	1	Transient response of series R-L-C circuits for sinusoidal1 Excitation using laplace transforms	Online Class(GJB)	14.9.2020	١
14	16.9.2020		Problems	Online Class(GJB)	16.9.2020	1

Justification for deviation (if Any)

No deviation



JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

S No	Proposed		Topics To Be Covered	Teaching	Execution	
	DATE	HOURS		Aids used	DATE	HOURS
1	18.9.2020	1	Introduction	Online Class(PPT)	18.9.2022	
2	28.9.2020	1	Network Topology - Definitions, Graph, Tree	Online Class(PPT)	28-9-2020	1
Ô	30.9.2020&5 .10.2020	2	Incidence Matrix, Basic Cut Set Matrices for planar networks	Online Class(PPT)	30.9.2020	9
4	7.10.2020&9 .10.2020	2	Basic Tie set Matrices for planar networks	Online Class(PPT)	7.10.2020	2
5	12.10.2020& 23.11.2020	2	Loop method for analysis of Networks with	Online Class(PPT)	12.10.2020	2
6	25.11.2020	1	Nodal method for analysis of Networks with Voltage and Current Sources	Online Class(PPT)	25.11.2020	1
7	27.11.2020	1	Duality & Dual Networks	Online Class(PPT)	27.11.202	» I
8	30.11.2020	1	Problems	Online Class(GJB)	30.11.2020	1

Unit-III

Justification for deviation (if Any)

No deviation

Course faculty



JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

S	Proposed			Teaching	Execution		
No	DATE	HOURS	- Topics To Be Covered	Aids used	DATE	HOURS	
1	2.12.2020	1	Introduction	Online(PPT)	2-12-2020	1	
2	3.12.2020	1	Two port network parameters – Z parameters	Online(PPT)	3.12.2020	J	
3	21.12.2020	1	Two port network parameters – Y parameters	Online(PPT)	21.12.2020	> 1	
4	23.12.2020	1	Two port network parameters – ABCD parameters	Online(PPT)	23.12.2020	. 1	
5	25.12.2020	1	Two port network parameters – Hybrid parameters	Online(PPT)	25.12.2020	, ,	
6	28.12.2020	1	Inter Relations	Online(PPT)	28.12.2020	1	
7	30.12.2020	1	Series connection of two port networks	Online(PPT)	30.12.2020	1	
8	4.1.2021	1	Parallel connection of two port networks	Online(PPT)	4.1.2024	1	
9	6.1.2021	1	Cascaded connection of two port networks	Online(PPT)	6.1.2021	1	
10	8.1.2021	1	Concept of transformed network	Online(PPT)	8.1.2021	1	
11	11.1.2020	1	Two port network parameters using transformed variables	Online(PPT)	11.1.2021	1	
12	13.1.2020	1	Problems	Online(PPT)	13-1-2021	1	

Unit-IV

Justification for deviation (if Any)

No deviation

Course faculty



(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to

JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

S No	Proposed		Topics To Be Covered	Teaching	Execution		
	DATE	HOURS		Aids used	DATE	HOURS	
1	15.1.2021	1	Introduction	Online Class(PPT)	15.1.2021	1	
2	18.1.2021	1	Three phase Circuits – Generation of Three Phase Voltage	Online Class(PPT)	18.1.2021	1	
3	20.1.2021 & 22.1.2021	2	Review of Voltage and Current relations in Star system	Online Class(PPT)	20.1.2024	2	
4	25.1.2021 & 27.1.2021	2	Review of Voltage and Current relations in Delta system	Online Class(PPT)	25.1.2021	2	
5	29.1.2021 &1.2.2021	2	Analysis of balanced three phase circuits- Measurement of active and reactive power	Online Class(PPT)	29.1.2024	2	
6	3.2.2021 &5.2.2021	2	Analysis of unbalanced three phase circuits- Measurement of active and reactive power	Online Class(PPT)	2·2·2024 5·2·2024	2	

Unit-V

Justification for deviation (if Any)

No deviation

Course faculty



Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Student List

II-A Section

S.No	Roll.No	Name of the Student
1	19911A0201	A Pavani
2	19911A0202	Ahankari Aditya
3	19911A0203	Ajmeera Rakesh
4	19911A0205	Algubelli Sindhu
5	19911A0206	Annaldas Aravind
6	19911A0207	Anthamgari Swathi Priya
7	19911A0208	Badagani Ganesh
8	19911A0209	Bandela Sumith
9	19911A0210	Banoth Sravan
10	19911A0211	Bhooma Rajashekar Goud
11	19911A0212	Bhukya Bhargav
12	19911A0213	Bhukya Naveen
13	19911A0214	Buchalwar Swennik
14	19911A0215	Chakali Praveen
15	19911A0216	Chennam Alekhya
16	19911A0217	Chitikela Chetana
17	19911A0218	Chittiprolu Anusha
18	19911A0219	Dara Uday Bhargav
19	19911A0220	Dasari Srinivas
20	19911A0221	Devaradeshi Udhay Kiran
21	19911A0222	Edula Bharath Kumar Goud
22	19911A0223	Gade Suprathika
23	19911A0224	Giddalapati Vamsi Ram Reddy
24	19911A0225	Goli Sai Prashanth
25	19911A0226	Gone Meghana
26	19911A0227	Gorla Anjali Raj
27	19911A0228	Govindreddy Asritha
28	19911A0229	Guguloth Kalyan
29	19911A0230	Gugulothu Rahul
30	19911A0231	Jarpala Nageswari
31	19911A0232	Jatavath Pavan
32	19911A0233	Joshi Sai Vivekanand
33	19911A0234	Kanaveni Akhila
34	19911A0235	Karike Srinu
35	19911A0236	Karukuri Sai Ram
36	19911A0237	Katna Srisailam
37	19911A0238	Kolluru Maheshwar
38	19911A0239	Koppera Vijendhar
39	19911A0240	Kottapeta Sanjeev Kumar Goud



Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

40	19911A0241	Kurva Krishna	
41	20915A0201	Boini Ramnesh	
42	20915A0202	Bonike Naveen	
43	20915A0203	Bowreshetty Sai Kiran	
44	20915A0204	D Hemanth Sagar	1
45	20915A0205	G Vishnu Vardhan	14
46	20915A0206	Gandham Sree Charan Deep	ć.
47	20915A0207	Gumdala Manikanta Goud	Ĩ.
48	20915A0208	Karumuru Hepsibha	
49	20915A0209	Kondoju Aparna	
50	20915A0210	Koppula Akanksha	
51	20915A0211	Kothuri Abhishek	
52	20915A0212	Kummari Yamuna	
53	20915A0213	M Raghavulu	



Vidya Jyothi Institute of Technology (An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Syllabus Covered As Per Course Delivery Plan

Details/Duration	First 4 Weeks	Second 4 Weeks	Third 4 Weeks	End Of Semester
Percentage of Syllabus covered	254.	50%.	75y.	1. 1. 1. 1. 1. 1. 1. 1. 1. 1. 1. 1. 1. 1
Signature of staff with date	Ralud	Paleet :-	Dut	Duly.
Signature of HOD with date	Honoyale	Adaradula	Leveretor P	Jaller
Signature of Auditor with date	C.N. Delle	C.N. Para	A BIT	A SHU
2.9 . Alexandress of	5/1/10		3/1/21	C-2-3-8/21



(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

ASSIGNMENT - I (AY - 2020-21)

COURSE NAME: Network Analysis

Year & Semester: II-I

S.No.	Questions	COs	POs	B.L
	State Norton's Theorem and find Norton Equivalent for the circuit shown			512
1	$E = 9 \nabla R_2 \leq 6 \Omega \leq R_L$	1	1,2,8	2
2	State and prove Maximum power transfer Theorem for both DC and AC excitation.	1	1,2,8,9	3
	Switch is moved from position 1 to 2 at $t = 0$ find the voltage $V_R(t)$ and $V_C(t)$ for t=0			
3	$100V - \frac{1}{2} + \frac{500 \Omega}{50V} + \frac{1}{1} + \frac{1}{1} + \frac{1}{1}$	2	1,2,8,9	4
4	In the circuit shown in figure, switch S is in position1 for a long time and brought to position 2 at time t=0.Determine the circuit current a	2	1,2,8,9	4
	$50 V = \frac{\left[+ \right]^{2}}{T^{-}} = \frac{10 V}{T^{-}} = 10 V$			
5		3	1,2,8	2
	For the following graph find the no.of possible trees.			



Vidya Jyothi Institute of Technology (An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

ASSIGNMENT - II (AY - 2020-21)

COURSE NAME: Network Analysis

Year & Semester: II-I

S.No.	Questions	COs	POs	B.L
1	0.20 0.20 0.50	3	1,2,8	2
2	Find the Z parameters for the following networks from basics. $3\Omega^{-}$ C S^{-} S^{-	4	1,2,8,9	3
3	Derive conditions for reciprocity and symmetry for Z, ABCD parameters	4	1,2,8,9	3
4	Obtain power equation using 2 wattmeter method for balanced and unbalanced systems.	5	1,2,8,9	5
5	A three phase balanced delta connected load of $(4+j8)\Omega$ is connected across a 400V, 3-Ø balanced supply. Determine the phase currents and line currents. Assume the phase of sequence to be RYB. Also calculate the power drawn by load.	5	1,2,8,9	2



(Accredited by NAAC & NBA, Approved By A.I.C.T.E., New Delhi, Permanently Affiliated to JNTU, Hyderabad) (Aziz Nagar, C.B.Post, Hyderabad -500075)

II B.Tech I Semester I Mid Examination, December-2020

Subject Name: Network Analysis Time: 1 Hour

BRANCH:EEE Max Marks:20

Note: This question paper contains six questions. Answer any three questions.

Bloom's Level:

Remember	L1
Understand	L2
Apply	L3
Analyze	L4
Evaluate	L5
Create	L6

	ANSWER ALL THE QUESTIONS	Bloom's Level	СО	РО	Marks
1	Using nodal analysis find all branch currents for the following circuit $10 V \stackrel{2\Omega}{\uparrow} \stackrel{8\Omega}{\downarrow}_{3\Omega}$ $10 V \stackrel{10}{\uparrow} \stackrel{2\Omega}{\downarrow}_{3\Omega} \stackrel{8\Omega}{\downarrow}_{4\Omega}$	L4	1	2	7M
	[(DR]			
2	Find Maximum power delivered to the load by using maximum power transfer theorem. 2Ω 3Ω $10V + 12\Omega \ge R\Omega \ge B$	L2	1	2	7М

3	In the circuit shown in figure, switch S is in position 1 for a long time and brought to position 2 at time t=0.Determine the circuit current. $50 v + \frac{50}{1 + 10} v = 2H$	L5	2	3	7M
		[OR]			
4	A series RC circuit with $R = 100 \Omega$ and $C = 25 \mu$ F has a sinusoidal excitation V(t) = 250 Sin 500t. Find the total current assuming that the capacitor is initially Uncharged.	L4	2	3	7M
5	For the circuit shown draw the graph and find the no. of possible trees r + r + r + r + r + r + r + r + r + r +	L4	3	2	6M
6	For the graph shown write the tieset	[OR]			
	matrix.	L5	3	3	6М

VJIT(A)



(Accredited by NAAC & NBA, Approved By A.I.C.T.E., New Delhi, Permanently Affiliated to JNTU, Hyderabad) (Aziz Nagar, C.B.Post, Hyderabad -500075)

II B.Tech I Semester II Mid Examination, February-2021

Subject Name: Network Analysis Time: 90 Min

BRANCH: EEE Max Marks:20

Bloom's Leve	<u>l:</u>
Remember	L1
Understand	L2
Apply	L3
Analyze	L4
Evaluate	L5
Create	L6

ANS	WER ALL THE QUESTIONS	Bloom's Level	со	РО	Marks
1.a)	Calculate twig voltages using KCL equation for the network shown $ \begin{array}{c} 2\Omega \\ 5\Omega \\ 5\Omega \\ 10\Omega \\ 910 \\ \end{array} $	L4	3	2	6M
	[OR]				
b)	Draw the dual of the network shown in the figure R_1 V R_2 R_3 R_4 R_4 R_5	L3	3	1	6M
2(a)	Find the Z parameters for the circuit shown in Figure $ \begin{array}{c} +1 & & & 5\Omega \\ & & & & & & & & \\ & & & & & & & & \\ & & & & $	L4	4	2	7M
	[OR]				Sec.
b)	Derive expressions for combined network when two two- port networks connected in cascade	L3	4	2	7M

3.a)	Derive the relation between line and phase currents and line voltage and phase Voltages in delta connection of a 3- Phase balanced system	L3	5	2	7M
	[OR]		S		Re El
b)	If loads are 4+j8, 3+j4, 15+j20 supply is 3 phase 3wire 400v, 50Hz obtain line currents and power delivered	L3	5	2	7M



(Accredited by NAAC & NBA, Approved By A.I.C.T.E., New Delhi, Permanently Affiliated to JNTU, Hyderabad)

(Aziz Nagar, C.B.Post, Hyderabad -500075)

Subject Code: A23204

B.Tech II Year II Semester Regular Examination, OCTOBER/NOVEMBER-2020

SUBJECT: Network Analysis Time: 3 Hours BRANCH: EEE Max. Marks: 75

Note: This question paper contains two parts Part A and PartB Part A is compulsory which carries 25 Marks.Answer all questions Part B consists of 5 questions.Answer all the questions.

Bloom's Level:

Remember	Ll	Analyze	L4	
Understand	L2	Evaluate	L5	
Apply	L3	Create	L6	

	PART-A ANSWER ALL THE QUESTIONS	со	PO	Bloom's	Marks
1	State Maximum Power Transfer theorem	1	1.10	Level	
2	Discuss and explain on supernode	1	1,12	L2	2M
3	Calculate the timeconstant of simple RL circuit with R=10M Ω and l=10 μ h	2	1,12	L2 L3	3M 2M
4	Review on the significance of initial conditions in a step response of series RL and RC circuits	2	1,4,5	L2	3M
5	Define a graph, tree with an example	3	1,12	L1	2M
7	Define the duality and dual elements with examples	3	1,12	LI	3M
8	Write a short notes on ABCD parameters	4	1,12	LI	2M
9	Derive the condition for reciprocity for Z parameters and Y parameters	4	1,4,5	L3	3M
10	Write the expression for active power and reactive power in a balanced three phase circuit	5	1,3,5	LI	2M
	PART-B ANSWER ALL THE QUESTIONS	СО	РО	Bloom's Level	Marks
11.i).a	Using the node voltage analysis, compute all the node voltages and currents in 1/3 Ω and 1/5 Ω resistances respectively	1	1,2,3,5	L3	5М
b)	Derive thevenin's theorem condition for DC excitation and verify with an example	1	1,2,3	L3	5M
	[OR]	6 1	1.000		1.00
ii.a)	Verify reciprocity theorem for the circuit shown in the figure 5Ω 2Ω 3Ω 4Ω \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow	1	1,2,3	L2	5M

R18

b)	Using Norton's theorem compute the current through 6Ω resistance shown in figure 20 V 10Ω 50Ω	1	1,2,3,5	L3	5M
12.i.a)	Image: Image with the series RC circuit shown in figure has sinusoidal voltage source $v(t)=100sin(100t+\Phi)$ volts. If the switch is closed when $\Phi=90^{\circ}$, calculate current assuming zero initial charge Image matrix in the series of the series	2	1,2,3,5	L3	5M
b)	A series RC circuit with R= $I00\Omega$ and C= $2S\mu$ F has a sinusoidal excitation V(t)= $250Sin500t$.Compute the total current assuming that the capacitor is initially uncharged	2	1,2,3,5	L3	5M
	[OR]				1.5
ii.a)	For the circuit shown in the figure determine the currents i_1 and i_2 when the switch is closed at t=0 $100 V = \frac{520 \Omega}{15 \Omega (12)}$ 30.5%	2	1,2,3,5	L3	5M
b)	A series RC circuit with R=100 Ω and L=5mH has a sinusoidal excitation of V(t)=250*sin500t.Find the total current assuming that the inductor is initially not charged	2	1,2,3,5	L4	5M
13.i.a)	For the following network obtain (A)basic tieset matrix and (B) basic cutset matrix	3	1,2,3	L3	5M
	Determine the branch currents in terms of link currents using tie-set matrix with an example	3	1,2,3	L3	5M
ii.a)	For the graph shown below find incidence and cutset matrices $a \xrightarrow{6} c$ $a \xrightarrow{2} b \xrightarrow{4} c$ $a \xrightarrow{3} 5$	3	1,2,3	L4	5M
	Explain graph, oriented graph, subgraph, tree, cotree, and 1 ink with neat diagrams for any typical circuit.	3	1,2,3	L3	5M
	The Z parameters of a two port network are $Z_{11}=10$ ohm, $Z_{22}=15$ ohm, $Z_{12}=Z_{21}=5$ ohms.Find the h parameters	4	1,2,3	L3	5M

b)	Find Y parameters for the circuit shown in the figure	4	1,2,3	L3	5M
	[OR]				C C C C C C C C C C C C C C C C C C C
ii.	Derive expressions for ABCD parameters of two-port networks connected in cascade.	4	1,2,3	L4	10M
15.i.a)	Derive the relation between line and phase currents and Voltages in delta connection of a 3-phase(balanced) system.	5	1,2,3	L3	5M
b)	 b) A balanced star-connected load 4+j3per phase isconnected to a balanced 3- phase 400v supply. The phase current is12A,find (A) The total active power (B) Reactive power and' (C) Total apparent power (D) Power factor 	5	1,2,3	L4	5M
e Ini	OR				
ii.	Three identical impedances are star connected across $440V,50Hz$ supply. The three line currents are IR= $20L-40^{\circ}$; ly= $20L-160^{\circ}$; IB= $20L80^{\circ}$; find the values of the elements, total power and the readings of wattmeter to measure power.	5	1,2,3	L3	5M

VJIT(A)**



(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

CONTENT BEYOND SYLLABUS

S.No.	Date	Topics Covered	Details Of The Resource Person	Mapping With POs, PSOs
1	8.2.2021	Substitution theorem and Tellegen's theorem	V.Vijaya Lakshmi	3,1
2	10.2.2021	Network functions, Driving Points and Transfer functions –using Transformed (S)Variables	V.Vijaya Lakshmi	3,1

TUTORIAL CLASSES

S.No.	Date	Period	Topics Covered	Related COs
2	12.2.2021	1	Problems on transients	2
3	15.2.2021	1	Problems on tieset and cutest	3
4	17.2.2021	1	Problems on Network parameters	4
5	20.2.2021	1	Problems on star and delta connected loads	5



(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Faculty Name: V.Vijaya Lakshmi

Course: Network Analysis

Class-Section: II-A

Innovative Method:Google-It Report Writing

Objective of the Method:

Students are expected to Google the content of the topic available in open source. He/ She is also expected to go through, understand& explore beyond class room. Student will be reporting the concept understood in writing.

Aim of the method:

- 1. To maximize the learning experience.
- 2. To identify and prioritize content
- 3. To identify gaps in understanding

Implementation/Portrayal of method:

- 1. Use this opportunity to clear up any misconceptions
- 2. Student will be in a position to present the report prepared.
- 3. The report can be used for further reference.

Topic Covered through activity: Norton's Theorem

Description of the Method: Students were asked to google about Norton theorem statement & procedure to apply the theorem for a given circuit. They were further asked to prepare a report accordingly.

Benefits of the method: students understood how to apply Norton's theorem for a given circuit. This activity enhances communication and writing skills, it further engages the students in self learning.



(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Name of the Student: G Kalyan Roll.No: 19911A0229 Year/Sem : II-I

Norton's theorem:


Statement: - Eny combination of linear bilateral circuit elements and active sources. regeodless of connection or complexity connected to a given load Ze. Can be replaced by a simple two terminal network. Considing a single current source of In anyers and a single impedance Zer is porallel with it. across the two-terminal of the load Ze. the In is the short circuit current flowing through the short executived path replaced instead of Ze. It is also called Norton's current the zer is the equivalent impedance of the given network as viewed through the load terminale, with Ze removed and all the active sources are replaced by short eircuit while the indepent current sources must be replaced by open circuit, while calculating Zer.

Explanation of Norton's theorem :


consider a network shown in fight below the terminal -S A-B are load terminals where load impedance ZL is connected -According to Norton's theorem the entire network can be replaced by a current resource In, and as equivalent impedance Ze in porallel with it, across the load terminals A-B as shown in fight



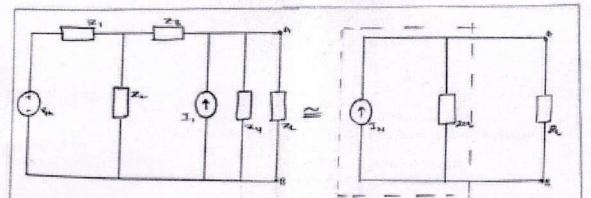
(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING



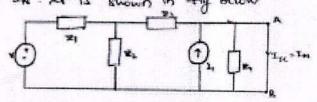-for obtaining current Ins. short the load terminals A.B. Calculate the current through the short circuited path by using any of the network amplification techniques this is Norton's current In. At is shown in fig below



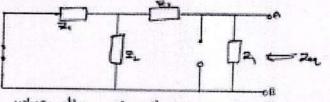while the equivalent impedance seq is to be obtained by -the -these procedure as in case of -thevinion's -theorem.



when the circust is replaced by mostor's equivalent ocross the load terminals, then the load current can be easily estained by using current division in a parallel circuit as

-this theorem is also called dual of the venion's theorem. This is because if the thevenion's equivalent voltage source is converted to an equivalent current sources the Norton's equivalent

(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENCONFERDING

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

is obtained. Thissis chown in fight from source transformation we can write Stores to opply Maton's theorem; step-1 : short the branch . through which the current is to be calculated by removing the impedance between the terminal - 5 Obtain the currant through this short circuited branch. step-2 > using any of the notwork reimplification techniques this current is miching but Norton's current IN. step-37 calculate the equivalent impedance sec. as viewed -through the two terminals of interest by removing the branch impediance and making all the independent sources in active step 4: Onow the Montoo's equivalent across the terminals of Interst, showing a current source In with the impedance Her porallel with it. Reconnect the branch impedance now let it be 24 the current through the branch of intervit is . I - In X Zee

Note: It dependent sources are precent in the circust this zeg = <u>Kin</u>

Outcome: Many students suggest that using the Google it-report writing strategy supported their ability to effectively explore and integrate thetopic and create flow and linkage amongst when writing their report.

Vide Jyothi Institute of Technology

(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

Department of Electrical and Electronics Engineering

BATCH: 2019-2023

Academic Year: 2020-2021 Course: NA Faculty: V.Vijaya Lakshmi

				Idim	Thresh	old 60%					MIDI	MID II Threshold 60%	40% PH			Threshold
	2			PART-A	I-A		PART-B	C-B		Same A	PART-A	T-A		PART-B	T-B	%09
S.No	Reg.No	(5) (5)	Q1(2M)	Q2(2M)	Q3 (2M)	Q4(5M)	Q5(5M)	Q6(4M)	(5) (5)	Q1(2M)	Q2(2M)	Q3 (2M)	Q4(5M)	Q5(SM)	Q6(4M)	End Exam (75M)
-	18911A0217	5	2	2	1	5	5	4	5	2	2	2	5	5	4	5
2	18911A0229	5	2	2	1	5	5	4	5	2	2	1	5	5	4	45
3	18911A0233	0	AB	AB	AB	AB	AB	AB	0	AB	AB	AB	AB	AB	AB	A
4	18911A0239	5	1	1	2	3	3	2	5	1	1	2	3	3	2	27
5	18911A0244	5	1	1	2	3	3	2	5	I	1	2	3	9	2	45
9	18911A0251	5	1	1	1	3	3	2	5	1	1	2	3	3	2	20
7	18911A0279	5	1	1	1	2	2	2	5	1	1	1	2	2	2	26
8	19911A0201	5	1	1	2	4	4	3	5	I	I.	1	4	4	3	45
6	19911A0202	5	2	2	1	4	4	3	5	2	2	1	4	4	3	26
10	19911A0203	5	AB	AB	AB	AB	AB	AB	5	AB	AB	AB	AB	AB	AB	A
Ξ	19911A0205	5	1	1	2	3	3	2	5	L.	1	1	3	3	2	50
12	19911A0206	5	2	2	1	5	5	4	5	2	2	2	5	5	4	47
13	19911A0207	5	2	2	2	5	5	4	5	2	2	1	5	5	4	49
14	19911A0208	5	2	2	1	4	4	3	5	2	2	2	4	4	3	29
15	19911A0209	5	2	2	1	5	5	4	5	2	2	1	5	5	4	45
16	19911A0210	5	2	2	1	4	4	3	5	2	2	2	4	4	9	52
17	19911A0211	5	1	1	1	4	4	3	5	1	L	2	4	4	3	45
18	19911A0212	5	1	1	2	4	4	3	5	I I	1	1	4	4	3	12
19	19911A0213	5	2	2	2	5	5	4	5	2	2	1	5	5	4	45
20	19911A0214	5	2	2	1	5	5	4	5	2	2	1	5	S	4	47
21	19911A0215	5	2	2	1	5	5	4	5	2	2	2	5	5	4	48
22	19911A0216	5	1 0	1	2	3	3	2	5	1	1	1	3	3	2	45
23	19911A0217	5	2	2	2	5	5	4	5	2	2	1	5	5	4	55
24	19911A0218	5	2	2	1	5	5	4	5	2	2	1	5	5	4	45
25	19911A0219	5	2	2	1	5	5	4	5	2	2	I	5	5	4	2
26	19911A0220	5	2	2	1	5	5	4	5	2	2	2	5	5	4	26
46	19911A0221	5	2	2	2	4	4	3	5	2	2	1	4	4	3	49
47	19911A0222	5	1	1	1	2	2	1	5	1	1	0	2	2	1	26
48	19911A0223	5	2	2	2	5	5	4	5	2	2	1	5	5	4	32
49	19911A0224	5	2	2	2	4	4	3	5	2	2	1	4	4	~	48

							-			-	Г	-	<u> </u>	-			-		Г	Г	—	Г	Г	-		-				<u> </u>								-	—	-	-			
A	28	48	64	45	49	45	47	45	57	18	6	26	31	0	48	28	6	5	28	27	45	46	48	27	46	0	12	48	0	45	52	28	48	49	. 49	12	26	51	54	26	31	26	27	36
AB	3	3	4	4	2	4	6	9	2	2	3	2	4	AB	3	3	3	4	2	4	1	4		4	0	AB	3	3	3	3	2	4	4	4	4	2	2	3	4	-	9	2	3	3
AB	4	4	5	5	3	5	4	4	3	2	4	3	5	AB	4	4	4	5	3	5	2	5	4	5	0	AB	4	4	4	4	3	5	5	5	5	2	3	4	5	1	3	2	4	4
AB	4	4	5	5	3	5	4	4	3	2	4	3	5	AB	4	4	4	5	3	5	2	5	4	5	0	AB	4	4	4	4	3	5	5	5	5	2	3	4	5	1	3	2	4	4
AB	1	2	1	2	1	2	1	-	-	0 .	1	2	2	AB	1	1	1	2	2	2	0	2	-	-	2	AB	1	1	2	1	1	2	1	2	2	0	2	2	1	0	1	0	2	2
AB	1	2	2	2	1	2	2	2	-	1	1	1	2	AB	2	1	1	2	1	2	1	2	2	2	0	AB	2	2	2	1	1	2	2	2	2	1	1	1	2	0	1	1	1	1
AB	1	2	2	2	1	2	2	2	1	1	1	-	2	AB	2	1	-	2	1	2	1	2	2	2	0	AB	2	2	2	1	1	2	2	2	2	1	1	1	2	0	1	1	1	1
5	5	5	5	5	5	5	5	5	5	5	5	5	5	0	5	5	5	5	5	5	s	s	5	5	5	0	5	5	5	5	5	5	5	5	5	5	5	5	5	5	5	5	5	5
AB	3	3	4	4	2	4	3	3	2	2	3	2	4	AB	3	3	3	4	2	4	-	4	3	4	0	AB	3	3	3	3	2	4	4	4	4	2	2	3	4	-	3	2	3	3
AB	4	4	5	5	3	5	4	4	3	2	4	3	5	AB	4	4	4	5	3	5	2	5	4	5	0	AB	4	4	4	4	3	5	5	5	5	2	3	4	5	1	3	2	4	4
AB	4	4	5	5	3	5	4	4	3	2	4	3	5	AB	4	4	4	5	3	5	2	5	4	5	0	AB	4	4	4	4	3	5	5	5	5	2	3	4	5	1	3	2	4	4
AB	1	1	1	2	1	1	2	2	2	2	-	2	-	AB	2	2	-	2	1	1	2	-	2	2	2	AB	1	2	2	2	2	1	2	1	1	1	1	2	1	1	1	2	1	2
AB	1	2	2	2	1	2	2	2	1	1	-	-	2	AB	2	-	-	2	1	2	-	2	2	2	0	AB	2	2	2	1	1	2	2	2	2	1	1	1	2	0	1	1	1	1
AB	1	2	2	2	1	2	2	2	1	1	1	1	2	AB	2	1	-	2	1	2	-	2	2	2	0	AB	2	2	2	1	1	2	2	2	2	1	1	1	2	0	1	1	1	1
5	5	5	5	5	5	5	5	5	5	5	5	5	5	0	5	5	5	5	5	5	5	5	5	5	5	0	5	5	5	5	5	5	5	5	5	5	5	5	5	5	5	5	5	5
19911A0225	19911A0226	19911A0227	19911A0228	19911A0229	19911A0230	19911A0231	19911A0232	19911A0233	19911A0234	19911A0235	19911A0236	19911A0237	19911A0238	19911A0239	19911A0240	19911A0241	19911A0242	19911A0243	19911A0244	19911A0245	19911A0246	19911A0247	19911A0248	19911A0249	19911A0250	19911A0251	19911A0252	19911A0253	19911A0254	19911A0255	19911A0256	19911A0257	19911A0258	19911A0259	19911A0260	19911A0261	19911A0262	19911A0263	19911A0264	19911A0265	19911A0266	19911A0267	19911A0268	19911A0269
	51 1			1.55			38 1			41 1	42 1		44 1	45 1		47 1				1			30	193	No.	1			60 1		62 1		64 1	1	66 1	67 1						73 1		

Theatt

76 11	19911A0270	0	7	7		0	0	4	0	7	2	2	5	S	4	H
17 10	19911A0271	5	2	2	1	5	5	4	5	2	2	1	5	5	4	45
78 1	19911A0272	5	0	0	2	0	0	0	5	0	0	2	0	0	0	49
79 1	19911A0273	5	2	2	2	5	5	4	5	2	2	2	5	5	4	26
80 1	19911A0274	5	2	2	2	4	4	3	5	2	2	1	4	4	3	45
81 1	19911A0275	5	2	2	1	5	5	4	5	2	2	I	5	5	4	28
	20915A0201	5	2	2	1	5	5	4	5	2	2	1	5	5	4	50
83 2	20915A0202	5	1	1	1	1	1	-	5	1	1	0	1	1	-	48
	20915A0203	5	2	2	1	4	4	3	5	2	2	1	4	4	3	45
	20915A0204	5	1	1	2	3	3	2	5	1	1	2	3	3	2	58
	20915A0205	5	2	2	2	5	5	4	5	2	2	1	5	5	4	29
	20915A0206	5	0	0	2	1	1	1	5	0	0	0	1	1	1	48
88 2	20915A0207	5	1	1	1	4	4	3	5	1	1	2	4	4	3	54
	20915A0208	5	1	1	2	3	3	2	5	1	1	1	3	3	2	45
90 2	20915A0209	5	2	2	1	5	5	4	5	2	2	1	5	5	4	39
	20915A0210	5	1	1	1	3	3	3	5	1	1	2	3	3	3	51
	20915A0211	5	2	2	2	5	5	4	5	2	2	2	5	5	4	48
93 2	20915A0212	5	2	2	2	4	4	3	5	2	2	1	4	4	3	62
	20915A0213	5	2	2	2	5	5	4	5	2	2	0	5	5	4	48
1.0	20915A0214	5	2	2	2	5	5	4	5	2	2	1	5	5	4	50
	20915A0215	5	2	2	2	5	5	4	5	2	2	1	5	5	4	38
	20915A0216	5	2	2	2	5	5	4	5	2	2	2	5	5	4	35
	20915A0217	5	2	2	1 - 1	4	4	3	5	2	2	1	4	4	3	61
99 2	20915A0218	5	2	2	2	4	4	3	5	2	2	2	4	4	3	46
100 2	20915A0219	5	1	1	1	2	2	1	5	1	1	0	2	2	1	48
2	20915A0220	5	1	1	2	3	3	3	5	2	2	1	4	4	3	14
102 2	20915A0221	5	2	2	2	5	5	4	5	2	2	1	5	5	4	49
	20915A0222	5	2	2	2	4	4	3	5	2	2	2	4	4	3	62
104 2	20915A0223	5	2	2	2	5	5	4	5	2	2	2	5	5	4	26
	20915A0224	5	2	2	2	5	5	4	5	2	2	1	5	5	4	56
106 2	20915A0225	5	2	2	1	4	4	3	5	2	2	2	4	4	3	39
Avera	Average marks	4.858491	1.509901	1.509901	1.514851	3.774752	3.774752	3.019802	4.858491	1.511881	1.511881	1.29703	3.779703	3.779703	3.023762	37.650485
No of stude	No of students attemped	106	101	101	101	101	101	101	106	101	101	101	101	101	101	103
No of students	No of students scored 60% and	103	61	17	101	82	82	61	103	17	17	91	82	82	62	59
%of studen	%of students scored 60%	97.169811	60.39604	60.39604	100	81.188119	81.1881.19	60.39604	97.169811	61.386139	61.386139	90,09901	81.188119	81.188119	61.386139	57.2815534
COATTAIN	CO ATTAINMENT LEVEL	0	1000	The second second	2 2	A CANADA CANADA	New Constant		11 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1		•		N. S.	Contraction of the	The same in the second second	「「日日」」「「日日」」」」

No. Barrow		ASSESS	ASSESSMENT OF COs FOR THE COURSE	THE COU	RSE	
со	Method	value	Average	Internal Exam	External Exam	Overall CO Attainment
	MID I QI	2.0			A DESCRIPTION OF THE OWNER OWNER OF THE OWNER OWNER OF THE OWNER OWNE	
CO.1	MID I Q3	3.0	2 2 2			
3	MID I Q4	3.0	C/-7			
MANAGERS	ASM-I	3.0		and the second second		
	MIDIQ2	2.0		and the		

0				230	07:7									
				1.00	W .1									
				02.0	2.4					A CONTRACTOR OF				
0	2.75 2.75 2.75 2.50													
3.0	3.0	3.0	2.0	3.0	3.0	3.0	2.0	3.0	3.0	3.0	2.0	3.0	2.0	3.0
MID1 Q3	MID I Q5	ASM-I	MID1Q6	MID 2 Q4	ASM-I	II-WSW	MID 2 QI	MID 2 Q3	MID 2 Q5	II-WSW	MID 2 Q2	MID 2 Q3	MID 2 Q6	ASM-II
003	4	Contraction of the second		503	3			LO1	+ 22			cos	3	



Vidya Jyothi Institute of Technology

(An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

BATCH 2019-2023

Course End Survey Analysis

Constant and the	II-I –A	Sec(Academic Y	ear 2020 - 20	21)	
Year/Sem:II-I	Substantially High	Moderate	Low	Total	Attainment
Network Analysis	44.4	8.2	0.4	53	2.82

	3	2	1	Assessment	TOTAL
CO1	44	8	1	2.81	53
CO2	45	8	0	2.84	53
CO3	43	10	0	2.81	53
CO4	48	5	0	2.90	53
CO5	42	10	1	2.75	53
	44.4	8.2	0.4	2.82	53

Vidya Jyothi Institute of Technology (Autonomous) (Accredited by NBA, Approved By A.I.C.T.E., New Delhi, Permanently Affiliated to JNTU, Hyderabad) (Aziz Nagar, C.B.Post, Hyderabad -500075)

			II EEE	-II sem-	A Sec	
S.No	Roll.No			NA		
	a the state of	CO1	CO2	CO3	CO4	COS
1	19911A0201	3	3	3	3	3
2	19911A0202	3	3	3	3	3
3	19911A0203	3	3	3	3	3
4	19911A0205	3	3	3	3	3
5	19911A0206	3	3	3	3	2
6	19911A0207	3	3	3	3	3
7	19911A0208	3	3	3	3	3
8	19911A0209	3	3	3	3	3
9	19911A0210	3	3	2	3	3
10	19911A0211	3	3	3	3	3
11	19911A0212	3	3	3	3	2
12	19911A0213	3	2	3	2	3
13	19911A0214	3	3	2	3	3
14	19911A0215	3	3	3	3	3
15	19911A0216	2	3	3	3	3
16	19911A0217	3	2	2	3	3
17	19911A0218	3	3	3	2	2
18	19911A0219	3	3	3	3	3
19	19911A0220	3	3	3	3	2
20	19911A0221	3	3	3	2	3
21	19911A0222	2	3	3	3	3
22	19911A0223	3	3	3	3	3
23	19911A0224	3	3	2	3	3
24	19911A0225	3	3	3	3	3
25	19911A0226	3	3	3	3	2
26	19911A0227	3	2	2	3	3
27	19911A0228	2	3	3	3	3
28	19911A0229	3	2	3	3	3
29	19911A0230	3	3	3	2	3
30	19911A0231	3	3	3	3	3
31	19911A0232	2	3	3	3	3
32	19911A0233	3	3	3	3	3
33	19911A0234	3	3	3	3	3
34	19911A0235	3	2	3	3	2
35	19911A0236	2	3	2	3	3
36	19911A0237	3	3	2	3	2
37	19911A0238	3	2	3	3	3
38	19911A0239	3	3	3	3	3
39	19911A0240	3	3	3	2	2
40	19911A0241	3	3	3	3	3
41	20915A0201	3	3	3	3	3
42	20915A0202	1	3	3	3	3
43	20915A0203	3	2	2	3	2

20915A0204	2	3	3	3	3
20915A0205	3	3	3	3	3
20915A0206	3	3	3	3	3
20915A0207	3	3	3	3	1
20915A0208	3	3	3	3	3
20915A0209	3	3	2	3	3
20915A0210	3	3	3	3	2
20915A0211	3	3	3	3	3
20915A0212	2	2	2	3	2
20915A0213	3	3	3	3	3
	2.83019	2.84906	2.81132	2.90566	2.75472
	20915A0205 20915A0206 20915A0207 20915A0208 20915A0209 20915A0210 20915A0211 20915A0212	20915A0205 3 20915A0206 3 20915A0207 3 20915A0207 3 20915A0208 3 20915A0209 3 20915A0210 3 20915A0211 3 20915A0212 2 20915A0213 3	20915A0205 3 3 20915A0206 3 3 20915A0207 3 3 20915A0207 3 3 20915A0208 3 3 20915A0209 3 3 20915A0210 3 3 20915A0211 3 3 20915A0212 2 2 20915A0213 3 3	20915A0205 3 3 3 20915A0206 3 3 3 20915A0207 3 3 3 20915A0207 3 3 3 20915A0207 3 3 3 20915A0208 3 3 3 20915A0209 3 3 2 20915A0210 3 3 3 20915A0210 3 3 3 20915A0211 3 3 3 20915A0212 2 2 2 20915A0213 3 3 3	20915A0205 3 3 3 3 20915A0206 3 3 3 3 20915A0206 3 3 3 3 20915A0207 3 3 3 3 20915A0207 3 3 3 3 20915A0208 3 3 3 3 20915A0209 3 3 2 3 20915A0210 3 3 3 3 20915A0211 3 3 3 3 20915A0212 2 2 2 3 20915A0213 3 3 3 3

Av	era	ge=	=2.	82
	Ciu	BC-		02



Vidya Jyothi Institute of Technology (An Autonomous Institution) (Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH) Aziz Nagar Gate, C.B. Post, Hyderabad-500 075 DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Batch 2019-2023

COURSE CLOSURE REPORT


S.No	Parameters	Section	A SEC
		Course Name	Network Analysis
_		Allotted Faculty	V.Vijaya Lakshmi
1	Quality of I/II-mid question paper or not) submitted to the exam sect	s(As per Blooms Taxonomy ion	
2	No of students registered for the ex-	xam	53
3	No of students appeared for the ex	am	
4	No of students passed		51
5	Pass percentage		45
6			88.23.1/2
1.1.1	End exam result analysis (pass per		p
7	End exam result analysis (pass per	centage 80% to 90%)	3
8	End exam result analysis (pass per		6
9	End exam result analysis (pass per		
10	End exam result analysis (pass per		12
	2nd chain result analysis (pass per	centage <00%)	32

ASSIGNMENT-1

Ch-Chetasa 19911A0217

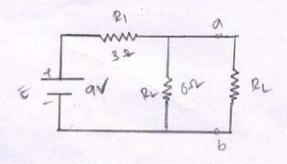
1. State Norton's Theorem and find Norton's Equivalent for the circuit shown.

In any linear bi-laternal network having number of active and passive elements , it can be replaced by single equivalent circuit consistiting of equivalent current source (IN) in parallel with equivalent resistance (RN).




To find RN ?-

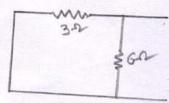Open circuit the load tarminal R' and shout circuit the voltage source


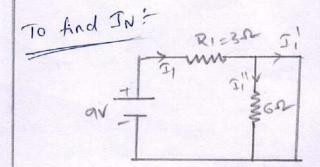
$$R_{\rm N} = \frac{3\times6}{3\times6} = \frac{18}{9} = 3\Omega,$$




Due to short circuiting the load terminal, arrent does not flow through Gal resistor.

$$\mathcal{D}_{N} = \frac{9}{6} = \frac{3}{2} A_{\parallel}$$

Novton's equivalent circuit

$$\int J_{L} = J_{N} \times \frac{R_{N}}{R_{N} + R_{L}}$$

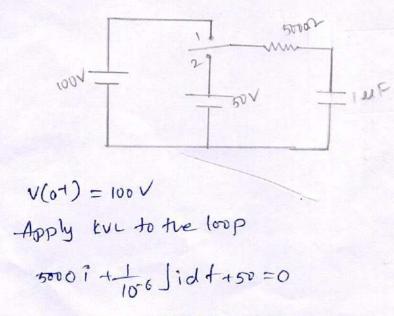2. Switch is moved from position I to 2 at 1=0 find the voltage Vp(1) and Vct) for 1=0



5000 i + 106 Jidt= - 50

differentiate on both sides

$$stoo \frac{di}{dt} + 15^{6} i = 0$$

$$\frac{di}{at} + \frac{10^{6}}{5tro} i = 0$$

$$\frac{di}{at} + \frac{10^{6}}{5tro} i = 0$$

$$\frac{di}{at} + 200i = 0$$

$$\frac{di}{at} + 20i =$$


1 Staff bab Stal

T=RC

3. State and Prove the maximum power transfer theorem for both Ac and DC excitation.

In an active network movimum power transfer to the load takes place when the load resistance is equal to equivalent resistance of the network as viewed from the terminals of the load.

Proof for DC

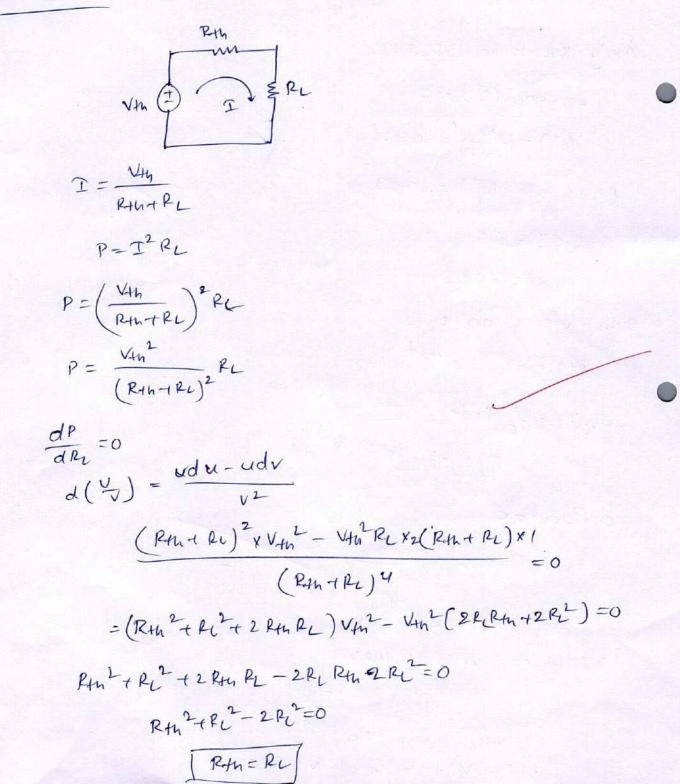

$$P_{max} = \frac{V_{h}n^{L}}{(P_{L}+P_{L})^{2}}P_{L}$$

$$= \frac{V_{h}n^{L}}{(22L)^{L}}P_{L} = 3 - \frac{V_{h}n^{L}}{(12L)^{L}} \times P_{L}$$

$$P_{max} = -\frac{V_{h}n^{L}}{(22L)^{L}} + \frac{V_{L}}{V_{L}}$$

$$P_{max} = -\frac{V_{h}n^{L}}{V_{L}}$$

$$P_{max} = -\frac{V_{h}n^{L}}{V_{L}}$$

$$T_{max} = -\frac{V_{h}n^{L}}{V_{L}}$$

$$T_{L} = -\frac{V_{h}n^{L}}{V_{L}} + \frac{V_{h}n^{L}}{(P_{h}n+P_{L})^{L}} + \frac{V_{h}n^{L}}{(P_{h}n+P_{L})^{L}}$$

$$T = -\frac{V_{h}n^{L}}{\sqrt{(P_{h}n+P_{L})^{L} + (X_{h}n+X_{L})^{L}}}$$

$$P = -\frac{V_{h}n^{L}}{(P_{h}n+P_{L})^{L} + (X_{h}n+X_{L})^{L}} \times P_{L}$$

$$\frac{dP}{dX_{L}} = 0$$

$$\frac{(P_{h}n+P_{L})^{L} - ((X_{h}n+X_{L})^{L} \times 0 - V_{h}n^{L}P_{L} \times 2(A_{h}n+X_{L})^{L})}{((P_{h}n+P_{L})^{L} - ((X_{h}n+X_{L})^{L})^{L}} = 0$$

$$\frac{1}{\sqrt{2}} \frac{1}{\sqrt{2}} \frac{1}{\sqrt{2}$$

$$\frac{dP}{dR_{L}} = 0$$

$$\frac{\left(R_{LM} + R_{L}\right)^{2} + \left(X_{LM} + X_{L}\right)^{2} \vee t_{M}^{2} - \vee t_{M}^{2} R_{L} + \Re\left(R_{LM} + R_{L}\right) \times 1\right)}{\left(R_{LM} + R_{L}\right)^{2}}$$

$$= > P_{LM}^{2} + 1 R_{L}^{2} + 1 R_{LM}R_{L} + 0 - 2 R_{L} R_{LM} - 2R_{L}^{2} = 0$$

$$R_{LM}^{2} - R_{L}^{2} = 0$$

$$\frac{R_{LM}^{2} - R_{L}^{2} = 0}{\left(\frac{R_{L}}{2} - \frac{R_{L}}{2}\right)^{2}}$$

$$P_{MW}(c_{L}(m_{M}R_{L})) = \frac{V_{LM}^{2}}{\left(\frac{R_{L}}{2} - \frac{R_{L}}{2}\right)^{2}}$$

$$P_{mak} = \frac{V_{LM}^{2}}{V_{RL}}$$

In the circuit shown in figure, switch S is in position I for a 4. long time and knought to position 2 in time . Detamine the circuit current. 3 2H $i(\bar{0}) = \frac{50}{5} = 10A$ 5012 i (ot)= 10A Apply KUL to the loop, -10+51 (1)+2 di(t) =0 $5i(t) + 2 \frac{di(t)}{dt} = 10$ $\frac{d_{i}(t)}{d_{i}(t)} \neq \frac{5}{2}i(t) = \frac{10}{2}$ did) + 5i(d) = 5 $e^{5/2t}\left(\frac{di(t)}{dt}+\frac{5}{2}i(t)\right)=5e^{3/2t}$ $e^{5/2} \frac{di(d)}{dt} + \frac{5}{2}i(d)e^{-5/2t} = 5e^{-5/2t}$ d+ (ill). e3/2t7 = 5 e3/2t d (it). e3/27 = 5e3/27 dt integrate on both sides]d (idt e3/2+]=5 [e3/2+ dt

$$i(t) \cdot e^{5ht} = 5 \int e^{5/2t} dt + C,$$

$$i(t) \cdot e^{5/2t} = 3 \frac{e^{5/2}}{5/2} + C,$$

$$i(t) \cdot e^{5/2t} = 2e^{5/2} + 9,$$

$$i(t) = 2 + C, e^{-5/2t} - 0,$$
Apply initial conditions; At $t = 0$, $i(0^{+}) = 10^{-1}$

$$i(0^{+}) = 2 + C, e^{-5/2t},$$

$$10 = 2 + C, e^{-5/2t},$$

$$10 = 2 + C, e^{-5/2t},$$

$$i(t) = 2 + 8e^{-5/2t},$$

$$i(t) = 2 + 8e^{-5/2t},$$

$$i(t) = 2 + 8e^{-5/2t},$$

N. 1.1.1

$$de+(A \times A^{T}) = \begin{pmatrix} 1 & 1 & 0 & 0 & 10 \\ 0 & -1 & 1 & 0 & 0 & -1 \\ 0 & 0 & -1 & 1 & -1 & 0 \end{pmatrix} \begin{pmatrix} 1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \\ 0 & 0 & 1 \\ 1 & 0 & -1 \\ 0 & -1 & 0 \end{pmatrix}$$

$$= \begin{bmatrix} 1+1+1 & -1 & -1 \\ -1 & 1+1+1 & -1 \\ -1 & -1 & 1+1+1 \end{bmatrix} = \begin{bmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix}$$

$$de + (A \times B^{\dagger}) = 3 \begin{vmatrix} 3 & -1 \\ -1 & 3 \end{vmatrix} - (-1) \begin{vmatrix} -1 & -1 \\ -1 & 3 \end{vmatrix} - (-1) \begin{vmatrix} -1 & -1 \\ -1 & -1 \end{vmatrix}$$
$$= 3 (9 - 1) + 1 (-3 - 1) - 1 (1 + 3)$$
$$= 3 (8) + 1 (-4) - 4$$
$$= 24 - 4 - 4$$
$$= 16\mu$$

Suled ...

The number of possible trees one 16,"

ASSIGNMENT-I

B Snavan 19911 # 0210

$$\frac{ABCD - Parameters}{Condition for Symmetry N/N
N_1 = AV_2 - BI2
I_1 = CV_2 - DI2
O.C port(2), I_2 = D
V_1 = AV2
I_1 = CV2
 $\frac{V_1}{I_1} = \frac{AV_2}{CV2} = \frac{A}{C}$
 $\frac{V_2}{I_1} = \frac{A}{C}$
O.C port(0) I_1 = 0
 $\frac{V_1}{I_1} = \frac{A}{C}$
O.C port(0) I_1 = 0
 $\frac{V_2}{I_1} = \frac{D}{C}$
 $\frac{V_2}{I_2} = \frac{D}{C}$
 $\frac{V_2}{I_2} = \frac{D}{C}$
 $\frac{V_2}{I_1} = \frac{V_2}{C} = \frac{A}{C} = \frac{D}{C}$
 $\frac{V_2}{I_1} = \frac{V_2}{C} = \frac{A}{C} = \frac{D}{C}$
 $\frac{V_2}{I_1} = \frac{V_2}{C} = \frac{A}{C} = \frac{D}{C}$$$

$$\begin{array}{c} \boxed{\text{ordition for } \text{ } \text{reciprocal } \text{ who}} \\ \hline{\text{short circuit } } \text{ } \text{ } \text{pat} (2) \ V_2 = D \\ V_1 = -B(-T_2) = BT_2^1 \\ \overrightarrow{H_2} = \overrightarrow{H_1} \rightarrow V_1 = V_2 = \overrightarrow{V_2} = \overrightarrow{H_1} \\ \overrightarrow{H_2} = \overrightarrow{H_1} \rightarrow V_1 = V_2 = \overrightarrow{V_2} = \overrightarrow{H_1} \\ \hline{H_2} = \overrightarrow{H_1} \rightarrow V_1 = V_2 = BT_2 \\ \overrightarrow{H_2} = AV_2 - BT_2 \Rightarrow AV_2 = BT_2 \\ \overrightarrow{H_2} = \overrightarrow{H_2} \vee 2 \\ \overrightarrow{H_2} = CV_2 - BT_2 \\ = CV_2 - BT_2 \\ \overrightarrow{H_2} = ABV_2 \\ \overrightarrow{H_1} = -BC - AD \\ \overrightarrow{H_2} = -BC \\ \overrightarrow{H_1} = -BC - BC \\ \overrightarrow{H_2} = V_2 \\ \overrightarrow{H_1} = -BC \\ \overrightarrow{H_2} = V_2 \\ \overrightarrow{H_1} = -BC \\ \overrightarrow{H_2} = V_2 \\ \overrightarrow{H_1} = -BC \\ \overrightarrow{H_2} = V_2 \\ \overrightarrow{H_1} = -CV_2 \\ \overrightarrow{H_2} = -CV_2 \\ \overrightarrow{H_1} \\ \overrightarrow{H_2} = -CV_2 \\ \overrightarrow{H_1} = -CV$$

E-T. Ghiveist

A three phase balanced delta connected load of (4-j8)l is connected across a roor, Z-& balanced Supply. Détermine the phase currents and line current Assume The phase of Sequence to be RUB also Calculate the power drawn by laad. Given data 80 F= 4-j8 $V_L = V_{Pb} = 400V$ Jph & IL = ? $\cos\phi = \frac{R}{121}$ Iph = Uph Rph = $\frac{4}{\sqrt{4^2+k^2}}$ = 400 Ppn = 100 A I = V3 Iph = $\frac{4}{\sqrt{80}}$ = 13 [100] $= \frac{4}{89}$ J_= 173.20 A Cost= 0.4 P=Jz V, I Cost $= \sqrt{3} (400) (17.3.20) (0.4) = 48026.3 M/$

(3) Find the z-parameters for the following reducers from basics,


$$1 + \frac{24}{1} + \frac{24$$

Put
$$eqn \oplus in \mathbb{O}$$

 $\Im_{1}^{2} - \Im_{3}^{2} = V_{1}$
 $\Im_{1}^{2} - \Im_{3}^{2} = V_{1}$
 $\Im_{1}^{2} - \Im_{3}^{2} = V_{1}$
 $\Im_{1}^{2} - \Im_{3}^{2} - 4\Upsilon_{1} + 6\Upsilon_{2}$
 $V_{1}^{2} = \frac{\Im_{1}^{2} - 4\Upsilon_{1} + 6\Upsilon_{2}}{\Im}$
 $V_{1}^{2} = \frac{\Im_{1}^{2} - 4\Upsilon_{1} + 6\Upsilon_{2}}{\Im}$
 $V_{1}^{2} = \frac{\Im_{1}^{2} - 4\Upsilon_{1} + 6\Upsilon_{2}}{\Im}$
 $V_{2}^{2} = 3\Im_{2}^{2} + \frac{\Im_{1}^{2}}{\Im}$
 $V_{2}^{2} = 3\Im_{2}^{2} + 3[\frac{2\Im_{1}^{2} - 3\Im_{2}}{\Im}]$
 $V_{2}^{2} = 3\Im_{2}^{2} + 3[\frac{2\Im_{1}^{2} - 3\Im_{2}}{\Im}]$

 $V_{1} = \frac{1}{5} I_{1} + \frac{3}{4} I_{2}$ $= \frac{3}{4} I_{1} + \frac{15}{8} I_{2}$ Compare the above eqn with z -parameter Conditions. $V_{1} = I_{1} z_{11} + I_{2} \overline{z}_{12}$ $V_{2} = I_{1} \overline{z}_{1} + I_{2} \overline{z}_{22}$ $V_{2} = I_{1} \overline{z}_{1} + I_{2} \overline{z}_{22}$ Then $z_{1} = \frac{1}{5} , \quad \overline{z}_{12} = \frac{3}{4}$ $\overline{z}_{31} = \frac{3}{4} , \quad \overline{z}_{32} = \frac{15}{8}$

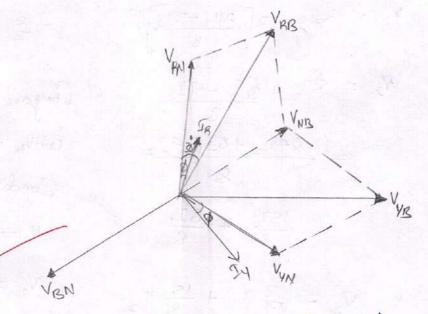(A) Obtain power equation using Q-Wattmeter method for Balanced and Unbalanced Systems. Measurement of Active power by Two-Wattmeter method. Fig shows a balanced star-Connected load and this load may be accumed to be inductive, het VRN, VYN and VRN be the three phase Whages and Ir, Iy and Is be the phase currents. The phase Currents will they behind their respective phase Chollages by angle of. Current through Courrent Coil of W, = IR Notage across Notage coil WI = VRB = VRN + VNB = VRN-VBN fig shows the phasor diagram of balanced star- Connected inductive load.



from the phasor diagram, it is clear that the phase angle blu VRB and IR is (20°-0) WI=VRBIRCOS(20°-0)

Current through Current Coil grow_= Iy Voltage across Voltage Coil of W2 = V4B = V4N +VNB = VAN -VBN

$$W_1 - W_2 = V_L I_L sind$$

The total reactive power in a three-phase System is given by . &= VIV_ISING = VI(W1-W2)

Thus, total reactive power of a three-phase system is obtained by multiplying the difference of two-wattmeter reading by v3.

Write down the indedence matrix and 0.252 6 atset matrices for the circuit shown 152 in the figure. (2) (4) (4) (5)incidence Matrix. => Reduced incidence Matrix $A = \begin{cases} 1 & 2 & 3 & 4 & 56 \\ 1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 4 & 0 & 1 \\ 3 & 0 & 0 & -1 & -1 & 1 & 0 \end{cases}$ ()) (6) (5) C-1: 21, 2, 3} C-2: {1,5,6} C-3: {3, 4, 5}


Network Analysis:

UNIT-I

Prepared by V. Vijaya Lakebroi EEE Dept.

Network Theorems (Dc & Ac), Mesh and Nodal Analysis

Mich: Mich (or loop) is a set of branches forming a closed path in a network in such a way that if one branch is removed then remaining branches do not form a closed path. A loop also can be defined as a closed path which originates from a particular mode, terminating at the same node, travelling through various other modes without travelling through any mode twice. In the fig. paths A-B-C-D-A, A-B-C-F-E-D-A, D-C-F-E-D etc are loops of the network.

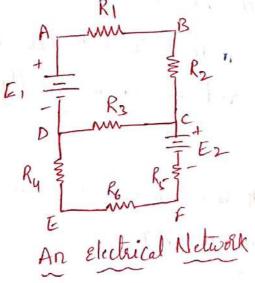

Node: A point at which two or more elemente are joined together is called a node. The junction pointe are also the modes of the network. In the network shown in the Fig. A, B, C, D, E and F are the nodes of the network.

Loop Analysis & Mesh Analysis:-

This method of analysis is specially usful for the circuite that have many moder and loops. The difference between application of kirchoff's laws and loop analysis is, in loop analysis instead of branch currente, the loop currente are considered for witting the equations. The another difference is each branch of the network may carry more than one current. The total branch current must be decided by the algebraic sum of all unrents through that branch. While in analysis using kischoff's laws, each branch current carries only one current. The advantage of this method is that for complex metwork the membra of unknowns reduces which greatly simplifies

calculation work.


Consider following metwork shown in Fig. There are two loops. So assuming two loop currents as I, and Ir $V_1 \bigoplus_{I_1}^{R_1} \frac{B}{I_2} \frac{R_2}{I_2} \bigoplus_{I_2}^{R_3} \frac{D}{I_2} \frac{V_2}{I_2}$


While assuming loop currente, Consider the loops such that each element of the network will be included atleast once in any of the loops.

Now Branch B-E Carries two currenté I, from Bto E and Iz from E to B. So not userent through branch B-E will, (I,-I2) and Corresponding deep across R3 must be as shown below in Fig.

For branch B-E, polarities of voltage drops will be B +ve, E -ve for current I, while E +ve, B -ve for current I list it. N D Consider loop A-B-E-F-A Is flowing through Rs. Now while writing loop equations assume main loop current as positive and remaining loop current must be treated as negative for common branches. Writing loop equations for the network shown in the Fig $\begin{array}{c} A \\ (\underline{+}) \\ ($ For loop A-B-E-F-A $-I, R, -I, R_3 + I_2 R_3 + V, = 0$ For loop B-C-D-E-B $-J_2R_2 - V_2 - J_2R_3 + I, R_3 = 0$ By solving above simultaneous equations any unknown branch current can be determined

I While assuming loop currents make sure that atleast one loop ausent links with every element. 2. No two loops should be identical. 3. Choose minimum number of loop currents. 4. If current in a particular branch is required, then try to choose loop current in such a way that only one loop current links with that branch. -> If a metwork has large no of voltage rouries it is useful to use Mech analysis. KVL + Ohm'e law = Mish analysie -> Mesh analysis is only applicable for planar network For non planar circuite mesh analysis is not applicable. A Circuit is said to be planar if it can be drawn on a planar surface without trossovers. A non planar circuit Carit be deavon on a plane kueface without a crossover.

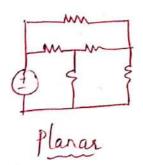

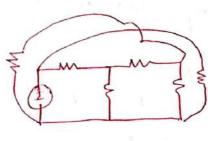

Non planar


¹⁴
Check:
→ Check whether the circuit is
planas or not:
→ Select mesh currents
→ While kvi for every loop & holve it
for mesh ()
$$V_{5} = \hat{i}_{1}R_{1} + R_{2}(\hat{i}_{2} - \hat{i}_{2})$$

($\hat{\mathbb{C}}$ $R_{3}i_{2} + R_{4}i_{2} + R_{2}(\hat{i}_{2} - \hat{i}_{1}) = 0$
No of Mich equations = No of branches - (No of moder-1)
 $M = B - (N - 1)$
In the above obt
 $M = 5 - (4 - 1) = 2$
Problem 1: Write mesh currents equations in the circuit shown
and determine the currents equations in the circuit shown
and determine the currents $-\frac{5D}{i_{1}} - \frac{1}{2}i_{0}D_{1}}{\int_{1} - \frac{2D}{i_{1}} - \frac{1}{2}i_{0}D_{1}} = 5 - \sqrt{1}$
Problem 1: Write mesh currents equations in the circuit shown
and determine the currents $-\frac{5D}{i_{1}} - \frac{1}{2}i_{0}D_{1}}{\int_{1} - \frac{2D}{i_{2}} - \frac{1}{1}} = 5 - \sqrt{1}$
Problem 1: The mesh ()
 $10 - 5i_{1} - 2(i_{1} - i_{2}) = D = -7i_{1} + 2i_{2} = -10 \rightarrow 0$

Apply KVL to mech @ -1012-50-2(12-1,)=) 21,-1212=50→@

 $i_1 = 0.25A$ $i_2 = -4.125A$

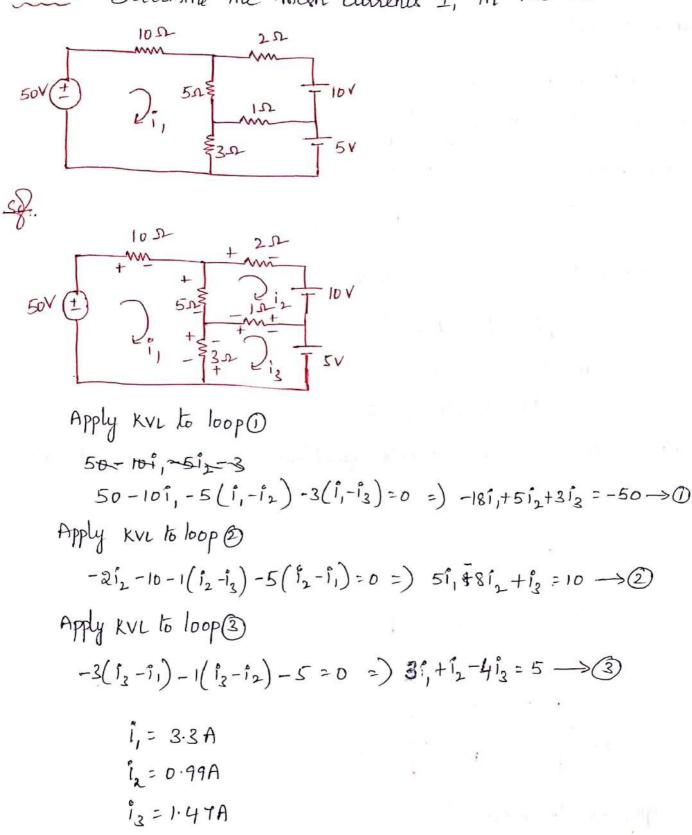Problem 2: Determine the mesh currente I, in the Circuit shown



Much Current Analysis with Current Source:
Much Current i, is equal to is

$$i_{1,c}$$
, $i_{1} = i_{3}$
 $\rightarrow klvite Kr. f.e. Accord loop
 $-R_{3}i_{3} - V_{5} - R_{2}(i_{2}-i_{1}) = 0$
 $V_{5} = i_{1}R_{2} - i_{2}(R_{2}+R_{3})$
Since $i_{1} = k$
 $\frac{V_{5} - i_{6}R_{2}}{R_{2}+R_{3}} = -i_{2} =) I_{2} = -\frac{V_{5} + i_{6}R_{4}}{R_{4}+R_{3}}$
 $\stackrel{V_{5}}{\longrightarrow} Reserve all Current Sources Acduces the model mesh equation
in mesh analysis.
Problem 1:-
Using mesh analysis find 'i' in the circuit shown in fig.
 $IIMA \bigoplus \sum_{i_{1}}^{2} \frac{V_{4}R_{4}}{V_{4}} = \frac{V_{5}}{R_{4}} \bigoplus UMA$
 $IIMA \bigoplus \sum_{i_{1}}^{2} \frac{V_{4}R_{4}}{V_{4}} = \frac{V_{5}}{R_{4}} \bigoplus UMA$
From the circuit $I_{1} = IIMA$, $i_{3} = -4MA$
Apply Kr. is mesh \bigotimes
 $-3000(i_{2}-5000(i_{2}-i_{3})-4000(i_{5}-i_{1})=0$
 $\frac{V_{600i_{1}}-12000i_{2}+5000(i_{3}=0)}{R_{4}} = 0$ where V is the end of V is the end V is the end V is the end V is the end V in V .$$


mann (D.D. 3) are mech equations $\rightarrow a, b, c, d$ (c/f/g/h) are mode /junctione. -> Mich ie defined as a loop which doesnot Contain any other loop. → loops → D, D, B, B, D, D are loops -> Much is always a loop . But every loop not a mesh Mech equations = M = [B - (N-1)] = 7 - (5-1) = 7 - 4 = 3 Supa Mush: A supament occurs when a current bource is contained between two exertial meshes. It is a larger much created from two methes that has an independent or dependent current tource as a common element. Super Mesh Analysie :-

When a cutrent tousce is common to two meshes then we use the concept of Ruper mesh to analyze the circuit using mesh current method.

A Supermech encloses more than one mech. for each common current source between two meches, the no. of meshes reduces by one, thus reducing the no of independent mesh equation Scanned by CamScanner by one.


If In the fig. is the current course common to mech DGD. Now we can create supermesh shown in dotted line as in fig that consists of the interior of mach OGD. 2 k_2 k_3 k_4 Now we can apply KVL for super mesh $R_{11} + R_{3}(i_{2} - i_{3}) = \vee =) R_{11} + R_{31} - R_{31} + \vee \longrightarrow \bigcirc$ Consider mech 3 $-R_{3}(i_{3}-i_{2})-R_{4}i_{3}=0=)R_{3}(i_{3}-i_{2})+R_{4}i_{3}=0\longrightarrow @$ Finally the current is from current source is equal to difference between two meshes currente i.e., $i_1 - i_2 = i_2 \rightarrow (2)$ From O, OG @ we calculate is. Super Mish analysis = Ohm's Law + KVL + KCL Problem: Determine userent in 552 resistor in the metuodic given in figure. 50V (=) 2°, 202 212 22 50V (=) 2°, 202 22 50V (=) 2° 1

1.8

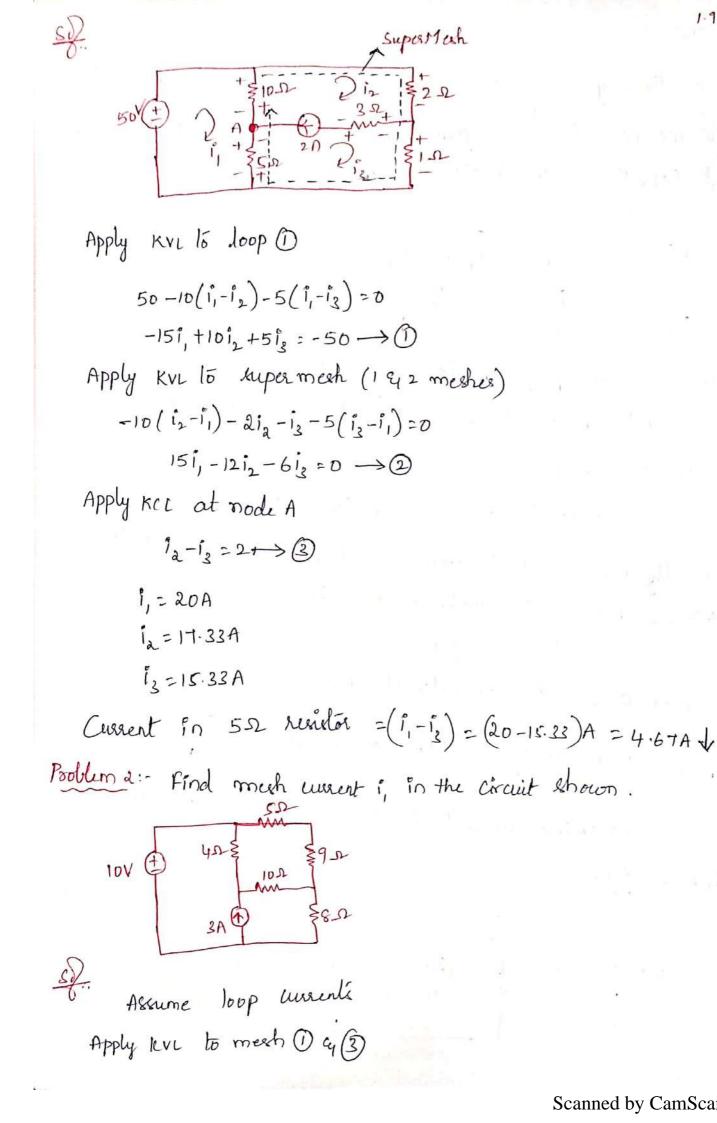

Scanned by CamScanner

1.9

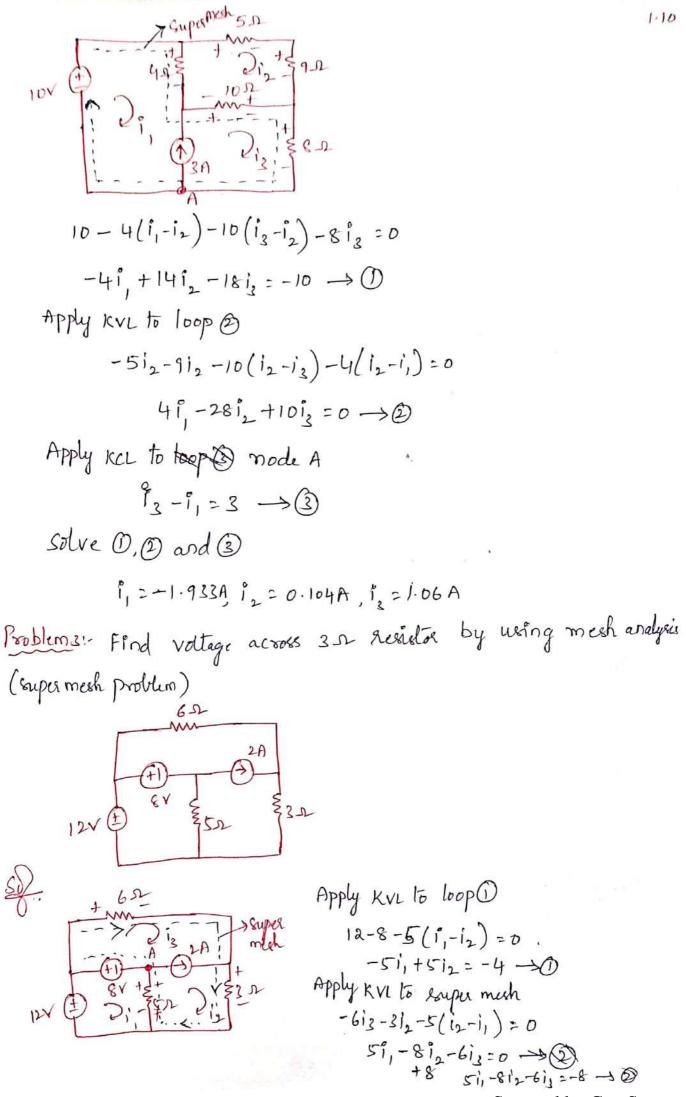


Apply KCL at node A

$$i_2 - i_3 = 2 \Rightarrow 3$$

 $i_1 = 3.46A$, $i_2 = 2.66A$, $i_3 = 0.66A$

Dependent Sources Mesh Method Problems:-

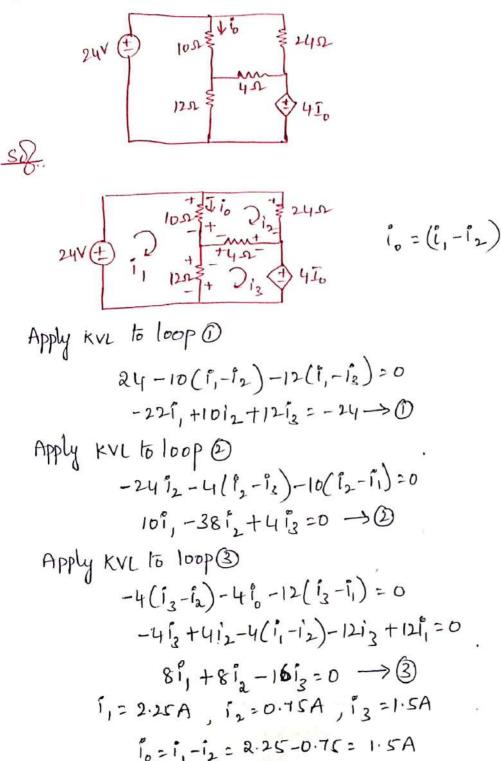
Problem 1: - Find the avent is for the Circuit known in the figure.




Scanned by CamScanner

1.11

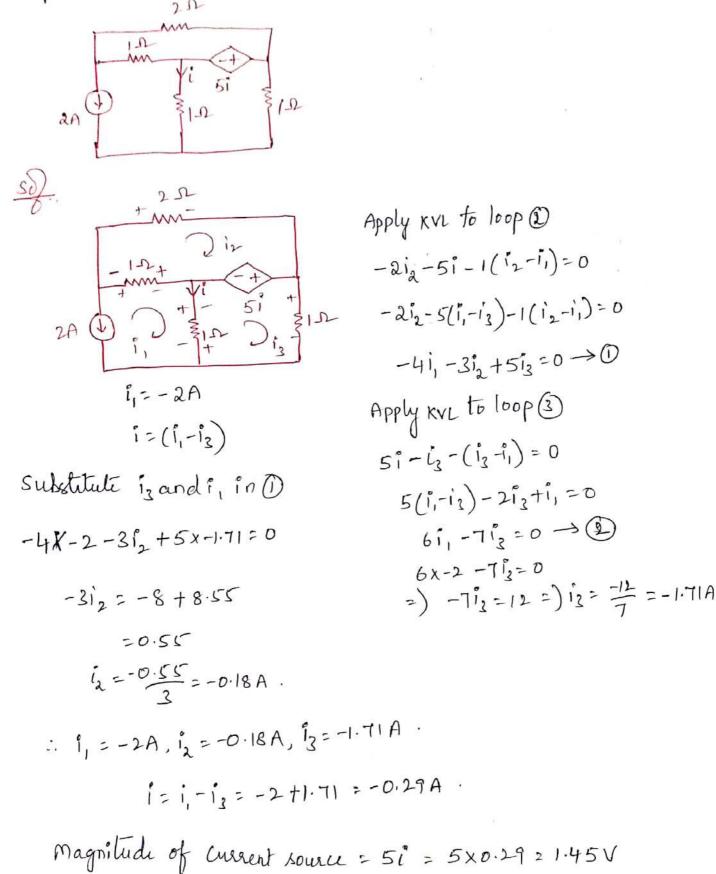Problem 2. Veing Mich analysis find the magnitude of Guarent 1.12 dependent source and current through 2D remetor.




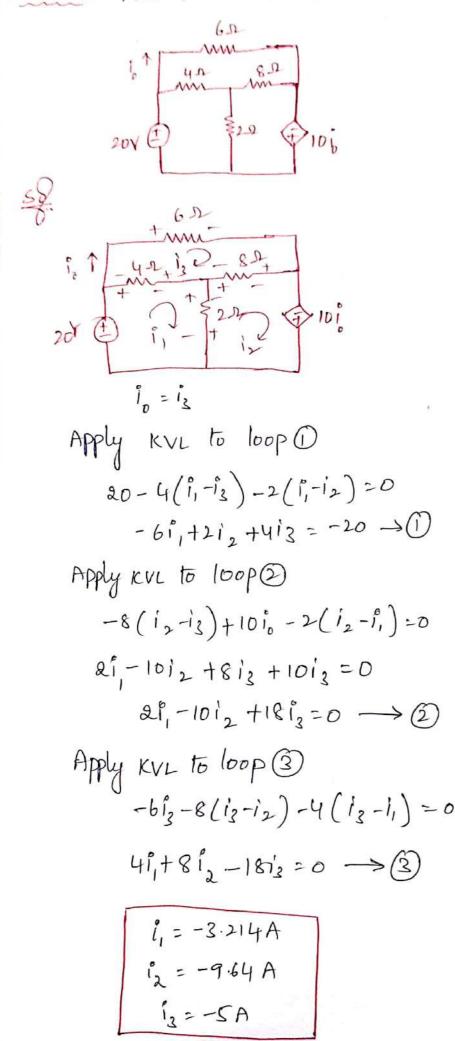
Problems ... Find the current is in the circuit shown in fig.



Dependent Source Super Mesh Problems:-

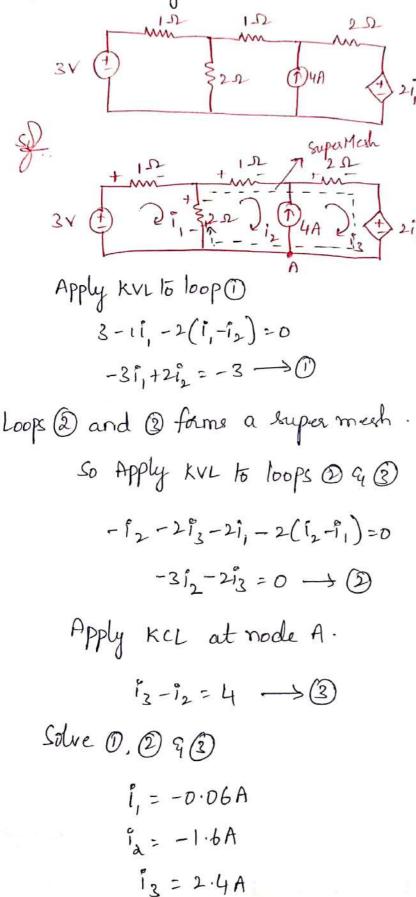Boblem: Find the loop currente i, , is and is in the metroork of by mesh analysie.



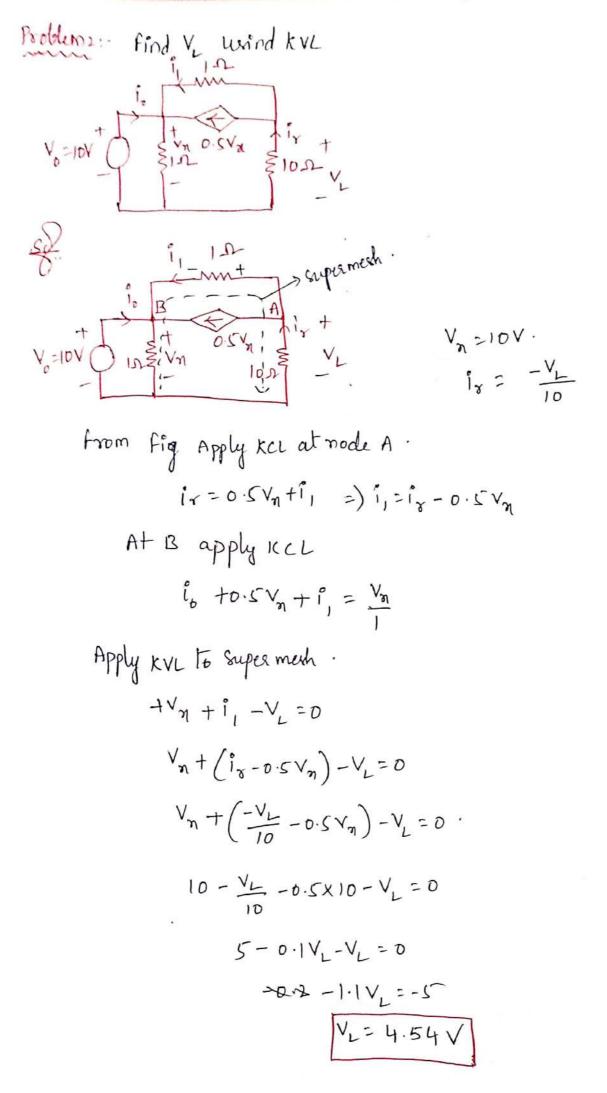

Nodal Analycia:-

This method is mainly based on Kirchoff's Current Law (KCI). This method uses the analysis of different modes of the network. Every junction point in a network where two or more branches much is called a mode.

If network has more current sources we use nodal analysie.


→ In general circuit in a'N' mode circuit, one of the modes is chosen as reference mode or datum mode, then it is possible to write (N-1) mode equations by assuming (N-1) mode voltages.

→ In general circuit reference mode we assume at zero potential of ground.

→ The mode voltage is the voltage of a given mode with respect to one particular mode, Called Reference mode which is assumed at zero potential.


→ Scheit a mode as a reference mode. Assign voltages to other modes as V, V2 ---- Vn-1 to remaining (m-1) modes. The voltages are referenced with respect to the reference mode-→ Apply KCL to each of the (m-1) non reference modes. Use ohm's law to express the branch cusents in terms of mode voltages

-> Solve the resulting simultaneous equations to obtain 1.17 the unknown mode voltages. The reference node is commonly called as ground since it is assumed to have zero potential. The node voltage is the voltage of a given node with respect to one particular node, called the reference node, which we assume at zero potential 1 fr f Current flows from higher potential to lower potential in a runeta. At mode () I (P) SR, TI (P) SR, TI (P) SR, $I_1 \oplus \frac{R_2}{R_1} = \frac{R_2}{R_2} = \frac{R_4}{R_1}$ Eg: Apply Kel at node O At node 2 Ra 2 Ry Ra Ra Ry TRE RE THE THE $\frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} - \frac{T_1}{T_1} = 0$ $\frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} = \tilde{I}, \longrightarrow \tilde{O}$ $\frac{V_2 - V_1}{R_2} + \frac{V_2}{R_2} + \frac{V_2}{R_3 + R_5} = 0 \longrightarrow (2)$ Reasoning the above equations $V_{1}(\frac{1}{R_{1}}+\frac{1}{R_{2}})-V_{2}(\frac{1}{R_{2}})=1,$ $V_{1}\left(\frac{-1}{R_{2}}\right) + V_{2}\left(\frac{1}{R_{2}} + \frac{1}{R_{2}} + \frac{1}{R_{4}}\right) = 0$ By solving the above equations, we obtain V, and V2 Vollagues at each mode.

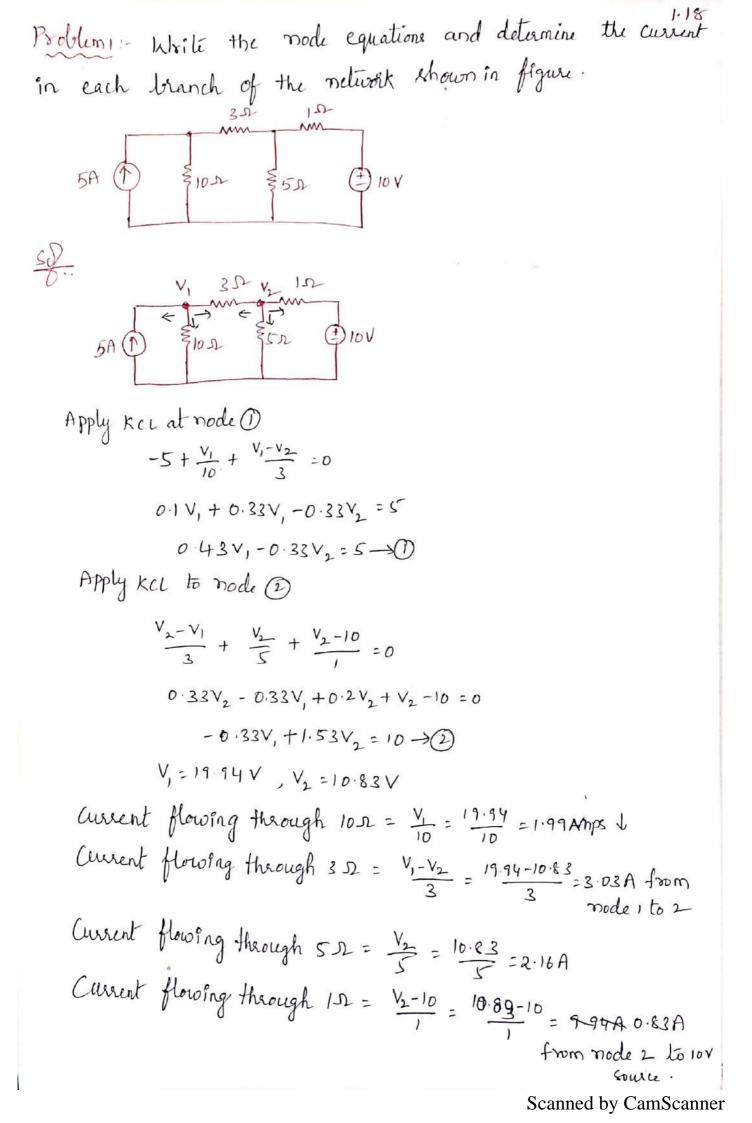

Determine the voltages at each node for the Circuit Problem 2:-V, 3-2 OSA 128 \$6.2 ION C 352 ION Apply KCL at node D $\frac{V_{1}-10}{10} + \frac{V_{1}}{5} + \frac{V_{1}-V_{2}}{10} = 0$ 0.1V, +0.2V, +0.66V, -0.66V2 = 1 0.96V, -0.66V2=1 →1 Apply KCL at mode @ $-5 + \frac{V_2 - V_1}{1 + \frac{V_2 - V_3}{2}} = 0$ 0.66V2 - 0.66V + 0.5V2 - 0.5V2 = 5 -0.66V, +1.16V2 -0.5V3=5 → € Apply KCL at node (3) $\frac{v_3 - v_2}{2} + \frac{v_3 + 0}{0.80} = 0$ 0.5V3-0.5V2+1.17V3=0 -0.5V2+1.67 V2=0-3 3 V, = 8.06V V2 = 10.21V V3 = 3.05V

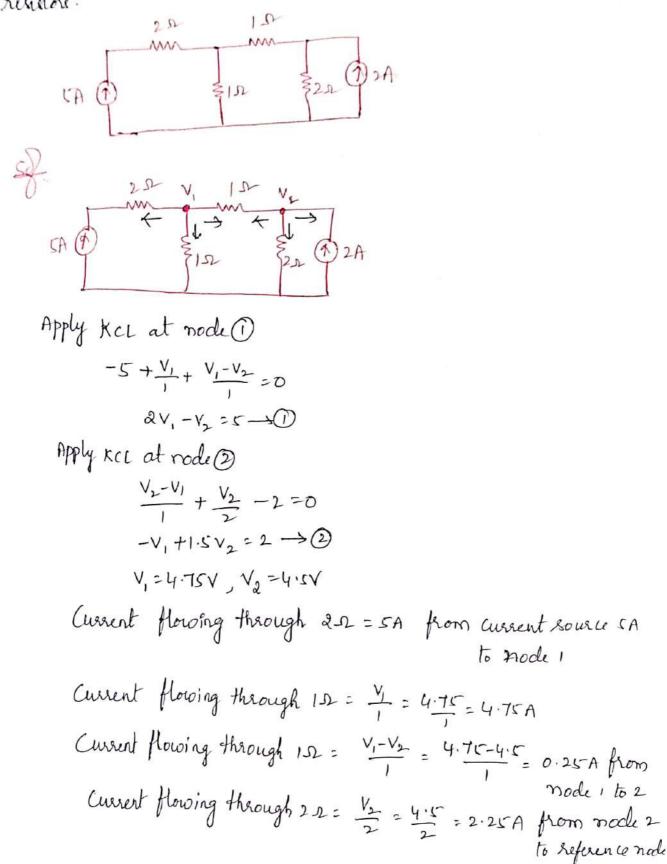Roblem 3: - Using nodal analysis, find the current in the 1.20 residere.



1.21 Dependent Source Nodal Analysis Problems:-Problem: Find mode vollages at three non reference nodes in the Circuit 32 24/in 44 862 IOA (MII $\frac{3\pi}{10} + \frac{1}{3} + \frac{1}{3} + \frac{1}{3} + \frac{1}{2} = 0$ $\frac{10 + \sqrt{1 - \sqrt{2}}}{3} + \frac{\sqrt{1 - \sqrt{2}}}{2} = 0$ $\frac{10 + \sqrt{1 - \sqrt{2}}}{3} + \frac{\sqrt{1 - \sqrt{2}}}{2} = 0$ $0 \cdot 333\sqrt{1 - 0 \cdot 3}3\sqrt{2} + 0 \cdot 5\sqrt{1 - 0 \cdot 5}\sqrt{2} = 10$ 10A 0.833, -0.333, - 0.5V, = 10 -3) Apply KCL at node @ $\frac{V_2 - V_1}{2} + im - 4i_a = 0$, $i_m = \frac{V_2}{4}$ $\frac{V_2 - V_1}{2} + \frac{V_2}{12} - 4\left(\frac{V_2}{11}\right) = 0$ 0.33V2-0.332V, +0.25V2-V2=0 -0.33 V, -0.42V2 = 0 -3 2 Apply KCL at node 3 $\frac{V_3}{1} + \frac{V_3 - V_1}{2} + 4 \ln = 0$ $0.160_3 + 0.5V_3 - 0.5V_1 + 4\left(\frac{V_2}{4}\right) = 0$ 0.16N3 + 0.5V2 - 0.5V, + V2 = 0 -D.SV, +V2 + D.666V2 = 0 V, =80.62V, V2 = -63.92 =64V, V3 = 156.51V

Problem 2: - obtain in, in and numerical value of current dependent source. 5A () x () Wan 1 1 win Apply KCL at node A. 5+ in -4 ia + iy = 0 Assume node voltage at A to be VA. $5 + \frac{V_A}{2} - \frac{V_C}{V_A} \left(\frac{V_A}{2}\right) + \frac{V_A}{V_A} = 0$ $-\frac{V_{A}}{2} = -5 = V_{A} = 10V$ $l_{m} = \frac{10}{2} = 5A$ Numerical value of Current dependent source = 4 in = 4x5 Problem 3: - If powerloss in 152 resistor is 25w, find the value of K in the dependent lource using nodel method. Ki 10V

Scanned by CamScanner

123 61 0 1 10 KT0 50 0 10V , Given V1=10V Apply KCL at node O $-6 + i_0 + V_1 + ki_0 - V_2 = 0$ $-6 + \frac{V_1}{1} + \frac{V_1 + K_1 - 10}{1} = 0$ $\frac{2V_{1}+V_{1}+K_{0}-10}{2}=6$ 3V, +Ki, -10 = 12 3V, + k (1)-10=12 $(K+3)V_1 - 10 = 12 \longrightarrow (1)$ Given Power loss in 1 a resistor = $i_0^{1} \times 1 = \left(\frac{v_1}{1}\right)^{1} \times 1 = 25$ V, = 25 substitute v, in () (K+3)5-10=1251(+15=22 5K=22-15=7 大 = 7/5= 1.4 ... K=1.4 Super Node: - Whenever a voltage Lource (Independent & Dependent) is connected between the two mon reference modes, then these two nodes form a generalized mode Called "Super Mode". A Supernode can be regarded as a surface enclosing the voltage source and its two modes.

Super Node Analysie:-

Suppose any of the branches in the network has a voltage source, then it is slightly difficult to apply modal analysis -> one way to overcome this difficulty is to apply the supernode technique.

→ In this method, the two adjacent modes that are connected by a voltage house are reduced to a single mode & then the equations are formed by applying KCL.

Super Node analysis = Ohm'slaw + KVL+KCL

Consider the Circuit below $I \bigoplus_{\substack{i=1\\j \neq i}} \frac{V_{1}}{R_{1}} + \frac{V_{2}}{R_{2}} + \frac{V_{3}}{R_{4}} = R_{5} \quad Node 1, 2, 3 \text{ are non reference}}{Node 4 is reference node}$ $Ppphy \ \text{kcc at node } \bigoplus_{\substack{i=1\\j \neq i}} \frac{V_{1}-V_{2}}{R_{2}} = O$ $=) \ I = V_{1}\left(\frac{1}{R_{1}} + \frac{1}{R_{2}}\right) - V_{2}\left(\frac{1}{R_{2}}\right) \rightarrow \bigcirc$ $\rightarrow V_{n} \text{ is between nodes } \bigoplus_{\substack{i=1\\j \neq i}} \frac{P_{1}}{P_{1}} + \frac{V_{1}-V_{2}}{P_{2}} = O$ find out the current the supernode technique can be conveniently applied in this case. $Accordingly we can write combined cquation for nodes <math>\bigoplus_{\substack{i=1\\j \neq i}} \frac{V_{1}}{P_{1}} + \frac{V_{1}-V_{2}}{P_{2}} = O$

 $\frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + \frac{V_3 - V_4}{R_4} + \frac{V_2}{R_5} = 0 \longrightarrow (2)$

Scanned by CamScanner

Since Vn is in between two non reference nodes 1.25 we apply KCL & KVL to determine the mode voltages. A Supernode may be regarded as a closed surface enclosing the voltage source and its two modes. $V_2 \cap V_3$ Apply KVL to path considing of Vn, V, & V2 $-V_{\eta} - V_{3} + V_{2} = 0$ $V_a - V_3 = V_a \longrightarrow 3$ By solving equations (D, (D) and (3) V, , V2 and V3 Can be obtained. Note the following properties of Super Node. 1. The Voltage Lource inside the supernode Provide. a Constraint equation needed to solve for node voltages. 2. A supernode has no voltage of ite own. 3. A Supernode requires the application of both KVL Note: If a voltage source is connected between the reference mode and non reference node we set the voltage at the non reference node equal to the voltage of the voltage Lource: for eg... V,=10V


Shown below.

10A () \$3.0 218 10A () 51 Since 200 Voltage source is in between two non référence nodes Nodes @ 43 form à Super Node Apply Kel to node O $-10 + \frac{V_1}{2} + \frac{V_1 - V_2}{2} = 0$ $V_1\left(\frac{1}{3}+\frac{1}{2}\right) - V_2\left(\frac{1}{2}\right) = 10$ 0.83BV, - 0.5V, = 10 -> 1) Apply KCL to Super Node. $\frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_3 - 10}{5} + \frac{V_2}{2} = 0$ $V_{1}\left(\frac{-1}{2}\right) + V_{2}\left(\frac{1}{2}+1\right) + V_{3}\left(\frac{1}{2}+\frac{1}{2}\right) = 2$ $-0.5V_1 + 1.5V_2 + 0.7V_3 = 2$ -2Apply KVL to the path Consisting of super node · V, -20 - V3 = 0 =) V2 - V3 = 20

Solve (D, O) 9 (3) equations

$$V_1 = 18 \cdot 95 \cdot V$$
, $V_3 = 11 \cdot 58 \cdot V$, $V_3 = -8 \cdot 41 \cdot V$
(unrent in S.n. Aucidat = $\frac{V_3 - 10}{5} = \frac{-8 \cdot 41 - 10}{5} = -3.68 \text{ Ample}$
from node 3 to 5
For the Circuit shown, find rede voltage.
 $V_1 = \frac{10 \cdot 10}{20}$
 $2 A$ (D) $\frac{10 \cdot 10}{20}$, $\frac{10 \cdot 10}{20}$, $\frac{10 \cdot 10}{20}$, $\frac{10 \cdot 10}{20}$
Apply Kel to (D & O) Node
 $-2 + \frac{V_1}{2} + \frac{V_2 - V_1}{10} + \frac{V_2 - V_1}{10} + \frac{V_2}{4} + 7 = 0$
 $V_1(\frac{1}{2} + \frac{V_1 - V_2}{10}) + \frac{V_2(-\frac{10}{10} + \frac{11}{10} + \frac{1}{10})}{10} = -5$
 $0 \cdot 5V_1 + 0 \cdot 95V_2 = -5 \rightarrow 0$
 $V_1(\frac{1}{2} + \frac{10}{10}) + V_2(\frac{-10}{10} + \frac{10}{10} + \frac{11}{10}) = -5$
 $V_1(\frac{1}{2} - \frac{10}{10}) + V_2(\frac{10}{10} + \frac{10}{10} + \frac{1}{10}) = -5$
 $V_1 + 2 - V_2 = 0$
 $V_1 - V_2 = -2 \rightarrow (1)$
Solve (D) § (2) equations to obtain $V_1 \in V_2$
 $V_1 = -7 \cdot 33V$
 $V_2 = -5 \cdot 33V$

Problems Find v sy i in the circuit.

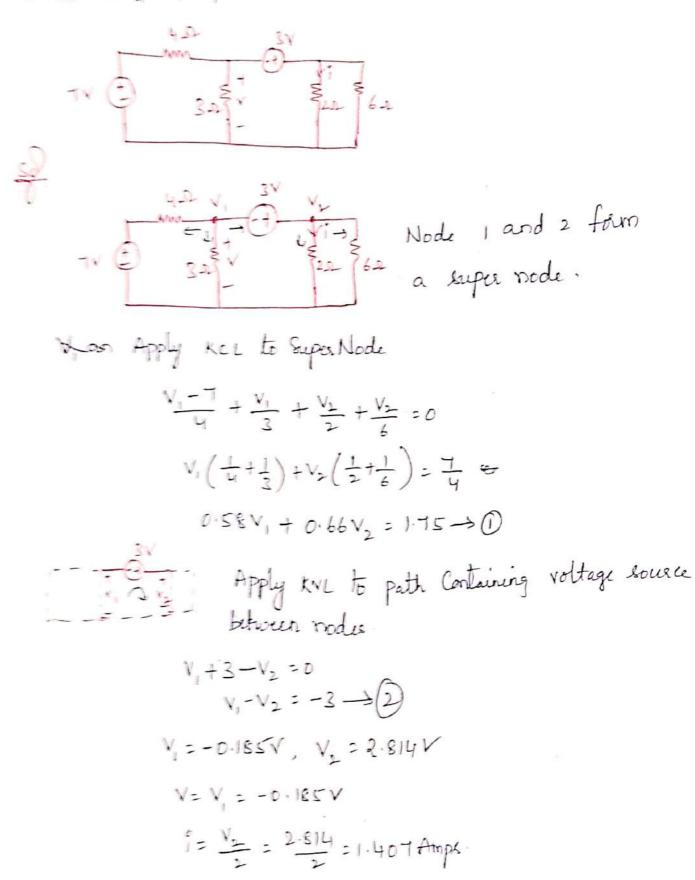


Scanned by CamScanner

128


Dependent sources Super Node analysis Problems:-

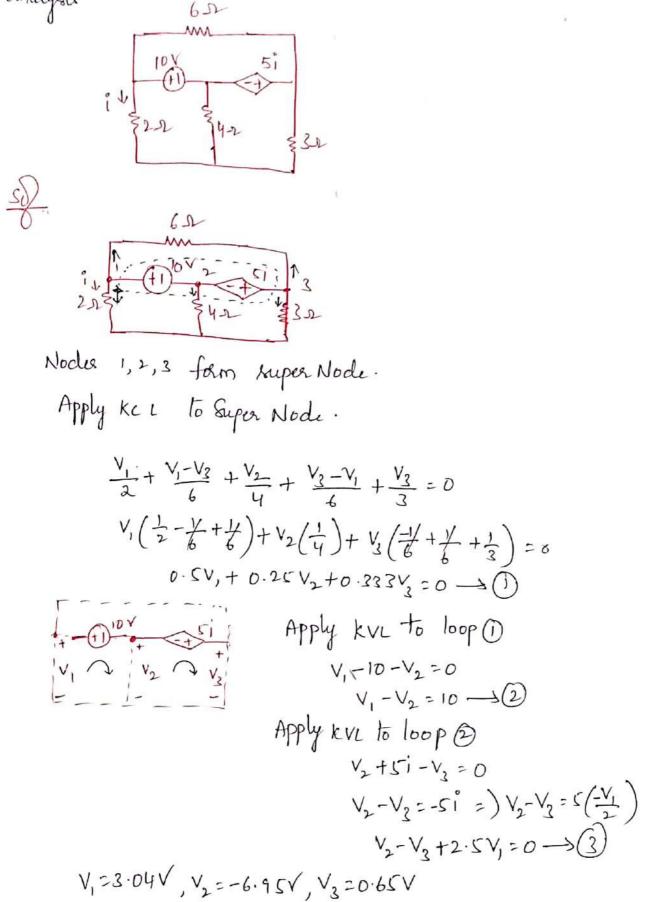Problem: Find V, V, and Vz in the Circuit shown using nodel analysis.



Scanned by CamScanner

129

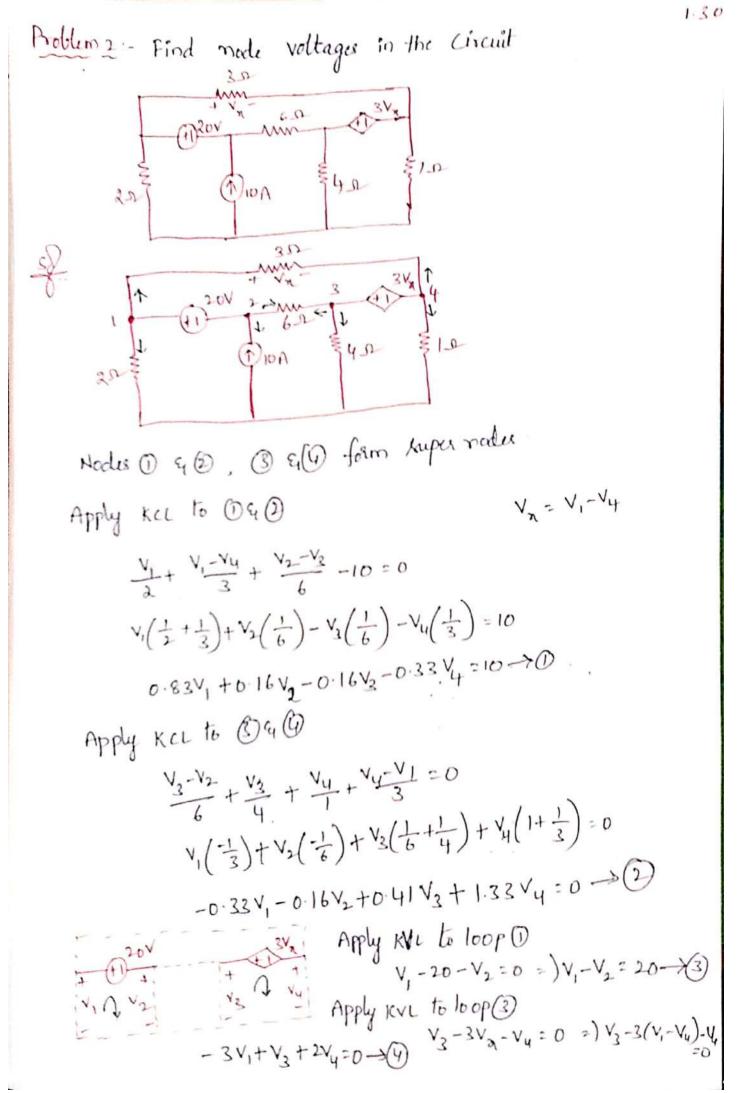


From (a)
$$V_3 = 3V_1 - 2V_4$$

Subditate in (b) (c) $4(3)$.
Prom(b) $83V_1 + 0.16V_2 - 0.16(3V_1 - 2V_4) - 0.33V_4 = 10$
 $0.35V_1 + 0.16V_2 - 0.01V_4 = 10 \rightarrow (c)$
From(c) $-0.32V_1 - 0.16V_2 + 0.41(3V_1 - 2V_4) + 1.33V_4 = 0$
 $0.9V_1 - 0.16V_2 + 0.51V_4 = 0 \rightarrow (c)$
From (c) $V_1 - V_2 = 20 \rightarrow (7)$
Solve (c) (c) $4(7) = V_1 = 25.04 + V_2 = 5.04V + V_3 = 3V_1 - 2V_4$
 $V_4 = -42.61V + V_3 = 160.24V = 0$
Produm3. Detamine vertige at the redet (Nodel analysis Problem)
 $V_1 = V_2 = 20$
 $V_1 = V_1 + V_2 = 10$
 $V_1 = V_1 + V_2 = 10$
 $V_1 = V_1 + V_2 = 20 \rightarrow (7)$
Solve (c) (c) $V_1 = 25.04 + V_3 = 5.04V + V_3 = 3V_1 - 2V_4$
 $V_4 = -42.61V + V_3 = 160.24V = 0$
Problem3. Detamine vertige at the redet (Nodel analysis Problem)
 $V_1 = V_1 + V_2 + V_2 + V_1 + V_2 + V_1 + V_1 = 0$
 $V_1 (\frac{1}{2} + \frac{1}{4}) + V_2 (\frac{1}{2}) + V_3 (\frac{1}{4}) = 3$
 $0.75V_1 - 0.35V_2 - 0.35V_3 = 3 \rightarrow (0)$
Apply ket at redet (c) Apply ket at redet (3)
 $V_2 - \frac{V_1 + V_2 - V_1}{V_1 + V_2 + V_1 + V_2 + V_2 + V_1 + V_2 +$

Norton's Theorem:-

Statement - Any combination of linear bilateral circuit elemente and active sources regardless of connection or Complexity, Connected to a given load ZL, Can be replaced by a simple two terminal metwork, consisting of a single current rousce of IN amperes and a single impedance zeg in parallel with it, across the two terminals of the load ZL. The IN is the short-Circuit Current flowing through the short circuited path, replaced Instead of Zh. It is also called Norton's current. The Req ie the equivalent impedance of the given metwork as viewed through the load terminale, with Zh Removed and dl the active sources are replaced by their internal impedances. If internal impedances are unknown then the independent vollage sources must be replaced by short circuit while the independent current sources must be replaced by open circuit, while Calculating Zig.

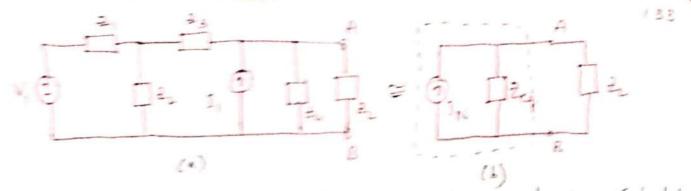Explanation of Norton's theorem: - Consider a network Shown in Fig (a) below. The terminals A-B are load terminals where load impedance Z_L is connected. According to Norton's theorem, the entire network can be replaced by a current Source I_N , and an equivalent impedance Z_{eq} in parallel with it, across the load terminals A-B as shown in Fig (b)



For obtaining cussort In their the bad terminals A-R Calculate the current thereagh the short circuited path by using any of the metanot templetication techniques, This is Nortonic current In It is shown in Fig below

While the equivalent impedance Rey is to be obtained by the

When the circuit is replaced by Nortonic equivalent accrese the load terminals, then the load current can be Easily obtained by using current division in a parallel circuit as $I_1 = I_{12} + \frac{2\pi q}{2 + 2\pi q}$

Thus theorem is also called dual of Therenin's theorem. This is because. If the theoremic equivalent voltage source is (orworked to an equivalent current source, the Norton's equivalent is obtained. This is shown in fig. From source transformation we can write $I_V = \frac{V_{H}}{2v_{H}}$ $V_{H} = \frac{V_{H}}{2v_{H}}$ $V_{H} = \frac{V_{H}}{2v_{H}}$ $V_{H} = \frac{V_{H}}{2v_{H}}$ $V_{H} = \frac{V_{H}}{2v_{H}}$ $V_{H} = \frac{V_{H}}{2v_{H}}$

steps to Apply Nortoni theorem.


Steps: short the branch, through which the current is to be Calculated by removing the impedance between the terminal steps: Obtain the Current through this short circuited branch, wing any of the network kimplification techniques. This current is nothing but Norton's Current IN. steps: Calculate the equivalent impedance zeq, as viewed through the two teaminals of interest by removing the branch impedance and making all the independent sources in active Steph: Draw the Norton's equivalent across the terminale of interest, showing a current know in with the impedance the parallel with H. Reconned the branch impedance now. Let it be 21. The under the ough the branch of interest is, $I = I_N \times \frac{2c_q}{2c_q + 2c}$ And the line line is used in the line it is the line is used in the line it is the line is used in the line is Problems: - Find the warent through branch b-e using Noton's theorem. \$ 0.22 \$ 52 SJ. 20.12 (1) 4V 1)2V 1026 202 step:-1 Remove 52 resistor and chat 20.252 \$552 0.125 Ciscuit it +)4V 102 1)2V +20.22 0.12 \$ e 1. \$4v Stop2: - Apply KVL to loop () 2-0.11,-101,=0=)-10.11,=-2=) 1,=2=0.198 Armys.

Scanned by CamScanner


$$\begin{array}{c} \text{My} \text{ tri } h \log \mathcal{D} \\ -20i_{2} - 0.2i_{2} - 4 = 0 \\ -10.2i_{2} = 4 = 2) i_{2} = \frac{-4}{20\cdot 2} = -0.198 \text{ angs} \\ \text{I}_{N} = \text{I}_{1} - \text{I}_{2} = 0.198 - (-0.198) = 0.376 \text{ angs} \\ \text{Step 3: Calculate equivalent impedance} \\ \hline 1000 \text{ fleg} = 0.22 \text{ Reg} = (0+0.1) \int / (20+0.2) \\ = 10\cdot 1 \int 20.2 \\ = 6.732.2 \text{ A} \\ \text{Step 4:= Draw Notoni equivalent Circuit sy find current through branch b-e' \\ \hline 1000 \text{ Step 4:= Draw Notoni equivalent Circuit sy find current through branch b-e' \\ \hline 1000 \text{ Step 4:= Draw Notoni equivalent Circuit sy find current through branch b-e' \\ \hline 1000 \text{ Step 4:= Draw Notoni equivalent Circuit sy find current through branch b-e' \\ \hline 1000 \text{ Step 4:= Draw Notoni equivalent Circuit sy find current through branch b-e' \\ \hline 1000 \text{ Step 4:= Draw Notoni equivalent Circuit sy find current through branch b-e' \\ \hline 1000 \text{ Step 4:= Draw Notoni equivalent Circuit sy find current through branch b-e' \\ \hline 1000 \text{ Step 4:= Draw Notoni equivalent Circuit sy find current through branch b-e' \\ \hline 1000 \text{ Step 4:= Draw Notoni equivalent Circuit sy find current through branch b-e' \\ \hline 1000 \text{ Step 4:= Draw Notoni equivalent Circuit sy find current through branch b-e' \\ \hline 1000 \text{ Step 4:= Draw Notoni equivalent Circuit sy find current through b-e' \\ \hline 1000 \text{ Step 4:= Draw Notoni equivalent Circuit sy find current through b-e' \\ \hline 1000 \text{ Step 4:= Draw Notoni equivalent through 560.2 Activate using Notoni through through 560.2 Activate using Notoni through t$$

steps Find JN
Nprly KNI to loop ()
10 - 10000 (1,-13) - 410 (1,-13) = 0
-14701, + 10001, + 47013 = -10
$$\rightarrow$$
 ()
Apply UL to loop (2)
-22012 - 1000 (12 - 11) = 0
10001, -122012, 0 \rightarrow (2)
Apply KNL to loop (3)
-10001, -122012, 0 \rightarrow (2)
Apply KNL to loop (3)
-10001, -122012, 0 \rightarrow (2)
 $47001, -122012, 0 \rightarrow$ (2)
 $1, = 10, 9400 \text{ A}, 13 = 16.29 \text{ MA}, 13 = 6.39 \text{ MA}, 13 = 500 \text{ A}, 14 = 100 \text{ MA}, 14 = 10000 \text{ MA}, 14 = 100000$

3

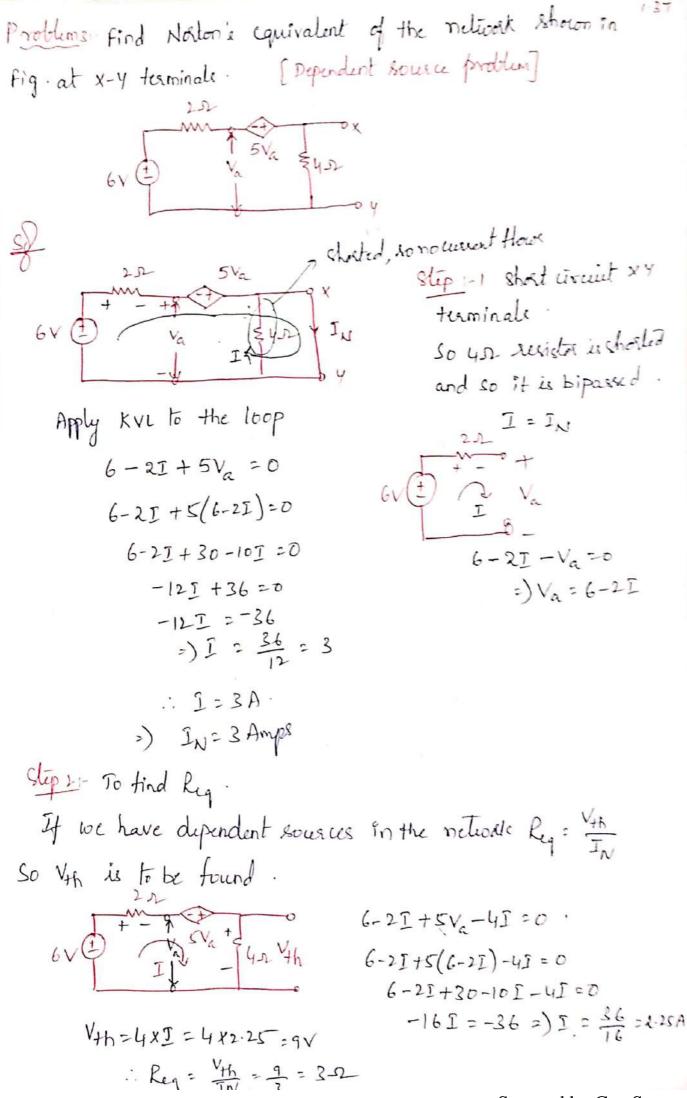


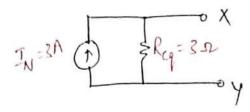Steps: - Draw Norton's equivalent Circuit.



AC Encitation Norton Theorem Problems:-

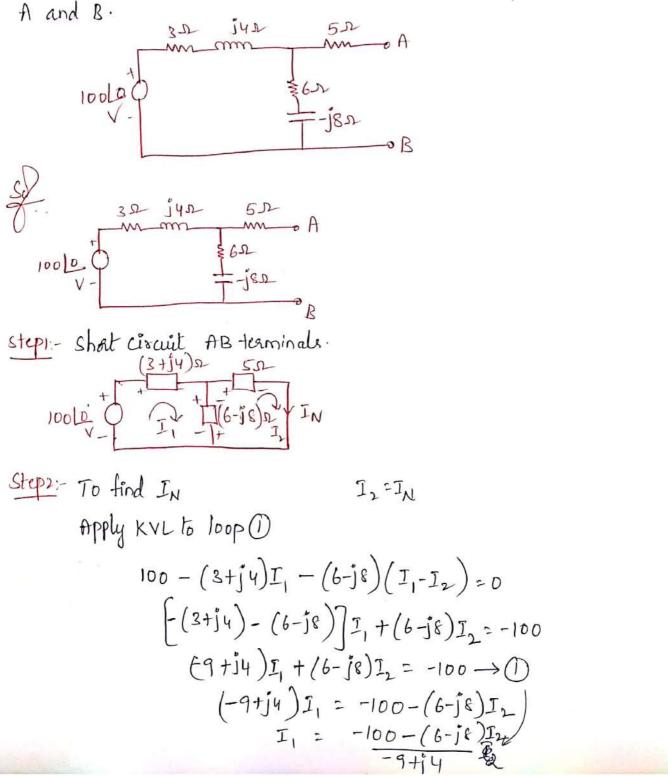Problem 1:- Obtain Norton equivalent circuit with Respect to terminate



Scanned by CamScanner

Apply KVL to keep (2)

$$-SJ_{-}(b-js)(J_{3}-J_{1})=0$$

$$-HJ_{3}+jsJ_{2}+6J_{1}-jsJ_{1}=0$$

$$J_{2}(-H+js) = (-b+js)J_{1} \rightarrow (2)$$
Subditute J_{1} in eq (2)

$$J_{2}(-H+js) = (-b+js)(-H0b+js)$$

$$J_{2}(-H+js)(-H0b+js)$$

$$J_{2}(-H+js)(-Hb+js)$$

$$J_{2}(-H+js)(-Hb+js)$$

$$J_{2}(-H+js)(-Hb+js)$$

$$J_{2}(-H+js)(-Hb+js)$$

$$J_{2}(-H+js)(-Hb+js)$$

$$J_{2}(-H+js)(-Hb+js)$$

$$J_{2}(-H+js)(-H-js)$$

$$J_{2}(-H+js)(-H+js)$$

$$J_{2}(-H+js)$$

$$J_$$

Manimum Power Transfer thedem:-

The maximum power transfer theorem can be stated as <u>Statement</u>. In an active network, mornimum power transfer to the load takes place when the load servicione is equal to equivalent resistance of the network as viewed from the terminde of the load (For De Excitation)

In an active network, manimum power transfer to the load takes place when the load impedience is the Complex Conjugate of an equivalent impedience of the network as viewed from the terminete of the load · (Foi the kneitation)

Replanation of Manimum Power transfer theorem to De Encitation:-

Many circuite basically consist of sources supplying voltage. Current of power to the load; for example a radio speaker seylin or a microphone supplying the input signale to voltage pre-amplifies. Sometimes it is necessary to transfer maximum voltage, current of power from source to the load. In the simple servicive circuit shown in Fig. Re is the source serviciance. Curr aim is to find the necessary Conditions so that the power delivered by the source to load is manimum.

It is a fact that more vollage is delivered to the load when is delivered to the load when is transferred to the load when load resistance of source compared to resistance is small compared to hource resistance is small

Scanned by CamScanner

is the for many applications, an important consideration transfer maximum power transfer to the load; for example forces is devisable from the output amplifier to the speater of an audio Lound system. The maximum power transfer theorem state that when manimum power is delivered from source to a load the load heristary is equal to the source reaction For the circuit shown above $\overline{I} = \frac{V_s}{R_s + R_s}$ Power delivered to bad R_L is $P = J^2 R_L = \frac{V_1^{\prime \prime}}{(R_1 + R_1)^{\prime \prime}} R_L$ To determine the value of Pi for manimum power to be transfused to the load, we have to set the first derivative of the above equation with supert to RL i, e, when dP is gas $\frac{dP}{dR_{L}} = \frac{d}{dR_{L}} \left[\frac{V_{L}^{\vee} R_{L}}{(R_{S} + R_{L})^{2}} \right] = \frac{(R_{S} + R_{L})^{2} V_{S}^{\vee} - V_{S}^{\vee} R_{L} (2(R_{S} + R_{L}))}{(R_{S} + R_{L})^{4}} = 0$ =) $V_{s}^{\prime}(R_{s}+R_{L})^{\prime} = V_{s}^{\prime} \times 2R_{L}(R_{s}+R_{L})$ $V_{S}^{\vee}R_{S} + V_{S}^{\vee}R_{L} = 2V_{S}^{\vee}R_{L} =) V_{S}^{\vee}R_{S} = 2V_{S}^{\vee}R_{L} - V_{S}^{\vee}R_{L} = (-V_{S}^{\vee}R_{L} - V_{S}^{\vee}R_{L} - V_{S}^{\vee}R_{L}$ $\frac{1}{12} = R_{L}, P_{max} = \frac{V_{s}^{*}}{R_{s}+R_{L}}R_{L} = \frac{V_{L}^{*}}{R_{s}+R_{L}}xR_{L} = \frac{V_{L}^{*}}{4R_{L}}xR_{L} = \frac{V_{L}^{*}}{4R_{L}}$ So, Maximum power is transferred to the load when load resistance is equal to source secretance. Emplanation of Monomum power Transfer Theorem for AL Encilation:-Consider a network shown in Fig (a) Let zeg be the equivalent impedance of the network as Viewed from the terminals A-B and applacing all the Independent house by their internal impedances, as those in Fig. (b)

Let Za be represented as Reg = R+j× Gier Chan Chan Chan That manimum proves will be pressioned to the lead of the in Complex (re ugali of Za The complex conjugate is wethernetically directed as 24 う日本言 So the tag = R-jx Thus for maximum power transfer to the load, the societion of bad ord savilars furt of 200 mud be same while the seatons of the load and try must also be same in prizzentitude but appointe in sign. So if Rey venetera is Inductive, R. must be capacitive and vicevess had of Maximum Power Transfer the Auto Let the given metanet in suplaced by its Throadin's equivalent access the load Equilitrix) A terminals as shown in fig 12 (tix) 40 Let Reg. = (R+jx).a $\mathfrak{L} = (\mathfrak{L} + \mathfrak{j} \mathfrak{L}) - \mathfrak{L}$ $I = \frac{v_{4b}}{2c_1 + 2c_2} = \frac{v_{4b}}{(k+jx) + (k_1+jx_2)}$ The proven delivered to load is R = I R. I: - 46 V(R-E)+(1+1)Y =) P. 46 V(R-E)+(1+1)Y =) P. 46

$$P_{L} = \frac{V_{+b}}{(R+R_{L})^{2} + (X+K_{L})^{2}} \times R_{L}$$

Now for load impedance ZL, both R, and X are variable and are to be decided such that power will be maximum. Hence according to maximax theorem we can write that for the maximum procer transfer, w. r to Variable X and fixed P.

$$\frac{d P}{dx_{L}} = 0$$

$$\frac{d}{dx_{L}} \left(\frac{v_{th} \tilde{R}_{L}}{(R+R_{L})^{\nu} + (x+x_{L})^{\nu}} \right) = 0$$

$$\left(\frac{R+R_{L}}{(R+R_{L})^{\nu} + (x+x_{L})^{\nu} + (x+x_{L})^$$

Thus load reactance must be same in magnitude of reactance of Reg but opposite in high. Similarly power transfer will be maximum wis to variable RL Similarly power and fixed X_L when, $\frac{dP_L}{dR_L} = 0$ $\frac{d\left(\frac{V_{4b}R_L}{(R+R_L)^2 + (V+1X_L)^2} \right) = 0 = 0$ Substitute $X_L = -x$ as already $\frac{dR_L}{dR_L} \left(\frac{V_{4b}R_L}{(R+R_L)^2 + (V+1X_L)^2} \right) = 0 = 0$ Substitute $X_L = -x$ as already $\frac{dR_L}{dR_L} \left(\frac{V_{4b}R_L}{(R+R_L)^2 + (V+1X_L)^2} \right) = 0 = 0$ Substitute $X_L = -x$ as already $\frac{dR_L}{dR_L} \left(\frac{V_{4b}R_L}{(R+R_L)^2 + (R+R_L)^2} \right) = 0$ $\frac{dR_L}{dR_L} = 0$ $\frac{dR_L}{(R+R_L)^2} = 0$ $\frac{dR_L}{dR_L} = 0$ $\frac{dR_L}{dR_L} = 0$ $\frac{dR_L}{dR_L} = 0$ $\frac{dR_L}{(R+R_L)^2} = 0$ $\frac{dR_L}{dR_L} = 0$ $\frac{dR_L}{(R+R_L)^2} = 0$

Scanned by CamScanner

143

1-44

AVAR(R+R): (1+P) VA $RR = R + R_{L}$ $R_L - R_L = R$ =) R_= R $R = R_{1}$ Thus the recipience of the load must be same as that of equivalant impedance of the network. Thus when Ze is the Complex Conjugate of Eq. the power transfer to the load in maximum and il given by as $I = \frac{V_{H}}{2R}$ Pmax = 1 (= - V4h - RL = - V4h - 4R : Pmax = Vth 4R


Where Vin = Therenin's Voltage as circuit is replaced by its Thevenin equalent Corollary: if pure reclatance is to be connected as lead for maximum prover transfer then its value must be equal to the absolute magnitude of Zy.

Ri = |Zeg | for Pmax when load is purely resistive and hence maximum power delivered the bad is and


to the load is given by $R_{max} = I^* R_L = \left(\frac{V_{H}}{x_{cy} + R_L}\right) R_L$ and it is not given by $\frac{V_{H}}{4R_L}$



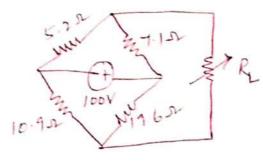Problem 1: - For the circuit, find the value of R that will receive maximum power. Determine this maximum power.






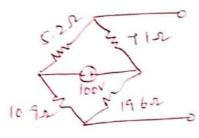

styp: Find Vth between the removed terminals

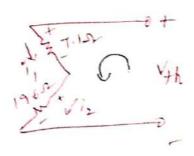=) $l_2 = \frac{100}{30.5} = 3.2 \text{ TA}$



Apply EVE to loop ()


$$-5.21, -7.1i, -100 = 0$$

 $-12.3i, = 100$
 $i_1 = \frac{-100}{12.3} = -8.13A$
Apply KVE to loop ()
 $-19.6i_2 = -10.9i_2 + 100 = 0$
 $-30.5i_2 = -100$

Scanned by CamScanner

Job '


Steps: To find Rith

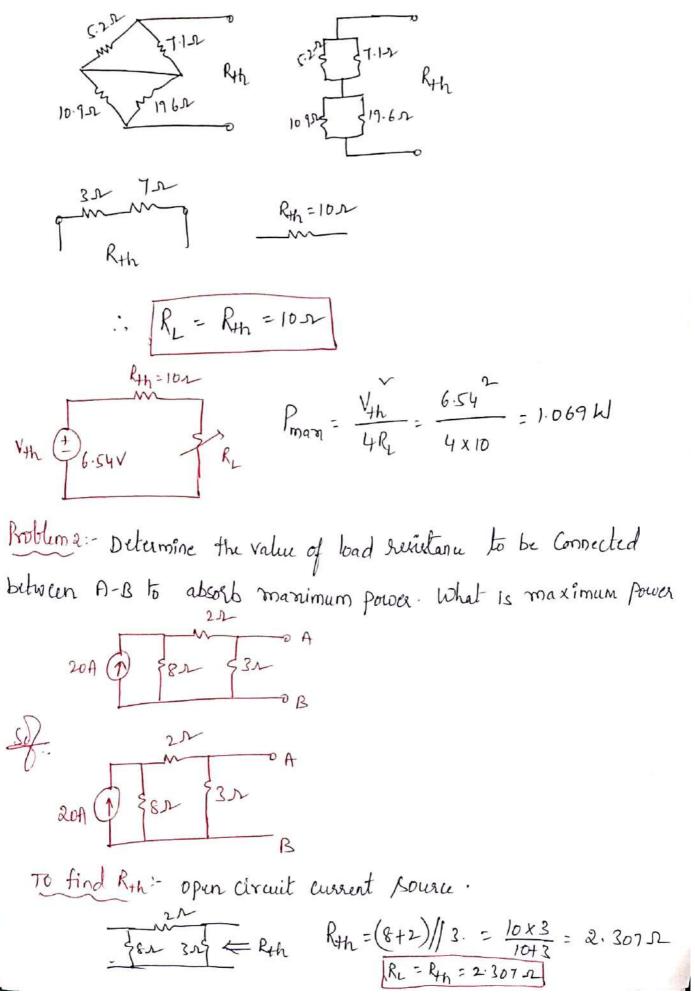


Scanned by CamScanner

To find
$$V_{4h}$$
:-
 147
To find V_{4h} :-
 1_{11} = 20A
Apply $k \vee L$ to loop \bigcirc
 $-2i_{2}^{2}-2i_{2}^{2}-6(i_{2}-i_{1}^{2})=0$
 $-13i_{2}^{2}+8i_{1}^{2}=0$
 $-13i_{2}^{2}+8i_{1}^{2}=0$
 $-13i_{2}^{2}=-160$
 $R_{hn}=2\cdot30TA$
 $V_{hn}=2k^{2}q^{2}$
 $R_{L}=2\cdot30TA$
 $P_{max}=\frac{V_{4b}}{V_{4}R_{L}}=\frac{36\cdot q^{2}}{4\times2\cdot30T}=147\cdot55K$

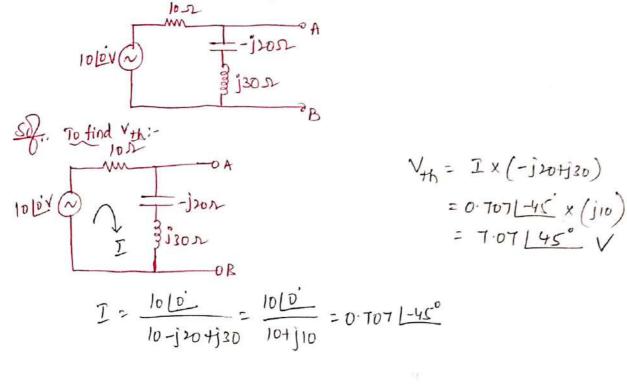Problem 3: (Ac Excitation) Find the load impedance required to be connected across the terminals A-B for the maximum power transfer, in the network shown. Also find maximum power delevered to the load.



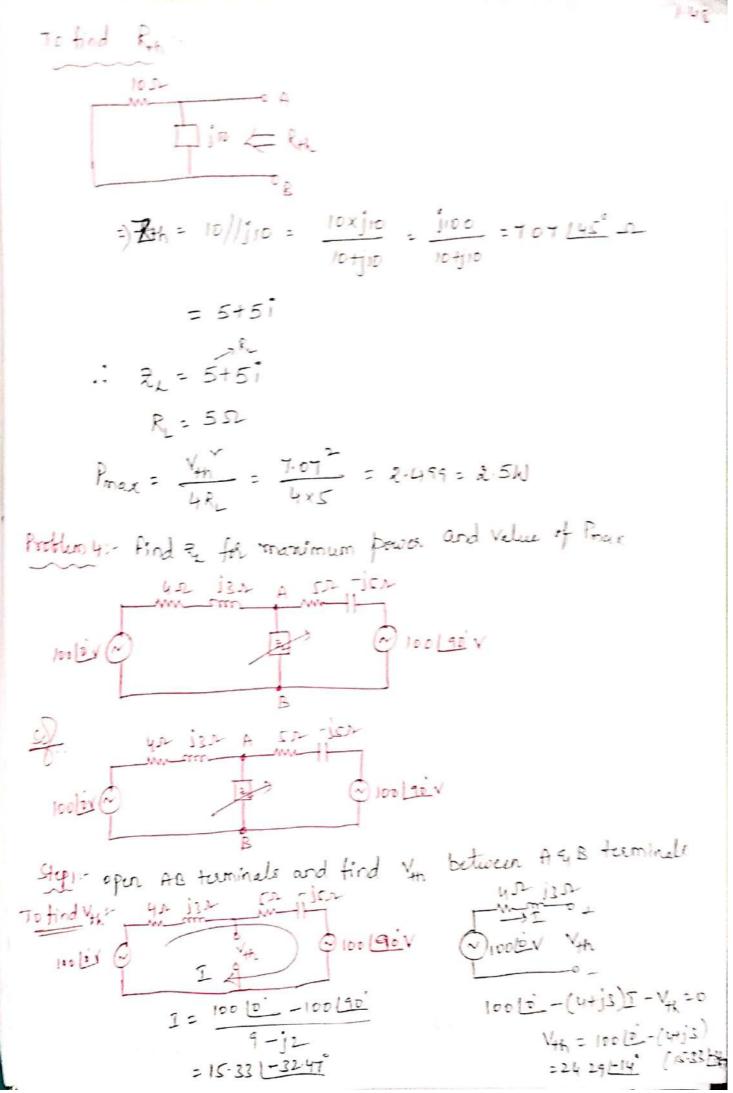

1.47

.. VH = 24 29 -14 V


To find $\frac{1}{24k}$: $\frac{4k}{2} = \frac{12k}{24k}$ $\frac{5k}{2} = \frac{16k}{4} = \frac{16k}{2} = \frac{16k}$

Reciprocity Theorem:

Reciprocity theorem states that In any linear network consisting of linear and bilateral elements and active sources, the vatio of voltage v introduced in one loop to the current I in other loop is same as the vatio obtained if the positions of v and I are interchanged in the votwork. While calculating the vatio, the sources other than one which is considered to obtain the vatio, must be replaced by their internal substances (th impedances) Exploration:-Consider the network shown

Visithe voltage introduced in loop 1 while I is the current in loops. The ratio of Voltage V to I is $\stackrel{\vee}{\pm}$

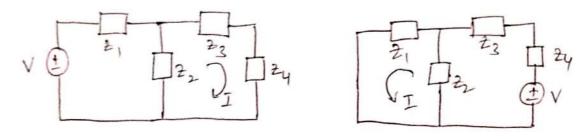Reciprocity theorem states that the vatio $\frac{1}{I}$ remains same, if the positions of V and I are interchanged in the network. as shown in Fig.



In other words, the vand I are mutually transferable. The ratio $\stackrel{\vee}{\pm}$ is Called transfer impedance where v is voltage introduced in loops and I is the response due to V in loop 2 Proof of Reciprocity Theorem:-

Consider the network shown in fig.
(
$$\overrightarrow{T}$$
) \overrightarrow{T}
 \overrightarrow{T}

Apply KVL to second loop $-2_{2}I_{2} - 2_{3}(I_{2} - J_{1}) = 0$ $(2_{3} + 2_{2})I_{2} = 2_{3}I_{1}$ $I_{1} = (\frac{2_{2} + 2_{3}}{2_{3}})I_{2}$ Substitute I_{1} in (1). $(\frac{2_{2} + 2_{3}}{2_{3}}) \times (2_{1} + 2_{3})I_{2} - I_{2}2_{3} = V_{1}$

$$\begin{cases} \left(\frac{2}{1}+\frac{2}{3}\right)\left(\frac{2}{2}+\frac{2}{3}\right) - \frac{2}{3} \quad J_{L} = V_{I} \\ \frac{1}{2}\left(\frac{2}{2}+\frac{2}{3$$

Scanned by CamScanner

Problems ... Verity reciprocity theorem for the vollage vand Current I in the network shown. 10V () 2.2 2.2 2.2 2.2 2.2 2.2 10V (2) (2) - 232 2; 222 Apply KUL to loop 1 $10 - 2i_1 - 3(i_1 - i_2) = 0$ -51,+312=-10 -> 1 Apply KVL to loop (2) $-2i_2 - 2i_2 - 3(i_2 - i_1) = 0 =) i_1 = 2.69 A$ $3i_1 - 7i_2 = 0 \rightarrow 2$: $I = i_2 = 1.15 A$ Interchange the voltage source to second loop and find $\therefore \stackrel{\vee}{\underline{\gamma}} = \stackrel{\vee}{\underline{\gamma}}_{\underline{\gamma}} : S \cdot 6 \xrightarrow{} \longrightarrow \textcircled{}$ aunt in knowla first loop Apply KVL to loop) 1,=-1.92A 12 = -1.15A . $-2i_2 - 3(i_2 - i_1) = 0$ $3i_1 - 5i_2 = 0 \rightarrow \bigcirc$ I = - 1, =1.15A. $\therefore \qquad \stackrel{}{\underline{Y}} = \frac{10}{1\cdot 1^{r}} = 8 \cdot 69 \longrightarrow (\mathbb{B})$ Since ratio's A GB are bame Kellpricity theorem is verified.

hoblim
$$\lambda = (Ac Enciption)$$

Verify recipionity theorem for the network shown in fig...
Note: A
 $V_{12} = 1012^{\circ} \times \frac{5}{5+4-j4} = 5.07/22.76 A$
 $V_{2} = -\frac{1}{2}\frac{2}{3}\frac{5}{5+4-j4} = 5.07/22.76 A$
 $V_{3} = -\frac{1}{2}\frac{2}{3}\frac{5}{5+4-j4} = 20.28/-66.04j V$
 $\frac{V_{3}}{2} = \frac{2}{20.28}\frac{1-66.04}{10} = 2.02/-66.04 \longrightarrow 10$
Now interchange the power home of V_{3} and Σ
 $V_{3} = \frac{51}{10}\frac{10}{10} \times \frac{-j4}{-j4+45} = 4.06 \frac{1-66.02}{10} A$
 $V_{3} = 51 = 5 \times 4.06 \frac{1-66.02}{10} = 2.0.3 \frac{1-66.04}{10} \sqrt{2}$
The values $A \in B$ are hare
So reciprociby theorem is verified.

Millimann's Theorem: - Milliman's theorem states that

If n voltages sources $V_1, V_2 - V_n$ having internal residences (or impedances) $2_1, 2_2 - 2_n$ respectively are in parallel, then there sources may be replaced by a single voltage source of voltage V_n having a series impedance 2_m or where V_m and 2_m are given by

$$V_{m} = \frac{V_{1}G_{1}+V_{2}G_{2}+V_{3}G_{3}+\dots-V_{n}G_{n}}{G_{1}+G_{2}+G_{3}-\dots-G_{n}} = \frac{E}{k=1}\frac{V_{k}G_{k}}{K}$$

where $G_{1,1}$, G_{2} are conductances corresponding to resistances $R_{1,1}$, R_{2} - $G_{1} = \frac{1}{R_{1}}$, $G_{2} = \frac{1}{R_{2}}$ ---- $G_{0} = \frac{1}{R_{0}}$ and $V_{m} = \frac{V_{1}Y_{1} + V_{2}Y_{2} + V_{2}Y_{3} + - - V_{0}Y_{0}}{Y_{1} + Y_{2} + Y_{3} + - - Y_{0}} = \frac{\sum_{k=1}^{n} V_{k}Y_{k}}{\sum_{k=1}^{n} Y_{k}}$ (F8 ac $\frac{V_{1} + Y_{2} + Y_{3} + - - Y_{0}}{Y_{1} + Y_{2} + Y_{3} + - - Y_{0}}$

where Y, , Y2 -- Yn are admittances corresponding to Impedances 2, , 22 -- 2n

$$Y_{1} = \frac{1}{z_{1}}, Y_{2} = \frac{1}{z_{2}} = ---Y_{2} = \frac{1}{z_{1}}$$

$$q_m = R_m = \frac{1}{q_1 + q_2 + \dots - q_n} = \frac{1}{\sum_{k=1}^{n} q_k}$$

$$z_m = \frac{1}{Y_1 + Y_2 + - - Y_n} = \frac{1}{\sum_{k=1}^{\infty} Y_k}$$

Scanned by CamScanner

1.54

n voltage sources V, V2 --- Vn. Knplanation: Consider the having suries impedances 2, 22 -- 2, Connected in parallel as shown. 2、中站中33 \$vn 12n v, PvE Pv3 120 Y=+ $y_1 = \frac{1}{z_1}, y_2 = \frac{1}{z_2} - - y_1 = \frac{1}{z_1}$ Then according to millimann's theorem, all voltage kources Can be combined to get a single voltage source Vm with a Maries impedance 2m as shown in fig ... $V_{m} = \frac{V_{1}Y_{1} + V_{2}Y_{2} + \dots + V_{n}Y_{n}}{Y_{1} + Y_{2} + \dots + Y_{n}}$ $2m = \frac{1}{4.442+12+-40}$ Proof of Millimann's theorem:-Consider n'voltage sources in parallel as known in fig. -0 A 王白动动 TZn Let us convert each voltage source into equivalent current v, q yq yq koura for kource 1, $\overline{I}_1 = \frac{V_1}{Z_1}$ B J. as Y,=1 = 4,4, Similarly for remaining kousces, we can write $I_2 = V_2 Y_2$, $I_3 = V_3 Y_3 - - - I_n = V_n Y_n$ where Y, Y2 -- Y, are admittances to be connected in Preally Hence circuit reduces là I, O IY, OI I'L PINT B

Hence the effective current known a crose the terminale A-E is In = In+I2+---In → O Im = Y1+Y2+---In → O This is because admittances in parallel get added to Cach other thence circuit reduces to as shown



Converting this quivalent current house into the voltage house. We get $V_{a} = \frac{2\pi}{2}$

$$r_m = \frac{1}{Y_m}$$

 $V_m = J_m \dot{z}_m$

Substituting In and 1/2 from equations () and ()

$$V_{m} = \left(\underline{1}_{1} + \underline{1}_{2} + \dots - \underline{1}_{n}\right) \cdot \frac{1}{\left(\frac{y_{1} + y_{2} + \dots - y_{n}}{2}\right)}$$
$$\underline{1}_{1} = \frac{v_{1}}{2} = v_{1}y_{1}, \quad \underline{1}_{2} = v_{2}y_{2}, \quad \dots - \underline{1}_{n} = v_{n}y_{n}$$

$$V_{m} = \frac{V_{1}Y_{1}+V_{2}Y_{2}+\cdots+V_{n}Y_{n}}{Y_{1}+Y_{2}+\cdots+Y_{n}}$$

$$z_m = \frac{1}{y_m} = \frac{1}{y_{1+y_1} + \dots + y_n}$$


Thus milliman's theorem is proved.

Scanned by CamScanner

1.56


Rother to Ver Milliman's theorem to find the current through 10.2 regition in the circuit.

224	5 JL
-0-	-MM7
- 45V	122
-0-	m
-120+	-m-
	102
N	v

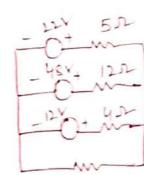


From given network we can write, $V_1 = 12V$, $V_2 = 48V$, $V_3 = 22V$ 2,=42, 22=122, 23=52 4, = 1 = 0.20, 42 = 12 = 0.0830, 43= 1=0.200 $V_{m} = \frac{V_{1}Y_{1} + V_{2}Y_{2} + V_{3}Y_{3}}{Y_{1} + Y_{2} + Y_{3}} = \frac{12 \times 0.257 + 48 \times 0.083 + 22 \times 0.25}{0.257 + 0.083 + 0.257}$ = 24 21.35V
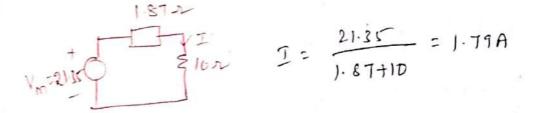
$$a_m = \frac{1}{y_1 + y_2 + y_3} = \frac{1}{0.25 + 0.083 + 0.2} = 1.87 \Omega$$



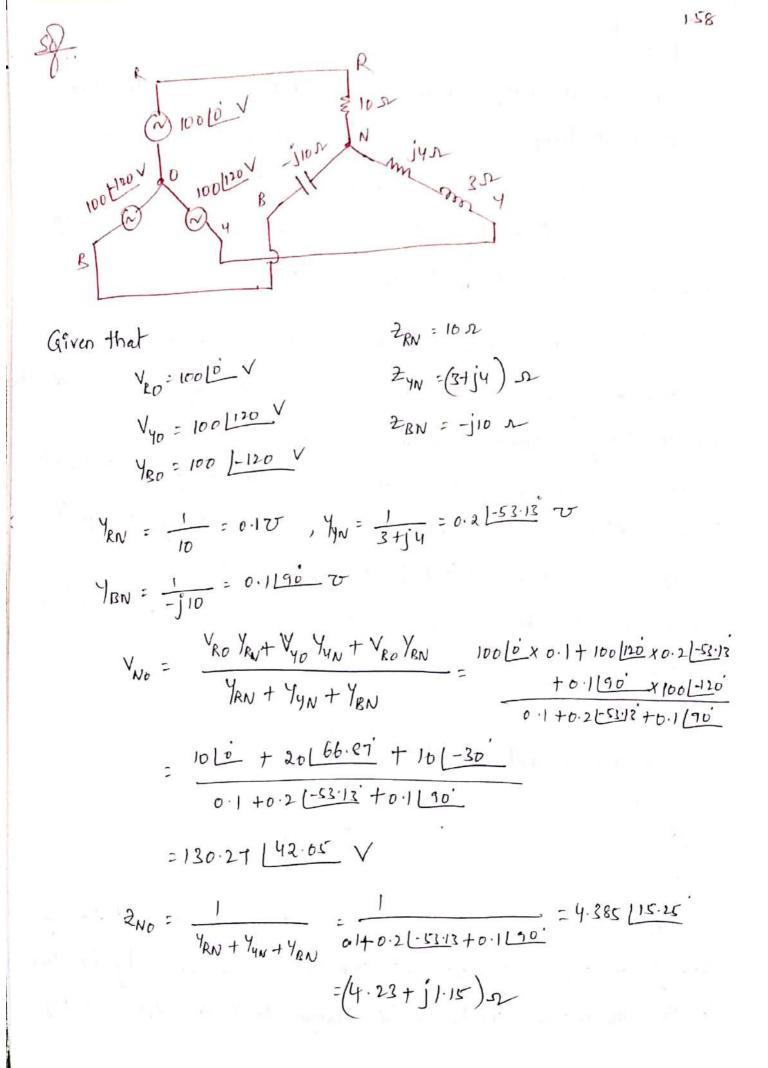Problem 2 1- AC Existation Using milliman's theorem find the neutral shift voltage Von 100thov Stocke 100 Lev -jor jyr 100 Liver - jor jyr 200 B 1 m 25-4



Compensation "Theorem -

In circuit analysis many times it is required to study the effect of change in resistance (or) impedance in one of the boarches on the corresponding voltages and currente of the network The compensation theorem provider a very simple way for studying such effects. The statement is as follows. Statement : In any linear network consisting of linear and bilateral resistances (or) impedances and active sources, if the impedance 2 of the branch carrying current I increases by SZ, then the increment or decrement of voltage or current in each branch of the network is that voltage or current that would be produced by an opposing Vollage source of value V (= I.SZ & I SR) introduced in the altered branch after replacing diginal sources by their internal impedances.

Koplanation: Consider a metwork shown in fig. V, Q, J, Z, Y, Q, J, Z, +52

V, is voltage applied to network, I is the current flowing through 2, 9, 2, . Consider that impedance 3, increases by 62. Due to this, the current in the circuit changes to I' as shown in Fig.

Then the effect of Change in impedable is the change in 160 warent which is given by

Now this current can be directly Calculated by using the Compareation theorem. first modify the branch of which impedance is changed, by connecting a voltage source Ve of Value I. 82. The new vollage source much be connected in the branch with Proper polarily. Then replace original active source V by ite. intunal impedance as shown in Fig. The voltage source introduced in modified branch, Vc is Called Compensation source with value I.SZ where I is current through impedance before impedance of branch is changed and Sz "is change in impedance Proof of Compensation Theorem :-Consider a metwork shown in Fig. (),), []22+52 V, @ 21 []22 $\mathbf{T}' = \frac{V_1}{\mathbf{z}_1 + \mathbf{z}_2 + \mathbf{\xi}_2}$ $J = \frac{v_1}{2+2}$ $\int \mathbf{I} = \mathbf{I} - \mathbf{I}' = \frac{V_1}{2_1 + 2_2} - \frac{V_1}{2_1 + 2_2 + S^2} = V_1 \left[\frac{1}{2_1 + 2_2} - \frac{1}{2_1 + 2_2 + S^2} \right]$ $= V_1 \left(\frac{2(1+2)(1+2)(-2)(-2)}{(2(1+2))(2(1+2)(1+2))} \right) = \frac{V_1}{2(1+2)}.$ 2, +2, +52

⁽s : j - j '

$$SI = \frac{I}{2_1 + 2_2 + S_2} = \frac{V_c}{2_1 + 2_2 + S_2} \rightarrow 0$$

Comparisating Vellige $V_c = I \cdot S_c^2$

Now Consider that the branch is modified as shown in

Fig and also diginal Vellige Krunce is ghost availed let the

Custor in civatit be I''

Apply $kv \in b \log p$

 $V_c - (b_1 + b_2)I'' - 2_1 I'' = D$

 $V_c - I'' (2_1 + b_2 + 2_1) = b$

 $J'' = \frac{V_c}{2_1 + 2_2 + b_2} = V_c - I'' (2_1 + b_2 + 2_1) = b$

 $I'' = \frac{V_c}{2_1 + 2_2 + b_2} = \frac{V_c}{2_1 + 2_2 + b_2 + b_2} = 0$

equations $(D = (D =)) SI = J''$

Thus Compensation theorem is proved.

Problems Using Compensation theorem, determine the animeta reading where H is connected to be a subscience in Fig. The internal serietance

 $d = animeter (c + 2 - n)$

 $V_1(\frac{1}{2}) + V_2(\frac{1}{2} + \frac{1}{2} + \frac{1}{2}) = 0 = 2 - 0 - 2V_1 + 0 - 86V_2 = 0$

 $V_1(\frac{1}{2} + \frac{1}{2}) - V_2(\frac{1}{2}) = 0 = 0 = 0$

 $V_1(\frac{1}{2} + \frac{1}{2}) - V_2(\frac{1}{2}) = 0 = 0 = 0$

 $V_1(\frac{1}{2} + \frac{1}{2}) - V_2(\frac{1}{2}) = 0 = 0$

 $V_2 = \frac{V_1 + V_2}{C} + \frac{V_2}{2} + \frac{V_2}{2} = 0$

 $V_1(\frac{1}{2} + \frac{1}{2} + \frac{1}{2}) = 0 = 2 - 0 - 2V_1 + 0 - 86V_2 = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_1 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_1 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 0$

 $V_2 = \frac{1}{2} + \frac{1}{2} + \frac{1}{2$


 $\underline{I}_{6} = \frac{10}{6} = 1.66 \text{ A}$

62 $\frac{1}{2}$ ₩ JL" () V2 = 3.32V - 1.66×2 = 3-32 V Ruf (5+3/12)+8 Ammeter Leading = I2 - I6 = 1.66 - 0.34 = 1.31A Problem 2: - Determine current florosing through ansmeter having 1-2revistance in series with 32 Clov for fir $\frac{50}{10\sqrt{2}} = \frac{10}{6\pi^2} = \frac{10}{4+2} = \frac{10}{6} = 1.66A$ $\frac{10}{4+6/13} = \frac{10}{4+2} = \frac{10}{6} = 1.66A$ $I_3 = I \times \frac{6}{6+3} = 1.66 \times \frac{6}{9} = 1.11 \text{A}$ 4 A FGA FIA GVE = I3 XAR 21.11×1=1.11V $I_{3}^{1} = \frac{V_{c}}{4 / l_{1} + 4} = \frac{1 \cdot 1}{6 \cdot 4} = 0.17A$ Ammeta reading = Iz-Iz = 1.11-0.17 = 0.93 A

Scanned by CamScanner

1.62

Problems - Ac Endeline " Calculate change in cussent in the network Shown in Fig by using Compensation theorem when the readlance has changed to joss a = 30 m 100/424 = 30sr = 140s Inderive ? 100 LUS = 2 [-8.13 A 1: 87 = j40 - j35 = j5 .r. \$302 .م. عدز (0 V2 - I - SZ = 2 -813 x j5 : 10 |81.57 $\begin{cases} 1 = \frac{V_{L}}{30 + j_{2}} = \frac{10 (s_{1} \cdot s_{7})}{30 + j_{2}} = 0.216 \frac{32.47}{32.47} A \cdot \frac{10}{32} \end{cases}$: charge in current = 0-216 [32-47" A.

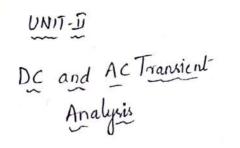

Transient response of R-L, R-C, R-L-C Circuits (series a Parallel) for DC cricitation - Initial Conditions - Solution method using differential equation and Laplace transforms.

Transient suponse of R-L, R-C, R-L-C circuits (serie and parallel) for sinceroidal excitation - Initial Conditions-Solution method using differential equation and Laplace transforme

∅,

De Transient Response of an RL Circuit:-

Consider a circuit consisting of a resistance and inductance as shown in fig. The inductor in the circuit is intially uncharged and is in series with the resistor when the switch is is cloud we can find the complete Solution of the current. Application of Kirchoff's voltage have to the circuit results in the following differential equation

V= Ri+ Ldi $V = L \int \frac{di}{dt} + \frac{R}{L} i \int$ $\frac{di}{dt} + \frac{R}{L} = \frac{V}{L}$ e Rht di + R c Pht i= V e Pht d (ie Rhet) = Ve Rhet d (ie Rht) = V e eht dt $\int d(ie^{k/Lt}) = \int \frac{v}{L} e^{k/Lt} dt^{-1}$ ic = v e eht x = + c i(t) = Verket xerte - R/Lt $i(t) = \frac{V}{R} + Ce^{-R/Lt}$ At t=ot iloj=0 $D = \frac{V}{p} + C = C = \frac{V}{R}$


$$i(t) = \frac{\sqrt{R}}{R} - \frac{\sqrt{R}}{R} e^{t/Lt}$$

$$i(t) = \frac{\sqrt{R}}{R} (1 - e^{R/Lt}) \rightarrow 0$$

cq O Consiste of two parti X & Y - X e - R/L t J, steadystate fransient partport A T

(1)

<

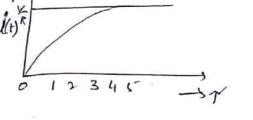

transient part is $i = -\frac{V}{R} e^{-R/LT}$

$$i(r) = -\frac{V}{R} e^{-t/r} = -0.368 \frac{V}{R}$$

$$i(r) = -\frac{V}{R} e^{-2} = -0.131 \frac{V}{R}$$

$$i(sr) = \frac{V}{R} e^{-3} = -0.0498 \frac{V}{R}$$

At one time constant, transient term reaches 30.8.7. q its initial value. $i(5r) = \frac{v}{R}c^{5} = -0.0067 \frac{v}{R}$ $v_{R} = iR = \frac{v}{q}yr(1-e^{-t/R})$ $= v(1-e^{-t/r})$ $v_{L} = L \frac{di}{dt} = tx \frac{v}{x} - c^{-t/r} - \frac{r}{L}$ $= ve^{-t/r}$ Power in the reductor $P_{R} = \frac{v}{L}i$ $= \frac{v^{2}}{R}(1-e^{-t/r})^{n}$ Power in the inductor $P_{L} = v_{L}i$ $= \frac{ve^{-t/r}}{R}(1-e^{-t/r})^{n}$

DC Transient Response of series RC Circuit

Consider a Circuit Consisting of resistance and Capacitance as shown In the fig. The Capacitor in the Circuit is initially uncharged and is in series with a resistor when the switch 's' is closed at t = 0we can determine the complete solution for the Current. Application of the Excholf's voltage law to the circuit results in the following differential equation.

$$V = Ri + \frac{1}{c} \int dt$$

$$v = R \frac{di}{dt} + \frac{1}{c} i$$

$$\frac{di}{dt} + \frac{1}{Rc} i = 0$$

$$\frac{d}{dt} (i e^{lRct}) = 0 =) i e^{lRt} = c$$

$$i(t) = c e^{-lRct}$$

At
$$t = o^{\dagger}$$
 condition acts as short circuit so $1(o) = \frac{V}{R}$

$$\frac{V}{R} = Ce^{\circ} = Ce^{\circ} C = \frac{V}{R}$$

$$i(t) = \frac{V}{R} e^{\frac{1}{R}e^{t}}$$

$$V_{R} = iR = \frac{V}{R} \times Re^{-\frac{1}{R}e^{t}}$$

$$V_{R} = iR = \frac{V}{R} \times Re^{-\frac{1}{R}e^{t}}$$

$$V_{R} = \frac{1}{C} \int i dt = \frac{1}{C} \int \frac{V}{R}e^{\frac{1}{R}e^{t}}$$

$$V_{R} = \frac{1}{C} \int i dt = \frac{1}{C} \int \frac{V}{R}e^{\frac{1}{R}e^{t}}$$

$$V_{R} = \frac{1}{C} \int i dt = \frac{1}{C} \int \frac{V}{R}e^{\frac{1}{R}e^{t}}$$

$$V_{R} = \frac{1}{C} \int i dt = \frac{1}{C} \int \frac{V}{R}e^{\frac{1}{R}e^{t}}$$

$$V_{R} = \frac{1}{C} \int i dt = \frac{1}{C} \int \frac{V}{R}e^{\frac{1}{R}e^{t}}$$

$$V_{R} = \frac{1}{C} \int i dt = \frac{1}{C} \int \frac{V}{R}e^{\frac{1}{R}e^{t}}$$

$$V_{R} = \frac{1}{C} \int i dt = \frac{1}{C} \int \frac{V}{R}e^{\frac{1}{R}e^{t}}$$

$$V_{R} = \frac{1}{C} \int \frac{V}{R}e^{\frac{1}{R}e^{t}}$$

$$V_{R} = \frac{V}{R}e^{\frac{1}{R}}e^{\frac{1}{R}e^{t}}$$

$$V_{R} = \frac{V}{R}e^{\frac{1}{R}}e^{\frac{1}{R}e^{t}}$$

$$V_{R} = \frac{V}{R}e^{\frac{1}{R}$$

De Transient Response of RLC series circuit:-

Consider a circuit Consisting of Texistance, inductance & Capacitance. The Capacitor & inductor are initially uncharged and are in series with a resistor. when saitch's is closed at t=0, we can determine the complete solution for the current. Application of Livehoff's voltage

haw results in the following differential equation .

$$V = Rit + dit + \frac{1}{c} (idt)$$

$$V = Rit + \frac{di}{dt} + \frac{1}{c} (idt)$$

$$Rdi + \frac{di}{dt} + \frac{1}{c} (i = 0)$$

$$\frac{d^{1}i}{dt^{2}} + \frac{R}{c} \frac{di}{dt} + \frac{1}{c} (i = 0) \rightarrow O$$

$$\frac{B^{2}}{B} + \frac{R}{c} + \frac{1}{c} \frac{1}{c} = 0 \rightarrow O$$

$$\frac{B^{2}}{B} + \frac{R}{c} + \frac{1}{c} \frac{1}{c} = 0 \rightarrow O$$

$$\frac{B^{2}}{B} + \frac{R}{c} + \frac{1}{c} \frac{1}{c} \frac{1}{c} = -\frac{R}{2c} \pm \sqrt{\frac{R}{2c}} - \frac{1}{cc}$$

$$= -\alpha \pm \sqrt{\alpha^{2} - \omega_{0}^{2}}$$
where $\alpha \leq \frac{R}{2c}$, $\omega_{0} = \frac{1}{\sqrt{cc}}$

$$\frac{1}{2}i \leq \text{ known as mper frequency } winter are neflec, we is known as$$
Microant frequency of undarged natural frequency of oscillations, uniterare rad/ac, three are three cases
when $\xi_{1,8} \propto > \omega_{0}$, $S_{1,5} \simeq -\alpha - \sqrt{\alpha^{2} - \omega_{0}^{2}}$
Solution of cq . is
$$i(t) = A_{1}c^{5t} + A_{2}c^{5t}$$

when
$$d:W_{i}$$
, critically damped :-
 $S_{i} = S_{i} = -\alpha$
 $i[t] = A_{1}c^{S_{i}t} + A_{3}c^{S_{i}t} = A_{3}c^{\alpha t}$
where $A_{2} = (A_{1}+A_{2})$ but there are two difficus q
we should have two fultial conditions q two constants Q
 $ive should have two fultial conditions q two constants ko this is
 $wrong$. Receiving $eq \cdot O$
 $ive det + \alpha di + \alpha i = 0$
 $ive det + \alpha di + \alpha i = 0$
 $dt = \frac{di}{dt} + \alpha di + \alpha i = 0$
 $dt = \frac{di}{dt} + \alpha i = f$
 $dt = \frac{di}{dt} + \alpha i = f$
 $dt = \frac{di}{dt} + \alpha i = f$
 $dt = A_{1}c^{\alpha t} + \alpha i$
 $izdt = A_{1}c^{\alpha t} + \alpha i$
 $dt = A_{1}c^{\alpha t} + \alpha i$
 $izdt = A_{1} = A_{1}c^{\alpha t} + A_{2}c^{\alpha t}$
 $izdt = A_{1} = A_{1}c^{\alpha t} + A_{2}c^{\alpha t}$
 $izdt = A_{1} = A_{1}c^{\alpha t} + A_{2}c^{\alpha t}$
 $iz = (A_{1} + A_{2})c^{\alpha t}$
 $iz = (A_{1} + A_{2})c^{\alpha t}$
 $i(A_{1} + A_{2})c^{\alpha t} + A_{2}c^{\alpha t}$$


when
$$\forall < w_0$$
, underdamped

$$i(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$= A_1 e^{\forall t} [\cos w_0 t + j \sin w_0 t] + A_2 e^{\forall t} [\cos w_0 t - j \sin w_0 t]$$

$$= e^{\forall t} [(A_1 + A_2) (\cos w_0 t + j(A_1 - A_2) \sin w_0 t]$$
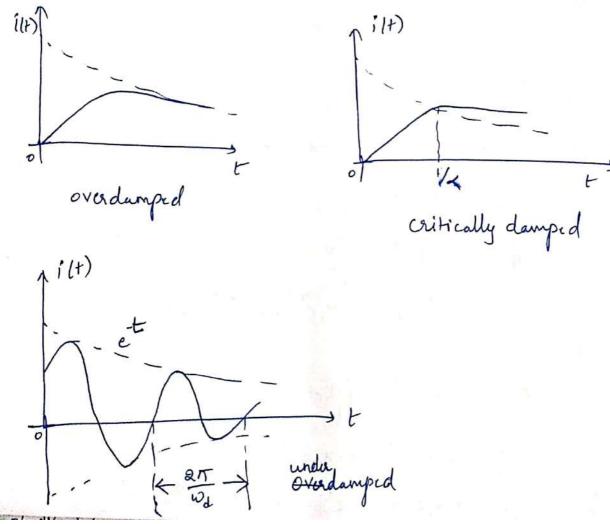
$$= e^{\forall t} [(B_1 (\cos w_0 t)] + B_2 \sin w_0 t]$$
where $B_1 = A_1 + A_2 + B_2 = j (A_1 - A_2)$



$$\begin{split} \frac{k_{1} = -k_{2}}{k_{1}} = \frac{1}{k_{1}} \frac{\pi_{1}}{\pi_{1}} + k_{1} \frac{\pi_{2}}{\pi_{2}} = \frac{\pi_{1}}{k_{2}} = \frac{1}{k_{2}} \frac{k_{3}(\pi_{1} - \pi_{1})}{k_{1}} = \frac{\pi_{2}}{c} \left[\frac{1}{2} - \frac{\pi_{2}}{\pi_{2} - \pi_{1}}\right] = \frac{\pi_{2}}{c} \left[\frac{\pi_{1}}{\pi_{1} - \pi_{1}}\right] \\ \frac{k_{1}}{k_{1}} = \frac{\pi_{2}}{c(\pi_{2} - \pi_{1})} \\ \frac{k_{1}}{k_{2}} = \frac{\pi_{2}}{c(\pi_{2} - \pi_{1})} \\ \frac{k_{1}}{k_{1}} =$$

 $\frac{J_{e}}{C} = (1 c^{2} (0 x (x_{e}))) (1 = \frac{J_{e}}{C})$ $V(t) = \frac{J_{0e}}{\sqrt{\frac{4}{2}}} \frac{4}{12} ct \qquad \text{for } \sqrt{\frac{4}{22}} \frac{1}{12} t$


Sinusoidal Response of RL circuit:-

Consider a circuit consisting of resistance and inductance as shown in Fig.. The moitch 's' is closed at t=0, a sinusoidal Voltage V cos(wit+0) is applied to series to R-L circuit where V is The amplitude of the wave & O is the phase angle. Vosulto) i(+) Apply KVL to the circuit Vos(wt+0) = Ri+Ldi $\frac{di}{dt} + \frac{R}{L}i = \frac{V}{L} (B(W t + 0)) \rightarrow (1)$ This eq. has two solutions, complementary function when D is equaled to zero & particular integral $i(+) = i_{c} + i_{r}$ $\frac{di}{dt} + \frac{R}{L}i = 0 =) i_c = c e^{-R/Lt}$ Let ip = A cos(wt+0) + B sin(wt+0) $i_p = -A\sin(\omega t + 0) \times \omega + B\omega\cos(\omega t + 0)$ substitute ip & ip in O. $-AWsin(wt+0) + BWCos(wt+0) + \frac{R}{L} (ALos(wt+0) + BSin(wt+0))$ 5) $= \frac{\sqrt{\cos(\omega t+0)}}{2}$

$$\begin{split} & \left(A \omega + \frac{BR}{L}\right) \operatorname{Sin}(\omega t + \varrho) + \left(B \omega + \frac{AR}{L}\right) \operatorname{crs}(\omega t + \varrho) : \underbrace{V_{L}}(s (\omega t + \varrho)) : \underbrace{V_{L}}(s (\omega t + \varrho))$$

 $i(f) = \frac{-V}{\sqrt{R^{2} + \omega_{1}^{2}}} \left(OS(0 - Tan' \frac{\omega_{L}}{R}) e^{-l_{1}l} + \frac{V}{\sqrt{R^{2} + \omega_{1}^{2}}} \left(OS(\omega + 10 - Tan' \frac{\omega_{L}}{R}) + \frac{V}{\sqrt{R^{2} + \omega_{1}^{2}}} \right)$

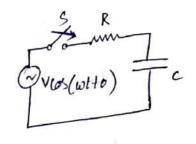Sinusoidal Response of BC Circuit: Consider the circuit consisting of circuit with R & C in series.



Apply KVL to the circuit

$$V(\omega s(\omega + t \theta)) = Ri + \frac{1}{C} \int i dt$$

$$-V\omega sin(\omega + \theta) = Ri + \frac{1}{C} \int i dt$$

$$-\frac{V\omega}{R} sin(\omega + \theta) = Ri + \frac{1}{Rc} i = i \quad (0)$$

$$-\frac{V\omega}{R} sin(\omega + \theta) = \frac{di}{dt} + \frac{1}{Rc} i = i \quad (0)$$

$$i(t) = i_{c} + i_{p} = i \quad (z) = ce^{\frac{1}{R}t}$$

$$i_{p} = Acs(\omega t + \theta) + Bsin(\omega + \theta)$$

$$i_{p} = Acs(\omega t + \theta) + Bsin(\omega + \theta)$$

$$i_{p} = Acs(\omega t + \theta) + Bw(cs(\omega t + \theta))$$

$$Put \quad i_{p} \leq i_{p} \quad i_{n} \quad (0)$$

$$-Awsin(\omega + \theta) + Bw(cs(\omega t + \theta)) + \frac{1}{Rc} \left(Acs(\omega t + \theta) + Rsin(\omega + \theta)\right)$$

$$= -Vwsin(\omega + \theta)$$

$$(-Aw + \frac{B}{Rc})sin(\omega + \theta) + \left(Bw + \frac{A}{Rc}\right)Cs(\omega + \theta) = \frac{-V\omega}{R}sin(\omega + \theta)$$


$$-Aw + \frac{B}{Rc} = -\frac{V\omega}{R}, \quad Bw + \frac{A}{Rc} = 0 = 0$$

$$Bs = -\frac{A}{wcc}$$

$$-Aw - \frac{A}{wccr} = -\frac{V\omega}{R}$$

$$Bz = -V \frac{\omega fcr}{Wccr} \times \frac{1}{Wwcr} \frac{V}{Kr}$$

$$Az = V \frac{\omega Rcr}{Wcr}$$

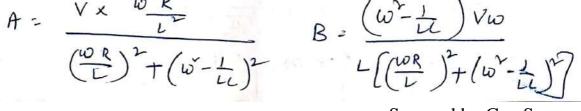

Scanned by CamScanner

Sinusoidal Response of Parallel RLC network :-Consider parallel RLC circuit with switch open at t20 I (witho) S R JL TC Apply KVC to the Circuit $I = \hat{I}_{p} + \hat{I}_{L} + \hat{I}_{c}$ $I (\omega s(\omega t + \theta)) = \frac{V}{R} + \frac{U}{U} \left(v dt + c \frac{dv}{dt} \right)$ -Iw sin(wt+0) = dVilling Lv + c dvo $\frac{d^{\prime}v}{dt^{\prime}} + \frac{1}{Rc}\frac{dv}{dt} + \frac{1}{Lc}v = -\frac{1}{2}\frac{\omega}{c}\sin(\omega t + \theta)$ $\left(\begin{array}{c}D^{+}+L\\Rc\end{array}D+L\\Rc\end{array}\right)v = -\frac{I\omega}{c}\sin(\omega t+\theta)$ Vp = A (os(wt+0)+Bsin(wt+0) V'= - AWSin(wt+0) + BW (W++0) $v_{p}'' = -A\omega^{2}\omega s(\omega + t\theta) - B\omega^{2}s(\omega + t\theta)$ $-A\tilde{\omega}(\omega(\omega t+\theta)) - B\tilde{\omega}(\omega t+\theta) + \frac{1}{RC} \left[-A\tilde{\omega}(\omega t+\theta) + B\tilde{\omega}(\omega(\omega t+\theta)) \right]$ $+ \frac{1}{LC} \left[A (\omega t + \omega) + B \sin(\omega t + \omega) \right] = -\frac{I \omega}{C} \sin(\omega t + \omega)$ $-A\omega + \frac{A}{Lc} cs(\omega t + \theta) + \frac{B\omega}{Rc} z \theta , -\frac{A\omega}{\theta_r} - B\omega + \frac{B}{Lc} z - \frac{I\omega}{c}$ $A = \frac{B \frac{\omega}{RC}}{\omega^{2} - L}, B = \frac{I \omega}{C} (\omega^{2} - \frac{L}{LC})$ $V_{p} = \frac{I_{w}}{Rc^{\nu}} / (w^{\nu} - \frac{1}{L_{v}})^{\nu} + (w^{\nu})^{\nu}$ $V_{p^{2}} \frac{I_{w^{*}}}{R_{c}^{*}} (\omega^{*}(\omega + \omega)) + \frac{I_{w}}{(\omega^{*}-\frac{1}{L_{c}})^{*}} (\omega^{*}-\frac{1}{L_{c}})^{*} (\omega + \omega) + \frac{I_{w}}{(\omega^{*}-\frac{1}{L_{c}})^{*}} (\omega^{*}-\frac{1}{L_{c}})^{*} (\omega^{*}-\frac{1}{L_{c}})^{*} (\omega^{*}-\frac{1}{L_{c}})^{*} (\omega^{*}-\frac{1}{L_{c}})$

$$i_{p}^{r} = \frac{V_{w}}{L^{k}} (es(wt+\theta) + (w^{r} - \frac{1}{L_{c}}) Vw - sindwt+\theta)$$

$$(w^{R} - \frac{1}{L_{c}})^{k} (w^{r} - \frac{1}{L_{c}})^{k} (w^{r} - \frac{1}{L_{c}})^{k}$$

$$(w^{R} - \frac{1}{L_{c}})^{k} (w^{r} - \frac{1}{L_{c}})^{k} (w^{r} - \frac{1}{L_{c}})^{k}$$

$$(w^{R} - \frac{1}{L_{c}})^{$$

-

2 mlos & los (wt+0) + msin & sin (wt+0) $MGS\phi = \frac{\underline{I}\,\omega^{*}}{Rc^{2}}, MSin\phi = \frac{\underline{I}\,\omega}{(\omega^{*}-\underline{i}_{c})^{2}} + (\underline{\omega})^{*}$ $\left(\omega^{2}-\frac{1}{1c}\right)^{2}+\left(\frac{\omega}{c}\right)^{2}$ $\phi = T_{\alpha}n^{-1}\left(R\left(\omega c - \frac{1}{\omega L}\right)\right)$ $m(\omega)\phi + m(\omega)\phi =) m = \frac{I\omega}{c}$ $\sqrt{(\omega^2 - L_c)^2 + (\frac{\omega}{R_c})^2}$ $V_{p} = \frac{I_{\omega}}{c} Cos(\omega t + \theta + T_{\omega}n^{-1}(R(\omega c - \frac{1}{\omega c})))$ $\sqrt{(6^{2} - \frac{1}{\omega c})^{2} + (\frac{\omega}{\rho c})^{2}}$ $\left(\tilde{D} + \frac{1}{Rc} D + \frac{1}{Lc} \right) V = 0$ $D_{1}, D_{2} = \frac{-1}{RL} \pm \sqrt{(\frac{1}{RL})^{2} - \frac{1}{LL}} = \frac{-1}{2RL} \pm \sqrt{(\frac{1}{2RL})^{2} - \frac{1}{LL}}$ 1 > 1 LC V(+) 2 A, C + A, C + A, C + C V(+): Vp + Ve $\frac{1}{2Rc} = \frac{1}{Lc} - \frac{V(t)}{c} e^{D_1(t)} (A_1 + A_2)$ V(+)= V0+ Vc $\sum_{2RC} C \frac{1}{LC} \qquad V_{c}(t) = A_{1}c^{D_{1}t} + A_{2}c^{D_{2}t}$ V(+)= V+Vc

Laplace Transform Method:-

3


The laplace transform is used to solve differential equations and corresponding initial and final value problems. Laplace transforms are widely used in engineering, particularly when the driving function has discontinuties and appears for a short period only.

In circuit analysis, the input and output functions donot exist forever in time. For casual functions, the function can be defined as f(t)ult). The integral for the Laplace transform is taken with the lower limit at 1=0 in order to include the effect of an descontinuity at t=0. Consider a function f(t) which is to be continuous q defined for values of t 7,0. The Laplace transform is then $L\{f(t)\} = F(L) = \int_{0}^{\infty} f(t)e^{-st}dt = \int_{0}^{\infty} f(t)e^{-st}dt$ For a function to have laplace transform it must s= -+jw patisfy the condition jo-fl+) cost dt < 00. $L^{1}[F(S)] = f(t) = \frac{1}{2\pi j} \int_{-1}^{1} F(S)e^{st} dS$ Laplace transform function 15 1 1. 1/5 2. t e-at-1/sta

tn.	$\frac{n!}{(s^{n+1})}$	(0)
Siniot	$\frac{\omega}{s^{*}+\omega^{*}}$	
Cesio F	<u>s</u> stw	
Coshat	S S'-a	
Sinhat	a s'-a	
e ^{at} cosuot	$\frac{s}{(s+a)^{\prime}+\omega^{\prime}}$	
e ^{-at} foinwt	(S+a) + 10	
$L\left\{\frac{df(t)}{dt}\right\}$	=) SF(S)-flo)	
$L\left\{\frac{d^{n}f(t)}{dt^{n}}\right\}$	$S^{2}F(s) - s^{2}f(o) - s^{2}f(o)$	0)
$L \left\{ \int f(t) \right\}$	$=) \frac{F(s)}{s}$	
L Stf(t)}	$z = \frac{d}{ds} F(s)$	
$L \left\{ \begin{cases} \frac{p}{t} \frac{f(t)}{t} \end{cases} \right\}$	$f = \int_{0}^{\infty} F(s) ds$	
Thitid Value	thosen -> it fit)= h	+ S F(S) -300
Final Value	theorem $\longrightarrow Lf f(t) = h$ $t \to \infty$	J- SF(S) ,→0
First shiping	morum L) C f(t) (->	(3) ()
Second shiftin	g theorem L flt-a)u(t-a)	$\rightarrow e^{-r}F(s)$

· tat the morran (11)-> In the circuit shown, delumine the current ilt) when the switch is changed from position 1 to 2. The switch is moved from Position 1 to 2 at t=0 IOV T T'SOV \$ 102 70.54 St. $i(o) = \frac{10}{10} = 1A$ When sivila is moved from ito 2 at t=0 50+0.53 = E15) (5+10) 50 = 101+0.5di SXD.5 $\frac{100+5}{5} = \frac{1}{2} \frac{1}{5} \frac{1}{5$ Apply Laplace method $I(s) = \frac{s+100}{s(s+20)}$ $\frac{50}{5} = 10 I(s) + 0.5 [SI(s) - i(0)]$ = A+ B+ 1+ 10 10I(s) +0.55I(s) -0.5 st100 = A(st20) + BS $A : \frac{109}{24} = 5$ -20B = 50R = -4 $\frac{50+0.5}{5} = I(s) [10+0.55]$ $\frac{50+0.55}{5} \underbrace{50}_{-5} \underbrace{1}_{-5} \underbrace{1}_{-5}$ 101 = I(S) (5+207 $= \frac{0.4}{S+a0} + \frac{50}{S(S+r0)} + \frac{50$ $J(\chi = \frac{101}{100})$ $= \frac{0.5}{(+20)} + \frac{A}{S} + \frac{B}{S+20}$ $\frac{10}{5(stpo)} = \frac{A}{5} + \frac{B}{5t20}$ $= \frac{0.5}{5+20} + \frac{5}{2} - \frac{5/2}{5+20}$ 50= A(S+20)+BS ilt) = 0.5e 20+ + 5 - 5 e -20L A= 5= = 2.5 B= - 4/2 = - 4.5 $= -2c^{-20H} + 2.5$ = 2.5 - 2 e^{-20I} $A[i(t) = 5 - 4e^{-20l^{-}} = X(0) + [X(0) - i(0)]e^{RLT}$

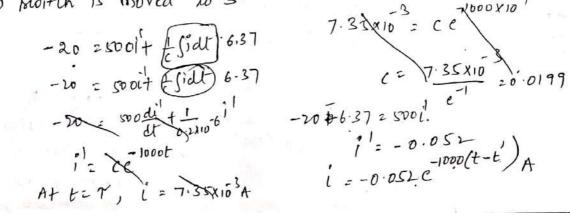⇒ In fig. the switch K is closed at position A at t=0. Afta
a lapse of one time contant the switch is moved into
position B. Detamine complete current
Att=0, Moiltch is closed.
So with 10V, Capaciton C is charged to 10V
ft 0
V = Ri +
$$\frac{1}{C}$$
 fielt
 $0 = 500i + \frac{1}{0.2x16^{L}}$
 $1 = 0.02i^{L}$
 1



$$\Rightarrow \text{ For the Circuit Mouon in figure, determine the transient current when the kwitch is moved from position i to 2 at t=0. The circuit is in Atady date with Revited in position 1.
$$\text{super switch is in position ()} = \frac{150(a(300+20))}{200} = \frac{150(a(300+20))}{200}$$$$

→ The shortch in the circuit has been cloud for a long time.
and it is opened at t=0. Find V(1) for t>0. Calculate the
initial energy stored in the Capacital.
SQ:
when switch has been closed for a long time.
At t ≤0

$$V_{c}(\bar{o}) = Vollage across 9.0. Secietx$$

 $= \frac{9}{9+3} \times (20) = 15V$
when switch is opened at t=20
 $V_{c}(o^{1}) = 15V$
 $T = R_{th} C = (9+1) \times 20 \times 10^{3}$
 $= 10 \times 20 \times 10^{3} = 0.2$
 $V_{c}(t) = V_{c}(0) e^{-t}t^{r} = 15e^{-t/0.2} = 15e^{-5t}V$
 $w_{c}(0) = \frac{1}{2} cl_{c}(0) = \frac{1}{2} \times 20 \times 10^{3} \times 15^{2} = 2.25 J$.
→ Find V(t) for two in the circuit in fig. Assume the switch
has been open for a long time and is cloud at t=0. Calculate
 $V(t)$ at t=0.5 % c.
 $V_{c}(t) = 10V$


when should is closed at too
10-21-61+5D=0

$$si=60=)i=60/s=16/2=7.5B$$

 $V_c(x) = r0-2x7.5 = 10-15=-5V$
 $V_c(x) = r0-2x7.5 = 10-15$

2.0

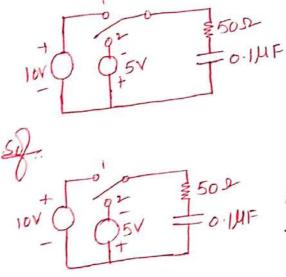Problem ... Steady state is seached in the circuit shown in Fig. When the switch is at 1 at t=0, the switch is moved to 2. When the switch is at 1 at t=0, the switch is moved to 2. Find the drop across the capacitor as well as at the securit Also find the energy stored across the Capacitor after t=0.100500 Also find the energy stored across the Capacitor after t=0.100500



Given that Given that When switch is at position 1, steady When switch is at position 1, steady when switch is at position 1, steady state is reached. Therefore Capacitor state is open circuited and charged to lov $V_c(\bar{o}) = 10V$, $i(\bar{o}) = 0A$

When switch is moved to position 2, Vc (ot) = 10V, but

$$i(o^{\dagger}) = ?$$

 $10^{\dagger} 0 = 2^{\circ} 0 + \frac{1}{2} = 50.0$ Apply KVL to the loop
 $-5 - 50i - 10 = 0$
 $-15 = 50i =)i = -15 = -0.3$
 $\therefore i(o^{\dagger}) = -0.3A$

Apply KVL to the loop

$$-5 - 50i - \frac{1}{0 \cdot 1 \times 10^6} \int i dt = 0$$

 $-5 = 50i + \frac{1}{0 \cdot 1 \times 10^6} \int i dt$
Differentiate on both sides
 $50 \frac{di}{dt} + \frac{1}{0 \cdot 1 \times 10^6} i = 0 = i \int \frac{di}{dt} + \frac{1}{50 \times 0 \cdot 1 \times 10^6} i = 0$

$$\frac{di}{dt} + 0.2 \times 10^{6} i = 0$$

$$i(t) = k_{1} e^{-0.2 \times 10^{6} t}$$

$$At t = 0^{4} i(0^{4}) = -0.3$$

$$-0.3 = k_{1} c^{0}$$

$$K_{1} = -0.3 e^{-0.2 \times 10^{6} t} \implies 0$$

$$Veltage a cross Capaciton$$

$$V_{c}(t) = \frac{1}{c} \int idt = \frac{1}{0.1 \times 0^{6}} \int -0.3 e^{-0.2 \times 10^{6} t}$$

$$= \frac{1}{0.1 \times 10^{6}} \frac{\times 70.3 \times e^{-0.2 \times 10^{6} t}}{70.2 \times 10^{6} t} + k_{2}$$

$$V_{c}(t) = 15 e^{-0.2 \times 10^{6} t} + k_{2} \implies 0$$

$$Veltage a cross + k_{2} = 0$$

$$At t = 0^{4} , v_{c}(o^{4}) = 10V$$

$$I0 = 15 e^{0.2 \times 10^{6} t} -5 = V_{c}(transient) - V_{c}(etiady dat)$$

$$= -5 + (10 - (-5)) e^{-1/2} (-5 + 15 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (10 - (-5)) e^{-1/2} (-5 + 15 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (5 e^{-0.2 \times 10^{6} t} + (-5 + 15 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (5 e^{-0.2 \times 10^{6} t} + (-5 + 15 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (-5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (-5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (-5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (-5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (-5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (-5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (-5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (-5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (-5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (-5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (-5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t}) + (-5 e^{-0.2 \times 10^{6} t})$$


$$= -5 + (-5 e^{-0.2 \times 10^{6} t} + (-5 e^{-0.2 \times 10^{6} t}) + (-5 e^{-0.2 \times 10^{6} t}) + (-5 e^{-0.2 \times 10^{6} t}) + (-5 e^{-0.2 \times 10^{6} t})$$

$$= -5 + (-5 e^{-0.2 \times 10^{6} t$$

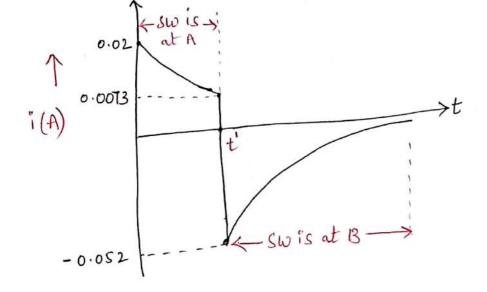Problem :-


In fig the switch K is cloud at position A at t=0. After the lapse of time equivalent to one time Constant, the switch is moved to position B. Determine the Complete current

10V Q Q20V T 0.2MF Switch is closed at position A at t=0 then $i(t) = i(o^{\dagger})e^{-t/\gamma}$ = $\frac{10}{500}e^{-t/500\times0.2\times10^{-6}}$ = $0.02e^{-1/100\times10^{-6}}$ = $0.02e^{-10ft}$ $10^{V} \bigcirc 0^{B} = \frac{1}{20^{V}} = \frac{1}{10^{-2}} = \frac{1}{10^{-2}$ r = RC = 500XD.2X10 At t= p j.e., one time constant = 104 i(r)=0.02e-10tx 104 $V_c(t) = V(1-c^{-t}/r)$ =0.020 = 10 (1-et/500×0.1×154) :0.0073A. = 10 (1-e-10 t) At $t = \gamma$ (one time constant) $v_{c}(\tau) = 10(1 - e^{-10T \times 10T}) = 10(1 - e^{-1}) = 6.32V$ That means when capacitor is charged to 6.32V when Switch isat position A . Before it is charged to IoV, Switch is moved to position B. $i(0^{+}) = -\frac{20 - 6 \cdot 32}{500} = -0.052 \text{ A}$ 10V Q 20V Q+6.32V i(t) = i(o) e = -0.052e (t-t) \$500x0.2x10 = -0.052e (t-t)/10-4 = -0.052e 104(t-t)



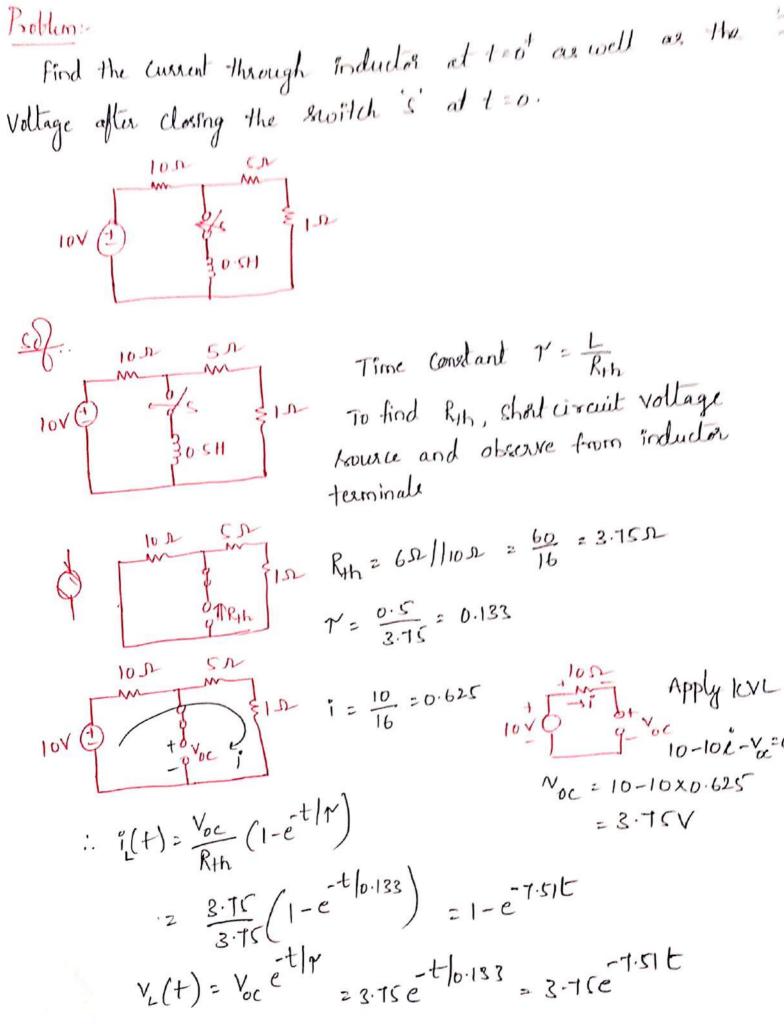Problem :find

ilt) when switch k is moved from A to B at t=0. 45) PB 411 When switch is position A strady 3411 state is reached, so inductor is s.c So (10) = 12 = 3A When switch is moved from A to B at t=0, i(ot)=3A Apply KVL to the loop $4x^2$ Apply KVL to the loop $4y^2$ $4t^2$ $4t^$ ilt) = etfetdt + get >) ilt) = et xet x6 + Get 2) ilt) = 6 + Get, At t= 0, i(0)=3 $3 = 6 + 4e^{\circ} = c_1 = 3 = -3 = i(+) = (6 - 3e^{-t})A$ $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\gamma} = \frac{24}{4} + [3 - \frac{24}{4}]e^{-t/4R}$ = 6+ [3-6]et 14/4 = 6-3et



Network Topology

Graph of a Network Concept of Tree and Co-tree Incidence Matrix Tie-set Tie-set Schedule Cut-set Cut-set Cut-set Schedule Formation of Equilibrium Equations in Matrix Form Solution of Resistive Networks Principle of Duality

I. Basic definitions:

Network Topology:

- Is another method of solving electric circuits
- Is generalized approach

Network:

A combination of two or more network elements is called a network.

Topology:

Topology is a branch of geometry which is concerned with the properties of a geometrical figure, which are not changed when the figure is physically distorted, provided that, no parts of the figure are cut open or joined together.

The geometrical properties of a network are independent of the types of elements and their values.

Every element of the network is represented by a line segment with dots at the ends irrespective of its nature and value.

Circuit:

If the network has at least one closed path it is a circuit.

Note that every circuit is a network but every network is not a circuit.

Branch:

Representation of each element (component) of a electric network by a line segment is a branch.

Node:


A point at which two or more elements are joined is a node. End points of the branches are called nodes.

Graph:

It is collection of branches and nodes in which each branch connects two nodes.

Graph of a Network:

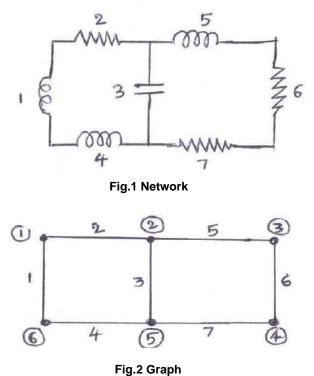The diagram that gives network geometry and uses lines with dots at the ends to represent network element is usually called a graph of a given network. For example,



Sub-graph:

A sub-graph is a subset of branches and nodes of a graph for example branches 1, 2, 3 & 4 forms a sub -graph. The sub-graph may be connected or unconnected. The sub- graph of graph shown in figure 2 is shown in figure 3.

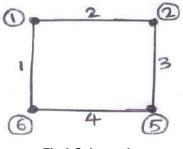


Fig.3 Sub-graph

Connected Graph:

If there exists at least one path from each node to every other node, then graph is said to be connected. Example,

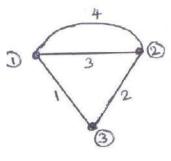


Fig.4 Connected Graph

Un-connected Graph:

If there exists no path from each node to every other node, the graph is said to be un-connected graph. For example, the network containing a transformer (inductively coupled parts) its graph could be un-connected.

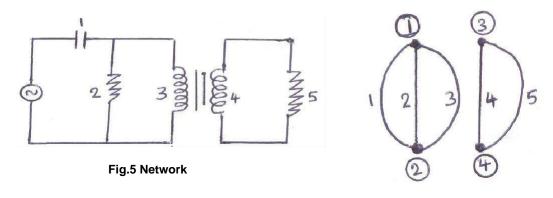


Fig.6 Un-connected Graph

Path (Walk):

A sequence of branches going from one node to other is called path. The node once considered should not be again considered the same node.

Loop (Closed Path):

Loop may be defined as a connected sub -graph of a graph, which has exactly two branches of the sub-graph connected to each of its node.

For example, the branches1, 2 & 3 in figure 7 constitute a loop.


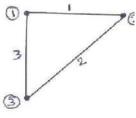


Fig.7 Loop

Planar and Non-planar Graphs:

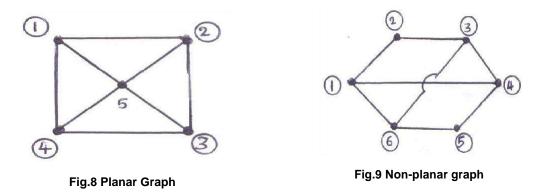A planar graph is one where the branches do not cross each other while drawn on a plain sheet of paper. If they cross, they are non-planar.



Oriented Graph:

The graph whose branches carry an orientation is called an oriented graph

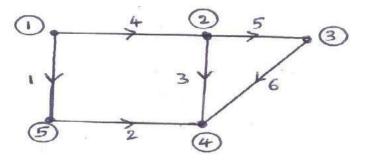


Fig.10 Oriented Graph

The current and voltage references for a given branches are selected with a +ve sign at tail side and -ve sign at head

↓⁺

Tree:

Tree of a connected graph is defined as any set of branches, which together connect all the nodes of the graph without forming any loops. The branches of a tree are called **Twigs**.

Co-tree:

Remaining branches of a graph, which are not in the tree form a co-tree. The branches of a co-tree are called **links** or **chords**.

The tree and co-tree for a given oriented graph shown in figure11 is shown in figure12 and figure13.

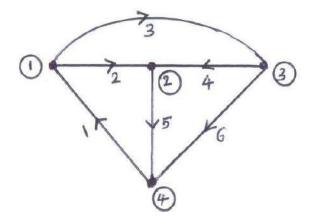


Fig. 11 Oriented Graph



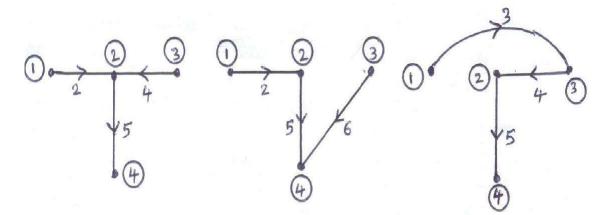


Fig.12 Trees

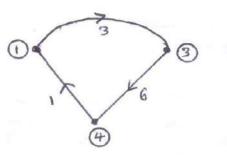

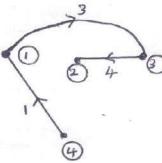

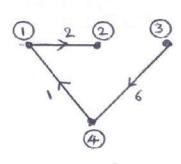


Fig.13 Co-trees

Tree	Twigs	Links (Chords)
1	2,4&5	1,3&6
2	3,4&5	1,2&6
3	2,5&6	1,3&4

Properties of Tree:

i) It contains all the nodes of the graph.

ii) It contains (n_t-1) branches. Where ' n_t ' is total number of nodes in the given graph.

iii) There are no closed paths.

Total number of tree branches, $n = (n_t-1)$

Where $n_t = Total$ number of nodes

Total number of links, l = (b-n)

Where b = Total number of branches in the graph.

Degree of Node:


The number of branches attached to the node is degree of node.

II. Complete Incidence Matrix (A_a):

Incidence matrix gives us the information about the branches, which are joined to the nodes and the orientation of the branch, which may be towards a node or away from it.

Nodes of the graph form the rows and branches form the columns. If the branch is not connected to node, corresponding element in the matrix is given the value '0'. If a branch is joined, it has two possible orientations. If the orientation is away from the node, the corresponding matrix element is written as '+1'. If it is towards the node, the corresponding matrix element is written as '-1'.

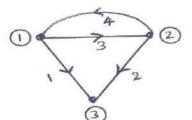Example: 1) Obtain complete incidence matrix for the graph shown



Solution:

		Branches					
	Nodes	1	2	3	4		
Aa =	1	1	0	1	-1		
	2	0	1	-1	1		
	3	-1	-1	0	0		

	1	0	1	-1	
A _a =	0	1	-1	1	
	-1	-1	0	0	

Properties of Incidence Matrix:

- i) Each column has only two non-zero elements and all other elements are zero.
- ii) If all the rows of ' A_a ' are added, the sum will be a row whose elements equal zero.


If the graph has 'b' branches and ' \mathbf{n}_t ' nodes, the complete incidence matrix is of the order ($\mathbf{n}_t \mathbf{x} \mathbf{b}$).

III. Reduced Incidence Matrix (A):

When one row is eliminated from the complete incidence matrix, the remaining matrix is called **reduced incidence matrix**

If the graph has 'b' branches and ' n_t ' nodes, the reduced incidence matrix is of the order (n_t -1) x b.

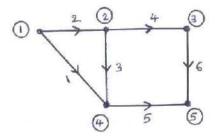Example: 2) Write the complete and reduced incidence matrix for the given graph shown



Solution:

Aa

	Nodes	Branches					
		1	2	3	4	5	6
	1	1	1	0	0	0	0
=	2	0	-1	1	1	0	0
	3	0	0	0	-1	0	1
	4	-1	0	-1	0	1	0
	5	0	0	0	0	-1	-1

	1	1	0	0	0 0
	0	-1	1	1	0 0
Complete Incidence Matrix, $A_a =$	0	0	0	-1	0 1
	-1	0	-1	0	10
	0	0	0	0	-1-1

Reduced Incidence Matrix,
$$\mathbf{A} = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 0 & 1 \\ -1 & & 0 & -10 & 1 & 0 \end{bmatrix}$$


Example: 3) Draw the oriented graph of incidence matrix shown below

$$\mathbf{A} = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix}$$

Solution: The given matrix is a reduced incidence matrix. Obtain the complete incidence matrix in order to draw the oriented graph.

$$\mathbf{A_a} = \begin{pmatrix} 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 \\ -1 & 0 & -1 & 0 & -1 & 0 & -1 \end{pmatrix}$$

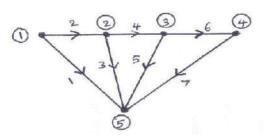Total number of nodes = $n_t = 5$ Total number of branches = b = 7




Oriented Graph

Example: 4) Draw the oriented graph of incidence matrix shown below

$$\mathbf{A_a} = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & -1 \\ -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -1 & 0 & 1 \\ 0 & 0 & -1 & 1 & -1 & 0 \end{bmatrix}$$

Solution:

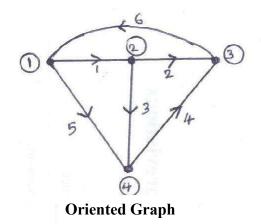Total number of nodes $= n_t = 4$ Total number of branches = b = 6




Example: 5) Draw the oriented graph of incidence matrix shown below

$$\mathbf{A} = \begin{bmatrix} -1 & -1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 1 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 1 \end{bmatrix}$$

Solution: The given matrix is a reduced incidence matrix. Obtain the complete incidence matrix in order to draw the oriented graph.

$$\mathbf{A}_{\mathbf{a}} = \begin{pmatrix} -1 - 10 & 0 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 1 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 1 \\ 1 & 0 & 0 & -1 & -1 & -1 & -1 \end{pmatrix}$$

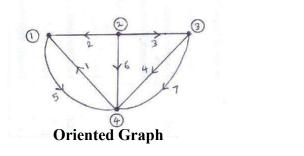Total number of nodes $= n_t = 4$ Total number of branches = b = 7



Example: 6) Show that determinant of the incidence matrix of a closed loop is zero.


Proof: let us consider a closed path ABC Total number of nodes = $n_t = 3$ Total number of branches = b = 3The complete incidence matrix is $A_a = \begin{pmatrix} -1 & 0 & -1 \\ 0 & 1 & 1 \\ 1 & -1 & 0 \end{pmatrix}$

The determinant of complete incidence matrix of the closed loop is

$$\begin{vmatrix} -1 & 0 & -1 \\ 0 & 1 & 1 \\ 1 & -1 & 0 \end{vmatrix} = -1(0+1)-0-1(0-1)=-1+1=0$$

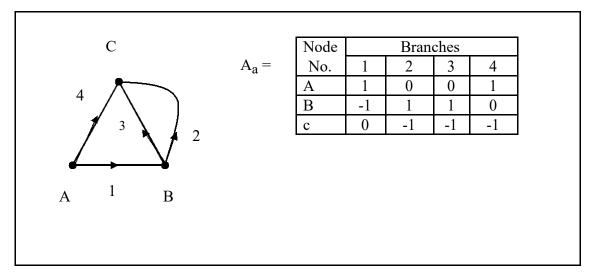IV. Number of Possible Trees of a Graph:

For the given network graph, it is possible to write several trees. The number of possible trees is equal to determinant of $[A] [A]^{t}$. Where [A] is the reduced incidence matrix obtained by removing any one row from complete incidence matrix and $[A]^{t}$ is the transpose of [A].



Node Pair Voltages:

The voltage between any two nodes of a network is known as the node-pair voltages. In general all branch voltages are node-pair voltages.

Network Variables:

In Loop analysis, the loop currents are unknown parameters. Once, they are evaluated, all branch currents can be determined in terms of these loop currents.

Similarly, in nodal analysis, the node-pair voltages are the unknown parameters. Once, they are evaluated, the voltages across any two nodes of the network can be found. Hence, the **node-pair voltages** and **loop currents** are called network variables.


The network variables are independent variables and all other quantities depend on these values.

V. Tie-set:

A tie-set is a set of branches contained in a loop such that each loop contains one link or chord and remainder are tree branches.


Or

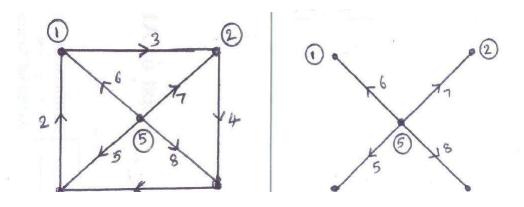The set of branches forming the closed loop in which link or loop current circulate is called a **Tie-set**.



Oriented Graph

Tree

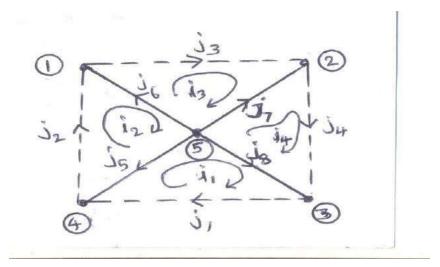

Let the branch currents in the network graph denoted by the symbol 'j' and various loop currents by symbol 'i'.

The orientation of a closed loop will be chosen to be the same as that of its connecting link.

For the given network graph,

Number of branches, b = 8

Number of nodes, $n_t = 5$

Number of closed loops = $[b-(n_t - 1)]$

Where $(n_t-1) =$ Number of tree branches.

VI. Tie-set Schedule:

For a given network tree, a systematic way of indicating the links is through use of a schedule called **Tie-set Schedule**

The tie-set schedule for the given network oriented graph is shown below

Link Current				Bran	ches			
	1	2	3	4	5	6	7	8
or Number								
1	1	0	0	0	-1	0	0	1
2	0	1	0	0	1	-1	0	0
3	0	0	1	0	0	1	-1	0
4	0	0	0	1	0	0	1	-1

The tie-set schedule can be written in matrix form is known as Tie-set matrix (B).

$$\mathbf{B} = \begin{pmatrix} 1 & 0 & 0 & 0 & -1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 1 & -1 \end{pmatrix}$$

After writing the schedule, the columns of a schedule or matrix gives branch currents in terms of link currents. Thus column 1 gives equation for j_1 in terms of link currents

i.e.
$$j_1 = i_1$$
 $j_5 = i_2 \cdot i_1$
Similarly, $j_2 = i_2$ $j_6 = i_3 \cdot i_2$
 $j_3 = i_3$ $j_7 = i_4 \cdot i_3$
 $j_4 = i_4$ $j_8 = i_1 \cdot i_4$

$$(1)$$

The rows of the schedule give KVL equations in terms of coefficients of the schedule or matrix. i. e. $e_1 - e_5 + e_8 = 0$

$$\begin{array}{cccc}
e_{2} + e_{5} - e_{6} &= 0 \\
e_{3} + e_{6} - e_{7} &= 0 \\
e_{4} + e_{7} - e_{8} &= 0
\end{array}$$
(2)

The set of equation (1) can be expressed in the matrix form as

$$\begin{pmatrix} j_{1} \\ j_{2} \\ j_{3} \\ j_{4} \\ j_{5} \\ j_{6} \\ j_{7} \\ j_{8} \end{pmatrix} = \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & 1 \\ 1 & 0 & 0 & -1 \end{pmatrix} \begin{pmatrix} i_{1} \\ i_{2} \\ i_{3} \\ i_{4} \end{pmatrix}$$
(3)

In compact form

Where

 $\begin{bmatrix} I_b \end{bmatrix}$ = is a column matrix of branch currents of the order (bx1).

$$\begin{bmatrix} B \end{bmatrix}^{T}$$
 = is the transpose of the fundamental tie-set matrix B.
 $\begin{bmatrix} I_{I} \end{bmatrix}$ = is a column matrix of loop currents or link currents of the order (lx1).
Where 'I' is the number of independent loops.

From set of equation (2),

$$\begin{pmatrix}
1 & 0 & 0 & 0 & -1001 \\
0 & 1 & 0 & 0 & 1 & -100 \\
0 & 0 & 1 & 0 & 0 & 1-10 \\
0 & 0 & 0 & 1 & 0 & 01-1
\end{pmatrix}$$


$$\begin{pmatrix}
e_1 \\
e_2 \\
e_3 \\
e_4 \\
e_5 \\
e_6 \\
e_7 \\
e_8
\end{pmatrix} = 0$$
(5)

In compact form

$$\left(\mathbf{B} \right) \left(\mathbf{E}_{\mathbf{b}} \right) = \mathbf{0}$$
 (6)

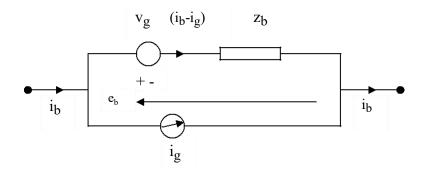VII. Equilibrium Equations with Loop Currents as Variables:

Consider a general branch of a network as shown in figure



Where $v_g = Total$ series voltage in the branch

 i_g = Total current source connected across the

branch z_b = Total impedance of the branch i_b =

Branch current

The voltage current relation for the branch can be written as

 $\mathbf{e}_{\mathbf{b}} = \mathbf{v}_{\mathbf{g}} + \mathbf{z}_{\mathbf{b}} \left(\mathbf{i}_{\mathbf{b}} - \mathbf{i}_{\mathbf{g}} \right) \tag{i}$

and $i_b = i_g + y_b (i_b - i_g)$ (ii)

15

Where $y_b = Total$ admittance of the branch.

For a network with more number of branches, equation (i) & (ii) may be written as

$$[E_b] = [V_g] + [Z_b] ([I_b] - [I_g])$$
(iii)

$$[I_b] = [I_g] + [Y_b] ([E_b] - [V_g])$$
(iv)

Where

 $[E_b]$, $[V_g]$, $[I_b]$, & $[I_g]$ are (bx1) matrices of branch voltages, source voltages in the branches, branch currents and source currents in the branches respectively. $[Z_b]$ & $[Y_b]$ are branch impedance and branch admittance matrices of the order (bxb).

We have

$$[E_b] = [V_g]_T + [Z_b] ([I_b] - [I_g])$$
(1)

$$[\mathbf{I}_{\mathbf{b}}] = [\mathbf{B}] \ [\mathbf{I}_{\mathbf{l}}] \tag{2}$$

$$[B] [E_b] = 0 (3)$$

Substituting (1) in (3), we get

$$[B] [V_{g}] + [B][Z_{b}] ([I_{b}] - [I_{g}]) = 0$$


$$[B][Z_{b}] [I_{b}] = [B][Z_{b}] [I_{g}] - [B] [V_{g}] \qquad (4)$$
Substituting (2) in (4)
T
$$[B][Z_{b}] [B] [I_{1}] = [B] [Z_{b}] [I_{g}] - [B] [V_{g}] \qquad (5)$$
Let $[B] [Z_{b}] [I_{g}] - [B] [V_{g}] = [V_{1}]$
and $[B] [Z_{b}] [B] = [Z_{1}] = Loop Impedance matrix$
Then equation (5) may be written as
$$[Z_{1}] [I_{1}] = [V_{1}] \text{ or }$$

$$[I_1] = [Z_1] [V_1]$$
(6)

Equations (5) and (6) represent a set of **Equilibrium Equations** with loop currents as independent variables. On solving these equations, loop currents are obtained. Once the loop currents are known, all the branch currents can be found. If the elements of the branches are known, then all branch voltages also can be found.

Example: 1)

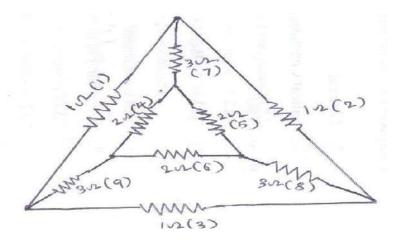
- (a) For the given network shown. Draw the graph, select a tree with branches 9, 4, 7, 5, & 8 and write the tie-set matrix. The number inside the brackets indicates branch numbers.
- (b) Using the above tie-set matrix formulate equilibrium equations.



Solution: Total number of branches, b = 9;

Total number of nodes $n_t = 6$;

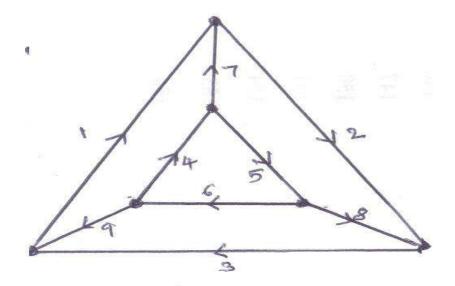Total number of tree branches, n = (nt-1) = (6-1) = 5; Total number of links, l = (b-n) = (9-5) = 4



Oriented Graph

$$\mathbf{B} = \begin{pmatrix} 1 & 0 & 0 & -1 & 0 & 0 & -1 & 0 & 1 \\ 0 & 1 & 0 & 0 & -1 & 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & 1 & 1 & 0 & 0 & 1 & -1 \\ 0 & 0 & 0 & 1 & 1 & 1 & 0 & 0 & 0 \end{pmatrix}$$

Rows of above matrix give KVL Equations

$$e_{1} - e_{4} - e_{7} + e_{9} = 0$$

$$e_{2} - e_{5} + e_{7} - e_{8} = 0$$

$$e_{3} + e_{4} + e_{5} + e_{8} - e_{9} = 0$$

$$e_{4} + e_{5} + e_{6} = 0$$
(1)

٦

Columns of above matrix give Branch Currents $j_1 = i_1$

We have, branch voltage is given by $e_k = r_k j_k$.

Where k=1, 2, 3 ...9.

(3)

 $e_1 = r_1 j_1$ $e_2 = r_2 j_2$ $e_3 = r_3 j_3$ $e_4 = r_4 j_4$ $e_5 = r_5 j_5$ $e_6 = r_6 j_6$ $e_7 = r_7 j_7$ $e_8 = r_8 j_8$ $e_9 = r_9 j_9$

Substituting equation (2) in (3) and resulting equations are substituting in equation (1) We get,


$$9i_{1}-3i_{2}-5i_{3}-2i_{4} = 0$$

-3i_{1}+9i_{2}-5i_{3}-2i_{4} = 0
-5i_{1}-5i_{2}+11i_{3}+4i_{4}=0
-2i_{1}-2i_{2}+4i_{3}+6i_{4} = 0 (4)


Set of equations (4) are called **Equilibrium Equations.** Solutions of these equations will give the **Link currents or Loop currents**. Then using these link currents, we can find out the branch currents

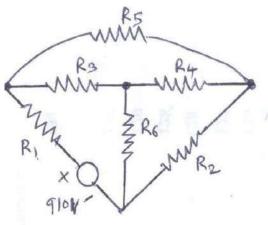Example: 2)

For the given resistive network, write a tie-set schedule and equilibrium equations on the current basis. Obtain values of branch current and branch voltages. Given that $R_{1}=5$; $R_{2}=5$; $R_{3}=R_{4}=R_{6}=10$ and $R_{5}=2$.



Solution:

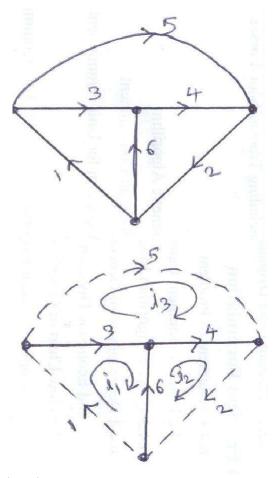

Total number of branches, b = 6; Total number of nodes nt = 4; Total number of tree branches, n = (nt-1) = (4-1) = 3; Total number of links, l = (b-n) = (6-3) = 3

Link	Branches							
Currents	1	2	3	4	5	6		
i1	1	0	1	0	0	-1		
i2	0	1	0	1	0	1		
i3	0	0	-1	-1	1	0		

The columns of the above schedule give branch currents in terms of link currents

$$j_{1} = i_{1}$$

$$j_{2} = i_{2}$$

$$j_{3} = (i_{1}-i_{3})$$

$$j_{4} = (i_{2}-i_{3})$$

$$j_{5} = i_{3}$$

$$j_{6} = (-i_{1}+i_{2})$$

(1)

The rows of above schedule, give the KVL Equations $e_1+e_3-e_6 = 0$ $e_2+e_4+e_6 = 0$ $-e_3-e_4+e_5 = 0$ (2) We have, branch voltage is given by $e_k = r_k j_k$. Where $k=1, 2, 3 \dots 6$. $e_1 = r_1 j_1-910 = 5i_1 - 910$ $e_2 = r_2 j_2 = 5i_2$ $e_3 = r_3 j_3 = 10i_1-10i_3$ $e_4 = r_4 j_4 = 10i_2-10i_3$ $e_5 = r_5 j_5 = 2i_3$ $e_6 = r_6 j_6 = -10i_1+10i_2$ (3)

Substituting equation (3) in (2) we get,

$$25i_{1} - 10i_{2} - 10i_{3} = 910$$

-10i_{1} + 25i_{2} - 10i_{3} = 0 (4) - 10i_{1} + 20i_{2} + 22i_{3} = 0

The set of equations (4) are called **Equilibrium Equations**.

$$\begin{cases} 25 & -10 & -10 \\ -10 & 25 & -10 \\ -10 & -10 & 22 \end{cases} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{cases} 910 \\ 0 \\ 0 \end{bmatrix}$$

i = $\Delta 1/\Delta$ = 40950/4550 = 90A
Where
$$= \begin{bmatrix} 25 & -10 & -10 \\ -10 & 25 & -10 \\ -10 & -10 & 22 \end{bmatrix} \text{ and } \Delta 1 = \begin{bmatrix} 910 & -10 & -10 \\ 0 & 25 & -10 \\ 0 & -10 & 22 \end{bmatrix}$$

 $\Delta 2/\Delta$ = 64A; where $\Delta 2 = \begin{bmatrix} 25 & 910 & -10 \\ -10 & 0 & -10 \end{bmatrix}$

$$i_2 = \Delta_2 / \Delta = 64 \text{A}; \text{ where } \Delta_2 = -10 \quad 0 \quad -10 \\ -10 \quad 0 \quad 22$$

is =
$$\Delta 3/\Delta$$
 = 70A; where $\Delta 3$ =
 $25 -10 910$
 $-10 20 0$
 $-10 -10 0$

From equation (1), Branch currents in terms of link currents are given by

 $j_1 = i_1 = 90A$ $j_2 = i_2 = 64A$ $j_3 = (i_1-i_3) = (90-70) = 20A$ $j_4 = (i_2-i_3) = (64-70) = -6A$ $j_5 = i_3 = 70A$ $j_6 = (-i_1+i_2) = (-90+64) = -26A$

From equation (3), Branch Voltages in terms of branch currents or link currents are given by

 $\begin{array}{ll} e_1 = r_1 \ j_1 - 910 = 5i_1 \ -910 = 460V\\ e_2 = r_2 \ j_2 &= 5i_2 \ = 320V\\ e_3 = r_3 \ j_3 &= 10i_1 - 10i_3 = 200V\\ e_4 = r_4 \ j_4 &= 10i_2 - 10i_3 = -60V\\ e_5 = r_5 \ j_5 &= 2i_3 \ = 140V\\ e_6 = r_6 \ j_6 &= -10i_1 + 10i_2 = -260V \end{array}$

VIII. Cut-set:

Tree branches connect all the nodes in the network graph. Hence, it is possible to trace the path from one node to any other node by traveling along the tree branch only. Therefore, potential difference between any two nodes called node-pair voltage can be expressed in terms of tree branch voltages.

The cut set is a minimal set of branches of the graph, removal of which cuts the graph into two parts. It separates the nodes of the graph into two groups. The cutset consists of only one tree branch and remainders are links. Each branch of the cutset has one of its terminal incident at a node in one group and its other end at a node in the other group and its other end at a node in the other group. The orientation of the cut-set is same as orientation of tree branch.


The number of cut -sets is equal to number of tree branches [i.e. (nt-1) = n where n_t is total number of nodes in the network graph].


IX. Cut-set schedule:

For a given network tree, a systematic way of indicating the tree branch voltage through use of a schedule called **cut-set schedule**

To write the cut-set schedule for network graph,

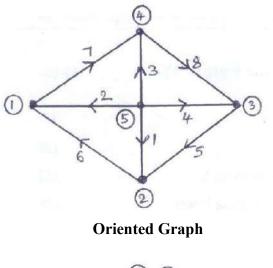- (i) Consider an oriented network graph
- (ii) Write any one possible tree of the network graph
- (iii)Assume tree branch voltages as (e1, e2...en) independent variables.
- (iv)Assume the independent voltage variable is same direction as that of a tree branch voltage
- (v) Mark the cut-sets (recognize) in the network graph.



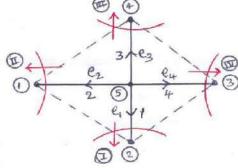

Tree and Cut-sets

The tree branch voltages e_1 , e_2 , e_3 , & e_4 entered in the first column of the schedule correspond to 4 branches 1, 2, 3 & 4. In order to fill the first row corresponding to the tree branch voltages e_1 , by looking into the direction of currents in the branches connected to the cut-set under consideration. If the direction of current in the cut-set branch is towards the cut-set node, write '+1' in the branch column of concerned cut-set branch. If the direction of current in the cut-set node, write '-1' in that particular cut-set branch column. Write '0' in the branch columns, which are not in that particular, cut-set.

Tree		Branches							
Branch	1	2	3	4	5	6	7	8	
Tree Branch Voltages									
e ₁	1	0	0	0	1	-1	0	0	
e ₂	0	1	0	0	0	1	-1	0	
e ₃	0	0	1	0	0	0	1	-1	
e4	0	0	0	1	-1	0	0	1	

Cut-set schedule:

The columns of the cut-set schedule give branch voltage equations;

$$\begin{array}{c} \text{i.e. } v_1 = e_1 \\ v_2 = e_2 \\ v_3 = e_3 \\ v_4 = e_4 \\ v_5 = (e_1 - e_4) \\ v_6 = (-e_1 + e_2) \\ v_7 = (-e_2 + e_3) \\ v_8 = (-e_3 + e_4) \end{array} \right\}$$
(1)

The rows of cut-set schedule give KCL equations;

$$\begin{array}{c}
 j_{1}+j_{5}-j_{6}=0 \\
 j_{2}+j_{6}-j_{7}=0 \\
 j_{3}+j_{7}-j_{8}=0 \\
 j_{4}-j_{5}+j_{8}=0
\end{array}$$
(2)

The cut-set schedule can be written in matrix form is known as **cut-set matrix**. This matrix can be represented by **Q**.

$$\mathbf{Q} = \begin{pmatrix} 1 & 0 & 0 & 0 & 1 & -1 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 1 & -1 \\ 0 & 0 & 0 & 1 & -1 & 0 & 0 & 1 \end{pmatrix}$$

From set of equations (1)

$$\begin{pmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ v_7 \\ v_8 \end{pmatrix} = \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & -1 \\ -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ 0 & 0 & -1 \end{pmatrix}$$

In compact form;

$$[\mathbf{V}_{\mathbf{b}}] = [\mathbf{Q}]^{\mathbf{T}}[\mathbf{V}_{\mathbf{T}}]$$
(3)

Where

 $[V_b]$ = Branch Voltage Column Matrix of order **bx1**

 $[V_T]$ = Tree Branch Voltage Column Matrix of order **nx1**


[Q] = Cut-set Matrix of order **nxb**

$$\begin{bmatrix} 10001-100\\ 010001-10\\ 0010001-1\\ 0001-1001 \end{bmatrix} \begin{bmatrix} j_1\\ j_2\\ j_3\\ j_4\\ j_5\\ j_6\\ j_7 \end{bmatrix} = 0$$

In compact form;

[Q] [I_b] = 0
Where
[I_b] = Branch Current Column Matrix of order
bx1 [Q] = Cut-set Matrix of order nxb

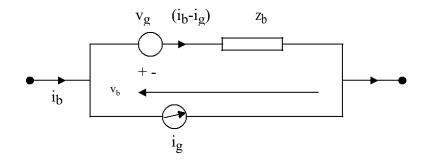Consider a general branch of a network as shown in figure



Where $v_g = Total$ series voltage in the branch

 i_g = Total current source connected across the branch

 z_b = Total impedance of the branch i_b = Branch current

(4)

The voltage current relation for the branch can be written as

$$\mathbf{v}_{\mathbf{b}} = \mathbf{v}_{\mathbf{g}} + \mathbf{z}_{\mathbf{b}} \left(\mathbf{i}_{\mathbf{b}} - \mathbf{i}_{\mathbf{g}} \right) \tag{1}$$

and
$$i_b = i_g + y_b (v_b - v_g)$$
 (2)

Where $y_b = Total$ admittance of the branch.

For a network with more number of branches, equation (i) & (ii) may be written as

$$[V_b] = [V_g] + [Z_b] ([I_b] - [I_g])$$
(3)

$$[I_b] = [I_g] + [Y_b] ([V_b] - [V_g])$$
(4)

Where

 $[V_b], [V_g], [I_b], \& [I_g]$ are (bx1) matrices of branch voltages, source voltages in the branches, branch currents and source currents in the branches respectively. [Zb] & [Yb] are branch impedance and branch admittance matrices of the order (bxb).

We have

$$[V_{b}] = [V_{g}] + [Z_{b}] ([I_{b}] - [I_{g}])$$

$$[V_{b}] = [Q]^{T} [V_{T}]$$
(5)
$$[Q] [I_{b}] = 0$$
(6)

$$[Q] [I_b] = 0 \tag{6}$$

Substituting (4) in (6), we get

$$[Q] [I_g] + [Q] [Y_b] \{ [V_b] - [V_g] \} = 0$$

 $[Q] [I_g] + [Q] [Y_b] [V_b] - [Q] [Y_b] [V_g] = 0$ (7)
Substituting (5) in (7), we get

Substituting (5) in (7), we get

$$[Q] [I_g] + [Q] [Y_b] [Q]^T [V_T] - [Q] [Y_b] [V_g] = 0$$
(8)

Let,

 $[Q] [Y_b] [Q]^{T} = [Y_c] = Cut-set admittance matrix$

Equation (8) becomes,

$$[Y_{c}] [V_{T}] = [Q] [Y_{b}][V_{g}] - [Q] [I_{g}]$$

$$Or$$


$$[V_{T}] = [Y_{c}]^{-1} \{[Q] [Y_{b}][V_{g}] - [Q] [I_{g}]\}$$
(9)

This equation (9) is known as **Equilibrium Equation**.

The solutions of equation (9) give the tree branch voltages and branch currents can be find using equation (5) and (4).

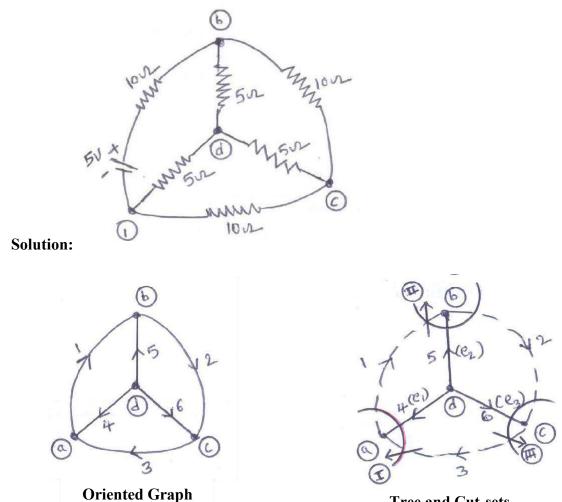Example: 1)

For the given resistive network, write a cut-set schedule and obtain equilibrium equations on the voltage basis. Solve these equations and hence calculate values of branch voltages and branch currents.



- - - - - **- -**

Tree and Cut-sets

Cut-set Schedule:							
Cut-sets or	ts or Branches						
Tree branch Voltages	1	2	3	4	5	6	
1 or (e_1)	-1	0	1	1	0	0	
2 or (e ₂)	1	-1	0	0	1	0	
3 or (e ₃)	0	1	-1	0	0	1	

Columns of the above schedule give branch voltages in terms of tree branch voltages

$$\begin{array}{c}
v_1 = -e_1 + e_2 \\
v_2 = -e_2 + e_3 \\
v_3 = e_1 - e_3 \\
v_4 = e_1 \\
v_5 = e_2 \\
v_6 = e_3
\end{array}$$
(1)

Rows of the above schedule give KCL equations

$$\begin{array}{c} -j_1 + j_3 + j_4 = 0 \\ j_2 - j_3 + j_6 = 0 \end{array}$$
 $j_1 - j_2 + j_5 = 0 \quad (2)$

We have from given network, $(v_{k^{\pm}} v_g) = j_k x r_k$ Where k=1, 2, 3 ...6.

Branch currents
$$j_k = (v_k \pm v_g)/r_k$$
. Hence,
 $j_1 = (v_1 + 5)/10 = (-e_1 + e_2 + 5)/10 = -0.1e_1 + 0.1e_2 + 0.5$
 $j_2 = v_2/10 = (-e_2 + e_3)/10 = -0.1e_2 + 0.1e_3$
 $j_3 = v_3/10 = (e_1 - e_3)/10 = 0.1e_1 - 0.1e_3$
 $j_4 = v_4/5 = e_1/5 = 0.2e_1$
 $j_5 = v_5/5 = e_2/5 = 0.2e_2$
 $j_6 = v_6/5 = e_3/5 = 0.2e_3$
Substituting set of equations (3) in (2), we get
 $0.4e_1 - 0.1e_2 - 0.1e_3 = 0.5$
 $-0.1e_1 + 0.4e_2 - 0.1e_3 = -0.5$ (4)
 $-0.1e_1 - 0.1e_2 + 0.4e_3 = 0$

The set of equations (4) are called **Equilibrium Equations**

0.4	-0.1	-0.1	e ₁		0.5
-0.1	0.4	-0.1	e ₂	=	-0.5
-0.1	-0.1	0 <u>.</u> 4	[e3]		

$$= \begin{vmatrix} 0.4 & -0.1 & -0.1 \\ -0.1 & 0.4 & -0.1 \\ -0.1 & -0.1 & 0.4 \end{vmatrix} = 50 \qquad = \begin{vmatrix} 0.5 & -0.1 & -0.1 \\ -0.5 & 0.4 & -0.1 \\ 0 & -0.1 & 0.4 \end{vmatrix} = 50$$


$$= \begin{vmatrix} 0.4 & 0.5 & -0.1 \\ -0.1 & -0.5 & -0.1 \\ -0.1 & 0 & 0.4 \end{vmatrix} = -50$$
$$= \begin{vmatrix} .4 & -0.1 & 0.5 \\ -0.1 & 0.4 & -0.5 \\ -0.1 & -0.1 & 0 \end{vmatrix} = 0$$

 $e_{1} = v_{4} = \frac{1}{1} / =1V$ $e_{2} = v_{5} = \frac{2}{2} / = -1V$ $e_{3} = v_{6} = \frac{3}{3} / = 0V$ $v_{1} = -e_{1} + e_{2} = -1 - 1 = -2V$ $v_{2} = -e_{2} + e_{3} = 1 + 0 = 1V$ $v_{3} = e_{1} - e_{3} = 1 - 0 = 1V$


From equation (3), $j_1 = (v_1 + 5)/10 = (-2+5)/10 = 0.3A$ $j_2 = v_2/10 = 1/10 = 0.1 A$ $j_3 = v_3/10 = 1/10 = 0.1 A$ $j_4 = v_4/5 = 1/5 = 0.2 A$ $j_5 = v_5/5 = 1/5 = 0.2 A$ $j_6 = v_6/5 = 0/5 = 0 A$

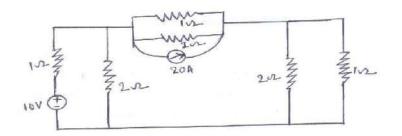
Example: 2)

Draw the graph for the network shown in figure below. Write the cut-set schedule & obtain equilibrium equations and hence calculate values of branch voltages and branch currents



Solution:

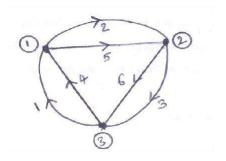

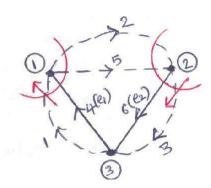

Oriented Graph



Cut-set Schedule:

Cut-sets or		Branches				
Tree branch Voltages	1	2	3	4	5	6
1 or (e_1)	1	-1	0	1	-1	0
$2 \text{ or } (e_2)$	0	-1	1	0	-1	1

Columns of the above schedule give branch voltages in terms of tree branch voltages

$$v_1 = e_1$$

 $v_2 = -e_1 - e_2$
 $v_3 = e_2$
 $v_4 = e_1$
 $v_5 = -e_1 - e_2$
 $v_6 = e_2$

(1)

Rows of the above schedule give KCL equations

$$j_{1} - j_{2} + j_{4} - j_{5} = 0$$

$$-j_{2} + j_{3} - j_{5} + j_{6} = 0$$
(2)

We have from given network,
$$(v_k \pm v_g) = j_k x r_k$$

Branch currents $j_k = (v_k \pm v_g) / r_k$. Hence,
 $j_1 = (v_1 + 10)/1 = (e_1 + 10)/1 = e_1 + 10$
 $j_2 = v_2/1 = (-e_1 - e_2)/1 = -e_1 - e_2$
 $j_3 = v_3/1 = e_2/1 = e_2$ (3)
 $j_4 = v_4/2 = e_1/2 = 0.5e_1$
 $j_5 = (v_5 + 40)/2 = [(-e_1 - e_2) + 40]/2 = -0.5e_1 - 0.5e_2 + 20$
 $j_6 = v_6/2 = e_2/2 = 0.5e_2$
Substituting set of equations (3) in (2), we get
 $3e_1 + 1.5e_2 = 10$ (4)
 $1.5e_1 + 3e_2 = 20$

The set of equations (4) are called Equilibrium Equations

$$\begin{pmatrix} 3 & 1.5 \\ 1.5 & 3 \end{pmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{pmatrix} 10 \\ 20 \end{bmatrix}$$

$$e_1 = \Delta_1 / \Delta \text{ where } \Delta = \begin{vmatrix} 3 & 1.5 \\ 1.5 & 3 \end{vmatrix} = 6.75 \text{ and } \Delta_1 = \begin{vmatrix} 0 & 1.5 \\ 20 & 3 \end{vmatrix} = 0$$


$$e_1 = 0/6.75 = 0 \text{ V.}$$

 $e_2 = \Delta_2 / \Delta$ where $\Delta = \begin{vmatrix} 3 & 1.5 \\ 1.5 & 3 \end{vmatrix} = 6.75$ and $\Delta_2 = \begin{vmatrix} 10 & 1.5 \\ 20 & 3 \end{vmatrix} = 45$ $e_2 = 45/6.75 = 6.667$ V.

The branch voltages are
$$v_1 = e_1 = 0 V$$
The branch currents are
 $j_1 = (v_1 + 10)/1 = 10 A$
 $j_2 = v_2/1 = 6.667 A$
 $j_3 = v_3/1 = 6.667 A$
 $v_4 = e_1 = 0 V$ $j_1 = (v_1 + 10)/1 = 10 A$
 $j_2 = v_2/1 = 6.667 A$
 $j_3 = v_3/1 = 6.667 A$
 $v_4 = e_1 = 0 V$ $v_5 = -e_1 - e_2 = -0 - 6.667 = -6.667V$ $j_5 = (v_5 + 40)/2 = (-6.667 + 40)/2 = 16.66 A$
 $v_6 = e_2 = 6.667 V$ $v_6 = e_2 = 6.667 V$ $j_6 = v_6/2 = 3.33 A$

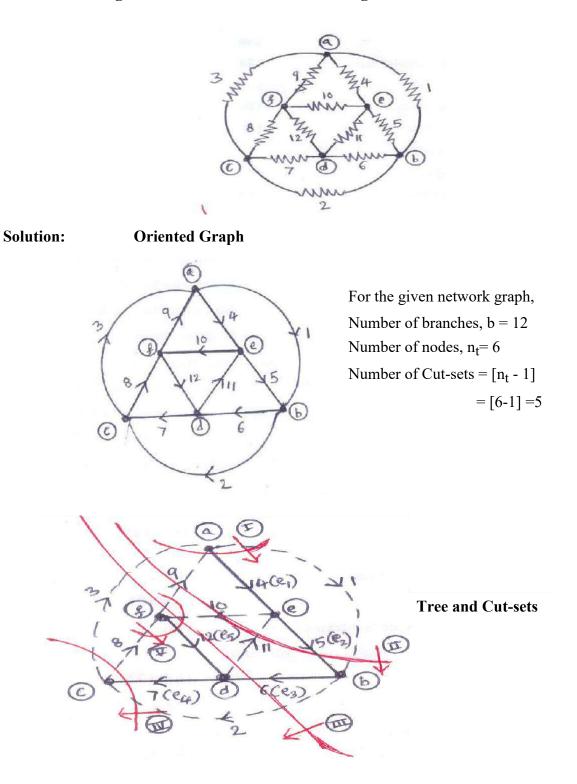Example: 3)

For the given network, draw the oriented graph and a tree. Select suitable tree branch voltages and write the cut-set schedule and also write the equations for the branch voltages in terms of the tree branch voltages.



Cut-set Schedule:

Tree Branch						Bra	nches					
Voltages or Cut-set	1	2	3	4	5	6	7	8	9	10	11	12
e ₁	1	0	-1	1	0	0	0	0	-1	0	0	0
e ₂	1	0	-1	0	1	0	0	0	-1	1	-1	0
e3	0	1	-1	0	0	1	0	0	-1	1	-1	0
e4	0	1	-1	0	0	0	1	-1	0	0	0	0
e5	0	0	0	0	0	0	0	-1	1	-1	0	1

Columns of the above schedule will give branch voltages in terms of tree branch voltages

$$v_{1} = e_{1}+e_{2}$$

$$v_{2} = e_{3}+e_{4}$$

$$v_{3} = -e_{1}-e_{2}-e_{3}-e_{4}$$

$$v_{4} = e_{1}$$

$$v_{5} = e_{2}$$

$$v_{6} = e_{3}$$

$$v_{7} = e_{4}$$

$$v_{8} = -e_{4}-e_{5}$$

$$v_{9} = -e_{1}-e_{2}-e_{3}-e_{5}$$

$$v_{10} = e_{2}+e_{3}-e_{5}$$

$$v_{11} = -e_{1}-e_{3}$$


$$v_{12} = e_{5}$$

XI. Principle of Duality:

Duality: is the mutual relationship.

We come across a number of similarities in analyzing the network on current (Loop) basis and voltage (Node) basis. The principal quantities (and concepts) involved in the two methods form pairs. Each of the quantity in such a pair thus plays a dual role. These quantities (or concepts) forming pair are called **dual quantities**.

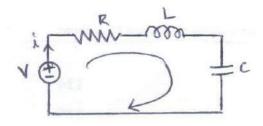
Consider a network containing R, L & C elements connected in series and excited by a voltage source as shown.



The integro- differential equations for the circuit is

$$R i + L (di/dt) + (1/C) i dt = v$$
 (1)

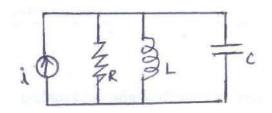Consider a network containing R, L & C elements connected in parallel and driven by a current source as shown.



The integro- differential equations for the circuit is

$$(1/R) v + C (dv/dt) + (1/L) v dt = i$$
 (2)
OR

$$G v + C (dv/dt) + (1/L) v dt = i$$
 (2)

If we observe both the equations, the solutions of these equations are the same.

Therefore, these two networks are called **duals**

XII. Construction of a Dual of a Network:


Only planar networks without mutual inductances have **duals.**

S.N.	Quantity or Concept	Dual Quantity or Concept		
1	Current	Voltage		
2	Resistance	Conductance		
3	Inductance	Capacitance		
4	Branch Current	Branch Voltage		
5	Mesh	Node		
6	Loop	Node-Pair		
7	Number of Loops	Number of Node-Pairs		
8	Loop Current	Node-Pair Voltage		
9	Mesh Current	Node Voltage or Node Potential		
10	Link	Tree Branch		
11	Tie-set	Cut-set		
12	Short Circuit	Open Circuit		
13	Parallel Path	Series Path		
14	Charge (Q)	Flux Linkages ()		


Procedure to draw a Dual Network:

- **Step 1:** In each Loop of a given network place a node and place an extra node called reference node outside the network.
- **Step 2:** Draw the lines connecting adjacent nodes passing through each element and also to the reference node by placing the dual of each element in the line passing through original elements.

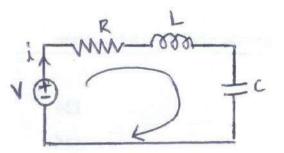Example: 1) Draw the dual of a network for given network shown in figure.




Solution:

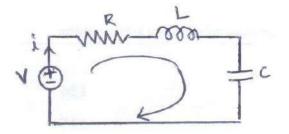

The integro- differential equations for the circuit is


$$R i + L (di/dt) + (1/C) idt = v$$
 (1)

Dual Network

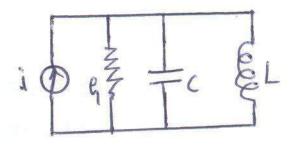


The integro- differential equations for the circuit is

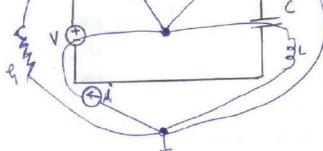
$$(1/R) v + C (dv/dt) + (1/L) v dt = i$$
 (2)
OR
 $G v + C (dv/dt) + (1/L) v dt = i$



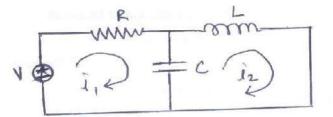Example: 2) Draw the dual of the network shown in figure.




Solution:

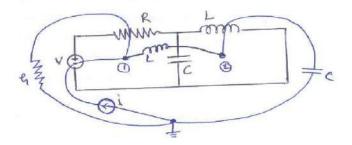

The integro- differential equations for the network is

$$R i_1 + (1/C) \quad i_1 - i_2) dt = v (t)$$
(1)

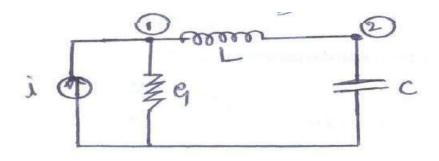
 $L (di_2/dt) + (1/C) \quad i_2 - i_1) dt = 0$ (2)




The integro- differential equations for the network is

$$C (dv_2/dt) + (1/L) v_2 - v_1) dt = 0$$
 (2)

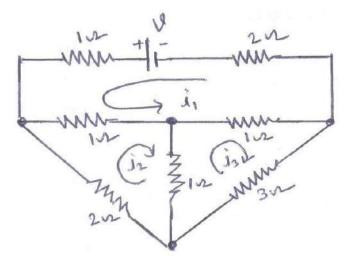
Example: 3) Draw the dual of the network shown in figure.



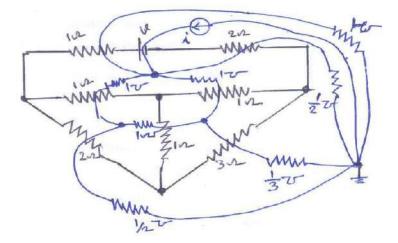

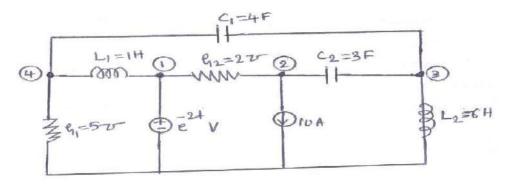Example: 4)

For the network shown in figure below, write the node equations. Draw the dual of this network and write mesh equations for the dual network. Verify whether these two sets of equations are dual equations



Node Equations:

At node (1);

$$(I/L_1) \ (e^{-2t} - v_4) \ dt + G_2 \ (e^{-2t} - v_2) = 0 \tag{1}$$

At node (2);


(G₂)
$$(v_2 - e^{-2t}) + C_2 [d(v_2 - v_3)/dt] + 10 = 0$$
 (2)
de (3):

At node (3);

$$(I/L_2) v_3 dt + C_2 [d (v_3 - v_2)/dt] + C_1 [d (v_3 - v_4)/dt] = 0$$
(3)

At node (4);
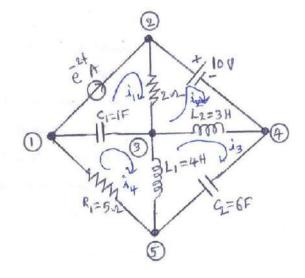
$$G_1 v_4 + (1/L_1) (v_4 - e^{-2t}) dt + C_1 [d (v_4 - v_3)/dt] = 0$$
(4)



Loop Equations for dual network are

$$(I/C_1) \ (e^{-2t} - i_4) \ dt + R_2 \ (e^{-2t} - i_2) = 0$$
(5)


R₂
$$(i_2 - e^{-2t}) + L_2 [d(i_2 - i_3)/dt] + 10 = 0$$
 (6)


$$(I/C_2) i_3 dt + L_2[d(i_3 - i_2)/dt] + L_1[d(i_3 - i_4)/dt] = 0$$
(7)

$$R_1 i_4 + (1/C_1) (i_4 - e^{-2t}) dt + L_1 [d(i_4 - i_3)/dt] = 0$$
(8)

By looking into two sets of equations, we can say that two sets of equations are dual equations.

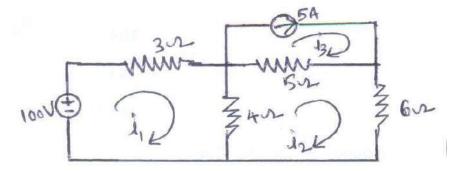Example: 5) Draw the dual of the network shown below




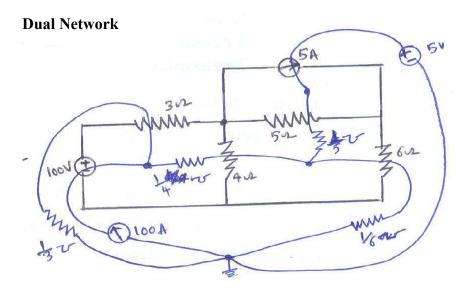



KVL Equations;		KCL Equations;	
$-100 + 3i_1 + 4(i_1 - i_2) = 0$		$100 = (1/3) v_1 + (1/4) (v_1 - v_2)$	
$7i_1 - 4i_2 = 100$ $4(i_2 - i_1) + 5(i_2 - i_3) + 6i_2 = 0$	(1)	$(7/12)v_1 - (1/4)v_2 = 100$ $(1/4)(v_2-v_1) + (1/5)(v_2-v_3) + (1/6)v_2=0$	(1)
$-4i_1 + 15i_2 - 5i_3 = 0$ $-5i_2 + 5i_3 = 0$	(2)	$(-1/4)v_1 + (9/20)v_2 - (1/5)v_3 = 0$ $(-1/5)v_2 + (1/5)v_3 = 0$	(2)
-5i ₂ +25=0	(3)	$(-1/5)v_2 + 1 = 0$	(3)
Since $i_3 = 5A$		Since $v_3 = 5v$	

By looking into two sets of equations, we can say that two sets of equations dual equations

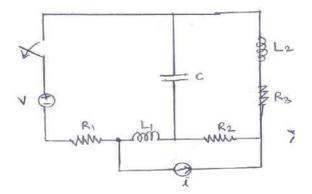
Example: 6) Draw the dual of the network shown below




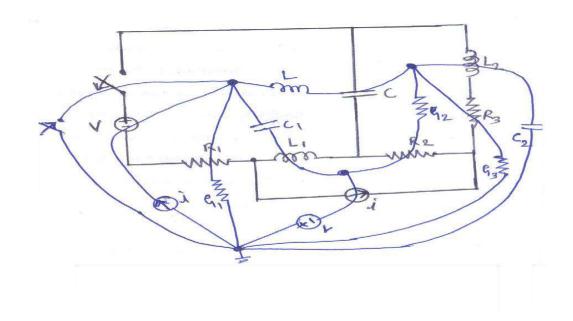

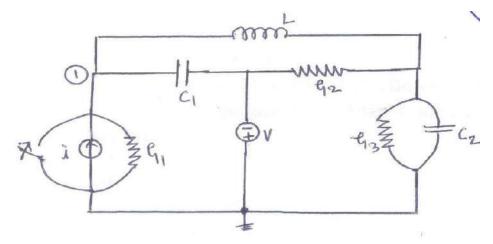


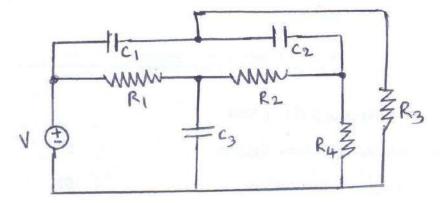
Example: 7) Draw the dual of the network shown below



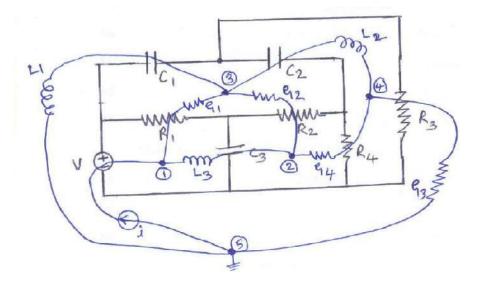


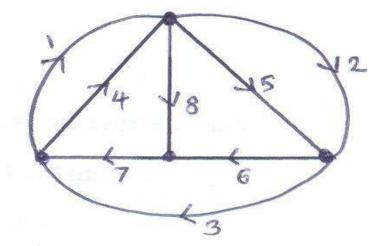Example: 8) Draw the dual of the given oriented graph




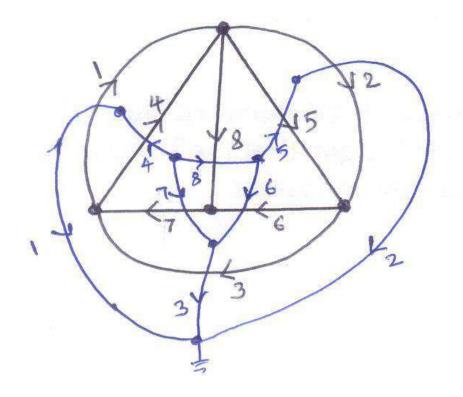

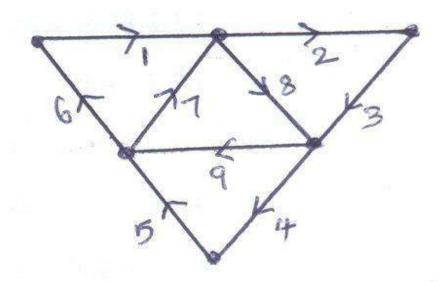
Example: 9) Draw the dual of the given oriented graph





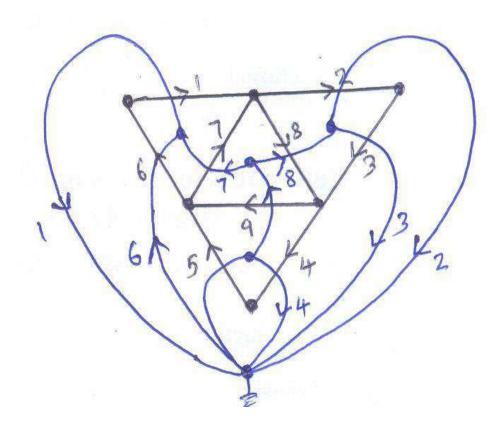



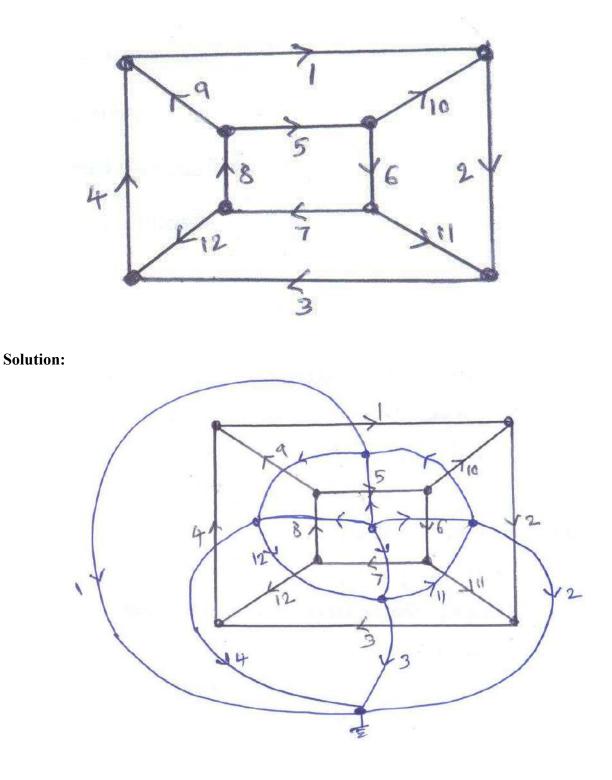

UNIT - IV Two port Networks

Introduction:

A two-port network has two pairs of terminals, one pair at the input known as input port and one pair at the output known as output port as shown in figure: 6.1. There are four variables V_1, V_2, I_1 and I_2 associated with a two port network. Two of these variables can be expressed in terms of the other two variables. Thus, there will be two dependent variables and two independent variables. The number of possible combinations generated by four variables taken two at a time is 4C_2 , i.e., six. There are six possible sets of equations describing a two-port network.



Figure: 6.1 Two-port network

Parameter	V	ariables	Equation
	Express	In terms of	1
Open-Circuit Impedance	V ₁ ,V ₂	I ₁ ,I ₂	$V_1 = Z_{11}I_1 + Z_{12}I_2$ $V_2 = Z_{21}I_1 + Z_{22}I_2$
Short-Circuit Admittance	I ₁ ,I ₂	V ₁ ,V ₂	$I_1 = Y_{11}V_1 + Y_{12}V_2 I_2 = Y_{21}V_1 + Y_{22}V_2$
Transmission	V ₁ ,I ₁	V ₂ ,I ₂	$V_1 = A V_2 - B I_2$ $I_1 = C V_2 - D I_2$
Inverse Transmission	V ₂ ,I ₂	V ₁ ,I ₁	$V_2 = A'V_1 - B'I_1$ $I_2 = C'V_1 - D'I_1$

Two-Port Parameters:

Hybrid	V ₁ ,I ₂	I ₁ ,V ₂	$V_1 = h_{11}I_1 + h_{12}V_2$ $I_2 = h_{21}I_1 + h_{22}V_2$
Inverse Hybrid	I ₁ ,V ₂	V ₁ ,I ₂	$I_1 = g_{11}V_1 + g_{12}I_2$ $V_2 = g_{21}V_1 + g_{22}I_2$

Open-Circuit Impedance Parameters (Z Parameters)

The Z parameters of a two-port network may be defined by expressing two-port voltages V_1 and V_2 in terms of two-port currents I_1 and I_2 .

$$(V_1, V_2) = f(I_1, I_2)$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

 $V_2 = Z_{21}I_1 + Z_{22}I_2$

In matrix form, we can write

 $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$ $\begin{bmatrix} V \end{bmatrix} = \begin{bmatrix} Z \end{bmatrix} \begin{bmatrix} I \end{bmatrix}$

The individual Z parameters for a given network can be defined by setting each of the port currents equal to zero.

Case 1: When the output port is open-circuited, i.e., $I_2 = 0$

$$Z_{11} = \frac{V_1}{I_1} / I_2 = 0$$

Where Z_{11} is the driving-point impedance with the output port open-circuited. It is also called open-circuit input impedance.

Similarly, $Z_{21} = \frac{V_2}{I_1} / I_2 = 0$

Where Z_{21} is the transfer impedance with the output port open-circuited. It is also called open-circuit forward transfer impedance.

Case 2: When the input port is open-circuited, i.e., $I_1 = 0$

$$Z_{12} = \frac{V_1}{I_2} / I_1 = 0$$


Where Z_{12} is the transfer impedance with the input port open-circuited. It is also called open-circuit reverse transfer impedance.

Similarly,
$$Z_{22} = \frac{V_2}{I_2} / I_1 = 0$$

Where Z_{22} is the open-circuit driving-point impedance with the input port open-circuited. It is also called open-circuit output impedance.

As these impedance parameters are measured with either the input or output port open-circuited, these are called open-circuit impedance parameters.

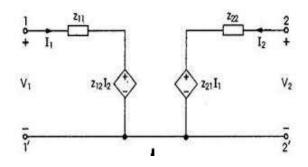The equivalent circuit of the two-port network in terms of Z parameters is shown in figure: 6.3



Equivalent circuit of the two-port network in terms of Z parameter.

Condition for Reciprocity:

If $Z_{12}=Z_{21}$, the network is said to be reciprocal network. Condition for Symmetry:

If $Z_{11}=Z_{22}$, the network is said to be symmetrical network.

Short-Circuit Admittance Parameters (Y Parameters)

The Y parameters of a two-port network may be defined by expressing two-port currents I_1 and I_2 in terms of the two-port voltages V_1 and V_2 .

$$\begin{aligned} (I_1, I_2) &= f(V_1, V_2) \\ I_1 &= Y_{11}V_1 + Y_{12}V_2 \\ I_2 &= Y_{21}V_1 + Y_{22}V_2 \end{aligned} \\ \text{In matrix form, we can write} \qquad \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \\ \begin{bmatrix} I \end{bmatrix} = \begin{bmatrix} Y \end{bmatrix} \begin{bmatrix} V \end{bmatrix} \end{aligned}$$

The individual Y parameters for a given network can be defined by setting each of the port voltages equal to zero.

Case 1: When the output port is short-circuited, i.e., $V_2 = 0$

$$Y_{11} = \frac{I_1}{V_1} / V_2 = 0$$

Where Y_{11} is the driving-point admittance with the output port short-circuited. It is also called short-circuit input admittance.

Similarly, $Y_{21} = \frac{I_2}{V_1} / V_2 = 0$

Where Y_{21} is the transfer admittance with the output port short-circuited. It is also called short-circuit forward transfer admittance.

Case 2: When the input port is short-circuited, i.e., $V_1 = 0$

$$Y_{12} = \frac{I_1}{V_2} / V_1 = 0$$


Where Y_{12} is the transfer admittance with the input port short-circuited. It is also called short-circuit reverse transfer admittance.

Similarly, $Y_{22} = \frac{I_2}{V_2} / V_1 = 0$

Where Y_{22} is the short-circuit driving-point admittance with the input port short-circuited. It is also called short-circuit output admittance.

As these admittance parameters are measured with either input or output port short-circuited, these are called short-circuit admittance parameters.

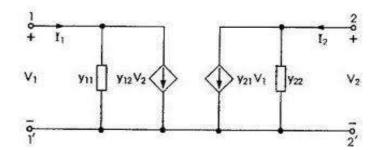The equivalent circuit of the two-port network in terms of Y parameters is shown in figure: 6.4



Equivalent circuit of the two-port network in terms of Y-parameters

Condition for Reciprocity:

If $Y_{12} = Y_{21}$, the network is said to be reciprocal network. Condition for Symmetry:

If $Y_{11} = Y_{22}$, the network is said to be symmetrical network.


Transmission Parameters (ABCD Parameters)

The transmission parameters or chain parameters or ABCD parameters serve to relate the voltage and current at the input port to voltage and current at the output port.

In equation form,

$$(V_1, I_1) = f(V_2, -I_2) V_1 = A V_2 - B I_2 I_1 = C V_2 - D I_2$$

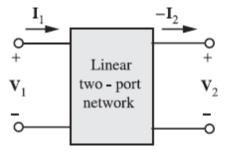Here, the negative sign is used with I_2 and not for parameters B and D. The reason the current I_2 carries a negative sign is that in transmission field, the output current is assumed to be coming out of the output port instead of going into the port.



Terminal variables used to define ABCD parameters

In matrix form, we can write

$[V_1]$	_ [A	B٦	$\begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$
$\begin{bmatrix} I_1 \end{bmatrix}^-$	= [<u>C</u>	D	$\left[-I_{2}\right]$

Where matrix $\begin{bmatrix} A & B \\ C & D \end{bmatrix}$ is called transmission matrix.

For a given network, these parameters are determined as follows:

Case 1 When the output port is open-circuited, i.e., I_2 =0 $A = \frac{V_1}{V_2} / I_2 = 0$

Where A is the reverse voltage gain with the output port open-circuited.

Similarly, $C = \frac{I_1}{V_2} / I_2 = 0$

Where C is the transfer admittance with the output port open-circuited.

Case 2 When the output port is short-circuited, i.e., $V_2=0$

$$B=-\frac{V_1}{I_2}/\,V_2=0$$

Where B is the transfer impedance with the output port short-circuited.

Similarly,
$$D = -\frac{I_1}{I_2}/V_2 = 0$$

Where D is the reverse current gain with the output port short-circuited.

Condition for Reciprocity:

If AD-BC=1, the network is said to be reciprocal network. Condition for Symmetry:

If A=D, the network is said to be symmetrical network.

Hybrid Parameters (h Parameters)

The hybrid parameters of a two-port network may be defined by expressing the voltage of input port V_1 and current of output port I_2 in terms of current of input port I_1 and voltage of output port V_2 .

$$(V_1, I_2) = f (I_1, V_2)$$

 $V_1 = h_{11}I_1 + h_{12}V_2$
 $I_2 = h_{21}I_1 + h_{22}V_2$

 $\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$

In matrix form, we can write

These parameters are particularly important in transistor circuit analysis.

Case 1 When the output port is short-circuited, i.e., $V_2=0$

 $\mathbf{h}_{11} = \frac{\mathbf{V}_1}{\mathbf{I}_1} / \mathbf{V}_2 = \mathbf{0}$

Where h_{11} is called as short-circuit input impedance.

Similarly, $h_{21} = \frac{I_2}{I_1} / V_2 = 0$ Where h_{21} is called as short-circuit forward current gain.

Case 2 When the input port is open-circuited, i.e., $I_1=0$

$$h_{12} = \frac{V_1}{V_2} / I_1 = 0$$


Where h_{12} is called as open circuit reverse voltage gain.

Similarly, $h_{22} = \frac{I_2}{V_2} / I_1 = 0$

Where h_{22} is called as open-circuit output admittance.

Since h parameters represent dimensionally impedance, admittance, voltage gain and current gain, these are called hybrid parameters.

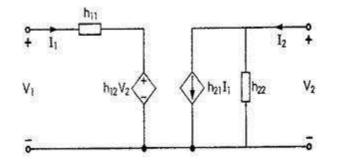The equivalent circuit of the two-port network in terms of hybrid parameters is shown in figure: 6.6



Equivalent circuit of the two-port network in terms of h-parameters

Condition for Reciprocity:

If $h_{21} = -h_{12}$, the network is said to be reciprocal network. Condition for Symmetry:

If $h_{11}h_{22}-h_{12}h_{21} = 1$ ($\Delta h = 1$), the network is said to be symmetrical network.

Inter-Relationships between the Parameters:

When it is required to find out two or more parameters of a particular network then finding each parameter will be tedious. But if we find a particular parameter then the other parameters can be found if the inter-relationship between them is known.

1. Z-parameters in terms of other parameters:

a) Z-parameters in terms of Y-parameters:

We known that

$$\begin{split} I_{1} &= Y_{11}V_{1} + Y_{12}V_{2} \\ I_{2} &= Y_{21}V_{1} + Y_{22}V_{2} \\ \\ By \ Cramer's \ rule, \ V_{1} &= \left| \frac{|I_{1}^{1} - Y_{12}|}{|Y_{21} - Y_{22}|} \right| = \frac{Y_{22}I_{1} - Y_{12}I_{2}}{Y_{11}Y_{22} - Y_{12}Y_{21}} = \frac{Y_{22}}{\Delta Y}I_{1} - \frac{Y_{12}}{\Delta Y}I_{2} \\ \\ Where & \Delta Y = Y_{11}Y_{22} - Y_{12}Y_{21} \\ Comparing with & V_{1} = Z_{11}I_{1} + Z_{12}I_{2} \\ \\ Z_{11} &= \frac{Y_{22}}{\Delta Y} \\ Z_{12} &= -\frac{Y_{12}}{\Delta Y} \\ \\ Also, \ V_{2} &= \frac{|Y_{11} - I_{1}|}{\Delta Y}I_{2} - \frac{Y_{21}}{\Delta Y}I_{1} \\ \\ Comparing with & V_{2} = Z_{21}I_{1} + Z_{22}I_{2} \\ \\ Z_{22} &= \frac{Y_{11}}{\Delta Y} \\ \\ Z_{21} &= -\frac{Y_{21}}{\Delta Y} \\ \\ \end{bmatrix}$$

b) Z-parameters in terms of ABCD parameters:

We know that
$$V_1 = A V_2 - B I_2$$

 $I_1 = C V_2 - D I_2$

Rewriting the second equation,

Comparing with

$$V_{2} = \frac{1}{C}I_{1} + \frac{D}{C}I_{2}$$

$$V_{2} = Z_{21}I_{1} + Z_{22}I_{2}$$

$$Z_{21} = \frac{1}{C}$$

$$Z_{22} = \frac{D}{C}$$
Also, $V_{1} = A\left[\frac{1}{C}I_{1} + \frac{D}{C}I_{2}\right] - BI_{2}$

 $\begin{bmatrix} A \\ C \end{bmatrix}_{1}^{C} I_{1} + \begin{bmatrix} A \\ C \end{bmatrix}_{2}^{T} = \begin{bmatrix} A \\ C \end{bmatrix}_{1}^{T} + \begin{bmatrix} A \\ C \end{bmatrix}_{1}^{T} = \begin{bmatrix} A \\ C \end{bmatrix}_{1}^{T}$

$$= \frac{A}{C}I_1 + \left[\frac{AD - BC}{C}\right]I_2$$

Comparing with $V_1 = Z_{11}I_1 + Z_{12}I_2$ $Z_{11} = \frac{A}{C}$ $Z_{12} = \frac{AD - BC}{C}$

c) Z-parameters in terms of A'B'C'D' parameters:

We know that
$$V_2 = A'V_1 - B'I_1$$

 $I_2 = C'V_1 - D'I_1$

Rewriting the second equation,

Comparing with

$$V_{1} = \frac{D'}{C'}I_{1} + \frac{1}{C'}I_{2}$$
$$V_{1} = Z_{11}I_{1} + Z_{12}I_{2}$$
$$Z_{11} = \frac{D'}{C'}$$
$$Z_{12} = \frac{1}{C'}$$

Also, $V_2 = A' \left[\frac{D'}{C'} I_1 + \frac{1}{C'} I_2 \right] - B' I_1 = \left[\frac{A' D' - B' C'}{C'} \right] I_1 + \frac{A'}{C'} I_2$ Comparing with $V_2 = Z_{21} I_1 + Z_{22} I_2$ $Z_{21} = \left[\frac{A' D' - B' C'}{C'} \right]$

$$Z_{21} = \left[\frac{A'D' - B'C'}{C'}\right]$$
$$Z_{22} = \frac{A'}{C'}$$

d) Z-parameters in terms of Hybrid parameters:

We know that

$$V_1 = h_{11}I_1 + h_{12}V_2$$
$$I_2 = h_{21}I_1 + h_{22}V_2$$

Rewriting second equation,

$$\mathbf{V}_2 = -\frac{\mathbf{h}_{21}}{\mathbf{h}_{22}}\mathbf{I}_1 + \frac{1}{\mathbf{h}_{22}}\mathbf{I}_2$$

Comparing with

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$
$$Z_{21} = -\frac{h_{21}}{h_{22}}$$

$$Z_{22} = \frac{1}{h_{22}}$$

Also,

$$\begin{split} V_1 &= h_{11}I_1 + h_{12} \left[-\frac{h_{21}}{h_{22}}I_1 + \frac{1}{h_{22}}I_2 \right] \\ &= h_{11}I_1 + \frac{h_{12}}{h_{22}}I_2 - \frac{h_{12}h_{21}}{h_{22}}I_1 \\ &= \left[\frac{h_{11}h_{22} - h_{12}h_{21}}{h_{22}} \right] I_1 + \frac{h_{12}}{h_{22}}I_2 \end{split}$$

$$V_{1} = Z_{11}I_{1} + Z_{12}I_{2}$$
$$Z_{11} = \frac{h_{11}h_{22} - h_{12}h_{21}}{h_{22}} = \frac{\Delta h}{h_{22}}$$
$$Z_{12} = \frac{h_{12}}{h_{22}}$$

2. Y-parameters in terms of other parameters:

a) Y-parameters in terms of Z-parameters:

We known that

 $V_1 = Z_{11}I_1 + Z_{12}I_2$ $V_2 = Z_{21}I_1 + Z_{22}I_2$

By Cramer's rule,

$$I_{1} = \frac{\begin{vmatrix} V_{1} & Z_{12} \\ V_{2} & Z_{22} \end{vmatrix}}{\begin{vmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{vmatrix}}$$
$$= \frac{Z_{22}V_{1} - Z_{12}V_{2}}{Z_{11}Z_{22} - Z_{12}Z_{21}}$$
$$= \frac{Z_{22}}{\Delta Z}V_{1} - \frac{Z_{12}}{\Delta Z}V_{2}$$
$$\Delta Z = Z_{11}Z_{22} - Z_{12}Z_{21}$$

Where

Comparing with

 $I_1 = Y_{11}V_1 + Y_{12}V_2$ $Y_{11} = \frac{Z_{22}}{\Lambda 7}$ $Y_{12} = -\frac{Z_{12}}{\Lambda 7}$ Also, $I_2 = \frac{\begin{vmatrix} Z_{11} & V_1 \\ Z_{21} & V_2 \end{vmatrix}}{\sqrt{2}}$ $=\frac{Z_{11}V_2 - Z_{12}V_1}{\Lambda 7}$ $=-rac{Z_{21}}{\Lambda Z}V_{1}+rac{Z_{11}}{\Lambda Z}V_{2}$ $I_2 = Y_{21}V_1 + Y_{22}V_2$

Comparing with

$$Y_{21} = -\frac{Z_{21}}{\Delta Z}$$
$$Y_{22} = \frac{Z_{11}}{\Delta Z}$$

b) Y-parameters in terms of ABCD parameters:

We know that

$$V_{1} = AV_{2} - BI_{2}$$

$$I_{1} = CV_{2} - DI_{2}$$
Rewriting the first equation,

$$I_{2} = -\frac{1}{B}V_{1} + \frac{A}{B}V_{2}$$
Comparing with

$$I_{2} = Y_{21}V_{1} + Y_{22}V_{2}$$

$$Y_{21} = -\frac{1}{B}$$

$$Y_{22} = \frac{A}{B}$$
Also,

$$I_{1} = CV_{2} - D\left[-\frac{1}{B}V_{1} + \frac{A}{B}V_{2}\right]$$

$$= \frac{D}{B}V_{1} + \left[\frac{BC - AD}{B}\right]V_{2}$$

Comparing with

$$Y_{11} = \frac{D}{B}$$
$$Y_{12} = \frac{BC - AD}{B}$$

 $I_1 = Y_{11}V_1 + Y_{12}V_2$

c) Y-parameters in terms of A'B'C'D' parameters:

We know that $V_2 = A' V_1 - B' I_1$ $I_2 = C' V_1 - D' I_1$

Rewriting the first equation, $I_1 = \frac{A'}{B'}V_1 - \frac{1}{B'}V_2$

Comparing with $I_1 = Y_{11}V_1 + Y_{12}V_2$

$$Y_{11} = \frac{A'}{B'}$$
$$Y_{12} = -\frac{1}{B'}$$

Also, $I_2 = C'V_1 - D' \left[\frac{A'}{B'}V_1 - \frac{1}{B'}V_2\right]$

$$= -\left[\frac{A'D' - B'C'}{B'}\right]V_1 + \frac{D'}{B'}V_2$$

Comparing with

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{21} = -\frac{A'D' - B'C'}{B'}$$

 $Y_{22} = \frac{D'}{B'}$

d) Y-parameters in terms of Hybrid parameters:

We know that,

$$V_1 = h_{11}I_1 + h_{12}V_2 I_2 = h_{21}I_1 + h_{22}V_2$$

Rewriting the first equation,

$$I_1 = \frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2$$

Comparing with

$$I_{1} = Y_{11}V_{1} + Y_{12}V_{2}$$
$$Y_{11} = \frac{1}{h_{11}}$$
$$Y_{12} = -\frac{h_{12}}{h_{11}}$$

Also,
$$I_2 = h_{21} \left[\frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \right] + h_{22} V_2$$

$$= \frac{h_{21}}{h_{11}} V_1 + \left[\frac{h_{11}h_{22} - h_{12}h_{21}}{h_{11}} \right] V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{21} = \frac{h_{21}}{h_{11}}$$

$$Y_{22} = \frac{h_{11}h_{22} - h_{12}h_{21}}{h_{11}}$$

3. ABCD parameters in terms of other parameters:

a) ABCD parameters in terms of Z-parameters:

We know that

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

 $V_2 = Z_{21}I_1 + Z_{22}I_2$

Rewriting the second equation,

$$I_1 = \frac{1}{Z_{21}} V_2 - \frac{Z_{22}}{Z_{21}} I_2$$

 $Comparing \ with, \ \ I_1 = CV_2 - DI_2$

$$C = \frac{1}{Z_{21}}$$
$$D = \frac{Z_{22}}{Z_{21}}$$

1

Also,
$$V_1 = Z_{11} \left[\frac{1}{Z_{21}} V_2 - \frac{Z_{22}}{Z_{21}} I_2 \right] + Z_{12} I_2$$

$$= \frac{Z_{11}}{Z_{21}} V_2 - \frac{Z_{22} Z_{11}}{Z_{21}} I_2 + Z_{12} I_2$$
$$= \frac{Z_{11}}{Z_{21}} V_2 - \left[\frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{21}} \right] I_2$$

 $Comparing \ with, \ \ V_1 = AV_2 - BI_2$

$$A = \frac{Z_{11}}{Z_{21}}$$

$$B = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}}$$

b) ABCD parameters in terms of Y-parameters:

We know that

$$I_1 = Y_{11}V_1 + Y_{12}V_2 I_2 = Y_{21}V_1 + Y_{22}V_2$$

Rewriting the second equation,

$$V_1 = -\frac{Y_{22}}{Y_{21}}V_2 + \frac{1}{Y_{21}}I_2$$

Comparing with

 $V_1 = AV_2 - BI_2$

$$\mathbf{A} = -\frac{\mathbf{Y}_{22}}{\mathbf{Y}_{21}}$$

$$B = -\frac{1}{Y_{21}}$$

Also, $I_1 = Y_{11} \left[-\frac{Y_{22}}{Y_{21}} V_2 + \frac{1}{Y_{21}} I_2 \right] + Y_{12} V_2$
$$= \left[\frac{Y_{12} Y_{21} - Y_{11} Y_{22}}{Y_{21}} \right] V_2 + \frac{Y_{11}}{Y_{21}} I_2$$

, $I_1 = CV_2 - DI_2$

Comparing with,

$$\begin{split} C = \left[\frac{Y_{12}Y_{21} - Y_{11}Y_{22}}{Y_{21}} \right] = -\frac{\Delta Y}{Y_{21}} \\ D = -\frac{Y_{11}}{Y_{21}} \end{split}$$

c) ABCD parameters in terms of hybrid parameters:

We know that,	$V_1 = h_{11}I_1 + h_{12}V_2$
	$I_2 = h_{21}I_1 + h_{22}V_2$

Rewriting the second equation, $I_1=-\frac{h_{22}}{h_{21}}V_2+\frac{1}{h_{21}}I_2$

Comparing with,
$$I_1 = CV_2 - DI_2$$

 $C = -\frac{h_{22}}{h_{21}}$
 $D = -\frac{1}{h_{21}}$
Also, $V_1 = h_{11} \left[\frac{1}{h_{21}} I_2 - \frac{h_{22}}{h_{21}} V_2 \right] + h_{12} V_2$
 $\left[h_{12} h_{21} - h_{11} h_{22} \right] V_1 = h_{11}$

$$= \left[\frac{h_{12}h_{21} - h_{11}h_{22}}{h_{21}}\right]V_2 + \frac{h_{11}}{h_{21}}I_2$$

 $Comparing with \qquad \qquad V_1 = AV_2 - BI_2$

$$A = \frac{h_{12}h_{21} - h_{11}h_{22}}{h_{21}}$$
$$B = -\frac{h_{11}}{h_{21}}$$

4. Hybrid parameters in terms of other parameters:

a) Hybrid parameters in terms of Z-parameters:

We know that
$$\begin{array}{ll} V_1 = Z_{11}I_1 + Z_{12}I_2 \\ V_2 = Z_{21}I_1 + Z_{22}I_2 \end{array}$$

Rewriting the second equation, $I_2 = -\frac{Z_{21}}{Z_{22}}I_1 + \frac{1}{Z_{22}}V_2$

Comparing with

$$I_2 = h_{21}I_1 + h_{22}V_2$$

 $h_{21} = -\frac{Z_{21}}{Z_{22}}$
 $h_{22} = \frac{1}{Z_{22}}$

Also,
$$V_1 = Z_{11}I_1 + Z_{12}\left[-\frac{Z_{21}}{Z_{22}}I_1 + \frac{1}{Z_{22}}V_2\right]$$

= $\left[\frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{22}}\right]I_1 + \frac{Z_{12}}{Z_{22}}V_2$

Comparing with

$$\begin{split} V_1 &= h_{11}I_1 + h_{12}V_2 \\ h_{11} &= \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{22}} = \frac{\Delta Z}{Z_{22}} \\ h_{12} &= \frac{Z_{12}}{Z_{22}} \end{split}$$

b) Hybrid parameters in terms of Y-parameters:

We know that

$$I_1 = Y_{11}V_1 + Y_{12}V_2 I_2 = Y_{21}V_1 + Y_{22}V_2$$

Rewriting the first equation, $V_1 = \frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2$

Comparing with
$$V_{1} = h_{11}I_{1} + h_{12}V_{2}$$

$$h_{11} = \frac{1}{Y_{11}}$$

$$h_{12} = -\frac{Y_{12}}{Y_{11}}$$

Also,
$$I_2 = Y_{21} \left[\frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2 \right] + Y_{22} V_2$$

$$= \left[\frac{Y_{11} Y_{22} - Y_{12} Y_{21}}{Y_{11}} \right] V_2 + \frac{Y_{21}}{Y_{11}} I_1$$

h $I_2 = h_{21} I_1 + h_{22} V_2$

Comparing with

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$h_{22} = \frac{Y_{11}Y_{22} - Y_{12}Y_{21}}{Y_{11}} = \frac{\Delta Y}{Y_{11}}$$
$$h_{21} = \frac{Y_{21}}{Y_{11}}$$

c) Hybrid parameters in terms of ABCD parameters:

 $\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$ We know that

Rewriting the second equation,	$\mathbf{I}_2 = -\frac{1}{D}\mathbf{I}_1 + \frac{C}{D}\mathbf{V}_2$
--------------------------------	---

 $I_2 = h_{21}I_1 + h_{22}V_2$ $h_{21} = -\frac{1}{D}$ $h_{22} = \frac{C}{D}$ Comparing with Also, $V_1 = AV_2 - B\left[-\frac{1}{D}I_1 + \frac{C}{D}V_2\right]$ $=\frac{B}{D}I_1 + \left[\frac{AD - BC}{D}\right]V_2$

with
$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$h_{11} = \frac{B}{D}$$
$$h_{12} = \frac{AD - BC}{D} = \frac{\Delta T}{D}$$

Comparing

Inter-relationship between parameters:

	Z	У	Т	h
¢	$\left[\begin{array}{cc} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{array}\right]$	$\left[\begin{array}{cc} \frac{y_{22}}{\Delta y} & \frac{-y_{12}}{\Delta y} \\ \frac{-y_{21}}{\Delta y} & \frac{y_{11}}{\Delta y} \end{array}\right]$	$ \begin{bmatrix} \frac{A}{C} & \frac{\Delta T}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix} $	$\left[\begin{array}{cc} \frac{\Delta h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ \frac{-h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{array}\right]$
ē.	$\left[\begin{array}{ccc} \frac{z_{22}}{\Delta z} & \frac{-z_{12}}{\Delta z} \\ \frac{-z_{21}}{\Delta z} & \frac{z_{11}}{\Delta z} \end{array}\right]$	$\left[\begin{array}{cc} \mathbf{y}_{11} & \mathbf{y}_{12} \\ \\ \mathbf{y}_{21} & \mathbf{y}_{22} \end{array}\right]$	$\left[\begin{array}{cc} \frac{\mathbf{D}}{\mathbf{B}} & \frac{-\Delta \mathbf{T}}{\mathbf{B}} \\ \frac{-1}{\mathbf{B}} & \frac{\mathbf{A}}{\mathbf{B}} \end{array}\right]$	$\left[\begin{array}{ccc} \frac{1}{h_{11}} & \frac{-h_{22}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{\Delta h}{h_{11}} \end{array}\right]$
ſ	$\left[\begin{array}{cc} \frac{\mathbf{z}_{11}}{\mathbf{z}_{21}} & \frac{\Delta \mathbf{z}}{\mathbf{z}_{21}} \\ \frac{1}{\mathbf{z}_{21}} & \frac{\mathbf{z}_{22}}{\mathbf{z}_{21}} \end{array}\right]$	$\left[\begin{array}{ccc} \frac{-\mathbf{y}_{22}}{\mathbf{y}_{21}} & \frac{-1}{\mathbf{y}_{21}} \\ \frac{-\Delta \mathbf{y}}{\mathbf{y}_{21}} & \frac{-\mathbf{y}_{11}}{\mathbf{y}_{21}} \end{array}\right]$	$\left[\begin{array}{cc} A & B \\ C & D \end{array}\right]$	$\left[\begin{array}{cc} \frac{-\Delta h}{h_{21}} & \frac{-h_{11}}{h_{21}} \\ \frac{-h_{22}}{h_{21}} & \frac{-1}{h_{21}} \end{array}\right.$
ı	$\begin{bmatrix} \frac{\Delta \mathbf{z}}{\mathbf{z}_{22}} & \frac{\mathbf{z}_{12}}{\mathbf{z}_{22}} \\ \frac{-\mathbf{z}_{21}}{\mathbf{z}_{22}} & \frac{1}{\mathbf{z}_{22}} \end{bmatrix}$	$\left[\begin{array}{cc} \frac{1}{\mathbf{y}_{11}} & \frac{-\mathbf{y}_{12}}{\mathbf{y}_{11}} \\ \frac{\mathbf{y}_{21}}{\mathbf{y}_{11}} & \frac{\Delta \mathbf{y}}{\mathbf{y}_{11}} \end{array}\right]$	$\left[\begin{array}{cc} \frac{B}{D} & \frac{\Delta T}{D} \\ -\frac{1}{D} & \frac{C}{D} \end{array} \right]$	$\left[\begin{array}{cc} \mathbf{h}_{11} & \mathbf{h}_{12} \\ \\ \mathbf{h}_{21} & \mathbf{h}_{22} \end{array} \right]$

Interconnection of two-port networks:


Interconnection of two-port networks, namely, cascade, parallel, seriesparallel and parallel-series are discussed below and the relation between the input and output quantities of the combined two-port networks is derived.

Cascade Connection:

Transmission Parameter Representation:

Figure: 6.8.1 shows two-port networks connected in cascade. In the cascade connection, the output port of the first network becomes the input port of the second network. Since it is assumed that input and output currents are positive when they enter the network, we have

$$I_{1}^{'} = -I_{2}$$

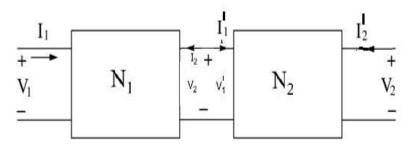

Cascade Connection

Let A_1, B_1, C_1, D_1 be the transmission parameters of the network N_1 and A_2, B_2, C_2, D_2 be the transmission parameters of the network N_2 .

For the network N_1 ,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 B_1 \\ C_1 D_1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$
(i)

For the network N_2 ,

$$\begin{bmatrix} V_1'\\ I_1' \end{bmatrix} = \begin{bmatrix} A_2 B_2\\ C_2 D_2 \end{bmatrix} \begin{bmatrix} V_2'\\ -I_2' \end{bmatrix}$$

Since $V_1^{'} = V_2$ and $I_2^{'} = -I_2$, we can write

$$\begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = \begin{bmatrix} A_2 B_2 \\ C_2 D_2 \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix}$$
(ii)

Combining equations (i) and (ii),


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 B_1 \\ C_1 D_1 \end{bmatrix} \begin{bmatrix} A_2 B_2 \\ C_2 D_2 \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix} = \begin{bmatrix} AB \\ CD \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix}$$

Hence,
$$\begin{bmatrix} AB\\CD \end{bmatrix} = \begin{bmatrix} A_1B_1\\C_1D_1 \end{bmatrix} \begin{bmatrix} A_2B_2\\C_2D_2 \end{bmatrix}$$
 (iii)

Equation (iii) shows that the resultant *ABCD* matrix of the cascade connection is the product of the individual *ABCD* matrices.

Parallel Connection:

Figure: 6.8.2 shows two-port networks connected in parallel. In the parallel connection, the two networks have the same input voltages and the same output voltages.

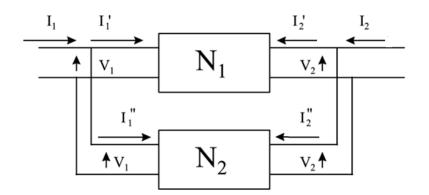

Parallel Connection

Let $Y_{11}, Y_{12}, Y_{21}, Y_{22}$ be the Y-parameters of the network N_1 and $Y_{11}, Y_{12}, Y_{21}, Y_{22}$ be the Y-parameters of the network N_2 .

For the network N_1 , $\begin{bmatrix} I_1'\\I_2'\end{bmatrix} = \begin{bmatrix} Y_{11}'Y_{12}'\\Y_{21}'Y_{22}'\end{bmatrix} \begin{bmatrix} V_1\\V_2\end{bmatrix}$

For the network N_2 , $\begin{bmatrix} I_1^{"} \\ I_2^{"} \end{bmatrix} = \begin{bmatrix} Y_{11}^{"} Y_{12}^{"} \\ Y_{21}^{"} Y_{22}^{"} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$


For the combined network, $I_1 = I_1^{'} + I_1^{''}$ and $I_2 = I_2^{'} + I_2^{''}$

Hence,
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_1^{'} + I_1^{''} \\ I_2^{'} + I_2^{''} \end{bmatrix} = \begin{bmatrix} Y_{11}^{'} + Y_{11}^{''}Y_{12}^{'} + Y_{12}^{''} \\ Y_{21}^{'} + Y_{21}^{''}Y_{22}^{'} + Y_{22}^{''} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Y_{11}Y_{12} \\ Y_{21}Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Thus, the resultant Y-parameter matrix for parallel connected networks is the sum of Y matrices of each individual two-port networks.

Series Connection:

Figure: 6.8.3 shows two-port networks connected in series. In a series connection, both the networks carry the same input current. Their output currents are also equal.

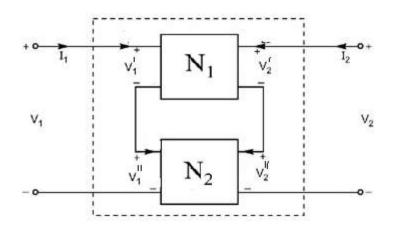

Series Connection

Let $Z_{11}, Z_{12}, Z_{21}, Z_{22}$ be the Z-parameters of the network N_1 and $Z_{11}, Z_{12}, Z_{21}, Z_{22}$ be the Y-parameters of the network N_2 .

For the network N_1 , $\begin{bmatrix} V_1'\\V_2' \end{bmatrix} = \begin{bmatrix} Z_{11}'Z_{12}'\\Z_{21}'Z_{22}' \end{bmatrix} \begin{bmatrix} I_1\\I_2 \end{bmatrix}$ For the network N_2 , $\begin{bmatrix} V_1'\\V_2'' \end{bmatrix} = \begin{bmatrix} Z_{11}'Z_{12}'\\Z_{21}'Z_{22}'' \end{bmatrix} \begin{bmatrix} I_1\\I_2 \end{bmatrix}$

For the combined network $V_1 = V_1^{'} + V_1^{''}$ and $V_2 = V_2^{'} + V_2^{''}$

Hence,
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_1^{'} + V_1^{''} \\ V_2^{'} + V_2^{''} \end{bmatrix} = \begin{bmatrix} Z_{11}^{'} + Z_{11}^{''} Z_{12}^{'} + Z_{12}^{''} \\ Z_{21}^{'} + Z_{21}^{''} Z_{22}^{'} + Z_{22}^{''} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Z_{11} Z_{12} \\ Z_{21} Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Thus, the ersultant Z-parameters matrix for the series-connected networks is the sum of Z matrices of each individual two-port network.

UNIT-V


ANALYSIS OF THREE PHASE CIRCUITS

In an ac kystim it is possible to connect two or more number of individual circuite to a Common polyphase Source. Though it is possible to have any number of phases sources in a polyphase system, the increase in available power is not significant beyond the three phase system. The power generated by the same machine increases 41.4 parcent from single phase to two phase and increase in the power is 50 per cent from single phase to three Phase . Beyond three phase, to the masumum possible increase is only seven percent, but the complications are many. So an increase beyond three phase does not justify the extra Complications. In view of this, it is only in exceptional Cases where more than these phases are used. Circuits supplied by six, twelve and more phases are used in high power radio transmitter statione. Two phase systems are used to supply two phase servo motors in feedback control systems.

Scanned by CamScanner

51

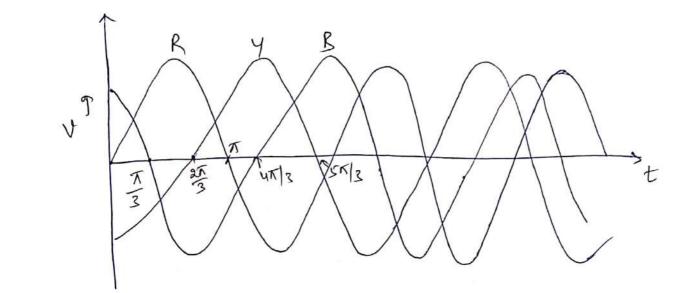In general, a three phase system of voltages (merente) is merely a combination of three single phase systeme of vollager (merente) of which the three voltages (merente) differ in phase by 120 electrical degrees from each other in a particular requence. One such three phase system of sinusoidal voltages is shown in figure below.



Advantages of a Three Phase System :-

1. The power in a single phase Circuit is pulsaling. When the power factor of the circuit is unity, the power becomes zero 100 times in a SOHZ Supply. Therefore, single phase motors have a pulsaling torque. Although power supplied by each phase is pulsaling, the total power (there phase) supplied to a balanced S-d circuit is constant at every instant of time. Because of this there phase motors have an abcolutely uniform torque. 2. TO transmit a given amount of power over a given length a 3-of transmit a given amount of power over a given length a 3-of transmit a given amount of power over a given length a 3-of transmitsion circuit requires less conductor material than single phase circuit. 3. In a given frame size a three phase motor of 3-pgenerated

4. Three phase motors are more easily started than single phase motors. Single phase motors are not self starting whereas 3-\$ motors are

5. operating characteristics of S-& motors (apparatus) are superior than those of a similar 1-& apparatus.

6. All 3-& machines are superior in performance. Their control equipments are smaller, cheaper, Lighter in weight and more efficient Generation of Three Phase Voltages:-

Three phase voltages can be generated in a stationary armature with a rotating field structure, or in a rotating armature with a stationary field as shown in fight(a) & 1.3(6)



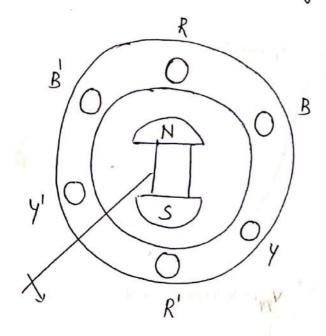


Fig1.3(a) Stationary Armature

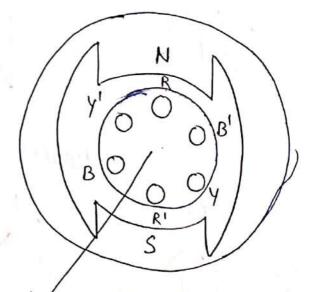


Figi3(b) Stationary field

Stople phase voltages and entroll and generaled by single phase generators as shown in lighters the monothis Cheer a Matining annations) of such an generater has any one uncerting at one of of calls 30 a live phase generator the annualises have live distinct wherehings an dive sele of calls that an displaced ne contributed dispanses apart so that the generaled vallages to the hear phases have all phase displacement as shown in fight () - Similarly there phase setting a me generated to three repeals but Rentical rete of whedings of coll that are displaced by no electrical digrees in the manufuse to that The voltages generated to them are tool apart to those please This recongement is shown to fighter) there the conditation one cail (R-phase); YY' another Call (Y-phase), and BR' Constitute the that Phase (B. Phase). The field magnets' are assumed in electronics relation,

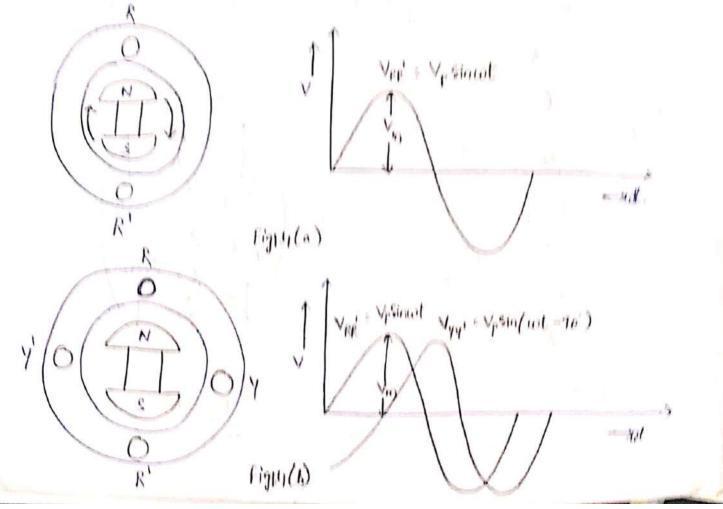

Scanned by CamScanner

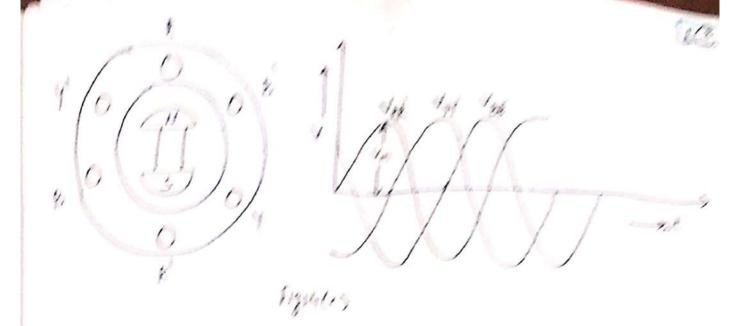


the utboyse greated by a term phase altorates is shown in highle) the three vellages are of some magnitude and frequency, but are eligitated from one another by soci-becoming the vellage so he derivated to be can cost the equations for the tradactorerow Value of the vellages of the true phases. Counting the time from the instant: when the vellage in phase & 2000. The equations are

> $V_{pp} = V_p \text{such}$ $V_{pp} = V_p \text{such}(wt - 126)$ $V_{pp} = V_p \text{such}(wt - 246)$


Let us consider the Y-connected vollages in Figures) for more the vollager Van, Vyn and Van are supportingly believe lines R.Y.8 and resultat line in the vollages are called <u>Phare Vollages</u>. If the vollage source have the same amplitude and perpused to and are of out of phase with cash other by 120, the vollage are baid to be <u>balanced</u>. This implies


 $V_{RD} + V_{RD} + V_{HD} = 0$ $|V_{i..}| = |V_{RD}| = |V_{iD}|$

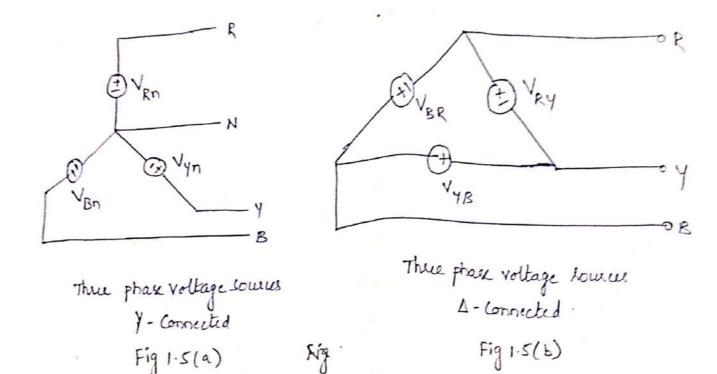Balanced phase voltages are equal in magnitude and are out of phase with each other by 120 ***



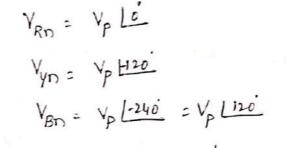Since the three phase voltages are 120 out of phase with each other, there are two possible combinations. One possibility is shown in fig1.6(a) and expressed mathematically as



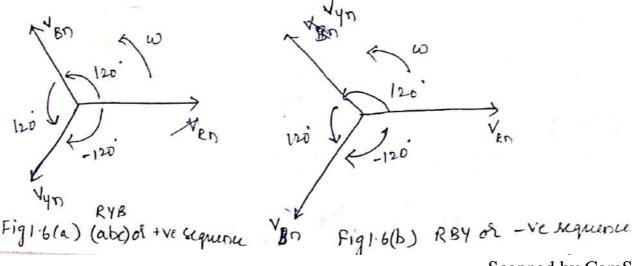

 $V_{Rn} = V_p Lo$ $V_{yn} = V_p \frac{L^{120}}{L^{240}}$ $V_{Bn} = V_p \frac{L^{-240}}{L^{240}} = V_p \frac{L^{130}}{L^{130}}$

where V_p is the effective of rms value of phase Voltages. This is known as RYB sequence of positive sequence. In this phase sequence V_{Rn} leads V_{Yn} which inturn leads V_{Bn} . This sequence is produced when the voltar in fig 1.3(b) rotates counter clockwise. The other possibility is shown in fig 1.6(b). and is given by

$$V_{RD} = V_{p} L^{0}$$

$$V_{BD} = V_{p} \frac{L^{-1>0}}{L^{-240}}$$

$$V_{yD} = V_{p} \frac{L^{-240}}{L^{-240}} = V_{p} \frac{L^{+1>0}}{L^{+1>0}}$$

This is called RBY sequence or negative sequence. For this phase sequence, V_{RD} leads V_{BD} which in turn leads V_{YD}. The RBY sequence is produced when the rolog in fig 1.3(b) rolates in the clockwise direction.

14* The phase sequence is the time order in which the voltages Pass through their respective maximum Values.

In fig 1.6(a) as the phasoes votate in Counterclockwise votation with frequery w, they pass through the horizontal axis in a sequence RYBRYBR...... Thus the sequence is RYIB & YBR or BRY. Similarly for the phasoes in fig 1.6(b) as they notate in counterclock wise direction they pass the horizontal axis in a sequence


Scanned by CamScanner

5.4

RBYRBYR..... This describes RBY sequence. It determines the direction of rotation of a motor connected to the power source for example.


Like the generator connections, a three phase load can be either Y-connected or delta connected depending on the end applications. Fig 1.7(a) shows Y-connected load, fig 1.7(b) shows A-connected load . The mentual line ing fig 1.7(a) may or maynot be these depending on whether the system is 4-coire of 3-wire.

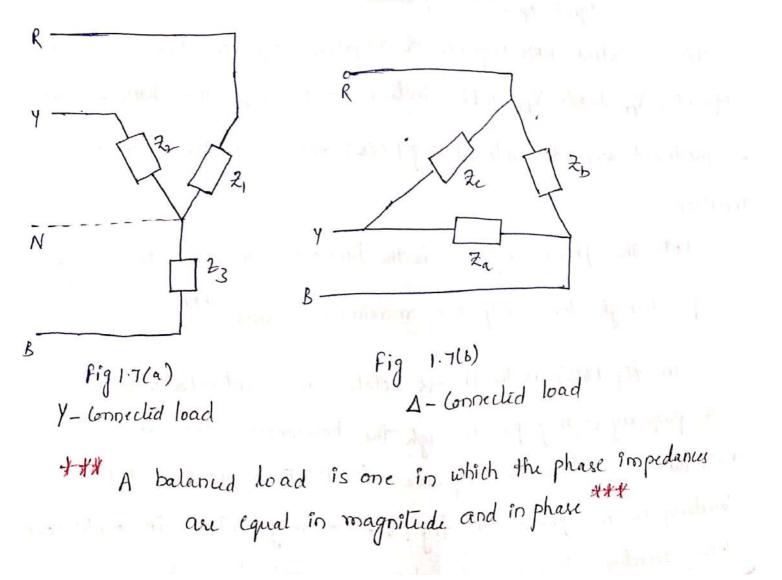
The phase impedances are not loyal in magnitude of phase



155 For a balanced Y- Connected load $R_1 = R_2 = 23 = 2y$ Zy is the load impedance per phose. For a balanced A-connected lood $z_a = z_b = z_c = z_\Delta$ where Zo is the load impedance per phase. Since both three phase source and three phase load can be either Y & A connected, we have four possible connections * Y-Y (Y-Connected bousce with Y-connected load) + Y-A connection * A-A Connection A-Y Connection ¥ Star to delta and delta to Star Transformation :while dealing with currents and voltages in loads, it is often necessary to convert a star load to delta load and Vice versa. we know that A connection of resistances can be replaced by an equivalent Y connection and vice versa. Similar methods can be applied in case of networks containing general impedances in complex form. So also with

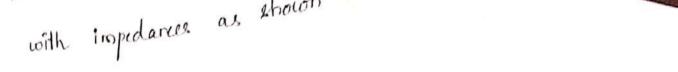Al where some formulae hold good except the resistance are reeplaced by the impedance. Thus considering fig 1.8(a) star load can be replaced by an equivalent delt load



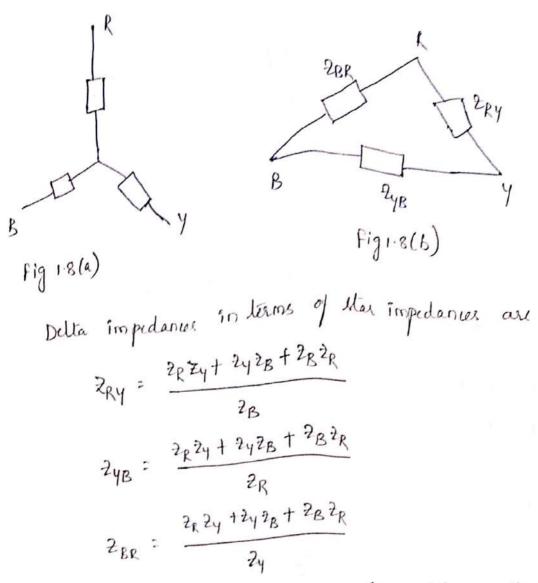

The converted network is shown in fig 1.8(6). Similarly we can replace the della load of Fig 1.8(6) by an equivalent star load with branch impedances as

$$Z_{R} = \frac{2_{RY} 2_{BR}}{2_{RY} + 2_{YB} + 2_{BR}}$$

$$Z_{Y} = \frac{2_{RY} 2_{YB}}{2_{RY} + 2_{YB} + 2_{BR}}$$

$$Z_{RY} + 2_{YB} + 2_{BR}$$

$$Z_{B} = \frac{2_{RY} 2_{YB}}{2_{RY} + 2_{YB} + 2_{BR}}$$


$$Z_{B} = \frac{2_{RY} 2_{YB}}{2_{RY} + 2_{YB} + 2_{BR}}$$
It should be noted that all impedances are to

e to be expressed in their complex form.

If three phase load is balances then the Conversion formulae get simplified. Consider a balanced Y-connected load having an impedance Z, in each phase and let the equivalent della Connected load have an impedance of Z_ in each phase as shown in Fig 1.9(b)

Applying conversion formulae della impedances interme of star impedances, we have

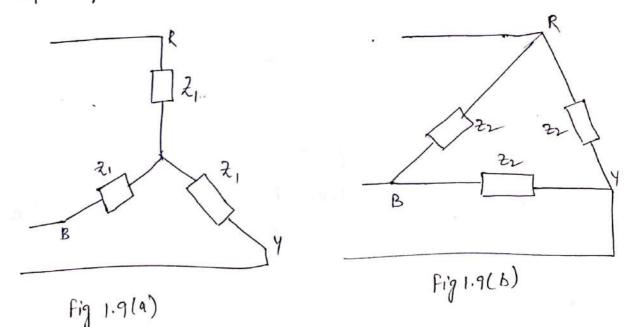 $Z_2 = 3 Z_1$, Similarly we can express star impedance in terms of della $Z_1 = \frac{Z_2}{3}$



Voltage, current and power in a Star Connected System:-Star Connected System:-Fig 1.10 shows a balanced three phase Y-connected system.

The voltage induced in each winding is called the phase

Voltage (Vpn). Likewise V_{RN}, VyN and V_{BN} represent the rms Values of the induced voltages in each phase the voltage available between any pair of terminals is called the line voltage (VL) Likewise V_{RY}, VyB and V_{BR} are known as <u>Line Voltages</u>. The double subscript notation is purposefully used to represent voltages and currents in polyphase circuits. Thus V_{RY} indicates the voltage N between points R and Y with R being positive with supped to point Y during its positive half cycle.

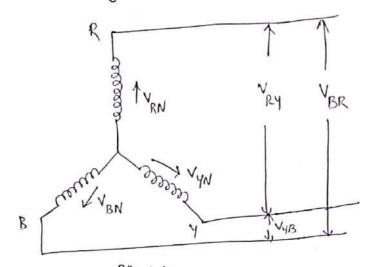


Fig 1.10 Similarly VyB means that Y is positive with respect to point B during its positive half cycle, it also means that $V_{RY} = -V_{YR}$.

Vollage Relation:-

The phasoes corresponding to the phase voltages constituting a three phase system can be represented by a Phasoe diagram as shown in fig 1.11

5.4-1

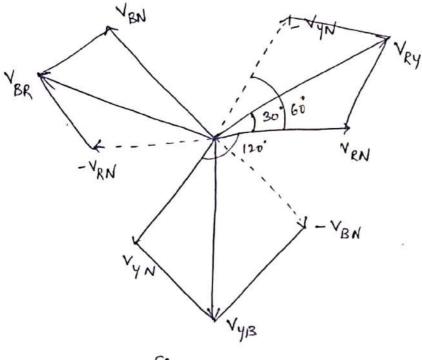


Fig 1.11

From fig 1.11 considering the lines R, Y, B, the line voltages V_{RY} is equal to phason sum of V_{RN} and V_{NY} which is also Phason difference of V_{RN} and V_{YN} ($V_{NY} = -V_{YN}$). Hence V_{RY} is found by compounding V_{RN} and V_{YN} reversed. To subtract V_{YN} from V_{RN} , we serverse the phason V_{YN} and find its phason sum with V_{RN} as shown in fig. The two phasons V_{RN} and $-V_{YN}$ ase equal in length and are Go" apart. $|V_{RN}| = -|V_{YN}| = V_{Ph}$ $V_{RY} = \sqrt{V_{RN}^2 + V_{YN}^2} + 2V_{RN}V_{YN}\cos 60^\circ$ $= \sqrt{V_{PD}^2 + V_{Ph}^2 + 2V_{RN}V_{YN}\cos 60^\circ}$

V= V3Vph

Similarly $V_{YB} = \int_{3} V_{Ph}$, $V_{BR} = \sqrt{3} V_{Ph}$

Hence in a balanced star Connected system

(i) Line Vollage = $\sqrt{3}$ times phase Vollage $V_L = \sqrt{3} V_{ph}$

(ii) All line voltages are equal in magnitude and are displaced by 120

(iii) All line voltages are 30 ahead of their respective phase voltages.

Current Relations :-

from fig 1.12(a) shows a balanced three phase, Y-connected system indicating phase currents and line currents. The arrows Placed alongside the currents, IR, Iy and IB flowing in three Phases producate the directions of currents when they are assumed to be positive and not the directions at that particular instant. The phason diagram for phase currents with respect to their Phase Voltages is shown in fig 1.12(6). All the phase currente are displaced by 120° with respect to each other, '\$' is phase angle between phase voltage and phase current-(lagging load is assumed). For a balanced load, all the phase currents are equal in magnitude. It can be observed from fig 1.12(a) that each line conductor is connected in series with its individual phase winding. Therefore the current in a line conductor is same as that in the phase to which the line conductor is connected.

 $J_{L} = J_{Ph} = J_{R} = J_{Y} = \underline{J}_{B}$

It can be observed that from fig 1.12(b) the angle between the line (Phase) current and the corresponding line voltage is $(30 + p)^\circ$ for lagging load. Consequently if the load is leading then the angle between the line (Phase) current and corresponding line voltage will be $(30 - p)^\circ$

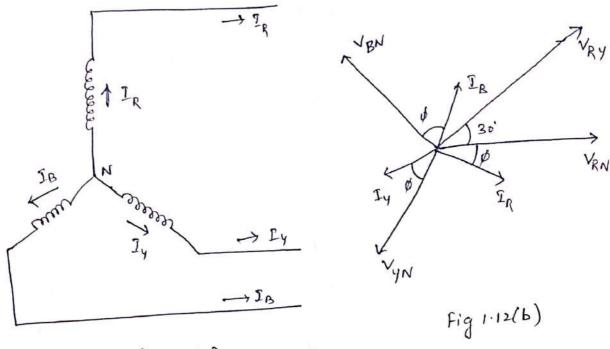


Fig 1.12(a)


Power in the Star Connected Network :-The total active power or true power in the three phase load is the sum of the powers in the three phases. For a balanced load, power in each phase is same, hence total power = 3× power in each phase P= 3× Vph × Iph Cord


Scanned by CamScanner

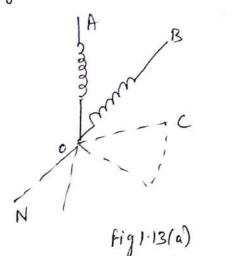5.8


It is usual practice to express the three phase power interms of line quantities as follows. $V_L = \sqrt{3} V_{ph}$ $I_L = I_{ph}$ $P = \sqrt{3} V_L I_L \cos\phi$ Int or active power Total reactive power is given by $Q = \sqrt{3} V_L I_L \sin\phi$ VAR Total apparent power or Volt-ampaces $= \sqrt{3} V_L I_L$ VA

N. Phase Star System: It is to be noted that star and mesh are general turns applicable to any no-of phases, but wye and delta are special cases of Y and mesh when the system is a three phase system cases of Y and mesh when the system with two adjacent consider an n-phase balanced star system with two adjacent phases as known in fig 1:12 (a). Its vector diagram is shown in fig 1:13(b)



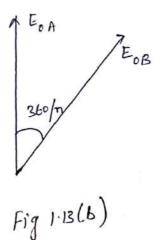

The angle of phase difference between adjacent phase. The Voltages is $360^{\circ}/m$. Let Eph be the voltage of each phase. The line Vollage i.e., the Voltage between A and B is equal to $\lim_{R \to S} = E_{L} = E_{RO} + E_{OIS}$. The vector addition is shown in fig. 13(c) $E_{RIS} = E_{L} = E_{RO} + E_{OIS}$. The vector addition is shown in fig. 13(c) It is evident that line current and phase current are same

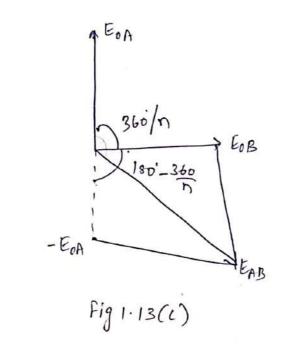


EAB = EAO + EOB

Ĩ

$$\begin{split} \mathbf{E}_{AB} &= \sqrt{E_{oB}} + E_{oA} + 2E_{oA} E_{oB} (ds(180^{-360} - 1)) \\ &= \sqrt{E_{ph}} + E_{ph} \cdot \frac{1}{2} 2E_{ph} (ds(360^{-}/n)) = \sqrt{E_{ph}} + E_{ph} - 2E_{ph} \cdot (ds(2\times 180^{-})) \\ &= \sqrt{E_{ph}} + E_{ph} - 2E_{ph} \cdot (ds(360^{-}/n)) = \sqrt{2E_{ph}} - 2E_{ph} \cdot (ds(2\times 180^{-})) \\ &= \sqrt{2E_{ph}} \cdot \frac{1}{1} - (ds(2\times 180^{-})) = \sqrt{2E_{ph}} \times \sqrt{2E_{ph}} \cdot \frac{1}{2} \frac{1}{2} \frac{1}{1} \frac{1}{2} \frac{1}{1} \frac{1}{2} \frac{1}{2} \frac{1}{1} \frac{1}{2} \frac{1}{2} \frac{1}{1} \frac{1}{2} \frac$$

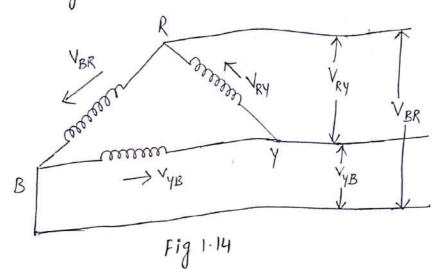Voltage, Current and Power in a Vella Connected System:-Della Connected System:-Fig 1.14 shows a balanced three phase, three-wise della Connected system. This assangement is refused to as mesh connection because it forme a closed circuit. It is also known a delta connection because the three branches in the circuit can also be assanged in the form of delta (D)



From the manner of interconnection of three phases in the Circuit, it may appear that the three phases are short circuite among themselves. However this is not the Case. Since the system is balanced, the sum of the three Voltages round the closed mesh is zero; consequently no current can flow around the mesh when the desiminals are open.

The carous placed along side the voltages, VRY, VyB & VBR of the three phases indicate that the terminals R, Y & B are positive with respect to Y, B and R respectively during their respective to the scanned by CamScanner

15.10 from tig 1.15 we notice that only one phase is connected Vollage Relation :between any two lines. Hence the voltage between any two lines (VL) is equal to the phase voltage (Vph) VRY = VL = Vph 120 120 120 120 VyB Fig 1.15 Since the system is balanced, all the phase voltages are equal but displaced by 120 from one another as shown in phase diagram of fig 115. The phase sequence RYB is assum $|V_{RY}| = |V_{YI3}| = |V_{BR}| = V_L = V_{ph}$

Current Relation: In Fig 1.16(a) since the system is balanced, the three phose currents (Iph) i.e., I_{RY} , I_{YB} , I_{IZR} are equal in magnitude but are displaced by 120° from one another as shown in fig 1.16(b) · I_R , I_Y and I_B are line currents (I_L) i.e., I_R is the line current in line connected to the common point R · Similarly I_Y and I_{IZ} are the line currents in lines Y and B connected to common points Y 4B Scanned by CamScanner respectively. Though here all live currents are directed outwards at no instant will all the line currente flow in the same direction either outward of provards. Because the three line currents are displaced 120° from one another, when one is possitive, the other two might both be negative of one positive and one negative. Also it is to be noted that associes placed alongside Phase aurents in fig 1.16(a) indicate the direction of aurente when they are assumed to be positive and not their actual direction at a particular instant. We can easily determine the line currents in fig 1.16 (a), JR, Jy & JB by applying KCL at the three terminals R, Y and B respectively. Thus the current in line P, IR = IRY-IBR i, e, current in any line is equal to the phasor difference of currents in the two phases attached to that line. Stroilarly the current in line Y, Iy = IYB-IRY and the current in line B, IB = IBR-IYB The phason addition of these currents is shown in fig 1.16(b).

from the figure

$$I_{R} = I_{RY} - I_{BR}$$

$$I_{R} = \sqrt{I_{RY}^{2} + I_{BR}^{2} + 2I_{RY} I_{BR}^{2}} (os 60)$$

 $I_R = \sqrt{3} I_{ph}$ since $I_R = I_B = I_{ph}$

Similarly the remaining two lines currents, Iy and IB are also equal to $\sqrt{3}$ times phase currents $I_L = \sqrt{3}$ Iph

As can be seen from fig1.16(b) all line currents are equal in mognitude but displaced by 120° from one another and line currents

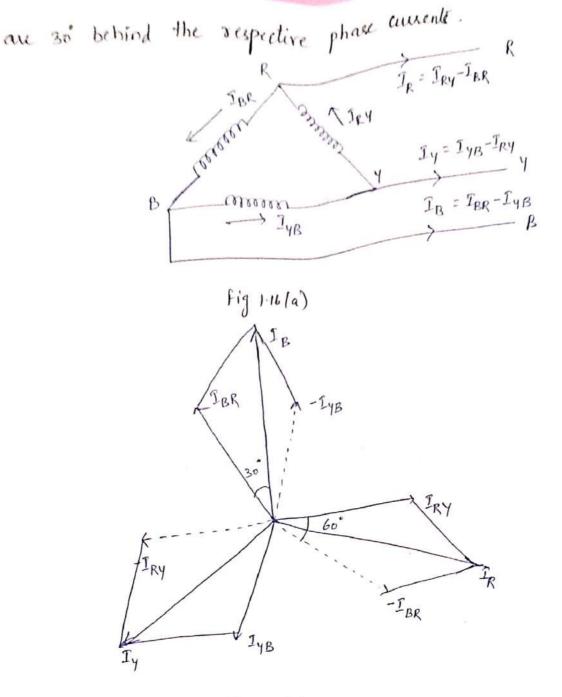


Fig 1.16(b)

Power in the Della Connected System:obviously total power in the delta circuit is the sum of the powers in the three phases. Since the load is balanced, the power consumed in each phase is the same. Total power the power consumed in each phase is the same. Total power is equal to three times the power in each phase.

Power per phase = Vpn Iph los\$ where of is the phase angle between phase vollage and phase current.

Scanned by CamScanner

511

Total power P = 3 x Vph Iph Cosof In terms of line quantities P= V3 VLIL COSØ W and $V_{Ph} = V_L \in I$ $I_{Ph} = \frac{I_L}{V_P}$ For a balanced system, whether star of delta, the expression for total power is the same. N Phase Mesh System:-Fig 1.17(a) shows part of n-phase balanced mesh system. Its vector diagram 15 shown in fig 1.17(b) 360/m EBC Fig 1.17 (b) Fig 1.17/a)

Let the current in line BB' be I_L . This is same in all the remaining lines of the nphase system. I_{AB} , I_{BC} are the phase current in AB and BC phases respectively. The vector addition of the line current is shown in Fig 1.17(c). It is evident from fig 1.17(b) that the line G phase voltages are equal.

$$\int_{L_{B}} \int_{L_{B}} \int_{L$$


The above equation is a general equation for the une cure in a balanced mphase mech system.

Analysis of Balanced Three Phase Circuits:-Balanced Three Phase System Delta Load:-

Fig 1.18 (a) shows a three phase, three wire, balanced system supplying procer to a balanced three phase delta load The phase sequence is RYB.

Let us assume the line voltage VRY = VLO' as the reference Phase. Then the three source voltages are given by

Thus voltages are represented by phasons in fig 1.18(6). Since the load is delta connected, the line voltage of the source is equal to the phase angle voltage of the load. The current in phase RY, I_R will lag(dead) behind (ahead of) the phase Voltage V_{RY} by an angle ϕ as directed by the nature of the load impedance. The angle of lag of I_Y with respect to V_{PR} as well as the angle of lag of I_R will be as well as the angle of lag of I_R with respect to V_{PR} in the load is balanced. All these quantities are represe in fig 1.18(b)

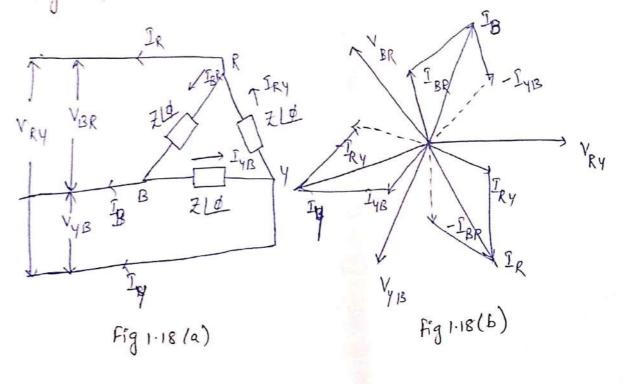

If the load impedance is ZLD, the current flowing in the

three load impedances are then


$$\begin{split} \overline{I}_{RY} &= \frac{V_{RY} [o']}{Z [\phi]} = \frac{V}{2} \frac{1-\phi}{2} \\ J_{YB} &= \frac{V_{YB} [-ho]}{Z [\phi]} = \frac{V}{2} \frac{1-ho}{2} \frac{1-ho$$

The line currents are 1/2 times phase currents and are 30° behind their respective phase currents.

$$\begin{split} I_{R} &= \sqrt{3} \left| \frac{V}{2} \right| \left| \frac{-\varphi - 3\dot{0}}{2} \right| \quad \text{of} \quad I_{RY} - I_{BR} \left(\begin{array}{c} Phavor \ difference \\ \end{array} \right) \\ \hline I_{Y} &= \sqrt{3} \left| \frac{V}{2} \right| \left| \frac{-\mu\dot{0} - \phi - 3\dot{0}}{2} \right| \quad \text{of} \quad I_{YR} - I_{RY} \\ \hline = \sqrt{3} \left| \frac{V}{2} \right| \left| \frac{(F15D - \phi)^{2}}{2} \right| \\ \hline I_{R} &= \sqrt{3} \left| \frac{V}{2} \right| \left| \frac{(-21)\dot{0} - \phi - 3\dot{0}}{2} \right| \quad \text{of} \quad I_{BR} - I_{Y13} \\ \hline = \sqrt{3} \left| \frac{V}{2} \right| \left| \frac{(-27)\dot{0} - \phi}{2} \right| \\ \hline \end{split}$$

Balanud Three phase System - Star Connected load :-

Fig 1.19(a) shows a three phase, three wire system supplying power to a balanced three phase star Connected load. The phase sequence RYB is assumed.

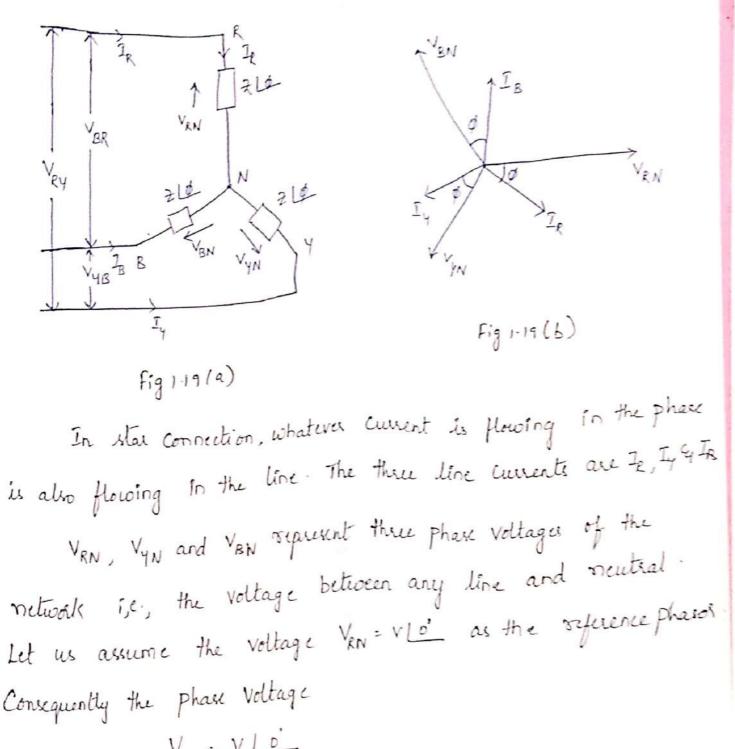

$$V_{RN} = V L_{D}^{-120}$$

 $V_{yN} = V L_{-120}^{-120}$
 $V_{BN} = V L_{-240}^{-240}$

Hence

$$\begin{split} I_{R} &= \frac{V_{RN}}{2L\phi} = \frac{V[0]}{2L\phi} = \left|\frac{V}{2}\right| \left|-\phi\right| \\ I_{Y} &= \frac{V_{YN}}{2L\phi} = \frac{V[-120]}{2L\phi} = \left|\frac{V}{2}\right| \left(-120-\phi\right) \\ \overline{I}_{B} &= \frac{V_{BR}}{2L\phi} = \frac{V[-240]}{2L\phi} = \left|\frac{V}{2}\right| \left(\frac{120-\phi}{2}\right) \\ \overline{I}_{B} &= \frac{V_{BR}}{2L\phi} = \frac{V[-240]}{2L\phi} = \left|\frac{V}{2}\right| \left(\frac{120-\phi}{2}\right) \\ \overline{I}_{B} &= \frac{V_{BR}}{2L\phi} = \frac{V[-240]}{2L\phi} = \left|\frac{V}{2}\right| \left(\frac{120-\phi}{2}\right) \\ \overline{I}_{B} &= \frac{V_{BR}}{2L\phi} = \frac{V[-240]}{2L\phi} = \left|\frac{V}{2}\right| \left(\frac{120-\phi}{2}\right) \\ \overline{I}_{B} &= \frac{V_{BR}}{2L\phi} = \frac{V[-240]}{2L\phi} = \left|\frac{V}{2}\right| \left(\frac{120-\phi}{2}\right) \\ \overline{I}_{B} &= \frac{V_{BR}}{2L\phi} = \frac{V[-240]}{2L\phi} = \left|\frac{V}{2}\right| \left(\frac{120-\phi}{2}\right) \\ \overline{I}_{B} &= \frac{V_{BR}}{2L\phi} = \frac{V[-240]}{2L\phi} = \frac{V[-240]}{2L\phi} = \frac{V[-240]}{2L\phi} \\ \overline{I}_{B} &= \frac{V_{BR}}{2L\phi} = \frac{V[-240]}{2L\phi} = \frac{V[-240]}{2L\phi} = \frac{V[-240]}{2L\phi} \\ \overline{I}_{B} &= \frac{V_{BR}}{2L\phi} = \frac{V[-240]}{2L\phi} = \frac{V[-240]}{2L\phi} = \frac{V[-240]}{2L\phi} \\ \overline{I}_{B} &= \frac{V_{BR}}{2L\phi} = \frac{V[-240]}{2L\phi} = \frac{V[-240]}{2L\phi} = \frac{V[-240]}{2L\phi} \\ \overline{I}_{B} &= \frac{V[-240]}{2L\phi} = \frac{V[-24$$

As seen from the above expressions, the currente IR, I, III -IB are equal in magnitude and have a 120 phase difference. The disposition of these vectors is shown in fig 1.19(b). Sometimes a fourtheoise called neutral wire is hun from the mentral Point if the source is also star connected. This gives three phase four wire star connected system. However if the three line currents are balanued, the current in fourth wire is zero; removing their Connecting wire between the source neutral and load neutral is therefore not going to make any change in the Condition of the system. The availability of the neutral wire makes it possible to use all the three phase voltages, as well as the three line Voltages Usually neutral is grounded for safety and for the design of insulation

Analysis of Unbalanced Three Phase Circuits:-

Types of Unbalanced loads:-

An unbalance exists in a circuit when the impedances in one or more phases differ from the impedances of the other phases. In such a case, line or phase currents are different and are displaced from one another by unequal angles. So for we have considered balanced loads connected to balanced systems. It is enough to solve problems, considering

one phase only on balanced loads; the conditions on other two phases being similar problems on unbalanced three phase loads are difficult to handle because conditions in three Phares are different. However, the source Voltages are assumed to be balanced. If the system is three wire system The cuerents flowing towards the load in the three lines must add to zero at any given instant. If the system is a four wire system, the sum of the three outgoing line currents is equal to the return current in the neutral wire. following are the unbalanced loads is Vobalanced delta Connected load (i) Unbalanced three wire star connected load and (iii) Unbalanud four wire star connected load Unbalanced Della Connected Load:-Fig 1.20 shows an unbalanced R J_R A JRY 2,19 IBR 23 193 della load connected to a balanud there phase supply 2142 $\mathcal{I}_{\mathcal{B}}$ B The unbalanced della Connected Load supplied from a Y-Fig 1.20 balanced three phase supply does not present any new problems becau The voltage across the load phase is fixed. It is independent of the nature of load and is equal to the line vollage of the supply

The current in each load phase is equal to line voltage The current in each load phase is equal to line voltage divided by the impedance of that phase The line current will be phasoe difference of Corresponding phase current taking V_{RY} be phasoe difference of Corresponding phase current taking V_{RY} as selecence phasoe. Assuming RYB phase sequence, we have $V_{RY} = VLO$, $V_{YB} = VL^{12O}$, $V_{BR} = VL^{-24O}$

Phase currents are

The three line cuerents are

 $J_{R} = I_{RY} - J_{BR}$ $J_{Y} = I_{YB} - J_{RY}$ $J_{B} = J_{BR} - J_{YB}$

Unbalanced Four Wire Star Connected Load:

Fig 1.21 Shows an unbalanced star load connected to a balanced 3 phase 4 wire supply.

The star point N_L, of the load is connected to the star point-N_s of the supply. It is the simplest case of an unbalanced load because of the presence of the neutral wire; the star points of the supply N_s (generator) and the load N_L are at the same potential Scanned by CamScanner It means that the voltage across each load impedance is equal to the phase voltage of the supply (generator) i, c, the Voltages across the three load impedances are equalised even though load impedances are unequal. However the current in each phase (or line) will be different obviously the vector hum of the current (or line) will be different obviously the vector hum of the current. In three lines is not zero; but is equal to mented current. The three lines is not zero; but is equal to mented current. Phase currents can be calculated in similar way as that followed in an upbalanced delta connected load.

Taking the phase voltage VRN = VLO V as reference and assuming RYB phase sequences, we have the three phase voltages as follows

B Zalle

NS JN= - (JE+24+JE) EN K

 $\rightarrow \mathcal{I}_{B}$

Iy

22/1/2

Fig 1.21

VyN,


Unbalanced Three Wire Star Connected load .. 5.16 In a three phase four wire system if the connection between Supply neutral and load neutral is broken, it would result in an unbalanced three wire star load This type of load is varely found in practice, because all the three wire star loade are balanced. Such as system is shown in fig 1.22. Note that the supply star point (Ns) is isolated from the load star point (NL) The potential of the load star point is diffuent from that of the supply star point. The result is that the load phase voltages is not equal to supply phase Voltage and they are not only frequal in magnitude but also subtend angles other than 120 with one another. The magnitude of each phase voltage depende upon the individual Phase loads. The potential of the load neutral point changes according to changes in the impedances of the phases, That is why sometimes the load neutral is also called a floating neutral Point. All star connected, unbalanced loads supplied from polyphase systeme without a neutral wise have floating neutral point. The Phason sum of the three unbalanced line currents is zero. The Phase voltage of the load is not 1/13 of the line voltage. The unbalanced three wise star load is difficult to deal with. It is because load phase vollages cannot be determined directly

The given supply line voltages. There are many methods to Y-connected loads. Two frequently Solve such unbalanced used methods are (i) Star-della Conversion method and IR que L (1) Application of Milliman's theorem. y Jy B Measurement of Active and Reactive power:-IR Fig 1:22 Power Measurement in a Single Phase Circuit by Wathmeter. Wattmeties are generally used to measure power on the A wattmeter principally consists of two Coils, one coil is called the Current Coil and the other the pressure or Vollage Coil. A diagramatic representation of a wattmetia Connected to measure power in a single phase circuit as Shown in fig 1.23 m rin + source Fig 1.23 The coil represented with less no of turns between M and L is the current coil, which carries the current in the load and has Very low impedance. The coll with more number of turns between the common terminal (comm) and V is the pressure cail which is connected

across the load and has high impedance. The load voltage is impressed across the pressure cir the forminal M dendes the mains side, L denotes load side, common denotes the common point of current coil and pressure Gy and V denotes the second teaminal of the pressure Gil, usually selected as per the range of the load Voltage in the circuit. From the fig 1.23 it is clear that the wattricter has four terminals, two for current coil and two for Potential coil . When the current flow through the two coils, they set up magnetic fields in space. An electromagnetic torque is produced by the interaction of the two magnetic fields. Under the influence of the terque one of the Gill moves on a Calibrated scale against the action of a spring. The instantaneous longue produced by elutionagnetic action is proportional to the product of Instantineous Values of currents in the two coils. The small current In the pressure coil is equal to the input voltage divided by the Empedance of the pressure cail. The Encertia of the moving system depotés not permit it la follow the instataneou fluctuations Pro toque. The waltmeter deflection is proportional to the average power (VICS\$) delivered to the circuit. Sometimes waternelie Connected to the Circuit gives downscale reaching of backward deflection. This is due to improper connection of current coil and presure coil.

To obtain upscale reading, the terminal marked as

Comm of the pressure coil is connected to one of the terminals of the current coil as shown in fig. 124. Note that the connection between the current coil terminal and pressure coil terminal is not inherent but has to made externally. Even with proper connections, sometimes the waterelie will give down scale reading whenever the phase angle between the voltage across the pressure coil and current through the current coil is more than 90°. In such a case connection of either current coil of pressure coil must be reversed.

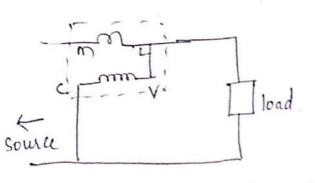

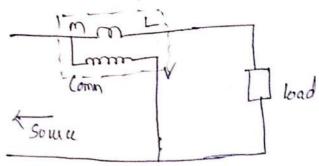


Fig 1.24

Three and Two Wattereta Method:

In this method, the three watterelies are connected in terms three lines as shown in fig 1.25 i, e, the current coils of three watterelies are introduced in the three lines and one terminal of each potential coil is connected to one terminal of the corresponding current coil, the other three being connected to some common point which forms an effective neutral n. The load may be either star connected or delta connected.


Let us assume a star Connected load, and let the III
related of this load be denoted by N. Now the reading on the
wattractic ldg evill correspond to the average value of the product
of instantaneous value of the current IR flowing in line 1 wither
voltage drop VRn, where VRn is the Voltage between points Randy.
This can be written as
$$V_{RD} = V_{RN} + V_{ND}$$
, where V_{RN} is the load
place voltage and V_{ND} is the voltage between load neutral N,
and the common point $The Voltage power W_R$ indicated by the
waltmetic is given by
 $W_R = \frac{1}{T} \int V_{RD} I_R dt$
where T is the time puried of the voltage wave
 $W_R = \frac{1}{T} \int V_{RD} I_R dt$
Similarly $W_Y = \frac{1}{T} \int V_{ND} I_R dt$
Similarly $W_Y = \frac{1}{T} \int V_{RD} I_R dt = \frac{1}{T} \int (V_{NN} + V_{ND}) I_Y dt$
and $W_B = \frac{1}{T} \int V_{RD} I_R dt = \frac{1}{T} \int (V_{RN} + V_{ND}) I_R dt$
Tetal average power $= N_R + N_Y + N_R$ J_R dt
 T total average power $= N_R + N_Y + N_R$ J_R J_R
 $= \frac{1}{T} \int (V_{RN} I_R + V_{ND}) I_R + V_{RD} I_R$ J_R


Since the system in the problem is a three wire system, the sum of the three currents IR, Iy and IB at any given instant is Juo. Hence the power read by the three waltenday is given by

$$W_{R} + W_{y} + W_{B} = \pm \int (V_{RN} I_{R} + V_{yN} I_{y} + V_{BN} I_{B}) dt$$

If the system has a fourth wire i.e., if the neutral wire is available, then the common point, n is to be connected to the system neutral N. In that case VWn would be Zero, and above equation for power would still be valid. In other words whatever be value of V_{Nn} , the algebraic hum of these currents IR IY G_1 Is is Zero. If ence the term $V_{Nn}(I_R + I_Y + I_n)$ would be Zero. Keeping this advantage in mind, suppose common point n' in Fig. 1.25 is connected to line B. In such case, $V_{Nn} = V_{NB}$; then the voltage across the potential will of watheredie W_B will be Zero and this watter will read Zero. Hence this can be removed from the Circuit. The total power is read by the remaining two watter less, W_R and why

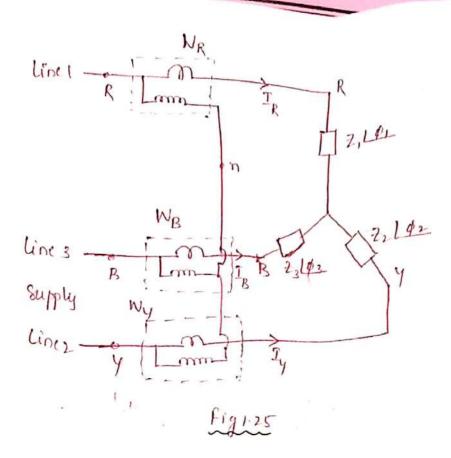:. Total power = $W_R + W_Y$ let we verify this fact from fig 1.26 The average power indicated by wattmeter W_R is $W_R = \pm \int V_{RB} I_R dt$ and that by $W_{R} = \pm \int V_{YB} I_Y dt$ Also $V_{RB} = V_{RN} + V_{NB}$ $V_{YB} = V_{YN} + V_{NB}$



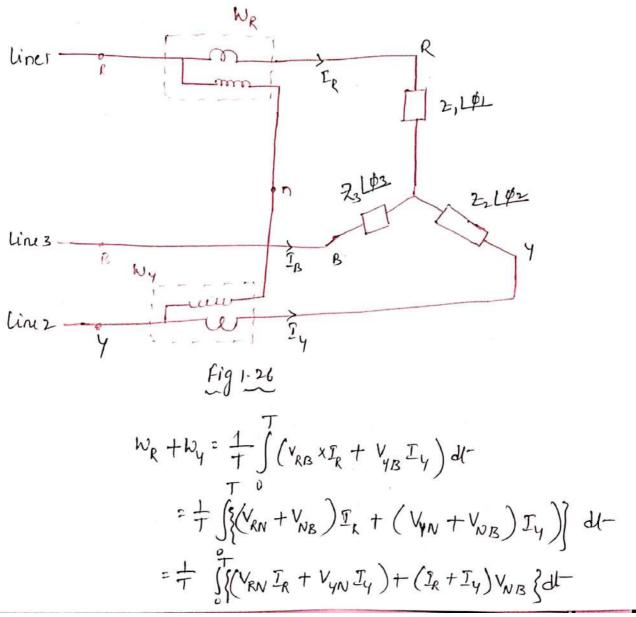

Scanned by CamScanner

15:19

We know that IR + Iy + IB 20 IR + IY = -IB

Substituting this value in the above equation, we get

$$W_R + W_Y = \frac{1}{T} \int_{0}^{T} (V_{EN} I_R + V_{YN} I_Y) + (-I_R) V_{NB} \int_{0}^{T} dt - V_{NB} - V_{BN}$$

 $W_R + W_Y = \frac{1}{T} \int_{0}^{T} (V_{RN} J_R + V_{YN} J_Y + V_{BN} I_B) \int_{0}^{T} dt$

which indicate total power in the load.

The power in a three phase load whether balanced or unbalanced, Star connected of delta connected, three wire of four wrre Can be measured with only two waltmeters. If neutral wrre is available in this method it should not carry any current, of the neutral of the load should be isolated from the neutral of the source.

The current flowing through the current (oil of each watteret is the line current and the voltage across the pressure coil is the line Voltage. In case the phase angle between line voltage and current is greater than 90°, the corresponding wattereter would indicate downscale reading. To obtain upscale reading, the Connections of either the current coil of pressure coil has to be intuchanged. Reading obtained after reversal of coil connection should be taken as negative. Then the algebraic sum of the two watterets readings gives the total power.

Power Factor by Two Wattender Method "

When we talk about the power factor in three phase circuits, it implies only to balanced circuits, since the powerfactor in a balanced load is the power factor of any phase. We cannot strictly define the power factor in three phase unbalanced circuits as every phase has a seperate power factor. The two wattmeter method when applied to measure power in a three phase balanced circuits, provider information that help us to calculate the power factor of the load.

Figure 1.27 shows the Vector diagram of the circuit shown in fig 1.26. Since the load is assumed to be balanced, we can take $Z_1 L_L = \overline{Z}_1 L_L = 2\underline{Z}_2 L_L = 2\underline{Z}_2 L_L$ for the star connected load Assuming RYR phase sequence, the three rms load phase voltages are $V_{\rm RN}$, $V_{\rm YN}$ and $V_{\rm BN} \cdot J_{\rm R}$, $J_{\rm Y}$ and $J_{\rm R}$ are the rms line (phase) currenter These currente will lag behind this respective phase voltages by an angle ϕ (An inductive load is considered.)

Now consider the readings of the two watterstere in fig 1.26. W_R recarries the product of effective value of the current through its current coil I_P , ciffective value of the current through its current coil I_R , effective value of the voltage across its pressure coil V_{PR} and the cosine of the angle between the phasors I_R and V_{RR} . the voltage

Scanned by CamScanner

1.20

across the pressure will of the is given as follows

V_{RB} = V_{RN} - V_{BN} phase difference


It is clear from the phases diagram that the phase angle between

$$V_{RB} = \{J_R \mid i \leq (20-\psi)\}$$

$$\therefore W_{R} = V_{RB} \times J_{E} \cos(30 - \psi)$$

Similarly Ny measures the product of effective value of current through its current loid Iy, the effective value of the voltage above its pressure Coil, Vy13 and the cosine of angle between the phasons Ny13 & Ty

$$V_{YB} = V_{YN} - V_{BN}$$

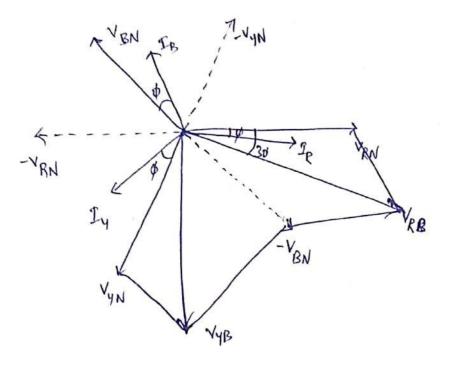



From fig 1.27 it is clear that the phase angle between VyB 4 Iy is (30+4) Wy = VyB × Iy 68(30+4)

Since load is balanced, the line voltage $V_{RB} = V_{YB} = V_{L}$ and Une current $I_{R} = I_{Y} = I_{L}$

$$W_{R} = V_{L} I_{L} \left(ls(30 - \phi) \right)$$

$$W_{Y} = V_{L} I_{L} \left(ls(30 + \phi) \right)$$
Adding W_{R} is W_{Y} gives total power in the circuit, thus
$$W_{R} + W_{Y} = \sqrt{3} V_{L} I_{L} \left(lsd \right)$$
from the two wattineta readings, it is clear that for the same load angle ϕ , wattineta W_{R} register more power when the load is
inductive. It is also connected in the leading phase as the phase inductive is RYB. Therefore W_{R} is higher reading wattineta in the second of fig 1.26. In other words if the load is Capacitive, the livenite connected in leading phase deads bees for the same loatinetic connected in leading phase deads the state inductive is also encode the mature of the load, we can easily load angle. So, if we know the mature of the load, we can easily load angle . So, if we know the mature of the load, be can easily load angle weak positive. By paper manipulation of two wattineta always weak positive. By paper manipulation of two wattineta readings, we can obtain the power factor of the load.
$$W_{R} = V_{L} I_{L} \left(ls(30 - \phi) \right) \quad (Higher reading)$$

$$W_{R} + W_{Y} = \sqrt{3} V_{L} I_{L} \left(ls(20 - \phi) \right) \quad (Higher reading)$$

$$W_{R} + W_{Y} = \sqrt{3} V_{L} I_{L} \left(ls(20 - \phi) \right) \quad (Higher reading)$$

$$W_{R} + W_{Y} = \sqrt{3} V_{L} I_{L} \left(ls(20 - \phi) \right) \quad (Higher reading)$$

$$W_{R} + W_{Y} = \sqrt{3} V_{L} I_{L} \left(ls(20 - \phi) \right) \quad (Higher reading)$$

$$W_{R} + W_{Y} = \sqrt{3} V_{L} I_{L} \left(ls(20 - \phi) \right) \quad (Higher reading)$$

$$W_{R} + W_{Y} = \sqrt{3} V_{L} I_{L} \left(ls(20 - \phi) \right) \quad (Higher reading)$$

$$W_{R} + W_{Y} = \sqrt{3} V_{L} I_{L} \left(ls(20 - \phi) \right) \quad (Higher reading)$$

$$W_{R} + W_{Y} = \sqrt{3} V_{L} I_{L} \left(ls(20 - \phi) \right) \quad (Lower reading)$$

$$W_{R} + W_{Y} = \sqrt{3} V_{L} I_{L} \left(ls(20 - \phi) \right) \quad (Lower reading)$$

$$W_{R} + W_{Y} = \sqrt{3} V_{L} I_{L} \left(ls(20 - \phi) \right) \quad (Lower reading)$$

$$W_{R} + W_{Y} = \sqrt{3} V_{L} I_{L} \left(ls(20 - \phi) \right) \quad (Lower reading)$$

$$\frac{w_{R} - w_{Y}}{w_{R} + w_{Y}} = \frac{4and}{\sqrt{2}}$$

$$Tand = \sqrt{3} \left[\frac{w_{R} - w_{Y}}{w_{R} + w_{Y}} \right]$$

$$d = Jan^{1} \sqrt{3} \left[\frac{w_{R} - w_{Y}}{w_{R} + w_{Y}} \right]$$
Hereafter cosp is found.

Variation in Wattmeter Readings with Load Power Factor:-

It is useful to study the effect of the p.f on the readings of the wattmeter. The readings of the two wattmeters depend on the load power factor angle \$\$, such that

 $W_{R} = V_{L} I_{L} \left(\omega s \left(30 - \phi \right)^{2} \right)$ $W_{Y} = V_{L} I_{L} \left(\omega s \left(30 + \phi \right)^{2} \right)$

We can therefore, make the following deductions:

(i) When of is zero i, e, power factor is unity from the above expressions we can conclude that the two waltmeters indicate equal and positive values.

(ii) When ϕ rises from 0 to 60 j.e., upto power factor 0.5, wattenda W_R reade positive (since it is connected in the leading phase); where as watteneta W_Y reade positive, but less than W_R . When $\phi = 60^\circ$, $W_Y = 0$ and the total power is being measured by only by watteneta W_R (iii) If the power factor is further reduced from 0.5 i, e., when ϕ is greater than 60°, W_R indicates positive Value whereas Scanned by CamScanner Wy reads down scale reading in such case. The connections of wither the current low or pressure coil of the corresponding wallmeter have to be interchanged to obtain an upscale reading and the reading thus obtained must be given a megative sign. The total power in the circuit would be $W_R + (-W_Y) = W_R - W_Y$. Waltmeter W_Y reads downscale for the phase angle between 60 and 90. When the powerfactor is $2exo(1, e., \phi = 90)$ the two wattmeter will read equal of opposite values.

i,c., $W_{R} = V_{L}J_{L}(os(30-90) = 0.5V_{L}J_{L})$ $W_{y} = V_{L}J_{L}(os(30+90) = -0.5V_{L}J_{L})$

Leading Power Factor Load :-

If the load is capacitive, the wattmeter connected in leading Phase would read less value . In that Case, We will be the lower reading wattmeter and by will be the higher reading wattmeter . Fig 1.28 shows the phasos diagram for leading P.f.

As the power factor is leading, the phase currents I_R , $I_Y \neq I_B$ are leading this respective phase voltage by an angle ϕ . From the fig 1.28, the reading of the wattmetic connected in the leading phase is given by

> NR = VRB X IR (08(30+ p)" = VL IL (05 (30+ p)" (lower reading watemeter)

Similarly the reading of waterneter connected in the lagging phase is given by

$$w_{y} = V_{yB} I_{y} \cos(30 - q)'$$

$$= V_{L}I_{L} \cos(30 - q)' \quad (higher reading watterets)$$
Again the total power is given by
$$w_{R} + w_{y} = \sqrt{3} V_{L} I_{L} \cos q$$

$$W_{R} + w_{Y} = \sqrt{3} V_{L} I_{L} \cos q$$

$$W_{V} - \omega_{R} = V_{L} Sin p$$
Hence $\tan q = \frac{3[w_{Y} - \omega_{R}]}{w_{Y} + w_{R}}$

$$V_{YN} + \frac{1}{\sqrt{20}}$$

A comparission of this expression with that of lagging p-1 reveals the fact that the two watherete readings are interchanged i.e., for lagging p.f., we is higher reading watherete & wy is the low reading watherete whereas for leading p.f. we is lower reading watterete why is higher reading watherete while using the expression for p.f., whatever may be the instrue of the low, the lower reading is to be subtracted from the higher reading in the numerator. The variation in the walterete reading with the capacifive load follows the same sequence as in inductive load, with the change in the roles of wallereter.

Reactive Power with Watteneter:


We have seen that the difference between higher readi wattmeter and lower reading wattmeter yielde V_I & Sinp. So the total reactive power = J3V_I I Sinp. Reactive power in the total reactive phase load can be calculated by using a balanced three phase load can be calculated by using

a single wattmeter. As shown in figures) the current coil of wattender is Connected in any one line (R in this case) and preserve Coil across the other two lines (between Yand B in this Case) Assuming phase requerce RYB and an inductive load of angle &, the phason diagram for the circuit is shown From the fig(a) it is clear that the wather power is proportional to the product of current through in fig (b) Fl& current bit, IR Voltage a crook ste pressure coil, VyB and Corine of angle between VyB and IR

YR: VYN-VBN = VL from the vector diagram the angle between YR and IR ie (90-7)

Scanned by CamScanner

523

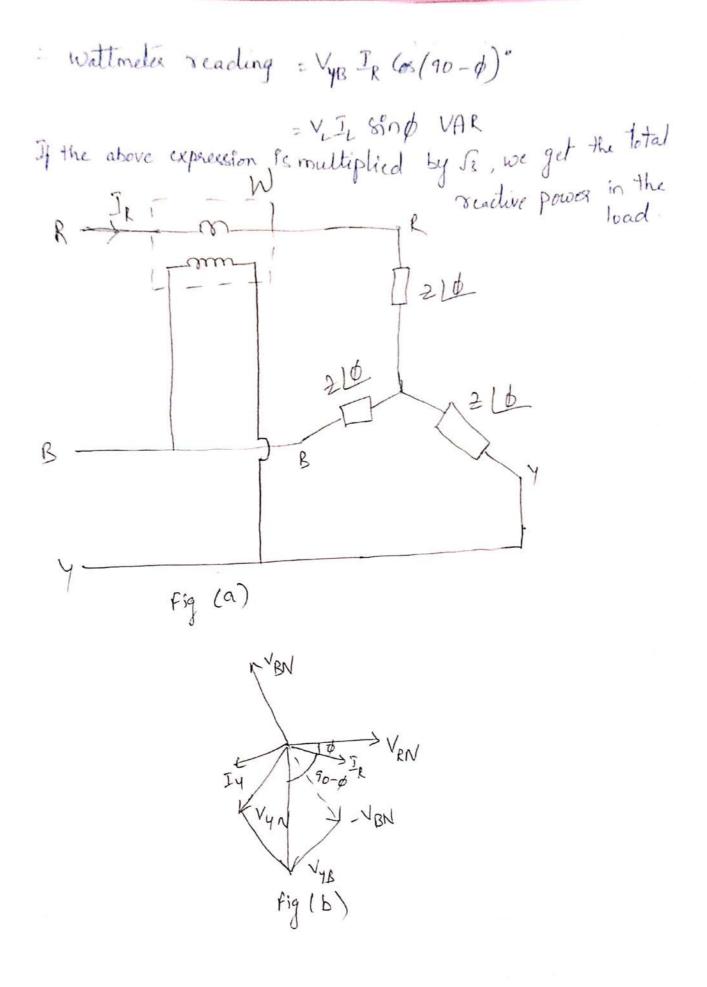

→ A 3 phase load has a resistance of 10.02 in each phase and is connected in is star is Delta against a 4000, 3 phase supply Compare the power consumed in both the cases.

Given that

 $R_{ph} = 10 \Omega = Z_{ph}$ $V_{L} = 400V$

is star Connection

 $V_{L} = 400V$, $V_{Ph} = \frac{V_{L}}{V_{3}} = \frac{400}{V_{3}} = 231V$ $I_{Ph} = \frac{V_{Ph}}{V_{Ph}} = \frac{2.31}{10} = 23.1A$.

Power Consumed P= 3 Vph Iph Cost = 3x231x23.1 × 1

(ii) Della Connection $V_{L} = V_{Ph} = 400V, \quad J_{L} = \frac{J_{Ph}}{V_{3}} = I_{Ph} = \frac{V_{Ph}}{2} = \frac{400}{10} = 40A$ $J_{L} = \frac{40}{V_{3}} = 1$


Power consumed = 3 Vph Iph losof = 3x 400 x 40x | = 48 KW

Polla = 3× Polar

-> Three identical inpedance of
$$(3\pm j4)$$
 a are Concreted in delta
Find an equivalent star reliced such that the line current is
the same when connected to the same supply
SZ.
 $Z = (3\pm j4) \Omega$
 $Z_R := \frac{2_{RY} \times 2_{AR}}{3_{RY} + 2_{VR} + 2_{BR}} = \frac{(3\pm j4)/(3\pm j4)}{9}$
 $= (1\pm j\pm 33) \Omega = 1.66153.15 \Omega$
 $Z_Y = 1.66153.13 \Omega$
 $Z_Y = 1.66153.13 \Omega$
 $Z_R := 1.66153.13 \Omega$
 $Z_Y = 1.66153.13 \Omega$
 $Z_Y = 1.66153.13 \Omega$
 $Z_Y = 1.66153.13 \Omega$
 $Z_R := 1.66153.13 \Omega$
 $Z_Y = 1.66153.13 \Omega$
 $Z_R := 1.66153.13 \Omega$
 $Z_Y = 2.60 \Omega$
 $Z_Y = 1.66153.13 \Omega$
 $Z_Y = 2.602 \Omega$
 Z_Y

$$\begin{split} \tilde{J}_{R} &= \frac{V_{RN}}{R} = \frac{230.94}{12.8 \left[-51.34 \right]} = 18.042 \left[51.34 \right] A \\ \tilde{J}_{Y} &= \frac{V_{4N}}{2} = \frac{230.94 \left[-120 \right]}{12.8 \left[-51.34 \right]} = 18.042 \left[-68.66 \right] A \\ \tilde{J}_{R} &= \frac{V_{BN}}{R} = \frac{230.94 \left[-120 \right]}{12.8 \left[-51.34 \right]} = 18.042 \left[-188.66 \right] A \\ Total Voll-amperes S = 3V_{Ph} E_{Ph} \\ &= 3x \, 230.94 \left[x + 18.042 \right] \\ &= 12499.98 VA \\ &= 12499.98 VA \\ P &= 3V_{Ph} J_{Ph} \left[sin \phi = 3x \, 230.94 \, x + 18.042 \right] \left[sin \left(51.34 \right) \right] \\ &= 7808.63 W \\ Q &= 3V_{Ph} J_{Ph} \left[sin \phi = 3x \, 230.94 \, x + 18.042 \right] sin \left((51.34 \right) \right] \end{split}$$

= 9760.72 VAR .

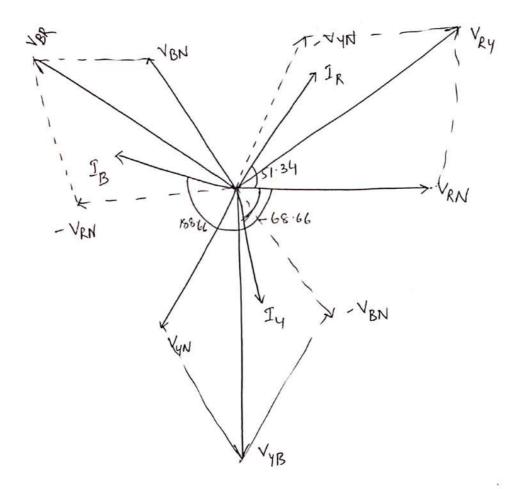

→ A balanced 3-phase system supplied from 400V, 50H 2 supply Mas R, L & C elements connected parallel in each phase. The values of R, L & C are 10-2, 1H & 100/1F supertively Calculate the line Current. The power & power factor

