



Vidya Jyothi Institute of Technology

(An Autonomous Institution)

(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

B. Tech. III Year II Semester

L	T	P	C
0	0	2	1

POWER ELECTRONICS AND SIMULATION LABORATORY

Course Code: A46289

Course Outcomes: Upon the completion of Laboratory course, the student will be able to

CO1. Examine the characteristics of SCR, MOSFET, & IGBT, and analyze triggering circuits.

CO2. Analyze input and output characteristics of AC-DC converters.

CO3. Synthesize characteristics of Cycloconverters.


CO4. Examine characteristics of DC-DC Converters and Inverters.


CO5. Design of converters and inverters using P-Spice software.

List of Experiments

Any ten of the following experiments are required to be conducted.

1. Study of characteristics of SCR, MOSFET & IGBT.
2. Gate Firing Circuits for SCRs (R- Triggering, RC Triggering & UJT Triggering).
3. Single Phase AC voltage Controller with R & RL Loads.
4. Single Phase fully Controlled Bridge Converter with R & RL Loads.
5. DC Jones Chopper with R & RL Loads.
6. Single Phase Parallel Inverter with R & RL Loads.
7. Single Phase Cycloconverter with R & RL Loads.
8. Single Phase Series Inverter with R & RL Loads.
9. Single Phase Half controlled converter with R Load.
10. Simulation of single-phase full converter using RLE loads and single-phase AC voltage controller using RLE loads.
11. Simulation of resonant pulse commutation circuit and Buck Chopper.
12. Simulation of single phase Inverter with PWM control.


Head of the Department
Department of Electrical & Electronics Engg
Vidya Jyothi Institute of Technology
HYDERABAD-500 075.


PRINCIPAL
Vidya Jyothi Institute of Technology
Himayatnagar (VIII), C.B. Post.,
Hyderabad-75.



Vidya Jyothi Institute of Technology

(An Autonomous Institution)

(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

Correlation of COs with Experiments

S.No.	Title of Experiment	COs Mapped
1	Study of characteristics of SCR, MOSFET & IGBT.	CO1
2	Gate Firing Circuits for SCRs (R- Triggering, RC Triggering & UJT Triggering).	CO1
3	Single Phase AC voltage Controller with R & RL Loads.	CO2
4	Single Phase fully Controlled Bridge Converter with R& RL Loads.	CO2
5	DC Jones Chopper with R & RL Loads.	CO4
6	Single Phase Parallel Inverter with R& RL Loads.	CO4
7	Single Phase Cycloconverter with R& RL Loads.	CO3
8	Single Phase Series Inverter with R& RL Loads.	CO4
9	Single Phase Half controlled converter with R Load.	CO2
10	Simulation of single-phase full converter using RLE loads and single-phase AC voltage controller using RLE loads.	CO2,CO5
11	Simulation of resonant pulse commutation circuit and Buck Chopper.	CO4,CO5
12	Simulation of single phase Inverter with PWM control.	CO4,CO5



Vidya Jyothi Institute of Technology

(An Autonomous Institution)

(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

Programme Outcomes (POs)

Engineering Graduates will be able to:

- 1. Engineering knowledge:** Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
- 2. Problem analysis:** Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
- 3. Design/development of solutions:** Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
- 4. Conduct investigations of complex problems:** Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.
- 5. Modern tool usage:** Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.
- 6. The engineer and society:** Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
- 7. Environment and sustainability:** Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
- 8. Ethics:** Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
- 9. Individual and team work:** Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.
- 10. Communication:** Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.
- 11. Project management and finance:** Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.
- 12. Life-long learning:** Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.

Program Specific Outcomes

PSO1: Conceptualize electrical and electronics systems, employ control strategies for power electronics related applications to prioritize societal requirements.

PSO 2: Apply the appropriate techniques and modern engineering hardware and software tools in electrical engineering to engage in multi-disciplinary environments



Vidya Jyothi Institute of Technology

(An Autonomous Institution)

(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

C328	POWER ELECTRONICS & SIMULATION LAB											
	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12
C328.1	3	2	2	2	-	-	-	-	3	-	-	3
C328.2	3	3	3	2	-	-	-	-	3	-	-	3
C328.3	3	3	3	2	-	-	-	-	3	-	-	3
C328.4	3	3	3	2	-	-	-	-	3	-	-	3
C328.5	3	3	3	2	-	-	-	-	3	-	-	3
	3	2.8	2.8	2	-	-	-	-	3	-	-	3

CO – PO Mapping

CO – PSO Mapping

POWER ELECTRONICS AND SIMULATION LAB		
C328	PSO1	PSO2
C328.1	3	-
C328.2	3	-
C328.3	3	-
C328.4	3	-
C328.5	3	3
	3	3



Vidya Jyothi Institute of Technology

(An Autonomous Institution)

(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

Rubrics for Power Electronics and Simulation Laboratory

Rubrics for Hardware based Experiments

Total Marks: 15M

S. No.	Assessment Criteria	Excellent (80 – 100%)	Good (60-80%)	Average (Below 60%)
1	Theoretical Knowledge to perform the experiment (2M)	Student replied to all the questions posed by Laboratory teacher	Student replies to a minimum of 50% questions posed by the laboratory teacher	Student could not answer in the first session
2	Preparation of list of equipment required (2M)	Correctness in the rating and type of the equipment required	Correctness in the rating and type of equipment required with minor corrections	Student could not prepare the list of equipment required
3	Making the circuit connections as per the circuit diagram. (3 M)	Correctness of connections	Correctness of connections with minor corrections.	Unable to connect
4	Performing the experiment and tabulating the values (3 M)	Independent performance of the experiment with correct values	Performance of the experiment with teacher assistance	Unable to perform the experiment
5	Record book (based on calculations, results, graphs) (5 M)	Practical values matching with theoretical values/ Expected graph obtained.	Minor deviation in the practical values/ expected graph	Deviation of practical values with theoretical values / expected graph.



Vidya Jyothi Institute of Technology

(An Autonomous Institution)

(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad-500 075

DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

Rubrics for Power Electronics and Simulation Laboratory

Rubrics for Software/Simulation based Experiments

Total Marks: 15 M

S. No	Assessment Criteria	Excellent (80 – 100%)	Good (60-80%)	Average (Below 60%)
1	Theoretical Knowledge to perform the experiment (2M)	Student replied to all the questions posed by Laboratory teacher	Student replies to a minimum of 50% questions posed by the laboratory teacher	Student could not answer in the first session
2	Writing a program / simulation diagram of the experiment (3M)	Correctness in the rating and type of the equipment required	Correctness in the rating and type of equipment required with minor corrections	Student could not prepare the list of equipment required
3	Execution of the program / simulation (5 M)	Executed without errors	Partially Executed	Unable to run the program
4	Record book (calculations, results, plots) (5 M)	Simulation output matching with theoretical values/ Expected plot obtained.	Minor deviation in the simulation output/ expected plot	Deviation of simulation output with theoretical values / expected plot.



Department of Electrical and Electronics Engineering

STUDENT PERFORMANCE EVALUATION

TOTAL MARKS (75M)

EXTERNAL EVALUATION (50 Marks)

Circuit Diagram	10M
Procedure write up	10M
Experiment connections & observations	10M
Calculations	10M
Viva Voce	10M

INTERNAL EVALUATION (25 Marks)

Day to day evaluation	10M
Record	5M
Internal Exam	10M

LABORATORY MANUAL
for
Power Electronics and Simulation Lab

III Year B.Tech II Semester

Prepared by
Mr. B. Rajesh and Mrs. P. Vaishnavi Devi,
Assistant Professors,
Department of Electrical and Electronics Engineering



VIDYA JYOTHI INSTITUTE OF TECHNOLOGY
(An Autonomous Institution)
C.B.Post, Aziznagar, Hyderabad



POWER ELECTRONICS AND SIMULATION LAB

INDEX

S.No.	Title	Page No.
1	Vision Mission of the Institute and Department	i
2	Course Outcomes and List of Experiments	ii
3	Correlation of COs with Experiments	iii
4	Program Outcomes and Program Specific Outcomes	iv
5	CO – PO and CO – PSO Mappings	v
	Experiments	
6	Study of characteristics of SCR, MOSFET & IGBT.	1-8
7	Gate Firing Circuits for SCRs (R- Triggering, RC Triggering & UJT Triggering).	9-13
8	Single Phase AC voltage Controller with R & RL Loads.	14-15
9	Single Phase fully Controlled Bridge Converter with R& RL Loads.	16-17
10	DC Jones Chopper with R & RL Loads.	18-19
11	Single Phase Parallel Inverter with R& RL Loads.	20-21
12	Single Phase Cycloconverter with R& RL Loads.	22-23
13	Single Phase Series Inverter with R& RL Loads.	24-25
14	Single Phase Half controlled converter with R Load.	26-27
15	Simulation of single-phase full converter using RLE loads and single-phase AC voltage controller using RLE loads.	28-31
16	Simulation of resonant pulse commutation circuit and Buck Chopper.	32-33
17	Simulation of single phase Inverter with PWM control.	34-35



Vision of the Institution

- To develop into a reputed Institution at National and International level in Engineering, Technology and Management by generation and dissemination of knowledge through intellectual, cultural and ethical efforts with human values.
- To foster Scientific temper in promoting the world class professional and technical expertise.

Mission of the Institution

- To create state-of-the-art infrastructure facilities for optimization of knowledge acquisition.
- To nurture the students holistically and make them competent to excel in the global scenario.
- To promote R&D and consultancy through strong industry-institute interaction to address the societal problems.

Vision of the Department

- To become a reputed department in the impartation of professional and technical expertise in the field of Electrical and Electronics Engineering.

Mission of the Department

- Imparting Quality Technical Education by provision of state-of-the-art learning facilities.
- Preparing the students to think innovatively and find effective solutions to address engineering and societal problems with a multi-disciplinary approach maintaining continuous industry interaction.
- Encouraging team work and preparing the students for lifelong learning with ethical responsibility for a successful professional career.

Programme Educational Outcomes (PEOs)

PEO1: To provide the students with a sound foundation in the mathematics, science and engineering fundamentals necessary to become employable.

PEO2: Graduates should apply their technical knowledge to take up higher responsibilities in industry, academics and create innovative ideas in the field of Electrical and Electronics Engineering.

PEO3: Equip graduates with communication skills, leadership qualities with ethical values, team work with multi-disciplinary approach and zeal to provide solutions for engineering and societal problems.



B. Tech. III Year II Semester

L	T	P	C
0	0	2	1

Course Code: A46289

Course Outcomes: Upon the completion of Laboratory course, the student will be able to

- CO1. Examine the characteristics of SCR, MOSFET, & IGBT, and analyze triggering circuits.**
- CO2. Analyze input and output characteristics of AC-DC converters.**
- CO3. Synthesize characteristics of Cycloconverters.**
- CO4. Examine characteristics of DC-DC Converters and Inverters.**
- CO5. Design of converters and inverters using P-Spice software.**

List of Experiments

Any ten of the following experiments are required to be conducted.

1. Study of characteristics of SCR, MOSFET & IGBT.
2. Gate Firing Circuits for SCRs (R- Triggering, RC Triggering & UJT Triggering).
3. Single Phase AC voltage Controller with R & RL Loads.
4. Single Phase fully Controlled Bridge Converter with R& RL Loads.
5. DC Jones Chopper with R & RL Loads.
6. Single Phase Parallel Inverter with R& RL Loads.
7. Single Phase Cycloconverter with R& RL Loads.
8. Single Phase Series Inverter with R& RL Loads.
9. Single Phase Half controlled converter with R Load.
10. Simulation of single-phase full converter using RLE loads and single-phase AC voltage controller using RLE loads.
11. Simulation of resonant pulse commutation circuit and Buck Chopper.
12. Simulation of single phase Inverter with PWM control.

**Correlation of COs with Experiments**

S.No.	Title of Experiment	COs Mapped
1	Study of characteristics of SCR, MOSFET & IGBT.	CO1
2	Gate Firing Circuits for SCRs (R- Triggering, RC Triggering & UJT Triggering).	CO1
3	Single Phase AC voltage Controller with R & RL Loads.	CO2
4	Single Phase fully Controlled Bridge Converter with R& RL Loads.	CO2
5	DC Jones Chopper with R & RL Loads.	CO4
6	Single Phase Parallel Inverter with R& RL Loads.	CO4
7	Single Phase Cycloconverter with R& RL Loads.	CO3
8	Single Phase Series Inverter with R& RL Loads.	CO4
9	Single Phase Half controlled converter with R Load.	CO2
10	Simulation of single-phase full converter using RLE loads and single-phase AC voltage controller using RLE loads.	CO2,CO5
11	Simulation of resonant pulse commutation circuit and Buck Chopper.	CO4,CO5
12	Simulation of single phase Inverter with PWM control.	CO4,CO5



Programme Outcomes (POs)

Engineering Graduates will be able to:

- 1. Engineering knowledge:** Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
- 2. Problem analysis:** Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
- 3. Design/development of solutions:** Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
- 4. Conduct investigations of complex problems:** Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.
- 5. Modern tool usage:** Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.
- 6. The engineer and society:** Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
- 7. Environment and sustainability:** Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
- 8. Ethics:** Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
- 9. Individual and team work:** Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.
- 10. Communication:** Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.
- 11. Project management and finance:** Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.
- 12. Life-long learning:** Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.

Program Specific Outcomes

PSO1: Conceptualize electrical and electronics systems, employ control strategies for power electronics related applications to prioritize societal requirements.

PSO 2: Apply the appropriate techniques and modern engineering hardware and software tools in electrical engineering to engage in multi-disciplinary environments



CO – PO Mapping

C328	POWER ELECTRONICS & SIMULATION LAB											
	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12
C328.1	3	2	2	2	-	-	-	-	3	-	-	3
C328.2	3	3	3	2	-	-	-	-	3	-	-	3
C328.3	3	3	3	2	-	-	-	-	3	-	-	3
C328.4	3	3	3	2	-	-	-	-	3	-	-	3
C328.5	3	3	3	2	-	-	-	-	3	-	-	3
	3	2.8	2.8	2	-	-	-	-	3	-	-	3

CO – PSO Mapping

POWER ELECTRONICS AND SIMULATION LAB		
C328	PSO1	PSO2
C328.1	3	-
C328.2	3	-
C328.3	3	-
C328.4	3	-
C328.5	3	3
	3	3

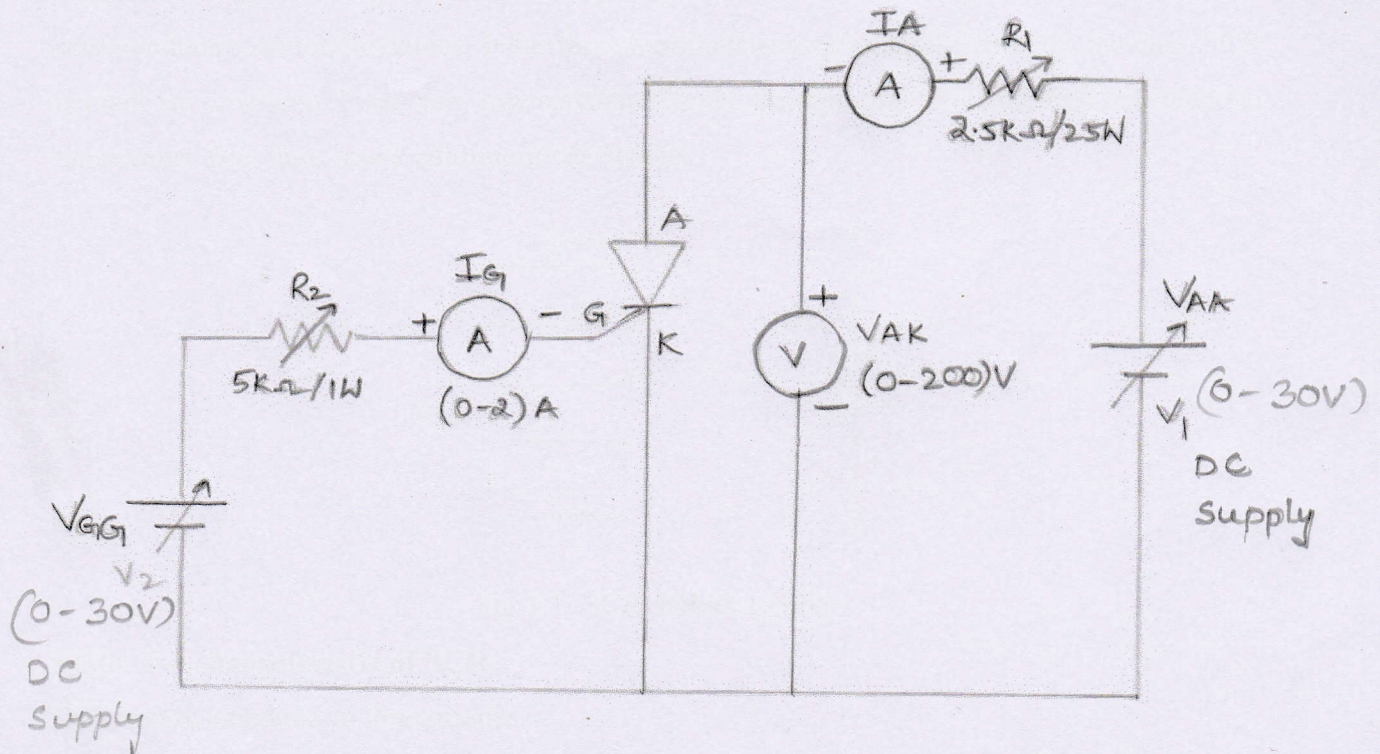
**1.a) STATIC CHARACTERISTICS OF SCR****CIRCUIT DIAGRAM:**

Fig. 1.1

1. a) STUDY OF CHARACTERISTICS OF SCR

AIM: To plot V- I characteristics of SCR and find the latching and holding currents of SCR

THEORY: Silicon Controlled Rectifier (SCR) is a four layered three junction P N P N semiconductor switching device. It has three terminals named as anode, cathode and gate. SCR is made up of silicon. It has very low resistance in the forward direction and high resistance in the reverse direction. It is a unidirectional device.

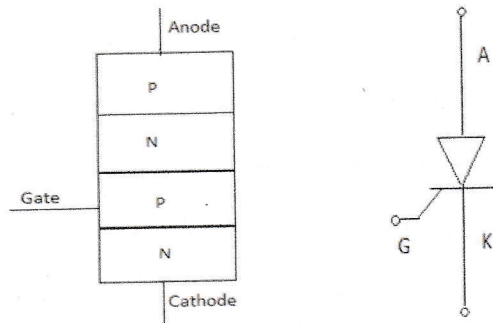


Fig 1.1: SCR and its symbol

Static V-I characteristic of SCR:

SCR can be operated in three modes.

1. Reverse blocking mode
2. Forward blocking mode (Off state)
3. Forward conduction mode (On state)

1. Reverse Blocking Mode:

When the cathode of SCR is made positive with respect to anode, SCR is reverse biased. Junctions J1 and J2 are reverse biased where junction J3 is forward biased. The device behaves as if two diodes are connected in series with reverse voltage applied across them.

A small leakage current of the order of few milli Amperes only flows. As SCR is reverse biased and in blocking mode, it is called as reverse blocking mode of operation. Now if the reverse voltage is increased, at a critical breakdown level called reverse breakdown voltage V_{BR} , an avalanche occurs at J1 and J3 and the reverse current increases rapidly through the SCR. This results in SCR damage as junction temperature may exceed its maximum temperature rise.

2. Forward Blocking Mode:

When anode is positive with respect to cathode, with gate circuit open, SCR is said to be forward biased mode. Then junction J1 and J3 are forward biased and J2 is reverse biased. As



TABULAR COLUMN:

V_{AK} (V)	I_G (mA)	I_A (mA)	V_{AK} (V)	I_G (mA)	I_A (mA)	V_{AK} (V)	I_G (mA)	I_A (mA)

$I_L = \underline{\hspace{2cm}}$ (mA) $I_H = \underline{\hspace{2cm}}$ (mA)

MODEL GRAPH :

 


Fig. 1.2



the forward voltage is increased, junction J2 will have an avalanche breakdown at a voltage called forward break over voltage V_{BO} . When forward voltage is less than , SCR offers high impedance. Thus an SCR acts as an open switch in forward blocking mode.

3. Forward Conduction Mode:

In this mode of SCR conducts current from anode to cathode with a very small voltage drop across it. An SCR can be brought from forward blocking mode to forward conducting mode:

1. By exceeding the forward break over voltage.
2. By applying a gate pulse between gate and cathode.

During forward conduction mode of operation, SCR is in on state and behaves like a closed switch. Voltage drop is of the order of 1 to 2mV. This small voltage drop is due to resistance drop across the four layers of the device.

Latching current: The latching current is the minimum value of anode current which must be attained by the SCR to turn ON.

Holding current: It is the minimum value of anode current below which the SCR turns off if it falls, the SCR will turn OFF.

APPARATUS:

1. SCR characteristics study unit.
2. Meters
 - a. Voltmeter (0-20) V - 1 No.
 - b. Ammeter (0-2) A - 1 No.
 - c. Ammeter (0-200) mA - 1 No.
3. Patch cords

PROCEDURE:

1. Make the connections as per the circuit diagram.
2. Switch ON the main supply and keep the voltages V_1 & V_2 at minimum position initially.
3. Vary V_1 and set the voltage V_{AK} to 10V.
4. Slowly vary V_2 in steps and note down I_G , I_A and V_{AK} values.
5. Vary V_2 till V_{AK} suddenly drops down. This indicates that the SCR started conduction.
6. Repeat the same procedure for $V_{AK} = 15V$ and 20V.



7. Draw the graph V_{AK} vs I_A for different values of I_G .

Procedure to find Latching current:

1. Apply about 20 V between Anode and Cathode by varying V_1 .
2. Keep the load potentiometer R_1 at minimum position.
3. The device must be in the OFF state with gate open.
4. Gradually increase Gate voltage - V_2 till the device turns ON.
5. The minimum anode current at which the SCR turns ON is the latching current.
6. Note down the latching current.

Procedure to find Holding current:

1. Increase the load current from the latching current level by increasing V_1 .
2. Open the gate switch permanently. The SCR must be fully ON.
3. Now start reducing the load current gradually by adjusting R_1 . If the SCR does not turn OFF even after the R_1 at maximum position, then reduce V_1 .
4. Observe when the device goes to Blocking mode. The load current through the device at this instant, is the holding current of the device.
5. Note down the holding current.

RESULT: The static characteristics (V I Characteristics) of SCR are studied and latching and holding currents of the SCR are found.



1 b) CHARACTERISTICS OF MOSFET


CIRCUIT DIAGRAM:

Fig 1.6

TABULAR COLUMN:

Output Characteristics :

S.NO.	$V_{GS} = 2V$		$V_{GS} = 2.7 V$		$V_{GS} = 2.9 V$	
	$V_{DS} (V)$	$I_D (mA)$	$V_{DS} (V)$	$I_D (mA)$	$V_{DS} (V)$	$I_D (mA)$

 

1. b) STUDY OF CHARACTERISTICS OF MOSFET

AIM: To plot the output and transfer characteristics of MOSFET.

THEORY:

A power MOSFET has three terminals called Drain (D), Source(S) and Gate(G). MOSFET is a voltage controlled device. It's operation depends on the flow of majority carriers only. MOSFET is a unipolar device.

 


Fig 1.2: MOSFET structure and Symbol

Power MOSFETs are of two types, n-channel enhancement MOSFET and p-channel enhancement MOSFET. Out of these two types, n-channel enhancement MOSFET is commonly used because of higher mobility of electrons.

The IGBT does not conduct when the gate circuit is open. When gate is made positive with respect to source, an electric field is established. Then negative charges are induced in the p-substrate below SiO₂ layer. The n-channel current flows from drain to source. If V_{GS} is made more positive, n-channel expands and therefore, more current flows from D to S. The drain current I_D is enhanced by the gradual increase of gate voltage. Hence the name enhancement MOSFET is used.

Output Characteristics: Power MOSFET output characteristics indicate the variation of drain current I_D as a function of drain-source voltage V_{DS} . For low values of V_{DS} , the graph between I_D & V_{DS} is almost linear. This indicates a constant value of on-resistance

$$R_{DS} = V_{DS} / I_D.$$

For given V_{GS} , if V_{DS} is increased, output characteristic is relatively flat indicating that drain current is nearly constant.



Transfer Characteristics :

S.NO.	$V_{DS} = 2.5V$	
	$V_{GS} (V)$	$I_D (mA)$

MODEL GRAPHS :

Output Characteristics:

 


Fig 1.7

Transfer Characteristics:

 


Fig 1.8



Transfer Characteristics: These characteristics show the variation of drain current I_D as a function of gate-source voltage V_{GS} . In the transfer characteristic, the device turns off if V_{GS} is decreased below the threshold voltage V_{GST} .

APPARATUS:

1. MOSFET characteristics study unit.
2. Meters
 - a. Voltmeter (0-20) V - 1 No.
 - b. Voltmeter (0-200) V - 1 No.
 - c. Ammeter (0-200) mA- 1 No.
3. Patch cords.

(a) Drain /Output Characteristics:

1. Make the connections as per the circuit diagram.
2. Vary the supply V_2 and adjust $V_{GS} = 2V$.
3. Vary the supply V_1 in steps and note down the values of V_{DS} & I_D
4. Repeat the procedure for different values of V_{GS} (at least two different values of V_{GS})
5. Plot the graph of V_{DS} vs I_D for different values of V_{GS} .

(b) Transfer Characteristics:

1. Set V_{DS} to 2.5V by varying V_1 .
2. Vary V_2 in steps, note down V_{GS} and I_D
3. Plot the characteristics V_{GS} vs I_D .

RESULT: The Output and Transfer characteristics of MOSFET are plotted and studied.



1 c) CHARACTERISTICS OF IGBT

CIRCUIT DIAGRAM:

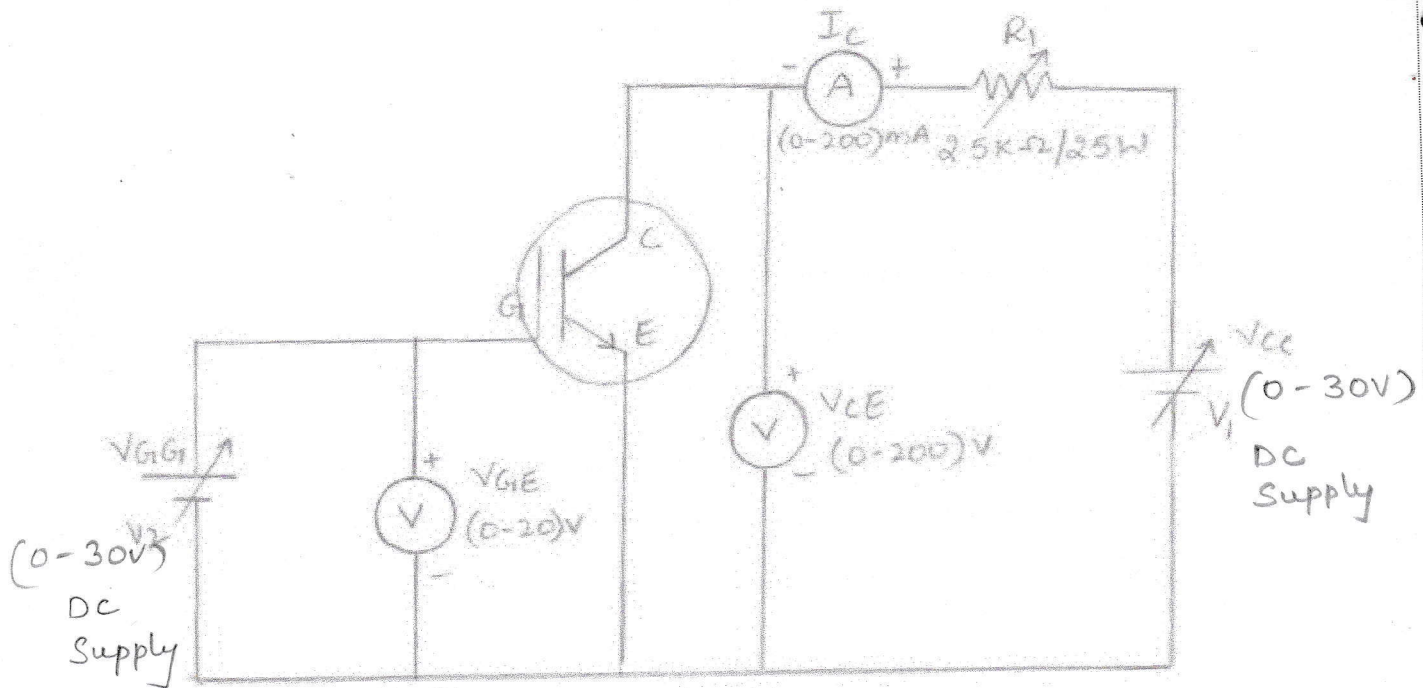


Fig 1.3

TABULAR COLUMN:

Output Characteristics:

S.NO.	$V_{GE} = 4V$		$V_{GE} = 5V$		$V_{GE} = 5.2V$	
	$V_{CE} (V)$	$I_C (mA)$	$V_{CE} (V)$	$I_C (mA)$	$V_{CE} (V)$	$I_C (mA)$

1. c) STUDY OF CHARACTERISTICS OF IGBT

AIM: To plot the output and transfer characteristics of IGBT.

THEORY:

An IGBT has three terminals called Collector, Gate and Emitter. When gate is positive with respect to emitter and with gate-emitter voltage more than threshold voltage of IGBT, an n-channel is formed in the p-regions as in a power MOSFET. This n-channel short circuits the n-region with n+ emitter regions. An electron movement in the n-channel, in turn, causes substantial hole injection from p+ substrate layer into the epitaxial n- layer. Eventually, a forward current is established. The three layers p+, n- and p constitute a pnp transistor with p+ as emitter, n- as base and p as collector. Also n-, p and n+ layers constitute npn transistor as shown in below fig 1.3.

 


Fig 1.3: IGBT Structure and Symbol

The output characteristics of an IGBT are plot for collector current I_C versus collector-emitter voltage V_{CE} for various values of gate-emitter voltages. The output of IGBT is controlled by gate emitter voltage V_{GE} . Hence IGBT is a voltage-controlled device.

The transfer characteristic of an IGBT is a plot of collector current I_C versus gate-emitter voltage V_{GE} . This characteristic is identical to that of power MOSFET. When V_{GE} is less than the threshold voltage V_{GET} , IGBT is in off-state. When the device is off, junction J2 blocks forward voltage and in case reverse voltage appears across collector and emitter, junction J1 blocks it.

APPARATUS:

1. IGBT characteristics study unit.
2. Meters
 - a. Voltmeter (0-20)V - 1 No.
 - b. Voltmeter (0-200)V - 1 No.
 - c. Ammeter (0-200)mA - 1 No.
3. Patch cords.



Transfer Characteristics :

S.NO.	$V_{CE} = 5V$	
	$V_{GE} (V)$	$I_C (mA)$

MODEL GRAPHS :

Output Characteristics :

 


Fig 1.4

Transfer Characteristics:

 


Fig 1.5



PROCEDURE:

(a) Output Characteristics:

1. Make the connections as per the circuit diagram.
2. Vary V2 and set V_{GE} to 4V.
3. Vary V1 in steps and note down V_{CE} and I_C for each step.
4. Plot the graph of I_C vs V_{CE} for different values of V_{GE} .

(b) Transfer Characteristics:

1. Vary V1 and set V_{CE} at 5V.
2. Vary V2 in steps and note down V_{GE} and I_C
3. Plot a graph for V_{GE} vs I_C .

RESULT: The output and transfer characteristics of IGBT are plotted and studied.



GATE FIRING CIRCUITS

CIRCUIT DIAGRAM:

 


Fig 2.1

TABULAR COLUMN:

S.No.	Firing angle (α)	Load voltage (V)



2. GATE FIRING CIRCUITS OF SCR

1. R TRIGGERING CIRCUIT

AIM: To study the switching control of SCR with R triggering circuit.

THEORY:

The conventional gate triggering circuits used to turn ON an SCR are:

1. Resistance triggering (amplitude control)
2. RC triggering (Phase control)
3. UJT triggering (Phase control)
4. Ramp and pedestal triggering
5. DC triggering.
6. Digital triggering schemes.
7. Microprocessor controlled triggering schemes.
8. Light triggering in LASCR.

Resistance Triggering: This is the simplest method of turning on an SCR in phase control circuit. A resistance of suitable value is connected between anode and gate through a diode. Whenever anode voltage is positive, current flows from gate to cathode circuit through this resistance. Hence SCR turns ON. But the gate current will remain as long as the anode to cathode voltage is positive. But the trigger angle can be controlled only from 0 to $\pi/2$ of the applied voltage. V_{GK} can be adjusted with R_2 but its phase positive is same as that of the AC supply voltage. Hence if SCR does not turn on at $\pi/2$, it cannot be turned on after $\pi/2$ since the magnitude of the voltage will decrease after this instant.

$$\text{Load voltage } V_{DC} = \frac{V_m(1+\cos\alpha)}{2\pi}$$

APPARATUS:

1. SCR Triggering module.
2. C.R.O.
3. Patch cords.
4. Multimeter

PROCEDURE:

1. Make the connections as per the circuit diagram.
2. Switch ON the supply.
3. Set the potentiometer to a particular position and observe the waveforms of V_{IN} , V_O ,



TABULAR COLUMN :

S.No.	Firing angle (α)	Load voltage (V)

S.No.	Firing angle (α)	Load voltage (V)



V_T , on the C.R.O. and note down the corresponding waveforms.

4. Vary the potentiometer in steps and note down the firing angle and the corresponding load voltage using multimeter.

RESULT: The switching control of SCR with R-triggering is observed and studied.

2 b) RC TRIGGERING

CIRCUIT DIAGRAM:

RC HALF WAVE TRIGGERING

 


Fig 2.3

RC FULL WAVE TRIGGERING

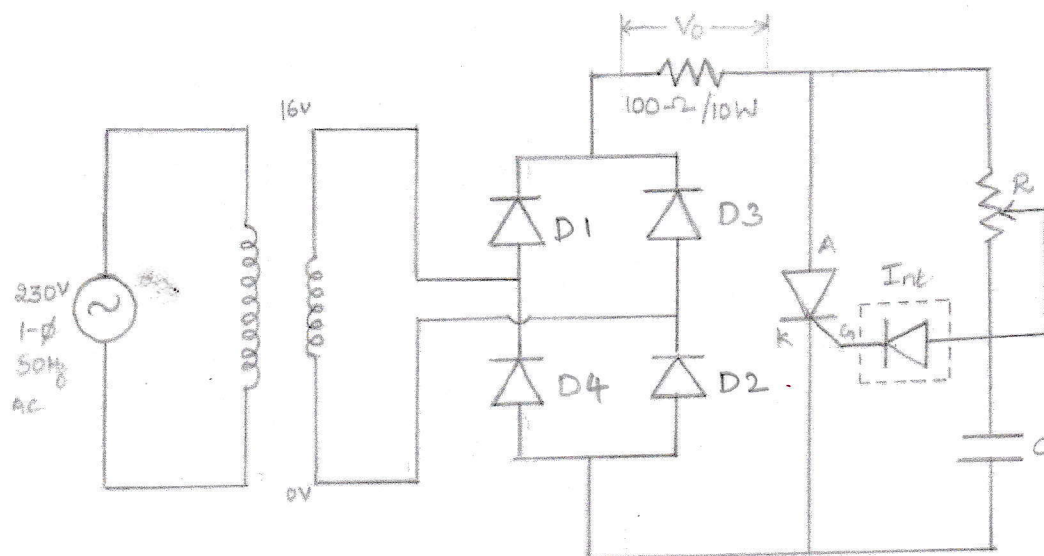


Fig 2.4



2 b) RC TRIGGERING

AIM: To study the phase control of SCR by RC triggering.

THEORY:

In case of resistance triggering, the firing angle of the SCR can be varied from 0 to 90° only. Hence resistance triggering cannot be employed in practice as the output voltage cannot be varied over a wide range (i.e., 0 to V_m / π in case of half wave and 0 to $2V_m / \pi$ in case of full wave).

To overcome the above limitations, Resistance and Capacitance (RC) triggering is employed so as to vary the triggering angle of SCR over the complete range 0 to 180°. RC triggering is very cheap and reliable for low voltage phase controlled circuits.

RC circuit helps to adjust the position of gate to cathode voltage as the voltage across the capacitor lags the current through it by 90°, by varying R, the phase angle w.r.t., applied voltage can be adjusted. Hence the triggering angle α can be varied over a wide range from 0 to 180°. By varying R, we can vary the triggering angle α . The load voltage can be obtained from $V_{DC} = \frac{V_m(1+\cos\alpha)}{2\pi}$

APPARATUS:

1. SCR Triggering module.
2. C.R.O.
3. Patch cords.
4. Multimeter.

PROCEDURE:

1. Make the connections as per the circuit diagram.
2. Switch ON the module.
2. Set the potentiometer to a particular position and observe the waveforms of V_{IN} , V_O , V_T , V_C on the C.R.O. and note down the corresponding waveforms.
3. Vary the potentiometer in steps and note down the corresponding load voltage using multimeter.

RESULT: The Phase control of SCR with RC triggering is studied.



2.c) UJT TRIGGERING CIRCUIT.

CIRCUIT DIAGRAM :

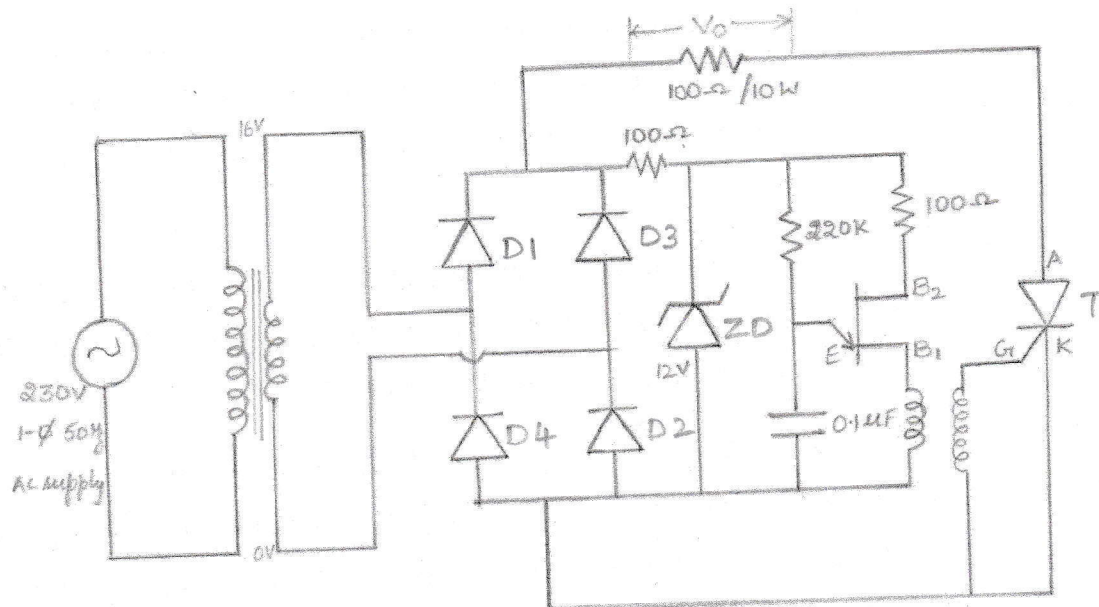


Fig 2.2

TABULAR COLUMN:

S.No.	Firing angle (α)	Load voltage (V)

2. c) UJT TRIGGERING CIRCUIT

AIM: To study triggering control of SCR using UJT triggering circuit.

THEORY:

Uni Junction Transistor (UJT) is a three terminal device with two bases (B_1 and B_2) and an Emitter (E) as shown in fig 2.1. Output pulses of variable time period are possible by suitably increasing the emitter to base voltage from valley voltage level to peak level either by employing a constant current source or by charging a capacitor by a resistor. The RC network can be easily employed to obtain output pulses, since the time period is fixed by RC circuit through the capacitor voltage V_C . The output pulses derived from the capacitor can be observed in fig 2.2.

 


Fig 2.1: UJT Symbol, Structure and simplified equivalent circuit

In phase controlled rectifier circuit, trigger pulses to SCR must be synchronized or phase locked with the AC supply frequency. This helps constant DC output voltage across the load for a specified triggering angle. On the other hand, if synchronization or phase locking is not achieved, then even for a minute variation in AC supply frequency, triggering angle of SCR varies from instant to instant, resulting in variation in DC output voltage across the load. To overcome this problem, the supply voltage to UJT circuit is derived from the AC mains using step down transformer, rectifier and Zener diode.



EXPECTED WAVEFORMS:

R - Triggering

 


Fig 2.5

RC Half-Wave Triggering

 


Fig 2.6

 
**RC Full-Wave Triggering**

Fig 2.7

 
UJT Triggering

Fig 2.8

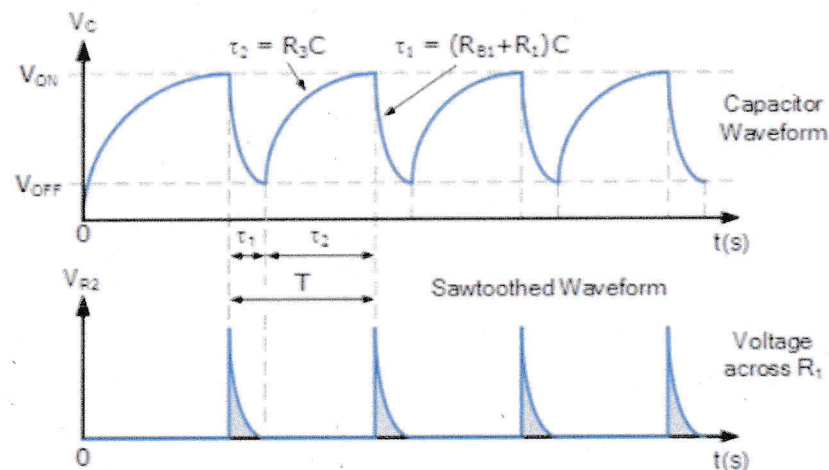


Fig 2.2: UJT Oscillator Waveforms

The rectifier circuit converts AC supply available at transformer secondary into full wave DC voltage. The DC voltage is clipped to the required DC voltage using a zener diode. The series resistance R_S limits the current through the zener diode. The clipped voltage V_Z is applied to the RC charging network and also to the UJT circuit. Depending on the resistance R and capacitance of C , trigger pulses can be obtained across isolation pulse transformer connected to base1. These pulses can be used to trigger SCRs. For SCRs of higher rating, this small pulse is amplified using a pulse amplifier and then by connecting across gate and cathode of the SCR.

APPARATUS:

1. SCR Triggering module.
2. C.R.O.
3. Patch cords.
4. Multimeter.

PROCEDURE:

1. Make the connections as per the circuit diagram.
2. Switch ON the module.
3. Set the potentiometer to a particular position and observe the waveforms of V_{IN} , V_O , V_T , V_C on the C.R.O. and note down the corresponding waveforms.
4. Vary the potentiometer in steps and note down the corresponding load voltage using multimeter.

RESULT: The UJT triggering circuit to trigger an SCR is connected and the phase control of SCR using UJT is studied.

SINGLE PHASE AC VOLTAGE CONTROLLER.

CIRCUIT DIAGRAM:

 


Fig 3.1

3. SINGLE PHASE AC VOLTAGE CONTROLLER WITH R AND RL LOADS

AIM: To obtain the output of Single phase AC Voltage Controller with R & RL load by implementing phase control technique.

THEORY:

AC Voltage Controller converts fixed alternating voltage to variable alternating voltage without change in frequency. The output of AC Voltage controller is controlled by Phase control technique. AC Voltage controller can be constructed using two antiparallel connected SCRs or a TRIAC. The arrangement of SCRs and TRIAC for the respective circuits can be understood from the following circuits.

 


Fig 3: Single Phase AC Voltage Controllers with anti parallel SCRs and TRIAC

In the first circuit with two antiparallel SCRs, T1 conducts for the positive half cycle and T2 conducts for negative half cycle.

In the second circuit, TRIAC conducts for both the half cycles of AC supply. Therefore, for the firing angle α symmetrical AC voltage is available across the load. The load voltage is given by

$$V_O = \frac{V_m}{\sqrt{2}} \left[\frac{1}{\pi} \left\{ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right\} \right]^{\frac{1}{2}}$$

The voltage control of AC Voltage controller can be done by simply adjusting the firing angle of the SCRs or TRIAC by using phase control. The output can be controlled from 0 to maximum value for both the half cycles.

APPARATUS:

1. Single Phase AC Voltage Controller Unit.
2. Loading Rheostat (50Ω/2A)
3. Loading Inductor (0-150 mH / 2A)
4. Digital Multimeter.
5. C.R.O.
6. Patch cords.

**TABULAR COLUMN:****For R Load:** $V_m = \underline{\hspace{2cm}}$ Volts

S.No.	Firing Angle α (deg)	$V_L(V)$
1	180	
2	150	
3	120	
4	90	
5	60	
6	30	
7	0	

For RL Load : $V_m = \underline{\hspace{2cm}}$ Volts.

S.No.	Firing Angle α (deg)	$V_L(V)$
1	180	
2	150	
3	120	
4	90	
5	60	
6	30	
7	0	



EXPECTED WAVE FORMS :

 


Fig 3.2



PROCEDURE:

1. Connect the circuit as per the circuit diagram.
2. Switch ON the mains supply to the unit.
3. The firing angle of the switching circuit can be varied in steps and the corresponding firing angle, Input voltage, Output voltage, SCR/TRIAC Voltage waveforms can be recorded from the C.R.O.
4. The load voltage is measured using a multimeter.
5. Then connect an Inductive load in series to the resistive load.
6. Repeat the above steps for AC Voltage controller with RL Load.

RESULT: The operation of a Single Phase AC Voltage Controller is observed and its control is output waveforms are obtained for R & R L Loads.

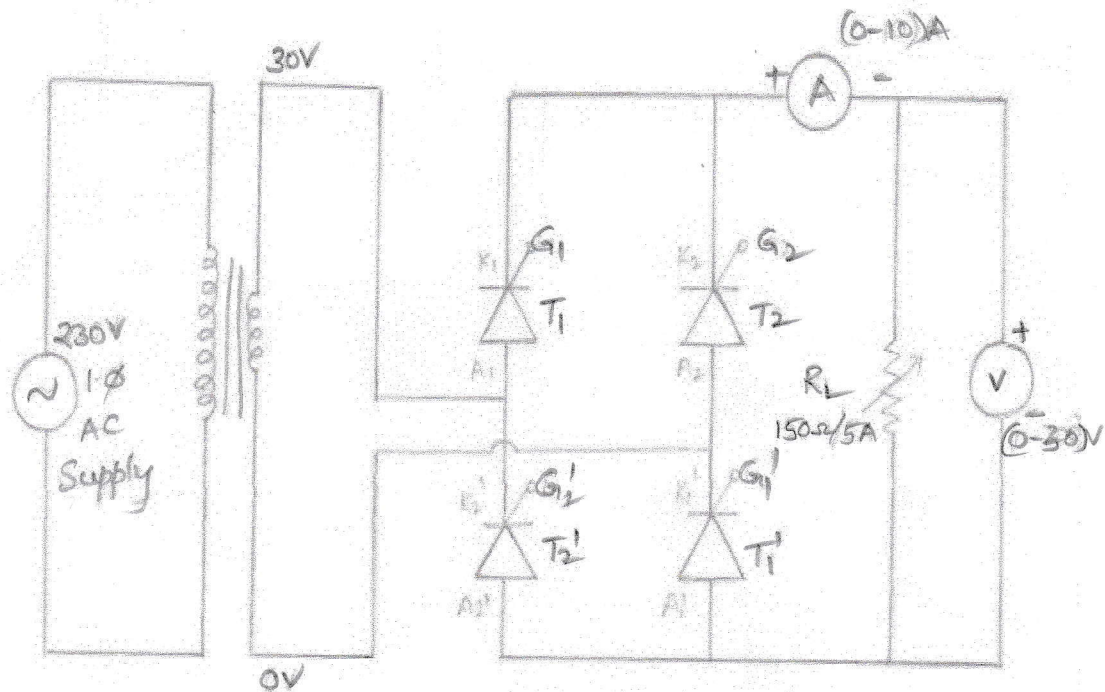
**SINGLE PHASE FULLY CONTROLLED BRIDGE CONVERTER.****CIRCUIT DIAGRAM:**

Fig 4.1



4. SINGLE PHASE FULLY CONTROLLED BRIDGE CONVERTER WITH R & RL LOADS

AIM: To obtain the output of Single phase Single Phase fully controlled converter with R & RL loads.

THEORY:

A Single Phase fully controlled converter converts Single phase AC supply to DC Supply.

The circuit of the converter is as shown in the circuit diagram.

 


Fig 4.1: Single Phase Fully Controlled Converter

Full Controlled Bridge Converter with R Load:

During positive half cycle, thyristors T_1 and T_2 are triggered simultaneously through independent isolated pulse transformers. The pair of SCR's conduct up to π . SCR T_3 & SCR T_4 are triggered in the next half cycle with another pair of isolated pulse transformers.

Full Controlled Bridge Converter with RL load :

During positive half cycle, thyristors T_1 & T_2 are forward biased and when these 2 thyristors are fired simultaneously, at $\omega t = \alpha$. the load is connected to the input supply through T_3 & T_4 . Due to inductive load, T_1 & T_2 will continue to conduct beyond $\omega t = \pi$, even though the input voltage is already negative. During negative half-cycle of the input voltage, thyristor T_3 & T_4 are forward biased, and firing of thyristors T_3 & T_4 will apply the supply voltage across the load. Due to inductive load, T_3 & T_4 will continue to conduct beyond $\omega t = 2\pi$, even though the input voltage is already positive.

During the period from α to π , the input voltage V_s and input current are positive and the current flows from the supply to the load. The converter is said to be operated in rectification mode. During the period from π to $\pi + \alpha$, the input voltage V_s is negative and the

**TABULAR COLUMN:****For R Load:**

$V_m = \underline{\hspace{2cm}}$ Volts.

S.No.	Firing Angle α (deg)	V_L (V)	I_L (A)	$V_L = \frac{V_m(1+\cos\alpha)}{\pi}$
1	180			
2	150			
3	120			
4	90			
5	60			
6	30			
7	0			

For R_L Load:

$V_m = \underline{\hspace{2cm}}$ Volts.

S.No.	Firing Angle α (deg)	V_L (V)	I_L (A)	$V_L = \frac{V_m(1+\cos\alpha)}{\pi}$
1	180			
2	150			
3	120			
4	90			
5	60			
6	30			
7	0			



EXPECTED WAVEFORMS:

 


Fig 4.2



input current I_s is positive and there will be reverse power flow from the load to the supply. The converter is said to be operated in inversion mode.

APPARATUS:

1. Single phase fully controlled bridge converter power unit
2. Single phase fully controlled bridge converter firing unit
3. Single phase Isolation transformer (0-230)V/5A with tapings.
4. Loading Rheostat - $150\Omega/5A$.
5. Inductor – 150 mH / 5A
6. C.R.O.
7. Patch cords.

PROCEDURE:

1. Make the connections as per the circuit diagram.
2. Switch on the Power Supplies of the main circuit and switching circuit.
3. Vary the firing angle in steps and record output voltage, thyristor voltage waveforms.
4. Note down the output voltage & output current from the voltmeter and ammeter.
5. Repeat the same procedure after connecting L load in series with the R load.

RESULT: The output of Single phase Single Phase fully controlled converter with R & RL loads is obtained and studied.



D. C. JONES CHOPPER

CIRCUIT DIAGRAM:

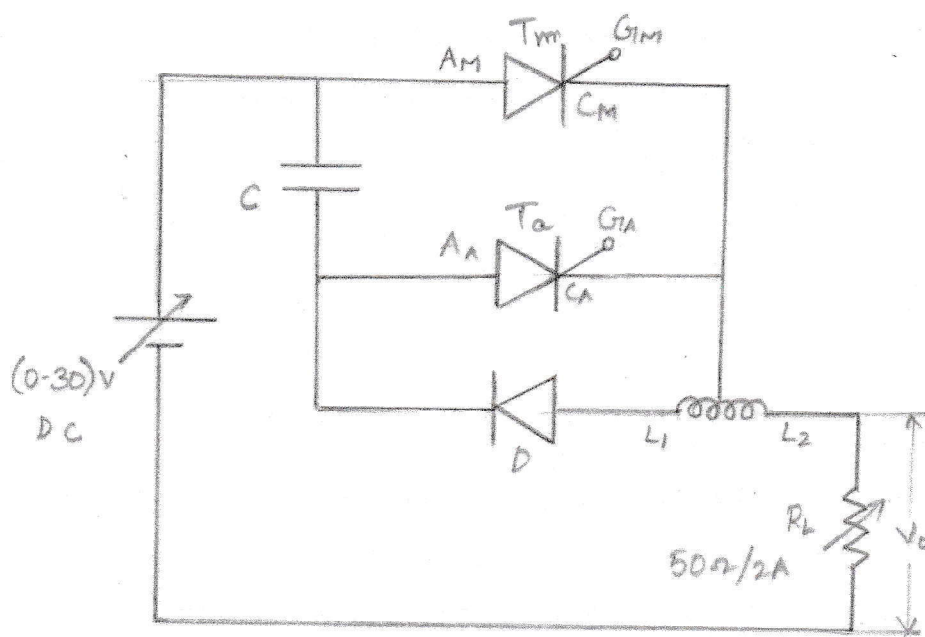


Fig 5.1

5. DC JONES CHOPPER WITH R & RL LOADS

AIM: To obtain the output of DC Jones Chopper with R and RL Load.

THEORY:

Chopper converts fixed DC Voltage to variable DC voltage. The control strategies used for control of DC DC choppers are Time Ratio Control and Current Limit Control.

Chopper circuit consists of a thyristor switch connected between the source and the load. The switch is closed & opened periodically such that the load is connected and disconnected from the supply alternatively. Thus the average voltage impressed on the load is controlled by controlling the ratio of ON state interval to one cycle duration.

The average output voltage of the chopper is given by

$$V_{avg} = \left(\frac{T_{ON}}{T} \right) V$$

Where V is input voltage, T_{ON} is ON time duration of the chopper. The ratio T_{ON} / T is called the duty ratio of the chopper. The duty ratio can be controlled in many ways such as by changing the ON period duty ratio by keeping frequency constant or by changing frequency and keeping ON period constant. Fixed frequency choppers with a variable ON period technique are generally used because of less harmonic contents.

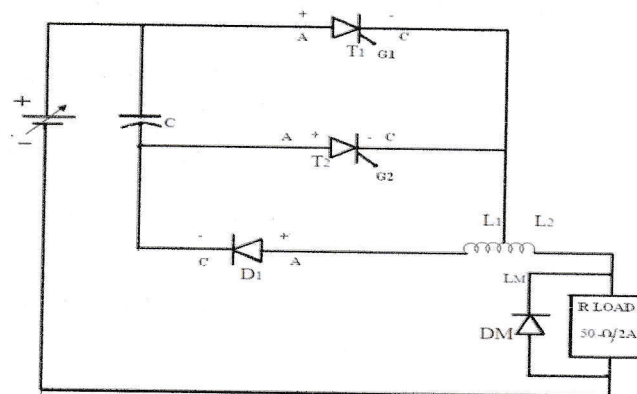


Fig 5.1: DC Jones Chopper

The Jones chopper circuit uses a Class-D commutation circuit. Here, an auxiliary thyristor is used to turn OFF the main SCR T_M. It is assumed that the capacitor C is initially charged to voltage with the polarity shown. When T_M is turned ON, the capacitor is discharged through it and through the inductor L. At the end of discharge cycle, the capacitor voltage will reverse and will be held by diode D to stay with this polarity when T_A is fired, the capacitor will discharge through T_M and will turn it OFF. Since a reverse voltage is applied across the

**TABULAR COLUMN :**

Frequency : _____

S.No.	Duty Ratio	T _{ON}	T _{OFF}	Load Voltage (V)

Duty Ratio : _____

S.No.	Frequency (Hz)	T _{ON} (ms)	T _{OFF} (ms)	Load Voltage (V)



TM immediately after turning ON the SCR, this phenomenon is known as Voltage Commutation.

APPARATUS:

1. Chopper power module
2. Chopper firing unit
3. Regulated Power supply (0-30)V
4. Loading Rheostat ($50\Omega/2A$)
5. Inductor – 50 mH /2A
6. Multimeter.
7. CRO
8. Patch cords

PROCEDURE:

1. Make the connections as per the circuit diagram with R Load.
2. Keep the frequency knob and duty ratio knob at some intermediate position.
3. Set the DC power supply to 30V & switch ON the DC power supply to the chopper and the firing circuit.
4. Observe V_O , V_{T1} , V_{T2} , V_{P1} , V_{P2} , V_C waveforms on the CRO and note down the corresponding waveforms.
5. Keeping the frequency constant, vary the duty cycle in steps & note down T_{ON} , T_{OFF} and load voltage for each step.
6. Repeat the above step by varying frequency and keeping duty ratio constant.
7. Connect RL load and note down the output voltage V_O & repeat the above procedure.

NOTE:

1. At lower frequencies, SCR may not turn ON due to insufficient voltage across the capacitor.
2. If the duty cycle is increased to large value, SCR may not turn OFF due to insufficient voltage across the capacitor to commutate the SCR. In such cases, switch OFF the kits and after some time switch ON and continue the procedure.

RESULT: The output of Single Phase Jones Chopper circuit and its operation is studied.

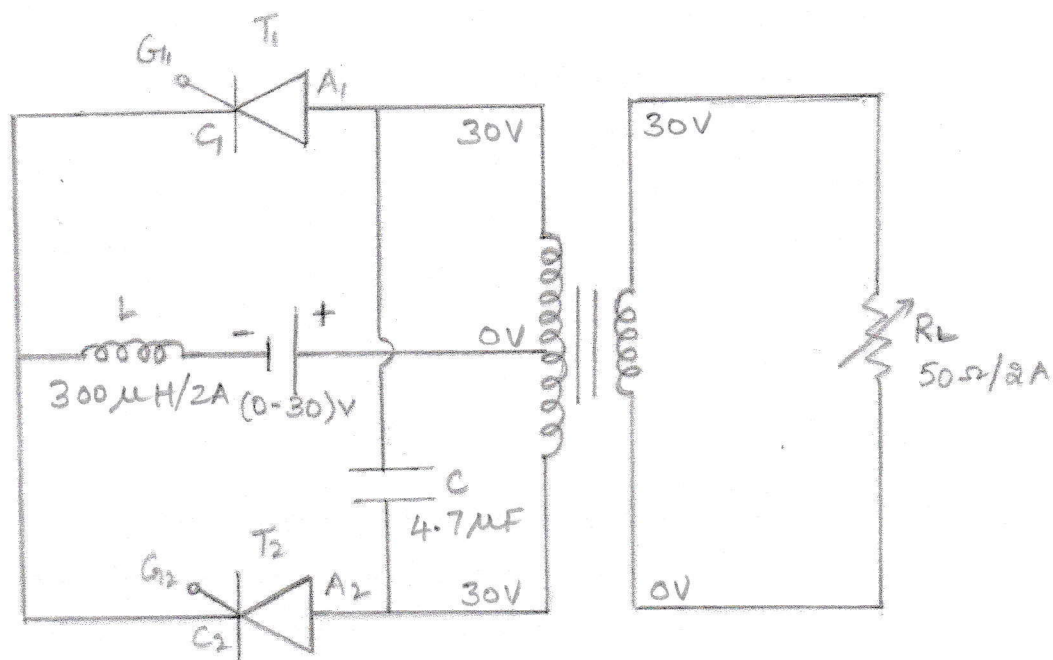
**SINGLE PHASE PARALLEL INVERTER****CIRCUIT DIAGRAM :**

Fig 6.1



6. SINGLE PHASE PARALLEL INVERTER

AIM: To obtain the output of Single phase Parallel Inverter and study its operation with R & RL load.

THEORY:

An Inverter converts DC power into AC power at desired output voltage and frequency.

 


Fig 6.1 Parallel Inverter

In Single Phase Parallel Inverter, the capacitor is used for commutation of two thyristors T_1 & T_2 . An inductor is connected in series with the supply voltage because the source current becomes constant. During the operation of this inverter circuit, commutating capacitor C comes in parallel due to this, it is called Parallel Inverter.

In mode 1 operation, when SCR T_1 is fired, the current flows in the upper half of the primary winding. Here, SCR T_2 is OFF. This current produces magnetic flux which links with both the halves of the primary winding. Due to this, the capacitor charges to the voltage V_{DC} with upper plate positive w.r.t. lower plate.

In mode 2 operation, when SCR T_2 is triggered, the capacitor starts discharging with upper plate negative. Then T_1 gets into OFF state. Based on capacitor charging and discharging, the SCRs get into OFF and ON states with positive and negative output voltages. When the capacitor current decays to zero, the capacitor voltage becomes $+2V_{DC}$. The same process is repeated for next cycle.

APPARATUS:


1. Parallel Inverter Module.
2. Regulated Power supply(0-30)V

**TABULAR COLUMN :****R Load**

S.No.	Frequency (Hz)	Output Voltage (V)

RL Load

S.No.	Frequency (Hz)	Output Voltage (V)

 



3. Loading Rheostat ($50\Omega/2A$)
4. Inductor – 50 mH /2A
5. Digital Multimeter.
6. Patch cords.
7. CRO.

PROCEDURE:

1. Make the connections as per the circuit diagram.
2. Adjust the DC supply to 15V and Switch ON the Main unit and the firing unit.
3. Set the frequency at a particular value and observe the load voltage waveform $V_O, V_{T1}, V_{T2}, V_{P1}, V_{P2}, V_C$ on CRO and note down the corresponding waveforms.
4. By changing the frequency, note down the output AC voltage using a multimeter.
5. Connect the RL load and repeat the same procedure

NOTE:

1. At lower frequencies SCR may not turn ON due to insufficient voltage across the capacitor. Hence adjust the frequency to a higher value (approximately above 100 Hz).
2. For commutation failure switch OFF the firing circuit as well as power circuit and switch it ON again.

RESULT: The output of Single Phase Parallel Inverter is observed and studied.

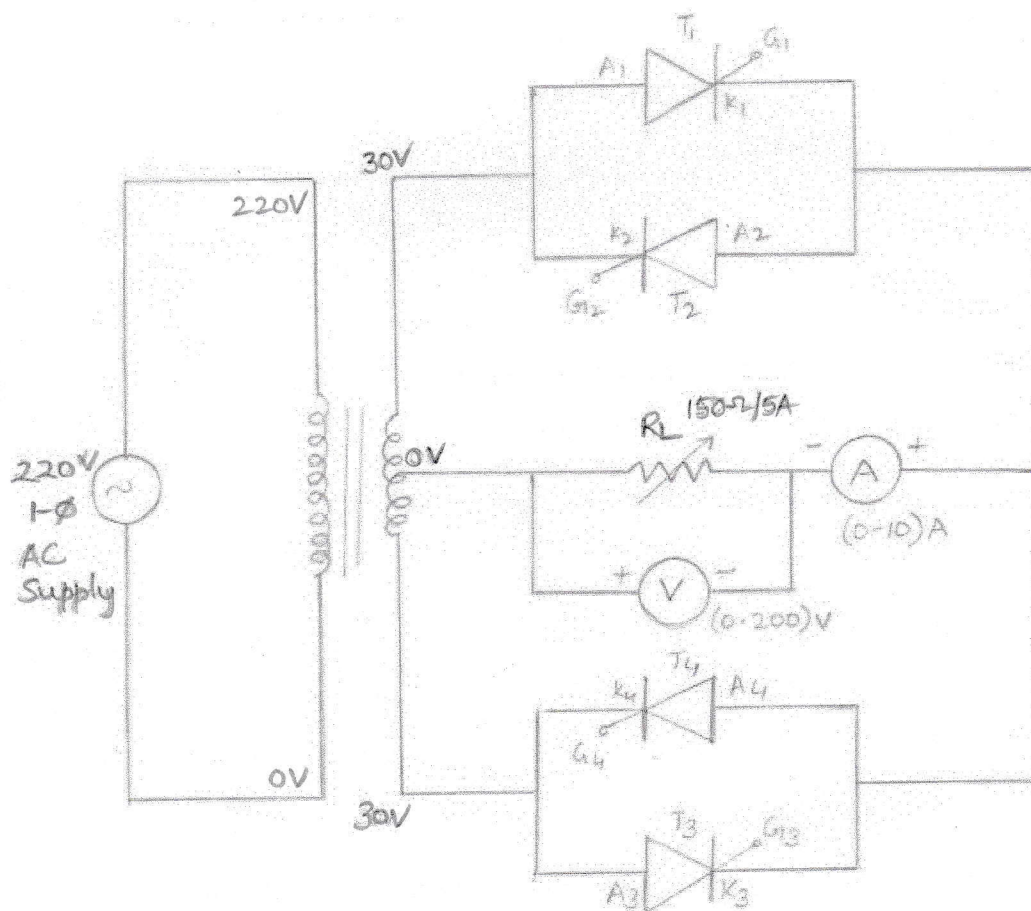
**SINGLE PHASE CYCLO CONVERTER.****CIRCUIT DIAGRAM:**

Fig 7.1

7. SINGLE PHASE CYCLO CONVERTER

AIM: To obtain the output of Single Phase Cyclo Converter circuit and to study its operation with R and RL loads.

THEORY:

Cyclo converter converts input power at one frequency to output power at a different frequency. Cyclo Converters are used in speed control of high power AC drives, induction heating etc.

 


Fig 7.1: Single Phase Cyclo converter

The Single Phase Cycloconverter circuit is as shown above. The following sequence of operation can be followed. One group of SCR's produces positive polarity load voltage and other group produces negative half cycle of the output. SCR's P1 & N2 of the positive group are gated together depending on the polarity of the input. Only one of them is allowed to conduct when 'a' is positive with respect to 'O'. SCR's N1 & P2 of the negative group are gated together depending on the polarity of the input. Only one of them is allowed to conduct when 'b' is positive with respect to 'O'. By triggering the respective SCR during negative or positive half cycles, any of the half cycle can be achieved at the load side. The order of switching sequence decides the frequency of Cyclo converter.

APPARATUS:

1. Cycloconverter Power unit.
2. Cycloconverter firing unit.

**TABULAR COLUMN:****For R Load:** $V_m = \underline{\hspace{2cm}}$ Volts.

S.No.	Frequency	V_L (V)
1		
2		
3		
4		
5		
6		
7		

For RL Load : $V_m = \underline{\hspace{2cm}}$ Volts.

S.No.	Frequency	V_L (V)
1		
2		
3		
4		
5		
6		
7		



EXPECTED WAVEFORMS :

 


Fig 7.2



3. Single Phase Isolation transformer (center tapped)
4. Loading Rheostat - $150\Omega/2A$
5. Inductor – (0-150 mH / 5A
6. Digital Multimeter.
7. C.R.O.
8. Patch cards.

PROCEDURE:

1. Make the connections as per the circuit diagram.
2. Switch ON the power unit and the firing unit .
3. Set the frequency division to 2., note down the waveform across the load V_o and note down the output voltage and current readings from the voltmeter and the ammeter.
4. Note down the output voltage waveform for different frequency divisions and note down the output voltages and currents.
5. Now connect RL load.
6. Repeat the above steps for Cyclo Converter with RL load.

RESULT: The output and operation of Single Phase Cycloconverter with R & RL load is observed.

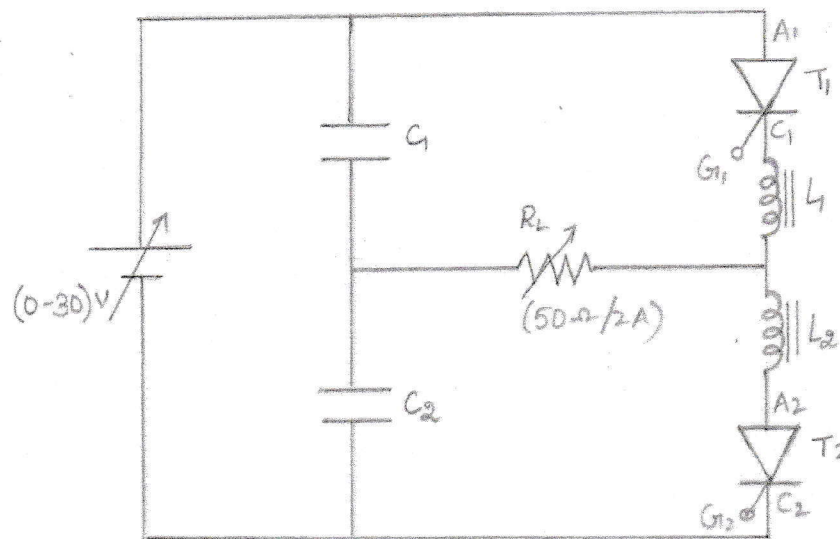
**SINGLE PHASE SERIES INVERTER****CIRCUIT DIAGRAM :**

Fig 8.1



8. SINGLE PHASE SERIES INVERTER

AIM: To obtain the output of Single phase Series Inverter circuit with R and RL Load and study its operation.

THEORY:

In Series Inverter, commutating components are permanently connected in series with the load. Series Inverters are also classified as self-commutated inverters & Load commutated Inverters.

 


Fig 8.1: Series Inverter

This circuit consists of load resistance R in series with commutating components L & C . The values of L & C are so chosen that the series RLC circuit forms an under damped circuit. Two thyristors T_1 and T_2 are turned on appropriately so that output voltage of desired frequency can be obtained.

When thyristor T_1 is turned ON with T_2 OFF, current starts building up in the RLC circuit. As the circuit is under damped, the load current after reaching peak value, decays to zero. After thyristor T_1 has commuted, upper plate of capacitor attains positive polarity. Now, when T_2 is turned ON, capacitor discharges and load current flows in reverse direction up to some peak negative value and then decays to zero. The capacitor stores charge during one half cycle and releases the same amount of charge during next half cycle.

APPARATUS:

1. Series Inverter unit
2. Loading Rheostat - $50\Omega/2A$
3. Regulated Power supply (0-30)V

**TABULAR COLUMN:****R Load**

S.NO.	Time Period (ms)	Frequency (Hz)	Output voltage (V)

RL Load

S.NO.	Time Period (ms)	Frequency (Hz)	Output voltage (V)



EXPECTED WAVEFORMS :

 


Fig 8.1



4. Inductor – 50 mH / 2A
5. Multimeter.
6. Patch cords
7. CRO

PROCEDURE:

1. Make the connections as per the circuit diagram with R Load.
2. Adjust the DC supply voltage to 30 V and Switch ON the DC power supply and the firing unit.
3. Set the frequency at a particular position and observe the output waveform $V_O, V_{T1}, V_{T2}, V_{P1}, V_{P2}, V_{C1}, V_{C2}$ on the CRO and note down the corresponding waveforms.
4. By varying the frequency in steps, note down the AC output voltage using multimeter.
5. Connect RL load and note down the output voltage V_O and repeat the same procedure.

NOTE: In case of Commutation failure, switch OFF the power module and the firing unit and again switch it ON.

RESULT: The output of Single Phase Series Inverter and its operation with R & RL load is observed and studied.



SINGLE PHASE HALF CONTROLLED CONVERTER

CIRCUIT DIAGRAM:


 


Fig 9.1

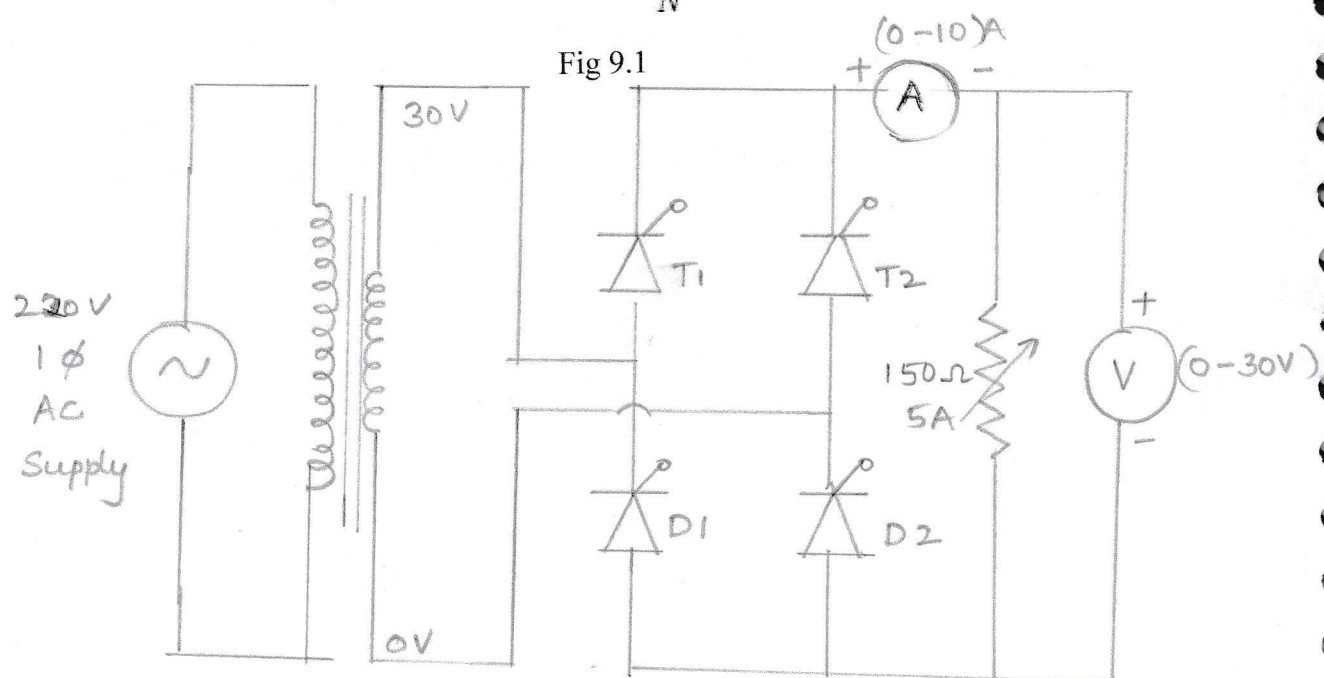

9. SINGLE PHASE HALF CONTROLLED CONVERTER

AIM: To obtain the output of Single phase Half Controlled Bridge Converter and study the operation.

THEORY:

 


Fig 9.1: Single Phase Half controlled Converter

The Single Phase Half controlled Converter circuit consists of two SCR's and two diodes. During the positive half cycle, the SCR T_1 and diode D_2 conduct when triggered at firing angle α . T_1 and D_2 conducts from α to π . For negative Half cycle, the SCR T_2 and diode D_1 conducts from $\pi + \alpha$ to 2π .

This converter will not allow negative voltage across the load as it turns off soon after the diode gets reverse biased. It has better power factor due to this reason and is commonly used in application up to 15KWatts and it has lot of advantages compare to fully controlled converter like low cost, good power factor and low load current ripple. Some of the disadvantages are higher harmonic content in the source current and since the output voltage cannot be made negative, inverter operation is not possible.

APPARATUS:

1. Single phase Half controlled Bridge Converter power circuit.
2. Single phase Converter firing circuit.
3. Single phase Isolation transformer 230V/2A
4. R Load – 50 ohms / 2Amps.



TABULAR COLUMN:

S.No	Input Voltage (V_{in})	Firing angle(α)	Output voltage(V)	Output Current



5. L Load

6. CRO

PROCEDURE:

1. Switch ON the Mains Supply to the Firing circuit. Observe all the test points by varying the firing angle and trigger outputs ON/OFF switch.
2. Switch ON the main circuit supply and firing circuit and note down the voltage wave forms across load and devices for firing angle zero.
3. Note down the wave forms across load and devices for different firing angles.
4. Repeat the same procedure for different firing angles.
5. Repeat the same for R-L load with and without freewheeling diode and note down the wave forms.

RESULT : The operation of single phase Half controlled converter and wave forms for different firing angles are observed.

SINGLE PHASE FULL CONVERTER USING RL and E LOAD

CIRCUIT DIAGRAM:


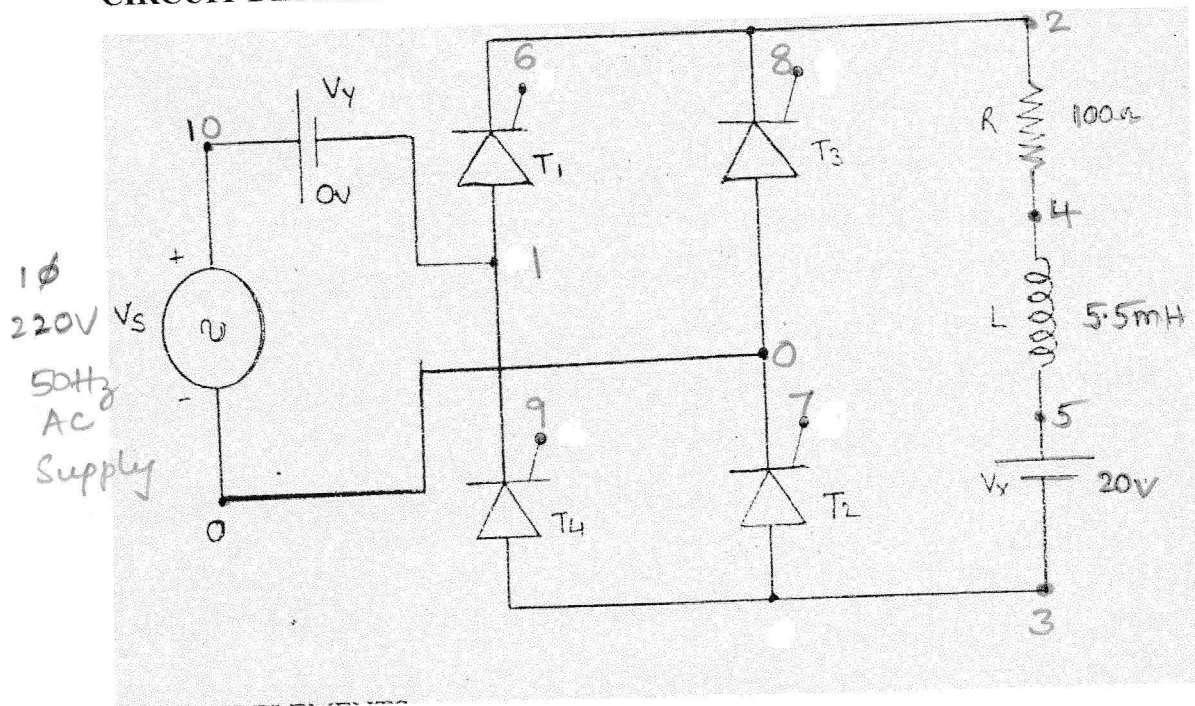


Fig 10.1

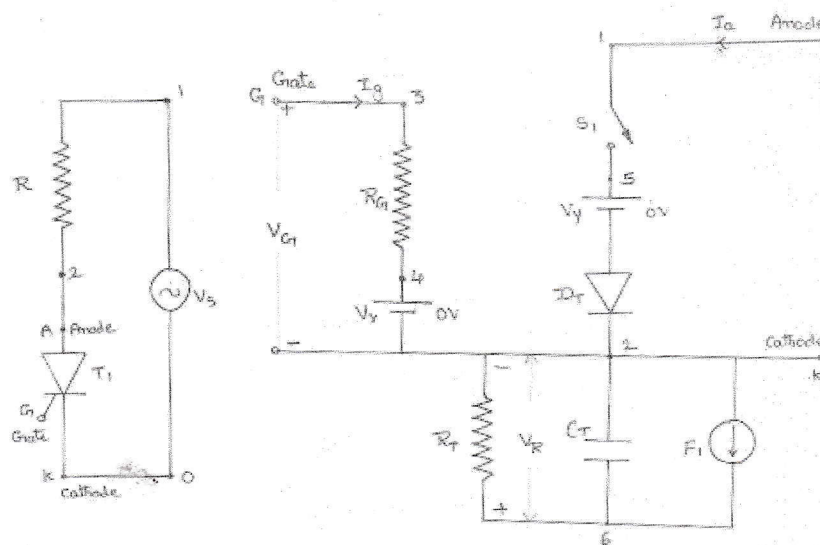

(a) Thyristor Circuit

(b) Thyristor model

SPICE Thyristor model

Fig 10.2



10. SIMULATION OF SINGLE-PHASE FULL CONVERTER USING RLE LOADS AND SINGLE-PHASE AC VOLTAGE CONTROLLER USING RLE LOADS.

a) SINGLE PHASE FULL CONVERTER USING RL AND E LOAD

AIM: To simulate single phase full converter using PSPICE and obtain its output.

APPARATUS: Computer and PSPICE Software

THEORY:

PSpice A/D is a simulation program that models the behaviour of a circuit containing any mix of analog and digital devices. Because the analog and digital simulation algorithms are built into the same program, PSpice A/D simulates mixed-signal circuits with no performance degradation because of tightly coupled feedback loops between the analog and digital sections.

PSpice A/D can perform DC, AC, and transient analyses, so the response of a circuit to different inputs can be tested. The range of models built into PSpice A/D include resistors, inductors, capacitors, and bipolar transistors, diodes and different types of sources.

.TRAN (transient analysis)

Purpose: The .TRAN command causes a transient analysis to be performed on the circuit and specifies the time period for the analysis.

General form .TRAN[/OP] +[no-print value [step ceiling value]][SKIPBP]

Examples .TRAN 1ns 100ns

.TRAN/OP 1ns 100ns 20ns SKIPBP

.TRAN 1ns 100ns 0ns .1ns

.TRAN 1ns 100ns 0ns {SCHEDULE(0,1ns,25ns,.1ns)}

.PROBE (Probe)

Purpose: The .PROBE command writes the results from DC, AC, and transient analyses to a data file used by Probe.

General form .PROBE[/CSDF][output variable]

Examples .PROBE .PROBE V(3) V(2,3) V(R1) I(VIN) I(R2) IB(Q13) VBE(Q13)

OPTIONS (analysis options)

Purpose: The .OPTIONS command is used to set all the options, limits, and control parameters for the simulator.

General form .OPTIONS [option name]* [<option name>= <value>]*



OUTPUT WAVE FORMS: -

 


Fig 10.3

Supply
Voltage

Load
voltage

Load
Current

Source
Current



FOURIER COMPONENTS OF TRANSIENT RESPONSE I(VY)

DC COMPONENT = -2.420296E-07

HARMONIC NO	FREQUENCY (HZ)	FOURIER COMPONENT	NORMALIZED COMPONENT (DEG)	PHASE (DEG)	NORMALIZED PHASE (DEG)
1	5.000E+01	2.495E+00	1.000E+00	-1.632E+01	0.000E+00
2	1.000E+02	5.052E-07	2.025E-07	1.474E+02	1.801E+02
3	1.500E+02	7.715E-01	3.092E-01	1.474E+02	1.963E+02
4	2.000E+02	4.720E-07	1.892E-07	3.130E+01	9.656E+01
5	2.500E+02	4.018E-01	1.610E-01	5.824E+01	1.398E+02
6	3.000E+02	5.385E-07	2.158E-07	-9.582E+01	2.072E+00
7	3.500E+02	1.976E-01	7.917E-02	-7.201E+01	4.220E+01
8	4.000E+02	4.328E-07	1.735E-07	1.469E+02	2.774E+02
9	4.500E+02	2.010E-01	8.054E-02	1.616E+02	3.085E+02

TOTAL HARMONIC DISTORTION = 3.664522E+01 PERCENT

JOB CONCLUDED

TOTAL JOB TIME .27 Sec

**OUTPUT:**

*****Diode

MODEL

PARAMETERS*****

	XT1.DMOD	XT2.DMOD	XT3.DMOD	XT4.DMOD
IS	2.200000E-15	2.200000E-15	2.200000E-15	2.200000E-15
BV	1.200000E+03	1.200000E+03	1.200000E+03	1.200000E+03

*****Voltage

Controlled

Switch

MODEL

PARAMETERS*****

	XT1.SMOD	XT2.SMOD	XT3.SMOD	XT4.SMOD
RON	.0105	.0105	.0105	.0105
ROFF	1.000000E+06	1.000000E+06	1.000000E+06	1.000000E+06
VON	.5	.5	.5	.5
VOFF	0	0	0	0

*****INITIAL TRANSIENT SOLUTION TEMPERATURE = 27.000 DEG C

NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE
 (1) 0.0000 (2) 10.0000 (3) -9.9998 (4) 10.0000
 (5) 10.0000 (6) 10.0000 (7) 0.0000 (8) 10.0000
 (9) 0.0000 (10) 0.0000 (XT1.4) 10.0000 (XT1.5) 10.00E-06
 (XT1.6) 10.0000 (XT1.7) 10.00E-06 (XT2.4) 0.0000 (XT2.5) -9.9998
 (XT2.6) -110.0E-12 (XT2.7) -9.9998 (XT3.4) 10.0000 (XT3.5) 10.00E-06
 (XT3.6) 10.0000 (XT3.7) 10.00E-06 (XT4.4) 0.0000 (XT4.5) -9.9998
 (XT4.6) -110.0E-12 (XT4.7) -9.9998

VOLTAGE SOURCE CURRENTS

NAME CURRENT

VS	4.163E-16
VG1	0.000E+00
VG2	0.000E+00
VG3	0.000E+00
VG4	0.000E+00
VX	-2.000E-11
VY	-4.163E-16
XT1.VX	0.000E+00
XT1.VY	-1.000E-11
XT2.VX	0.000E+00
XT2.VY	-1.000E-11
XT3.VX	0.000E+00
XT3.VY	-1.000E-11
XT4.VX	0.000E+00
XT4.VY	-1.000E-11

TOTAL POWER DISSIPATION 4.00E-10 WATTS

*****FOURIER ANALYSIS TEMPERATURE = 27.000 DEG C

**PROCEDURE:**

1. Write the Program in PSPICE .cir file or in .txt file, by identifying nodes in the circuit.
2. Save the program and run it in PSPICE A/D.
3. Observe the Output file for outputs like nodal voltages, source currents and power dissipated.
4. Open probe and enter the waveforms to be plotted and get the plots.
5. Note down the plots in graph sheets and verify it with theoretical values.

PROGRAM:

```
*****SINGLE PHASE AC SUPPLY*****
VS 10 0 SIN(0 325V 50HZ)
*****MAIN CIRCUIT*****
VG1 6 2 PULSE(0V 10V 3333.33US 1NS 1NS 100US 20000US)
VG2 7 0 PULSE(0V 10V 3333.33US 1NS 1NS 100US 20000US)
VG3 8 2 PULSE(0 10V 13333.33US 1NS 1NS 100US 20000US)
VG4 9 1 PULSE(0 10V 13333.33US 1NS 1NS 100US 20000US)
*****LOAD*****
R 2 4 100OHM
L 4 5 5.5MH
VX 5 3 DC 20V
VY 10 1 DC 0V
*****SWITCHES*****
XT1 1 2 6 2 SCR

XT2 3 0 7 0 SCR
XT3 0 2 8 2 SCR
XT4 3 1 9 1 SCR
*****Begin of Sub circuit for SCR*****
.SUBCKT SCR 1 2 3 2
S1 1 5 6 2 SMOD
RG 3 4 50
VX 4 2 DC 0V
VY 5 7 DC 0V
DT 7 2 DMOD
RT 6 2 1
CT 6 2 10UF
F1 2 6 POLY(2) VX VY 0 50 11
.MODEL SMOD VSWITCH (RON=0.0105 ROFF=10E+5 VON=0.5V VOFF=0V)
.MODEL DMOD D(IS=2.2E-15 BV=1200V TT=0 CJO=0)
.ENDS SCR
*****End of Sub circuit for SCR*****
.TRAN 50US 100MS 30MS 50US
.OPTIONS ABSTOL=1.00N RELTOL=1.0M VNTOL=0.01 ITL5=20000
.FOUR 50HZ I(VY)
.PROBE
.END
```

RESULT: The response of single phase full wave bridge converter is verified using SPICE software.



10.b) SINGLE PHASE AC VOLTAGE CONTROLLER USING RL LOAD **CIRCUIT DIAGRAM:**


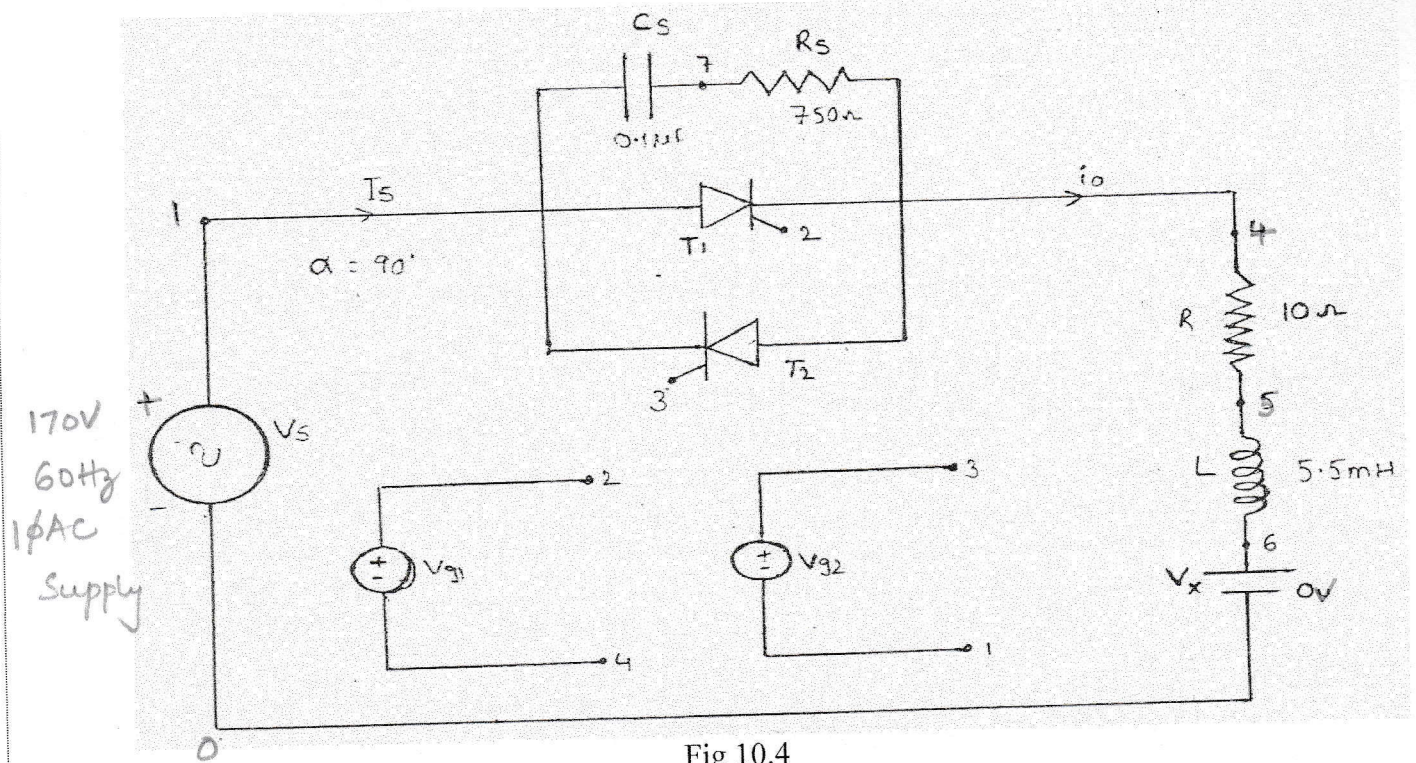


Fig 10.4

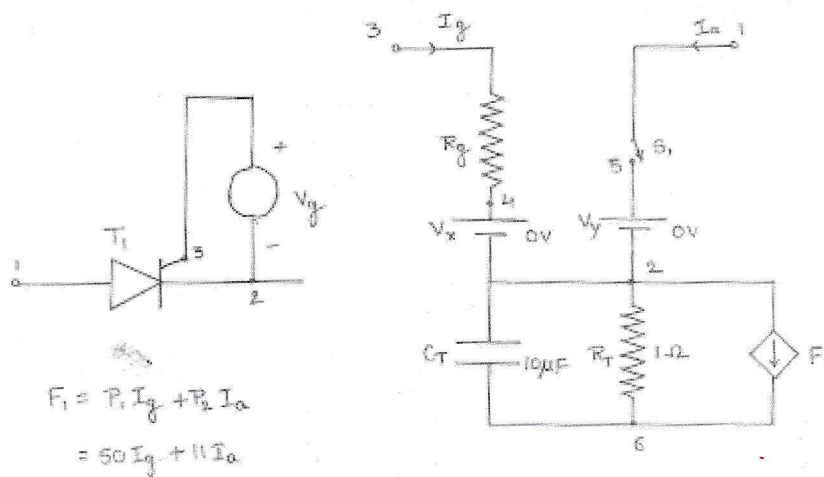


AC Thyristor SPICE model

Fig 10.5



OUTPUT WAVE FORMS: -

 

**OUTPUT:**

*****VOLTAGE CONTROLLED SWITCH MODEL
PARAMETERS*****

	XT1.SMOD	XT2.SMOD
RON	.01	.01
ROFF	1.000000E+06	1.000000E+06
VON	.1	.1
VOFF	0	0

*****INITIAL TRANSIENT SOLUTION TEMPERATURE = 27.000 DEG C

NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE
(1) 0.0000 (2) 0.0000 (3) 0.0000 (4) 0.0000
(5) 0.0000 (6) 0.0000 (7) 0.0000 (XT1.4) 0.0000

VOLTAGE SOURCE CURRENTS

NAME	CURRENT
VS	0.000E+00
VG1	0.000E+00
VG2	0.000E+00
VX	0.000E+00
XT1.VX	0.000E+00
XT1.VY	0.000E+00

TOTAL POWER DISSIPATION 0.00E+00 WATTS

*****FOURIER ANALYSIS TEMPERATURE = 27.000 DEG C

FOURIER COMPONENTS OF TRANSIENT RESPONSE V(4)

DC COMPONENT = -5.019307E-04

HARMONIC	FREQUENCY	FOURIER COMPONENT	NORMALIZED COMPONENT (DEG)	PHASE	NORMALIZED PHASE (DEG)P
NO	(HZ)				

1	6.000E+01	1.011E+02	1.000E+00	-1.788E+01	0.000E+00
2	1.200E+02	9.565E-04	9.459E-06	-8.191E+01	-4.614E+01
3	1.800E+02	6.167E+01	6.098E-01	6.883E+01	1.225E+02
4	2.400E+02	9.083E-04	8.982E-06	-6.561E+01	5.928E+00
5	3.000E+02	3.372E+01	3.335E-01	-6.876E+01	2.067E+01
6	3.600E+02	9.699E-04	9.591E-06	-5.180E+01	5.551E+01
7	4.200E+02	7.505E+00	7.421E-02	1.232E+02	2.484E+02
8	4.800E+02	1.003E-03	9.921E-06	-4.581E+01	9.727E+01
9	5.400E+02	1.308E+01	1.293E-01	-1.270E+02	3.397E+01

TOTAL HARMONIC DISTORTION = 7.108297E+01 PERCENT

JOB CONCLUDED

TOTAL JOB TIME .05 sec



.OPTIONS ABSTOL=1.00n RELTOL=1.0m VNTOL=1.0m ITL5=10000

.FOUR 60HZ V(4)

.END

RESULT: The response of single phase AC voltage controller is verified using SPICE software.



SIMULATION OF RESONANT PULSE COMMUTATION CIRCUIT

CIRCUIT DIAGRAM:

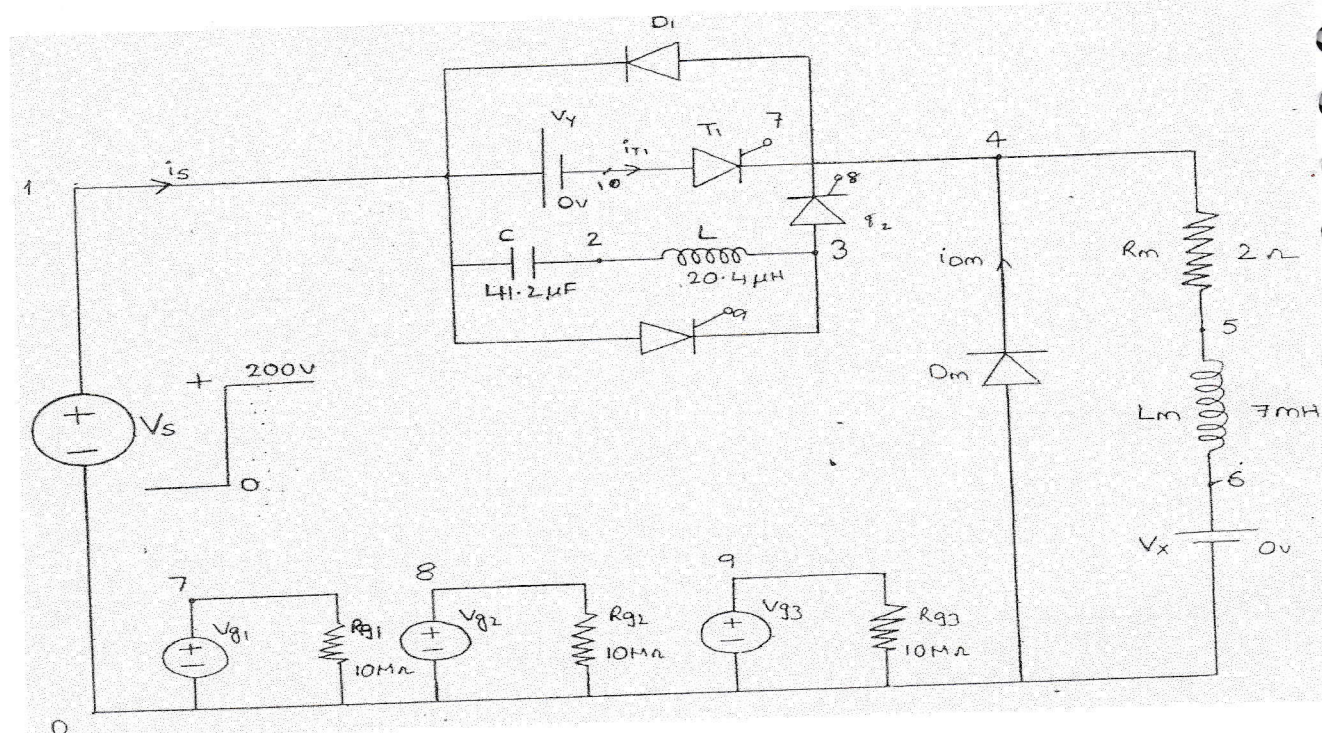


Fig 11.1



11. SIMULATION OF RESONANT PULSE COMMUTATION CIRCUIT

AIM: To simulate Resonant commutation using PSPICE and obtain its output.

APPARATUS: Computer and PSPICE software

PROCEDURE:

1. Write the Program in PSPICE .cir file or in .txt file, by identifying nodes in the circuit.
2. Save the program and run it in PSPICE A/D.
3. Observe the Output file for outputs like nodal voltages, source currents and power dissipated.
4. Open probe and enter the waveforms to be plotted and get the plots.
5. Note down the plots in graph sheets and verify it with theoretical values.

PROGRAM:

```
*****SINGLE PHASE AC SUPPLY*****
VS 1 0 DC 200V
*****MAIN CIRCUIT*****
VG1 7 0 PULSE(0V 100V 0 1US 1US 0.4MS 1MS)
VG2 8 0 PULSE(0V 100V 0.4MS 1US 1US 0.6MS 1MS)
VG3 9 0 PULSE(0V 100V 0 1US 1US 0.2MS 1MS)
*****LOAD*****
RG1 7 0 10MEG
RG2 8 0 10MEG
RG3 9 0 10MEG
L 2 3 20.4UH
C 1 2 41.2UF IC=200V
D1 4 1 DMOD
DM 0 4 DMOD
.MODEL DMOD D(IS=1E-25 BV=1000V)
RM 4 5 2
LM 5 6 7MH
VX 6 0 DC 0V
VY 1 10 DC 0V
*****SWITCHES*****
XT1 10 4 7 0 TMOD
XT2 3 4 8 0 TMOD
XT3 1 3 9 0 TMOD
*****Begin of Sub circuit for SCR*****
.SUBCKT TMOD 1 2 3 4
DT 5 2 DMOD
ST 1 5 3 4 SMOD
.MODEL DMOD D(IS=2.22E-15 BV=1200V CJO=0 TT=0)
.MODEL SMOD VSWITCH (RON=0.01 ROFF=10E+6 VON=10V VOFF=5V)
.ENDS TMOD
*****End of Sub circuit for SCR*****
.PROBE
.TRAN 1US 6MS 4MS
```




OUTPUT WAVE FORMS: -

 


Fig 11.2

**OUTPUT:**

MODEL

*****DIODE

PARAMETERS*****

	DMOD	XT1.DMOD	XT2.DMOD	XT3.DMOD
IS	100.000000E-27	2.220000E-15	2.220000E-15	2.220000E-15
BV	1.000000E+03	1.200000E+03	1.200000E+03	1.200000E+03

*****Voltage

Controlled

Switch

MODEL

PARAMETERS*****

	XT1.SMOD	XT2.SMOD	XT3.SMOD
RON	.01	.01	.01
ROFF	10.000000E+06	10.000000E+06	10.000000E+06
VON	10	10	10
VOFF	5	5	5

*****INITIAL TRANSIENT SOLUTION TEMPERATURE = 27.000 DEG C

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	200.0000	(2)	39.88E-09	(3)	39.88E-09	(4)	39.88E-06
(5)	0.0000	(6)	0.0000	(7)	0.0000	(8)	0.0000
(9)	0.0000	(10)	200.0000	(XT1.5)	.5928	(XT2.5)	40.31E-09
(XT3.5)	.5928						

VOLTAGE SOURCE CURRENTS

NAME CURRENT

VS	-1.994E-05
VG1	0.000E+00
VG2	0.000E+00
VG3	0.000E+00
VX	1.994E-05
VY	1.994E-05

TOTAL POWER DISSIPATION 3.99E-03 WATTS

JOB CONCLUDED

TOTAL JOB TIME .08 Sec



```
.OPTIONS ABSTOL=1.000U RELTOL=0.01 VNTOL=0.1 ITL5=20000  
.END
```

RESULT: The response of Resonant commutation circuit is verified using SPICE software.



SIMULATION OF SINGLE PHASE INVERTER WITH PWM CONTROL.

CIRCUIT DIAGRAM:

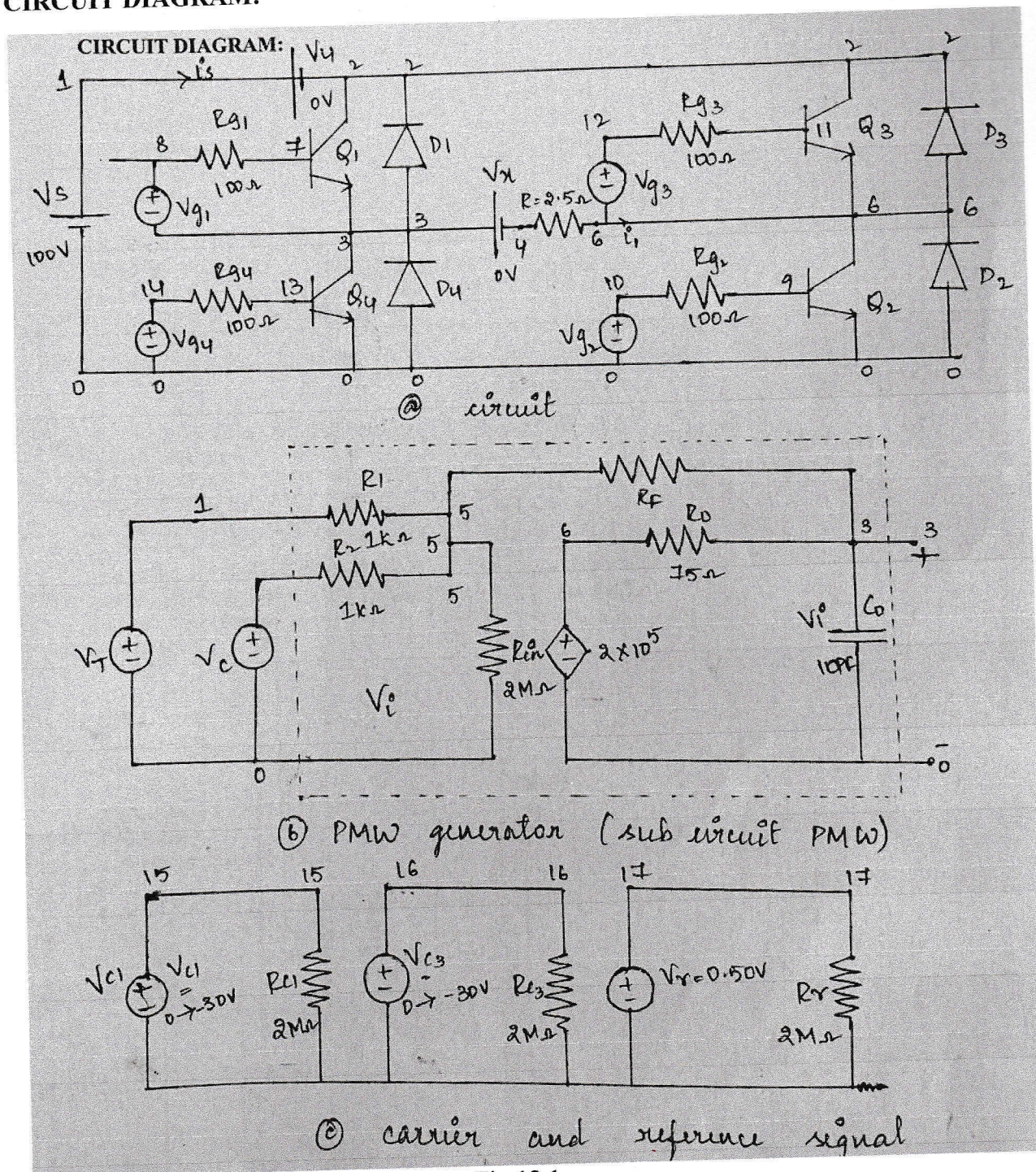


Fig 12.1



12. SIMULATION OF SINGLE PHASE INVERTER WITH PWM CONTROL.

AIM: To simulate single phase inverter with PWM controller using PSPICE and obtain its output.

APPARATUS: Computer and PSPICE software

PROCEDURE:

1. Write the Program in PSPICE .cir file or in .txt file, by identifying nodes in the circuit.
2. Save the program and run it in PSPICE A/D.
3. Observe the Output file for outputs like nodal voltages, source currents and power dissipated.
4. Open probe and enter the waveforms to be plotted and get the plots.
5. Note down the plots in graph sheets and verify it with theoretical values.

PROGRAM:

**** CIRCUIT DESCRIPTION : 1-PH PWM INVERTER


```
VS 1 0 DC 100V
VR 17 0 PULSE(50V 0V 0 1MS 1MS 1NS 2MS)
RR 17 0 2MEG
VC1 15 0 PULSE(0 -30V 0 1NS 1NS 10MS 20MS)
RC1 15 0 2MEG
VC3 16 0 PULSE(0 -30V 10MS 1NS 1NS 10MS 20MS)
RC3 16 0 2MEG
R 4 6 2.5OHM
VX 3 4 DC 0V
VY 1 2 DC 0V
D1 3 2 DMOD
D2 0 6 DMOD
D3 6 2 DMOD
D4 0 3 DMOD
.MODEL DMOD D(IS=2.2E-15 BV=1890V)
Q1 2 7 3 QMOD
Q2 6 9 0 QMOD
Q3 2 11 6 QMOD
Q4 3 13 0 QMOD
.MODEL QMOD NPN(IS=6.73F BF=416.4 CJC=3.638P CJE=4.493P)
RG1 8 7 100OHM
RG2 10 9 100OHM
RG3 12 11 100OHM
RG4 14 13 100OHM

XPW1 17 15 8 3 PWM
XPW2 17 15 10 0 PWM
XPW3 17 16 12 6 PWM
XPW4 17 16 14 0 PWM

.SUBCKT PWM 1 2 3 4
R1 1 5 1K
R2 2 5 1K
```



OUTPUT WAVEFORMS

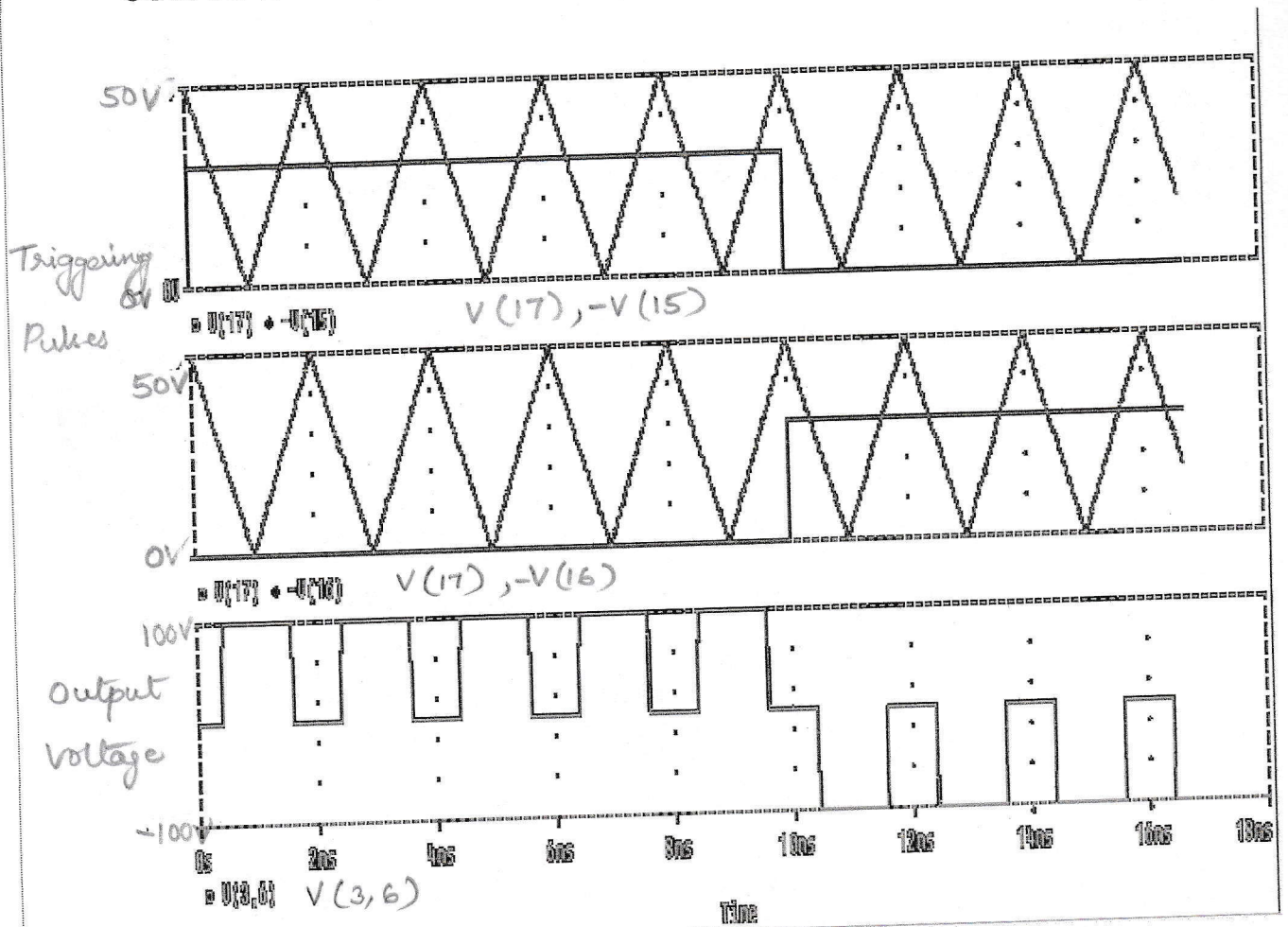



```
RIN 2 0 2MEG
R0 6 3 75OHM
C0 3 4 10PF
RF 5 3 100K
E1 6 4 0 5 2E+5
.ENDS PWM
.TRAN 10US 16.67MS 0 10US
.OPTIONS ABSTOL=1.00N RELTOL=0.01 VNTOL=0.1 ITL5=20000
.PROBE
.END
```

RESULT: The output voltage and currents of PWM Inverter are observed by simulating the circuit in PSPICE.

Vidya Jyothi Institute of Technology (Autonomous Institution)

(Accredited by NAAC, Approved by AICTE New Delhi & Permanently Affiliated to JNTUH)

Aziznagar Gate, C.B. Post, Hyderabad-500 075



Department of Electrical and Electronics Engineering (Accredited by NBA)

LAB ASSESSMENT

2020-21

Name of the Laboratory: Power

Electronics & Simulation

Branch/Section: A


Year/Sem: III-II

Page:

Day to Day Assessment																		Day To Day	Record (5)	Intern al	Total Mark
S.N os.	Roll Number	Week																			
		1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16				
1	18911A0201	9	9	9	9	9	10	10	10	10	10							10	5	8	23
2	18911A0202	9	9	9	10	10	10	10	10	10	10							10	5	8	23
3	18911A0203	8	8	8	8	9	9	9	9	9	9							9	5	7	21
4	18911A0204	7	7	7	8	8	8	8	8	8	8							8	5	AB	13
5	18911A0205	7	7	8	8	8	8	8	8	8	8							8	5	7	20
6	18911A0206	8	8	8	9	9	9	9	9	9	9							9	5	7	21
7	18911A0208	9	9	9	10	10	10	10	10	9	10							10	5	8	23
8	18911A0209	8	8	8	9	9	9	9	9	9	9							9	5	8	22
9	18911A0210	8	8	9	9	9	9	9	9	9	9							9	5	7	21
10	18911A0211	9	9	9	10	10	10	10	10	10	10							10	5	8	23
11	18911A0212	8	8	9	9	9	9	9	9	9	9							9	5	9	23
12	18911A0213	8	8	8	9	9	9	9	9	9	9							9	5	7	21
13	18911A0214	8	8	9	9	9	9	9	9	9	9							9	5	8	22
14	18911A0215	7	7	8	8	8	8	8	8	8	8							8	5	10	23
15	18911A0216	8	8	9	9	9	9	9	9	9	9							9	5	7	21
16	18911A0218	9	9	9	10	10	10	10	10	10	10							10	5	8	23
17	18911A0219	8	8	9	9	9	9	9	9	9	9							9	5	7	21
18	18911A0220	8	8	9	9	9	9	9	9	9	9							9	5	8	22
19	18911A0221	7	7	8	8	8	8	8	8	8	8							8	5	9	22
20	18911A0223	8	8	8	9	9	9	9	9	9	9							9	5	7	21
21	18911A0224	6	6	7	7	7	7	7	7	7	7							7	5	8	20
22	18911A0225	8	8	8	9	9	9	9	9	9	9							9	5	7	21
23	18911A0226	7	7	8	8	8	8	8	8	8	8							8	5	6	19
24	18911A0227	9	9	10	10	10	10	10	10	10	10							10	5	8	23
25	18911A0228	7	7	8	8	7	7	8	8	8	8							8	5	9	22

		1	2	3	4	5	6	7	8	9	10							DAI	REC	EXAM	TOTAL
26	18911A0230	8	8	8	8	9	9	9	9	9	9							9	5	7	21
27	18911A0231	9	9	9	9	10	10	10	10	10	10							10	5	8	23
28	18911A0232	8	8	9	9	9	9	9	9	9	9							9	5	8	22
29	18911A0234	8	8	9	9	9	9	9	9	9	9							9	5	10	24
30	18911A0237	8	9	9	9	9	9	9	9	9	9							9	5	7	21
31	18911A0238	8	8	9	9	9	9	9	9	9	9							9	5	7	21
32	18911A0240	8	8	9	9	9	9	9	9	9	9							9	5	7	21
33	18911A0241	8	8	9	9	8	9	9	9	9	9							9	5	10	24
34	18911A0242	9	9	10	10	10	10	10	10	10	10							10	5	8	23
35	18911A0243	7	7	8	8	8	8	8	8	8	8							8	5	8	21
36	18911A0245	9	9	10	10	10	10	10	10	10	10							10	5	8	23
37	18911A0246	9	9	10	10	10	10	10	10	10	10							10	5	8	23
38	18911A0247	9	9	9	10	10	10	10	10	10	10							10	5	8	23
39	18911A0248	8	8	8	9	9	9	9	9	9	9							9	5	7	21
40	18911A0249	9	9	10	10	10	10	10	10	10	10							10	5	8	23
41	18911A0250	8	8	9	9	9	9	9	9	9	9							9	5	8	22
42	18911A0252	9	9	10	10	9	10	10	10	10	10							10	5	8	23
43	18915A0216	6	6	7	7	6	7	7	7	7	7							7	5	8	20
44	19915A0201	9	9	10	10	10	10	10	10	10	10							10	5	9	24
45	19915A0202	9	9	10	10	10	10	10	10	10	10							10	5	8	23
46	19915A0203	8	8	9	9	9	9	9	9	9	9							9	5	10	24
47	19915A0204	9	9	10	10	10	10	10	10	10	10							10	5	8	23
48	19915A0205	7	7	8	8	8	8	8	8	8	8							8	5	8	21
49	19915A0206	7	7	8	7	8	8	8	8	8	8							8	5	8	21
50	19915A0207	9	9	10	10	10	10	10	10	10	10							10	5	8	23
51	19915A0208	10	9	10	10	10	10	10	10	10	10							10	5	8	23
52	19915A0209	7	7	8	8	8	8	8	8	8	8							8	5	7	20
53	19915A0210	9	9	10	10	10	10	10	10	10	10							10	5	8	23
54	19915A0211	9	9	10	9	10	10	10	10	10	10							10	5	8	23
55	19915A0212	10	10	10	10	9	10	10	10	10	10							10	5	9	24
56	19915A0213	7	7	8	8	8	8	8	8	8	8							8	5	9	23
57	19915A0214	9	8	9	9	9	9	9	9	9	9							9	9.5	7	21
58	19915A0215	7	7	8	8	8	8	8	8	8	8							8	5	9	22
59	19915A0216	10	9	10	10	10	10	10	10	10	10							10	5	8	23


 Name & Signature of the Faculty


 HOD/EEE

VIDYA JYOTHI INSTITUTE OF TECHNOLOGY

(An Autonomous Institution)

(Accredited by NAAC & NBA, Approved by AICTE New Delhi & Permanent Affiliated to JNTUH)

Aziz Nagar Gate, C.B. Post, Hyderabad - 500 075. Phone: Off. 76 76 637 637

Fax: 08413 - 235509 e-mail : info@vjit.ac.in www.vjit.ac.in

Name of the College:.....Vidya Jyothi Institute of Technology.....

Certificate

This is to certify that the bonafide record of the practical work carried out by

Mr/Miss.....B. Aditya..... Roll No.....18911A0202.....

of ClassEEE-A..... in thePES Lab (Power Electronics
& Simulation).....

laboratory during the academic year2021-22.....

B. Rajesh
Faculty In-charge

Head of the Dept.

External Examiner


INDEX

S. No.	Date	Name of the Experiment	Page No.	Remarks
1.	26/7/21	study of characteristics of SCR, MOSFET & IGBT	1-7	BK Rajal 28/7/21 (A)
2.	26/7/21	Gate firing circuits for SCR's [R-Triggering, RC-Triggering & UJT Triggering]	8-13	BK Rajal 28/7/21 (A)
3.	26/7/21	Single phase AC voltage controllers with R & RL loads	14-16	BK Rajal 28/7/21 (A)
4.	28/7/21	single phase fully controlled bridge converter with R & RL loads	17-19	BK Rajal 30/7/21 (A+)
5.	28/7/21	DC Jones chopper with R & RL loads	20-22	BK Rajal 30/7/21 (A+)
6.	28/7/21	single phase parallel inverter with R & RL loads	23-24	BK Rajal 30/7/21 (A+)

INDEX

S. No.	Date	Name of the Experiment	Page No.	Remarks
7.	30/7/21	Single phase cyclo-converter with R & RL loads	25-27	BRjl 2/8/21 At
8.	30/7/21	Single phase series inverter with R & RL loads	28-30	BRjl 2/8/21 At
9.	30/7/21	Simulation of 1- ϕ full converter using RLE loads & 1- ϕ AC voltage controller using RLE loads	31-36	BRjl 2/8/21 At
10.	30/7/21	Simulation of 1- ϕ inverter with PWM control	37-39	BRjl 2/8/21 At

Circuit diagram.

 

Aim: To plot the characteristics of SCR and to find the latching & holding currents.

Apparatus:-

1. SCR characteristic study unit.

2. Meter unit - voltmeter (0-20)V - INO
Ammeter (0-2)A - INO
Ammeter (0-200)mA - INO

Theory:- SCR is a semi conductor device which acts as an electronic switch. It controls the amount of power fed to load. SCR is most popular member of thyristor family. It is a four layers three junction PNPN device having three terminals & used as a switch. SCR has two states i.e it does not conduct & conducts heavily.

Observations.

V _{AK} (V)	I _G (mA)	I _A (mA)	V _{AK} (V)	I _G (mA)	I _A (mA)	V _{AK} (V)	I _G (mA)	I _A (mA)
10	0.002	0	15	0.002	0	20	0.002	0
10	0.004	0	15	0.003	0	20	0.003	0
10	0.005	0	14.9	0.004	0	20	0.004	0
10	0.006	0	14.9	0.005	0	20	0.005	0
9.3	0.007	0.1	14.9	0.006	0	20	0.006	0
0.2	0.008	3.9	0.2	0.007	6.3	19.9	0.007	0
0.2	0.009	3.9	0.2	0.008	6.4	0.2	0.008	8.6
0.2	0.01	3.9	0.2	0.009	6.4	0.2	0.009	8.6

Procedure :-

- 1) Make the connections as shown in fig. including meters
- 2) switch ON the main supply to the unit & keep the voltage V_1 & V_2 at min position.
- 3) set $V_{AK} = 10V$ by varying V_1
- 4) slowly vary V_2 in steps & note I_G , I_A & V_{AK} values
- 5) vary V_2 till SCR conducts which can be noticed by sudden drop of V_{AK} & rise of I_A .
- 6) Repeat same procedure for $V_{AK} = 15V$ & $20V$
- 7) draw V_{AK} vs I_A graph for different values of I_G .

Scale

x-axis unit = 2V

y-axis unit = 5mA

5A

2.0

1.5

1.0

0.5

0

2

4

6

8

10

12

14


16


18

20

$V_B(V)$

at 1.6

 

 

$$V_1 > V_2 > V_3$$


$$J_{G1} < J_{G2} < J_{G3}$$

Title :


Result :- we have done the characteristics of SCR and determined the latching & holding current.

syil
28/8/21
A


Circuit diagram.

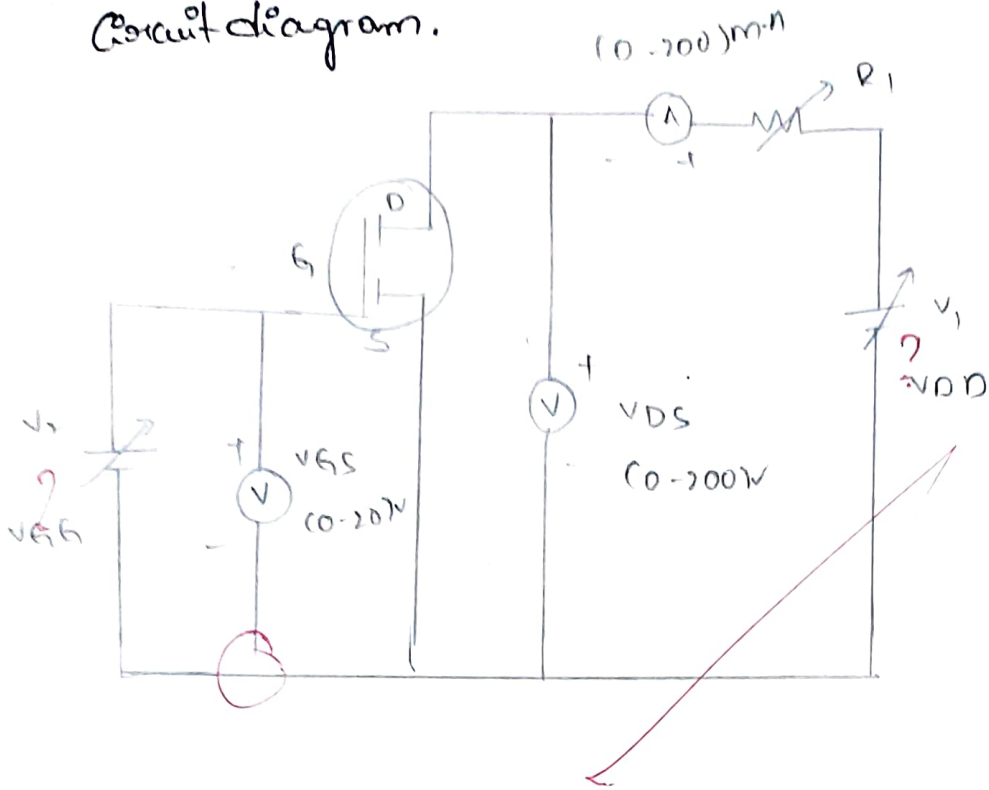

o/p characteristics:

 

Transfer characteristics

 

Aim :- To plot the drain and transconductance characteristics of MOSFET.

Apparatus :-

1. MOSFET characteristics study unit.

2. Meas unit - Voltmeter (0-20)V - 1NO
Voltmeter (0-200)V - 1NO
Ammeter (0-200)mA - 1NO

3. patch cords.

Theory :-

A power MOSFET has three terminals called

drain, source and gate.

MOSFET is a voltage controlled device & its operation depends on flow of majority carriers only. MOSFET is unipolar device. The control signal & base current required in MOSFET is less. This is because the gate circuit impedance in MOSFET extremely high.

o/p characteristics

$V_{GS} = 2V$		$V_{GS} = 2.3V$		$V_{GS} = 3.1V$	
$V_{DS}(V)$	$I_D(mA)$	$V_{DS}(V)$	$I_D(mA)$	$V_{DS}(V)$	$I_D(mA)$
0.01	0.0	2.1	0	2.75	0.1
2.2	0.1	2.8	0.1	2.79	0.1
2.85	0.2	2.9	0.3	2.83	0.2
3.08	0.5	3.0	0.6	2.94	0.5
3.2	0.6	3.2	0.7	3.0	0.8
4.0	0.6	3.4	0.7	3.1	0.9
5.0	0.6	5	0.7	4	0.9


transfer characteristics

$V_{DS} = 2.5V$	
$V_{GS}(V)$	$I_D(mA)$
1.23	0
2.7	0.1
2.9	0.4
3.0	0.7
3.1	0.8
3.2	0.9

Drain character

x-axis unit: 0.5V

y-axis unit: 0.5V

 

V_{DS}

$V_{DS} = 2.5V$

Bayi

0.5 1 1.5 2 2.5 3 3.5 4 4.5 5 5.5 6 6.5 V_{GS}

Procedure :-

a) Drain / output characteristic :-

1. Give the connections as shown in circuit diag. with meters.

2. slowly vary V_2 & adjust $V_{GS} = 2V$.

3. vary V_1 in steps & note V_{DS} & I_D .

4. Repeat procedure $V_{GS} = 2.7V$ & $2.9V$.

5. plot V_{DS} vs I_D for different V_{GS} values.

b) Transfer characteristic :-

1). Set $V_{DS} = 2.5V$ by varying V_1 .


2) By varying V_2 in steps, note V_{GS} & I_D for each step, adjust $V_{DS} = 2.5V$ & note V_{GS} vs I_D values.

3) plot V_{GS} vs I_D for V_{DS} .


Result :- we have studied drain & transconductance characteristics of MOSFET.

OK
28/7/21 (A)

Circuit diagram.

 

Model graph

 

Aim: To plot the collect & transfer characteristics of IGBT.

Apparatus:

1. IGBT characteristics study unit.
2. Meter unit -
 - voltmeter (0-20)V - INO
 - voltmeter (0-200)V - INO
 - ammeter (0-200)mA - INO.
3. patch cords.

procedure:

a) collect characteristics :-

- 1) Give connections as shown in circuit diagram.
- 2) slowly vary V_2 & adjust $V_{GE} = 4V$.
- 3) Now vary V_1 in steps & note down V_{CE} & I_C for each step.
- 4) plot V_{CE} & I_C for different values of V_{GE} .

DP characteristics


$V_{GS} = 2V$		$V_{GS} = 3V$		$V_{GS} = 4V$	
$V_{CE} (V)$	$I_C (mA)$	$V_{CE} (V)$	$I_C (mA)$	$V_{CE} (V)$	$I_C (mA)$
1.2	0	0.5	0.3	0.4	0.3
2.8	0	1.0	0.5	0.5	0.5
3.9	0	2.0	0.5	0.6	0.3
4.0	0	1.5	0.5	0.7	0.7
5.0	0	4	0.5	0.8	0.7
7	0	4.5	0.5		

transfer characteristics

$V_{CE} = 5V$	
V_{GS}	$I_C (mA)$
1.21	0
2.03	0
3	0
4	0
4.2	0.1
4.91	0.3
5.1	0.5
6.02	0.9
7	0.9


o/p characteristics

x-axis unit: 0.5V
y-axis unit: 0.5mA

 

transfer characteristics

$V_{ce} = 5V$

 

b) Transfer characteristics:


- 1) Set $V_{CE} = 5V$ by varying V_1 .
- 2) By varying V_2 in steps, note V_{GE} & I_C for each step, adjust $V_{CE} = 5V$ & note V_{GE} & I_D .
- 3) plot V_{GE} vs I_C for different values of V_{CE} .

Result: we have studied the characteristic of collector & transfer of IGBT.

OK
28/7/24

A

Circuit diagram.

 

[R. Triggering, R_c triggering & UJT triggering]

Aim: To study the amplitude control of SCR with R triggering.

Apparatus:

1. SCR triggering module.
2. CRO
3. patch cards
4. Multimeter.


Theory:

SCRS can widely used as controlled rectifiers to obtain variable DC voltage from fixed AC source. SCR conducts like a diode only when its anode is positive w.r to cathode and on application of sufficient gate current at specified gate to cathode voltage.

Observations.

Firing angle	load voltage
min	9.1
36°	9.61
50°	9.22
max	7.2

Model graphs

 

Procedure:-


- 1) Give the connections as per the circuit diagram.
- 2) Switch ON module.
- 3) Set the potentiometer to any particular position & observe the waveforms of V_{IN} , V_O , V_T , V_P on CRO & note waveforms.
- 4) Vary potentiometer & note firing angle & corresponding load voltage using multimeter.

Results: Amplitude control of SCR with R-triggering was studied.

BRJ²⁸ 28/7/21

(A)

Circuit diagram.

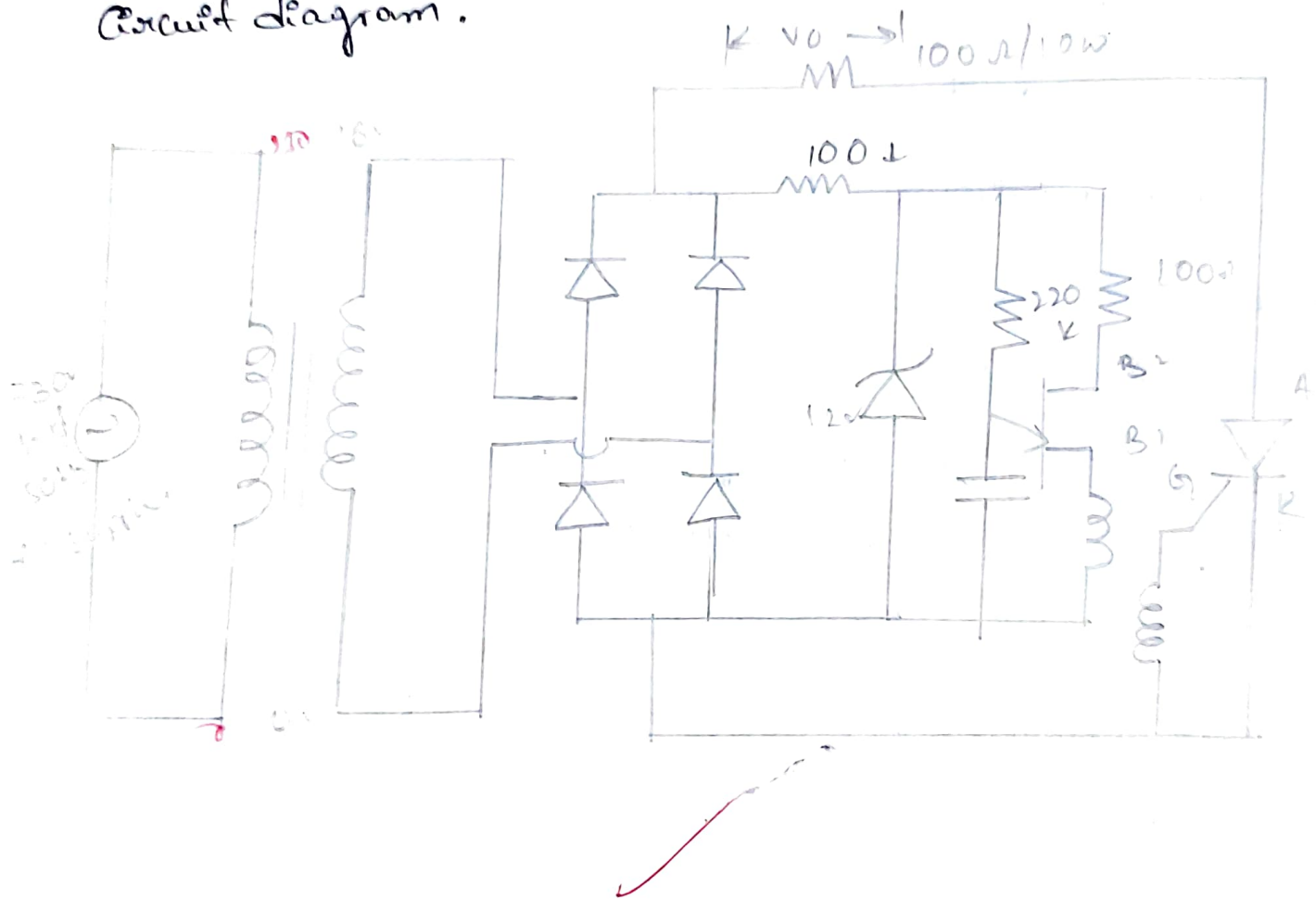

Aim :- To construct & study VJT triggering circuit to trigger an SCR.

Apparatus :-

1. SCR Triggering module.
2. CRO
3. patch cords
4. multimeter.


Theory :-






VJT works as Relaxation oscillator. output pulses of variable time period are possible by suitably increasing the emitter to base voltage from valley voltage level to peak level either by employing a constant source & by charging a capacitor by a resistor. The RC network can be easily employed to obtain alp pulses.

Observations

iring angle (α)	load voltage (V)
18	2.4
36	2
90	4.1
162	0.1

Model graph.

 

     

32/10


Procedure:-

- 1) Give the connections as per circuit diagram.
- 2) Switch ON the module.
- 3) Set potentiometer & observe the waveforms V_{IN} , V_O , V_T , V_P , V_D , V_Z , V_C on CRO & note waveforms.
- 4) By varying R , note down the firing angle & load voltage.


Result: The ~~VLT~~ triggering circuit to trigger an SCR was studied.

BRJL
28/7/21
(A)

2c half wave triggering

 

2c full wave triggering

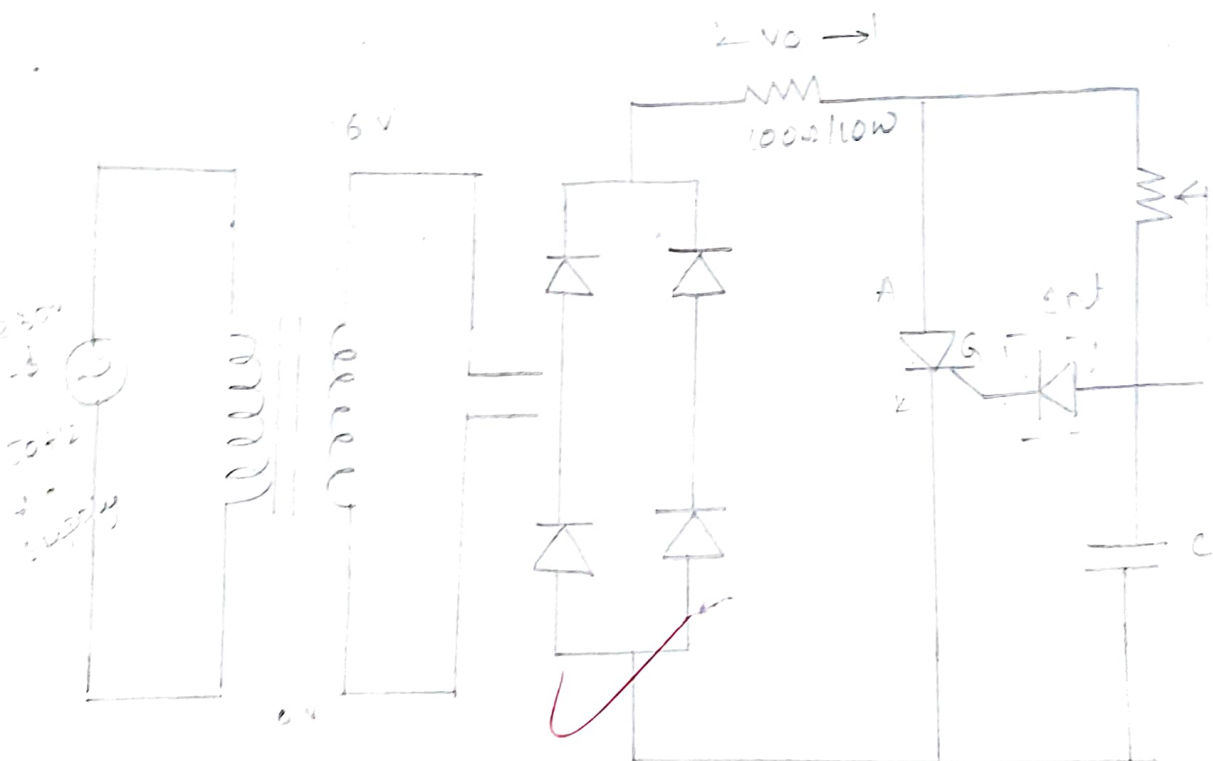

Aim: To study the phase control of SCR by RC triggering.


Apparatus:






1. SCR triggering module.
2. CRO
3. patch cards
4. Multimeter.

Procedure:

- 1) Give the connections as per circuit diagram.
- 2) Switch ON the module.
- 3) Set potentiometer to observe waveform of V_{in} , V_o , V_T , V_P , V_c on CRO & note waveforms.
- 4) Vary the potentiometer & note down the corresponding load voltage using multimeter.

Firing angle	load voltage (V)
0°	9.2
36°	9.2
90°	7.46

 

     

Title :

Date :


Page No. : 13

Result: Phase control of SCR with RC triggering
was studied.

(A) B.R. Jit 28/11/21



Circuit diagram

 

Aim: To construct single phase AC voltage controller circuit & to study its operation with R & RL loads.

Apparatus:-

1. Single phase AC voltage controller unit.
2. Loading Rheostat (50 Ω / 2A)
3. Loading Inductor (0-150mH / 2A)
4. Digital multimeter.
5. CRO
6. patch cords.

Theory: AC voltage controller convert fixed alternating voltage directly to variable alternating voltage without change in frequency. Some of main application of AC voltage controller are domestic and industrial heating.

Observations

R


$V_m = 22.3V$

iring angle α	V_L
180	0
150	0.5
120	6.6
90	9.9
60	14.9
30	19.6
0	22.3

FL

$V_m = 22.1V$


iring angle α	V_L
180	0
150	2.4
120	6.6
90	10.4
60	15.6
30	20.1
0	22.1

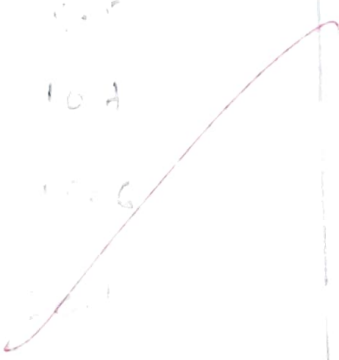

Procedure:-




- 1) switch ON the main supply to unit.
- 2) Give the connections as shown in circuit diagram for single phase AC voltage controller using SCR / TRIAC connect the AC supply to circuit through step down T/P.
- 3) connect the diggus o/p's T_1 & T_2 from firing circuit to SCR / TRIAC. select SCR / TRIAC switch to SCR for AC voltage.
- 4) keeping firing angle knob at some intermediate position, switch ON the step down T/P supply & diggus o/p's & observe the o/p voltage waveform.
- 5) vary the firing angle & measure the load voltage using multimeter.
- 6) For the single phase AC voltage controller.

Model graph 1.

 

AC voltage P-load.

   $x_{crit} = 60 \text{ unit}$
 $y_{crit} = 10 \text{ V}$



BR gel

for RL load, connect the inductor in series with load P .


7) Repeat above steps for AC voltage controller with RL load.

Result: A single phase AC voltage controller was constructed & its operation with R & RL load is observed.

BKJil
28/7/21
(A)



Circuit diagram.

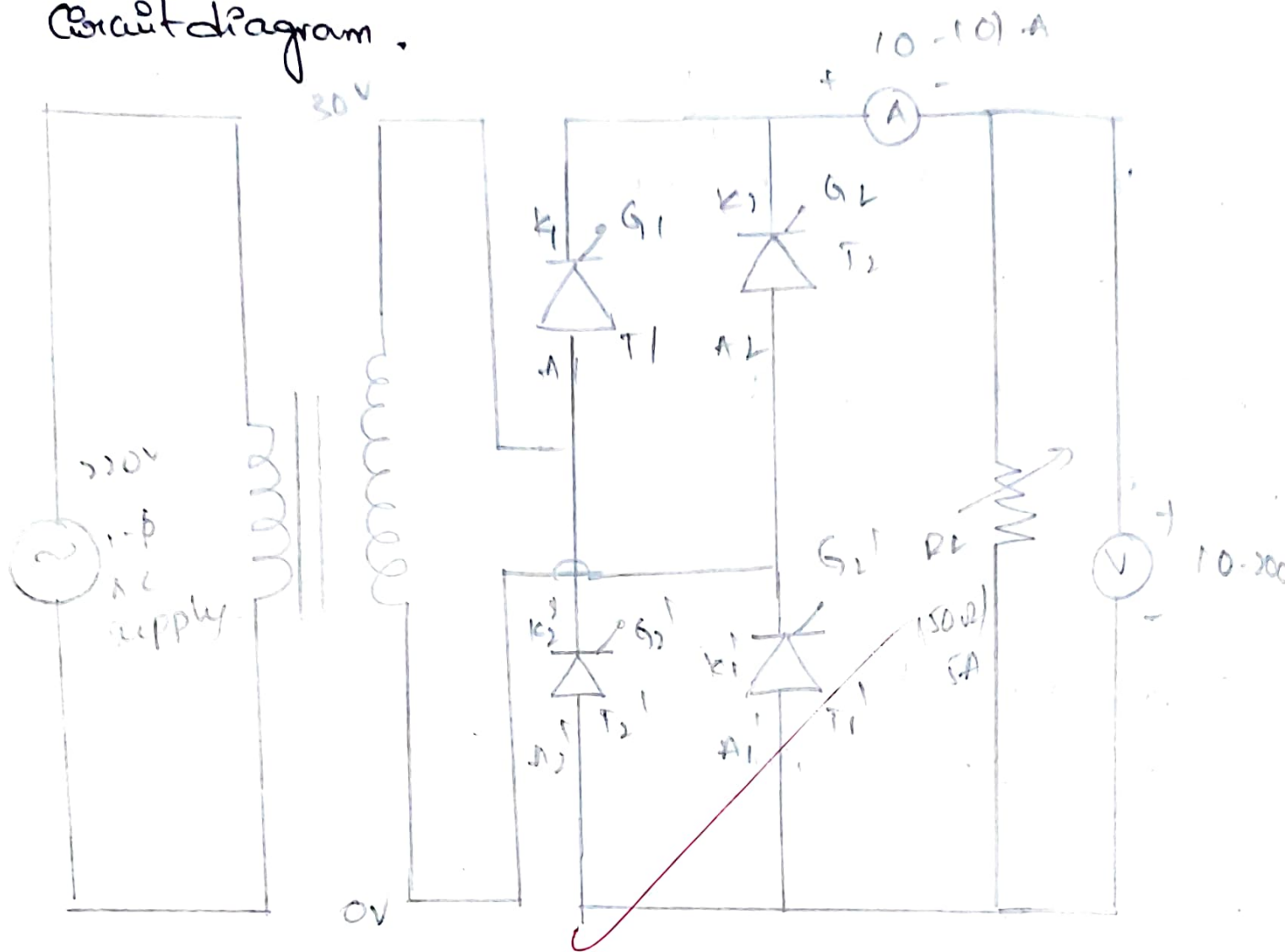

Bridge converter

Aim: To construct single phase fully controlled bridge converter circuit & do study its operation with R & RL load.

Apparatus:-

- 1) single phase fully controlled bridge converter power unit.
- 2) single phase fully controlled bridge converter firing unit.
- 3) 1- ϕ isolation transformer (0-230V/5A) with tappings.
- 4) loading Rheostat - 150 Ω / 5A.
- 5) Inductor - 150 mH / 5A.
- 6) CRO
- 7) patch cords

Study: In bridge converter, all the four arms of SCR's are connected as control switches. This is called Fully controlled bridge as all the SCR's are connected in bridge form.

Observation.

R-load

Firing angle α	V_L	I_L	$V_L = \frac{V_m(1 + \cos \alpha)}{\pi}$
180	0	0	0
150	2	0.05	1.2
120	10	0.22	6.4
90	17	0.35	12.8
60	22	0.50	19.2
30	24	0.56	24.05
0	25	0.56	25.7


RL





Firing angle (α)	V_L	I_L	$V_L = \frac{V_m(1 + \cos \alpha)}{\pi}$
180	0	0	0
150	1	0.01	1.2
120	6	0.12	6.4
90	11	0.24	11.8
60	21	0.43	17.5
30	24	0.5	21.7
0	25	0.54	25.7

procedure:



- 1) Give the connections as shown in circuit diagram.
- 2) connect 30V tapping of isolation T/F secondary to power circuit.
- 3) connect R-L load (150 Ω / 5A) between the o/p points.
- 4) connect the trigger pulses from converter using firing circuit T_1, T_1' & T_2, T_2' to corresponding SCR's (T_1, T_1' & T_2, T_2') in power circuit.
- 5) switch ON main supply to firing circuit.
- 6) switch ON MCB in power circuit & switch ON trigger o/p's in firing unit.
- 7) keep the firing angle at some position & draw waveforms in V_{in} & V_o .
- 8) draw the waveforms across the load for different firing angles & note o/p voltage & o/p current from voltmeter & ammeter.

Model graph.

 

    

$P = 1000$

  


1000

1) At any firing angle, note the o/p waveform
v_o & for different firing angle note o/p voltage &
o/p current from voltmeter & ammeter.


Result: A 1- ϕ fully controlled bridge constructed
& its operation with R & RL load observed.

At
30/7/28

Circuit diagram.

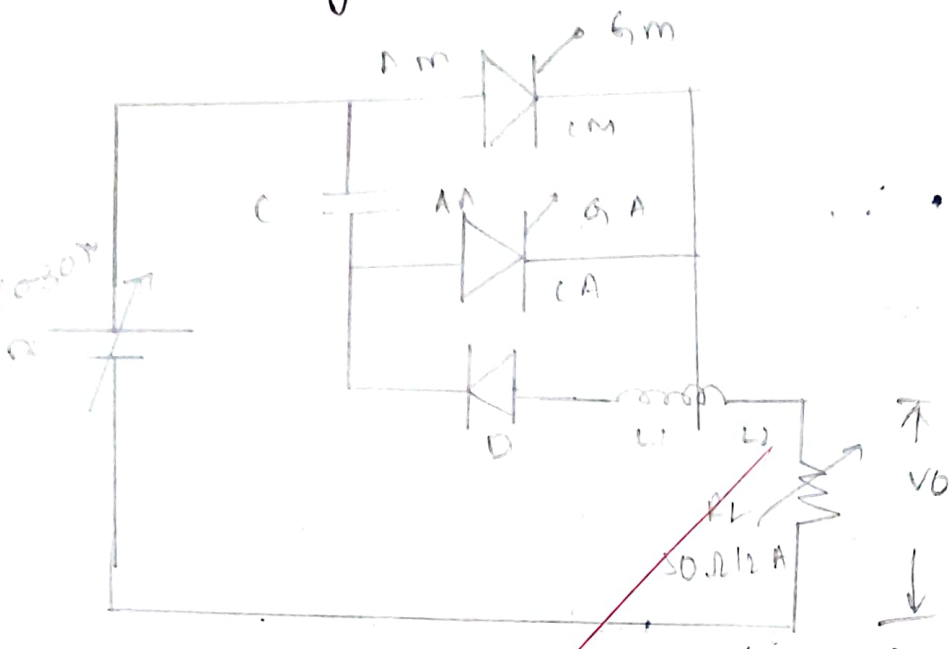

Model graph.

 

RL loads

Aim: To construct Jones chopper circuit & to study its operation with R & RL load.

Apparatus:

1. chopper power module.
2. chopper firing unit.
3. Regulated power supply (0-30)V
4. loading rheostat (50 Ω / 2A)
5. Inductor - 50 mH / 2A
6. Digital multimeter.
7. CRO
8. patch cords.

Study: Chopper converts fixed DC voltage to variable DC voltage. The DC to DC converters have gained popularity in modern industry. Some practical applications of DC to DC converters include armature voltage control of DC motors converting one DC voltage level to another level.

Observations.

Duty ratio	T_{ON}	T_{OFF}	(V)
57.1	8	6	9
50	7	7	9
42	6	8	9
35.7	5	9	9
28	4	10	9

Observations.

Frequency	T_{ON}	T_{OFF}	V
66	6	9	9
83.6	5	7	9
111.1	4	5	9
128	3	5	9

Procedure :-

- 1) Give connections as per circuit diagram with R load.
- 2) connect Gate cathode terminals of SCR's to respective points on firing unit.
- 3) keep the frequency knob & duty ratio knob at some intermediate position.
- 4) set DC power supply to 30V & switch ON the DC power supply to chopper.
- 5) observe V_0 , V_{T1} , V_{T2} , V_{P1} , V_{P2} , V_C waveforms on CRO & note down the corresponding waveforms.
- 6) keeping the frequency const. vary duty cycle in steps & note T_{ON} , T_{OFF} & load voltage for each step.

V_{OA}
10
5

0 2 4 6 8 10 12 14 16 18 20

V_{OA}
10
5

0 2 4 6 8 10 12 14 16 18 20 22 24 26

V_{OA}
10
5

0 2 4 6 8 10 12 14 16 18 20 22

constant duty cycle run - time 3.8 min

0 2 4 6 8 10 12 14 16 18 20 22 24

0 2 4 6 8 10 12 14 16 18 20 22

0 2 4 6 8 10 12 14 16 18 20 22


7. Repeat step 6 by varying frequency & keeping duty ratio constant.
8. connect R_L load & note O/P V_o & repeat step 6.

Result : we have studied the characteristics of D.C Jones chopper.


ABR/20/7/21
(AT)



circuit diagram

 

Waveform graph.

 

R and RL loads

Aim: To construct single phase parallel inverter circuit & to study its operation with R & RL load.

Apparatus:

1. parallel inverter module.
2. Regulated power supply (0-30) V
3. loading Rheostat (50 Ω / 2A)
4. Inductor - (50mH) 2A.
5. Digital multimeter.
6. patch cards
7. CRO.




Theory: A device that converts DC power in to AC power at desired output voltage and frequency is called as inverter. Some industrial applications of inverters are for adjustable speed AC drives, inductive heating, standby aircraft power supplies, UPS.

P load Observations

frequency	o/p (V)
89.25	63.212
92.49	62.812
100.56	64.812

full load

frequency	o/p voltage	V _T	V _C
109.25	38.12	53.612	36.6
82.4	32.81	22.1	36.6

   


Procedure:

- 1) Give the connections as shown in circuit diagram.
- 2) connect the firing unit to main unit.
- 3) Adjust the DC supply to 13V & switch on the main unit & firing unit.
- 4) Set the frequency at a particular value & observe the load voltage waveforms V_o , V_T , V_{T2} , V_{P1} , V_{P2} , V_c on CRO & note waveforms.
- 5) By varying the frequency, note O/P AC voltage using multimeter.
- 6) connect RL load & note O/P V_o .
- 7) Repeat step 5 for RL load.

Result:- Here studied the 1- ϕ parallel inverter with R & RL load.

BRJL
(A+) 30/7/24

Circuit diagram

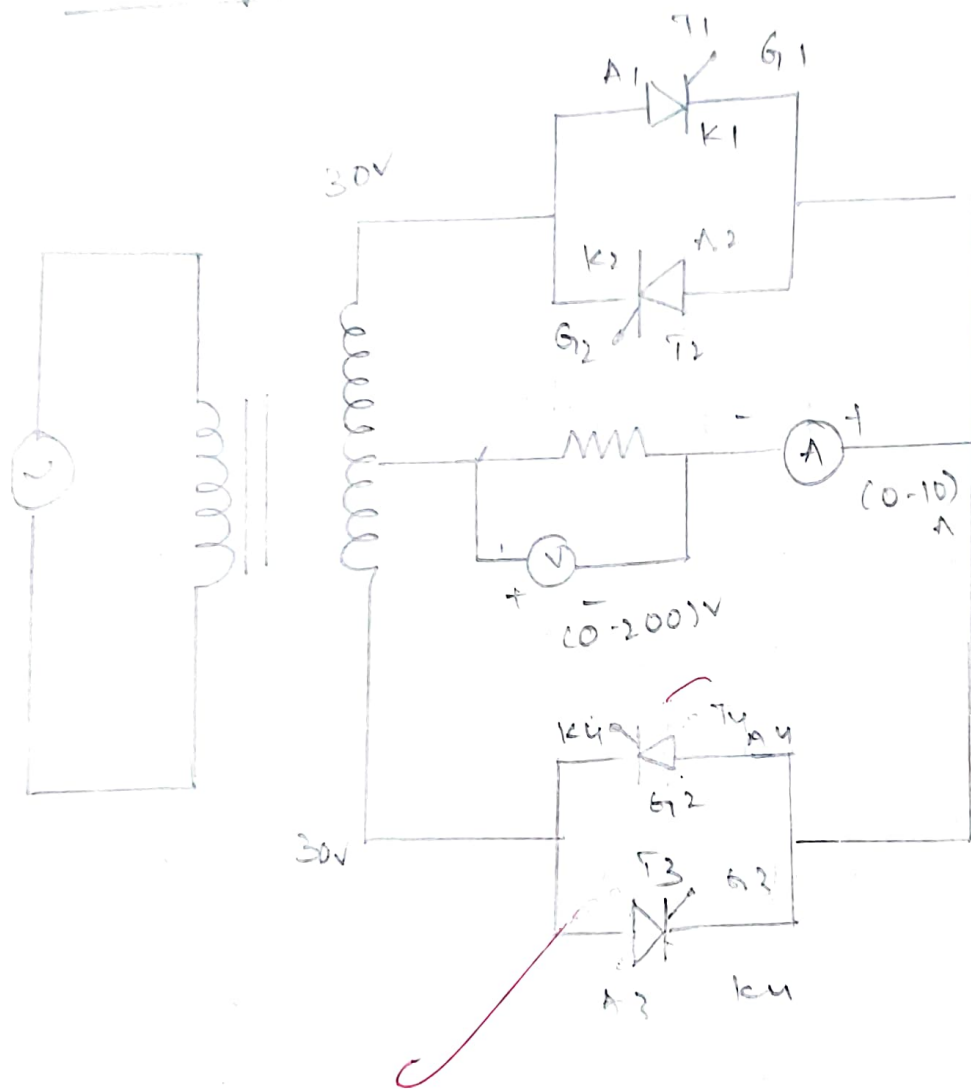

Title: 1. Single phase cyclo-converter
with R and RL loads

Date : 30-7-21
Page No. : 25

Aim: To construct a single phase cyclo converter circuit & to study its operation with R & RL loads.

Apparatus:

- 1) cycloconverter power unit.
- 2) cycloconverter firing unit.
- 3) single phase isolation transformer.
- 4) loading rheostat - 150 Ω / 2A.
- 5) Inductor (0 - 150 mH / 5A)
- 6) Digital multimeter
- 7) CRO
- 8) patch cords

Theory:- A circuit which converts input power at one frequency to output power at different frequency with one stage conversion is called a cyclo converter. Cyclo converters are used in speed control of high power AC drives, induction heating etc.

Observations

R

f_s	voltage	current
f_s	27	0.22
$\frac{f_s}{2}$	27	0.22
$\frac{f_s}{3}$	27	0.22
$\frac{f_s}{4}$	27	0.22




RL

frequency	V	I
f_s	22.7	0.22
$\frac{f_s}{2}$	22.7	0.22
$\frac{f_s}{3}$	22.7	0.22
$\frac{f_s}{4}$	22.7	0.22

procedure:-

- 1) Give the connections as per circuit diag. with R load with ammeter & voltmeter.
- 2) connect the firing pulses from the firing unit to respective SCR's in power unit.
- 3) connect the i/p supply of 30-30V from the centre tapped, T/F & loading rheostat at o/p terminals.
- 4) switch ON power unit & the firing unit switch ON the MCB in power unit & switch ON triggering pulses in firing unit.
- 5) set frequency division to 2. At any firing angle, note waveform across load V_o & note o/p voltage & current readings from voltmeter & ammeter.

cycle converted

   


1/2

-) note o/p voltage waveform for different frequency division
- 8) note o/p voltage & current.
- 9) connect to RL & repeat the above steps.


Result: Hence we studied the 1- ϕ cyclo converter with R & RL load is verified.

BY / 2/8/21
(A+)

Circuit diagram:

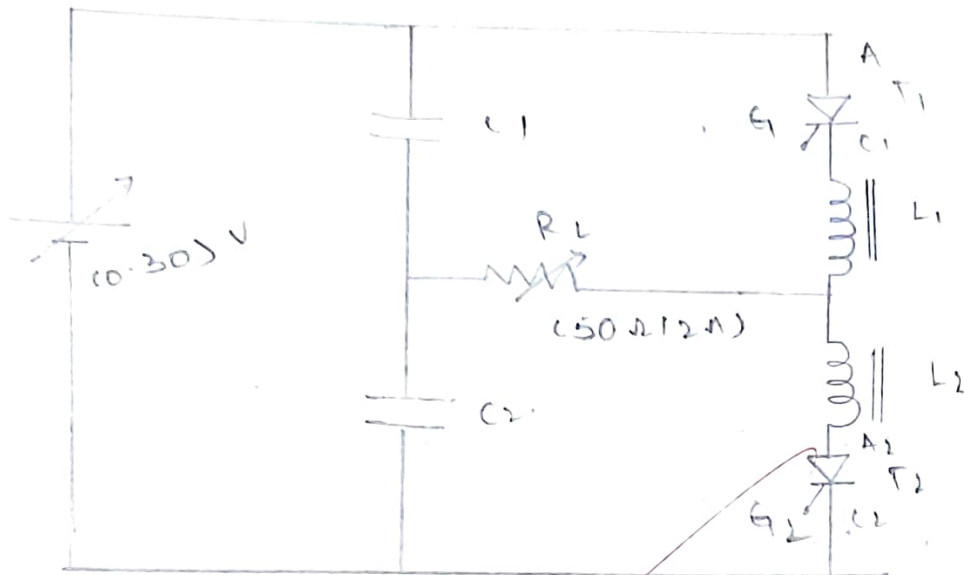

Flodd graph

 

Aim: To construct single phase series inverter circuit
& to study its operation with R & RL load.

Apparatus:-

- 1) Series inverter unit.
- 2) Loading Rheostat - $50\Omega / 2A$.
- 3) Regulated power supply - (0-30)V
- 4) Inductor - $50mH / 2A$.
- 5) Digital multimeter.
- 6) patch cords.
- 7) CRO.

Study:- The inverter in which commutating

components are permanently connected in series with load called series inverter. Series inverter can also be classified as self commutated inverter & load commutated inverter.

$$F = \frac{1}{2(\tau_{ON} + \tau_{OFF})} \quad HZ$$

Observations

R V = 6.18

Time Period	Frequency (Hz)	o/p voltage (V)
5ms	83.2	64.1mV
5ms	86.6	83.2mV
5ms	91.3	85.1mV
5ms	94.9	63.1mV
5ms	101.2	-24.8mV
5ms	121	20.9
5ms	151	-5.25
5ms	170	44.4




R2

Time period	Frequency	o/p V
5ms	81.4	26mV
5ms	83.4	40.9mV
5ms	93.6	51.1mV
5ms	96.6	34.9mV
5ms	98.9	-53.0mV
5ms	26	-31.1
5ms	80	37.2

Procedure:-

- 1) Give the connections per circuit diagram with R-load.
- 2) connect the gate cathode terminals of SCR's to respective points on firing unit.
- 3) Adjust the DC supply voltage to 30V & switch on DC supply & firing unit.
- 4) set frequency at particular position & observe o/p waveform V_{O1} , V_{T1} , V_{T2} , V_{T1} , V_{T2} , V_{C1} on CRO & note waveform.
- 5) vary frequency in steps and note corresponding waveforms.
- 6) connect R-load & note o/p voltage & repeat above steps.

x-axis unit = 5ms
y-axis unit = 5V

   

Title :



Date :
Page No.: 30

Result : Hence observed the single phase
series circuit with R & RL load.

B. A. J. L. 1/8/21
A4



Circuit diagram

  

Title: q. single phase full converter using
R_L and ϵ load.

Date : 28-7-21
Page No. : 31

Aim : To simulate single phase full converter using
PSPICE.

Apparatus:- computer
PSPICE software.

code:-

```
VG16      2      PULSE      0V      10V      3333.33US      1NS      1NS  
                                     100US      20000US )  
  
VG21      0      PULSE      0V      10V      3333.33US      1NS      1NS      100US  
                                               20000US )  
  
VG38      2      PULSE      0.10V      13333.33US      1NS      1NS      100US  
                                               20000US )  
  
VG49      1      PULSE      0      10V      13333.33US      1NS      1NS      100US  
                                               20000US )
```


R2 4 100 OHM

L 45 5.5 MH

Vx 5 3 DC 20V

Vy 10 1DC 10V

OUTPUT WAVE FORMS: -

 

XT₁ 1 2 6 7 SCR

XT₂ 3 0 4 0 SCR

XT₃ 0 2 8 2 SCR

XT₄ 3 1 9 1 SCR

• SUB CKT

SCR 1 2 3 2

S1 15 6 2 S MOD

R_G 3 4 50

V_X 4 2 DC 0V

V_Y 5 7 -DC 0V

D1 7 2 D MOD

R_T 6 2 1

C_T 6 2 10 uF

F₁ 2 6 POW(L) V_X V_Y 0 50 11.

• MODEL S MOD USWITCH (R_{ON} = 0.0105 R_{OFF} = 10E+5
V_{ON} = 0.5V V_{OFF} = 00 |

• MODEL D MOD D (I_S = 2.2E-15 B V = 1200V TT = 0
CBO = 0]

• ENDS SCR



- TRAN 50 μ s 100 ms 30 ms 50 μ s
- OPTIONS ABSTOL = 1.00 N RETOL = 10 N UNTOL = 0.01
ITLS = 20000
- FOUR 50Hz ICuY)
- PROBE
- END.

Result : verified single phase fully converter
using RL & E loads

Brij 2/8/21

(A+)

② Circuit Diagram

  

Title: 10 Single phase AC voltage controller
using RL load

Date : 30-7-21
Page No.: 34

Aim: To simulate single phase AC voltage controller using PSpice.

Apparatus:-


computer
pspice software.

Program:-

```
VS      1  0  SIN      (0 1000 60HZ)
VG1     2  4  PULSE    (0 100 4166.70S 1NS 1NS
                        1000S 16666.70S)
VG2     3  1  PULSE    (0 100 125000S 1NS 1NS 1000S
                        16666.70S)

R       4  5      2.5
L       5  6      6.5 mH
VX      6  0      0 C  0V
CS      1  7      0.0F
RS      7  4      750
XG1     1  4      2      4  SCR
```


OUTPUT WAVE FORMS: -

 

XTD 4 1 3 1 SCR .

• SUBCKY SCR 1 2 3 2

SI 1 5 6 2 S MOD

RG 3 4 50

VX 4 2 DC 10V

VY 5 2 DC 0V

RT 2 6 1

CT 6 2 100F

I1 2 6 POLY(2) VX VY 0.50 11

• MODEL S MOD USWITCH (RON=0.01 ROFF=10H3 VON=0.1
VOFF=0V)

• ENDS SCR

• TRAN 10US 33.33ms

• PROBE

• OPTIONS ABSTOL = 1.00N RELTOL = 1.0m UNTOL = 10m
STES = 1000

• FOUR 60Hz 4y

• END

Title :

Date :


Page No. : 36

Result :- Hence verified V voltage controlled
using R_L load.

BKyl 2/2/21
(A+)



Circuit Diagram.

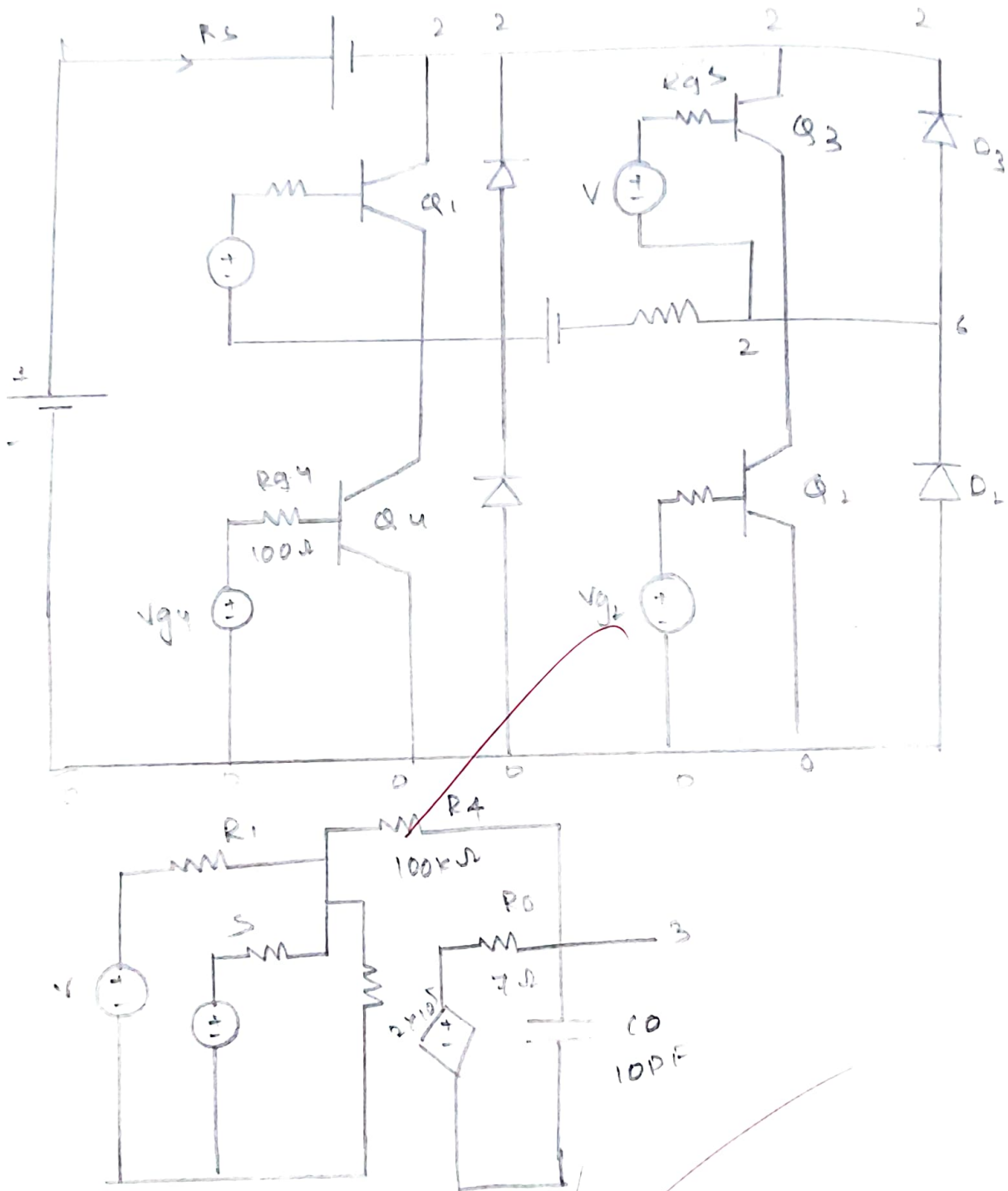

Title :

Single phase PWM inverter

Date : 30-7-21

Page No. : 37



Aim : to simulate single phase PWM inverter using PSPICE.


Apparatus :-

1. computer and PSPICE software.

Program :-

V _S	1	0	DC 100V
V _R	17	0	PULSE (50V 0V 0 1MS 1MS 1MS 2MS)
R _R	17	0	2MEG
V _{C1}	15	0	PULSE (0-30V 0 1MS 1MS 10MS 20MS)
R _{C1}	15	0	2MEG
V _{C3}	16	0	PULSE (0-30V 10MS 1MS 1MS 10MS 20MS)
R _{C3}	16	0	2MEG
R	4	6	2-50HM
V _X	3	4	DC 0V
V _Y	1	2	DC 0V
D ₁	3	2	DMOD
D ₂	0	6	DMOD
D ₃	6	2	DMOD
D ₄	0	3	DMOD

  

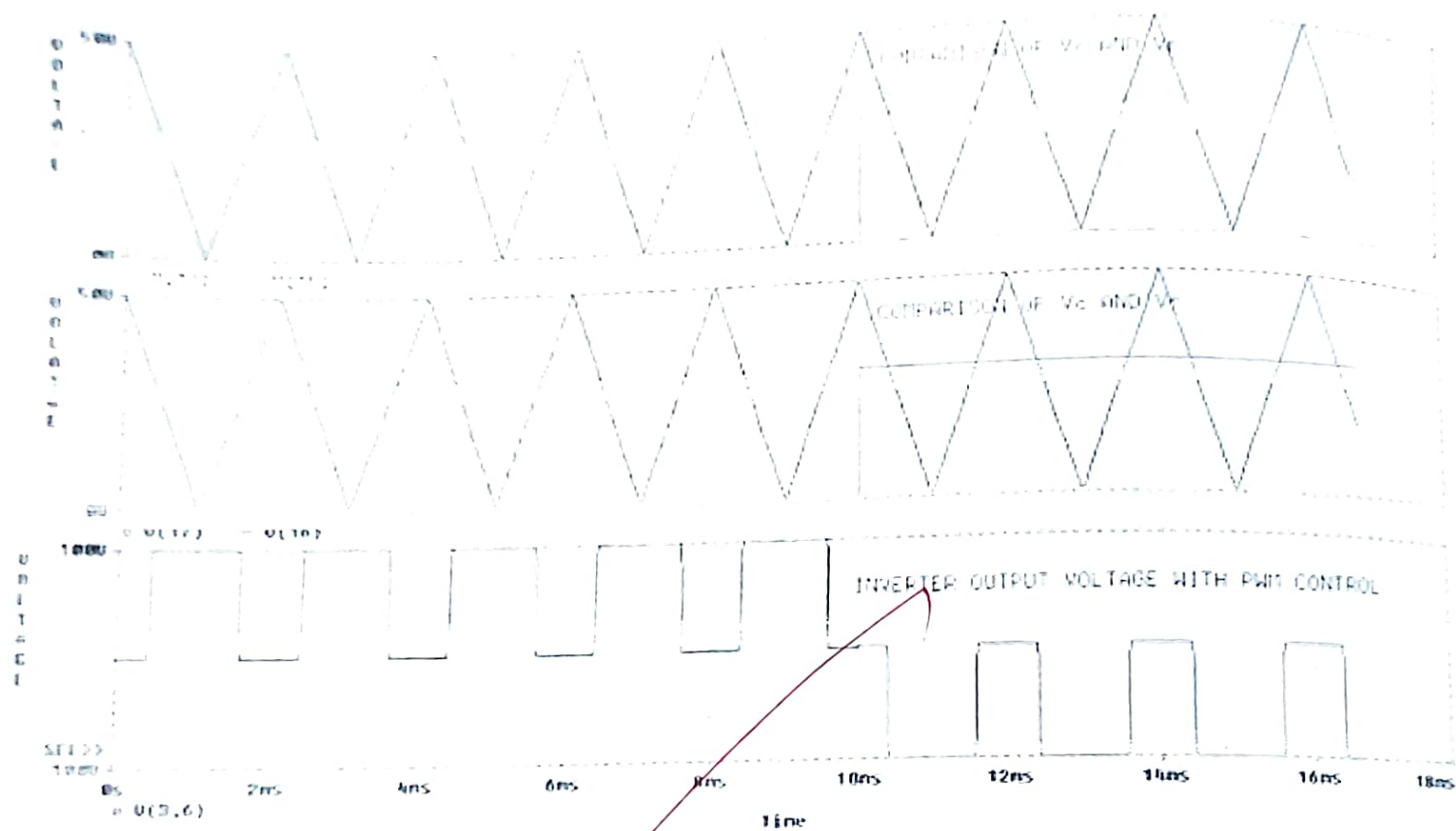

• MODEL DMOD D (IS = 2.2E - 15 BV = 1890 V)

Q1	2	1	3	Q MOD
Q2	6	9	0	Q MOD
Q3	2	11	6	Q MOD
Q4	3	13	0	Q MOD

• MODEL QMOD NTN (IS = 6.73 F BE = 4164 CJC = 3.68 FP
CJE = 4.493 P)

RG1	8	7	100 OHM
RG2	10	9	100 OHM
RG3	12	11	100 OHM
RG4	14	13	100 OHM
XPW1	17	15	8 3PWM
YPW2	17	15	10 0PWM
XPW3	17	16	12 6 PWM
XPW4	17	16	14 0 PWM

• SUBCKT PWM 1 2 3 4

R1	1	5	1K
R2	2	5	1K
RIN	5	0	2MEG
RO	6	3	750 HM
CO	3	4	10 PF
RF	5	3	100K
E1	6	4	0 5 2E+5

• ENDS PWM

• TRAN 100S 16.67 NS 0 100S

• PROBE

• OPTIONS ABSTOL = 1.00D RELTOL = 0.01 UNTOL = 0.1

ITLS = 20000

• END

Result: Verified the working & operation of
1- ϕ PWM inverter using PSpice.

BK/jil
2/8/21
(A+)